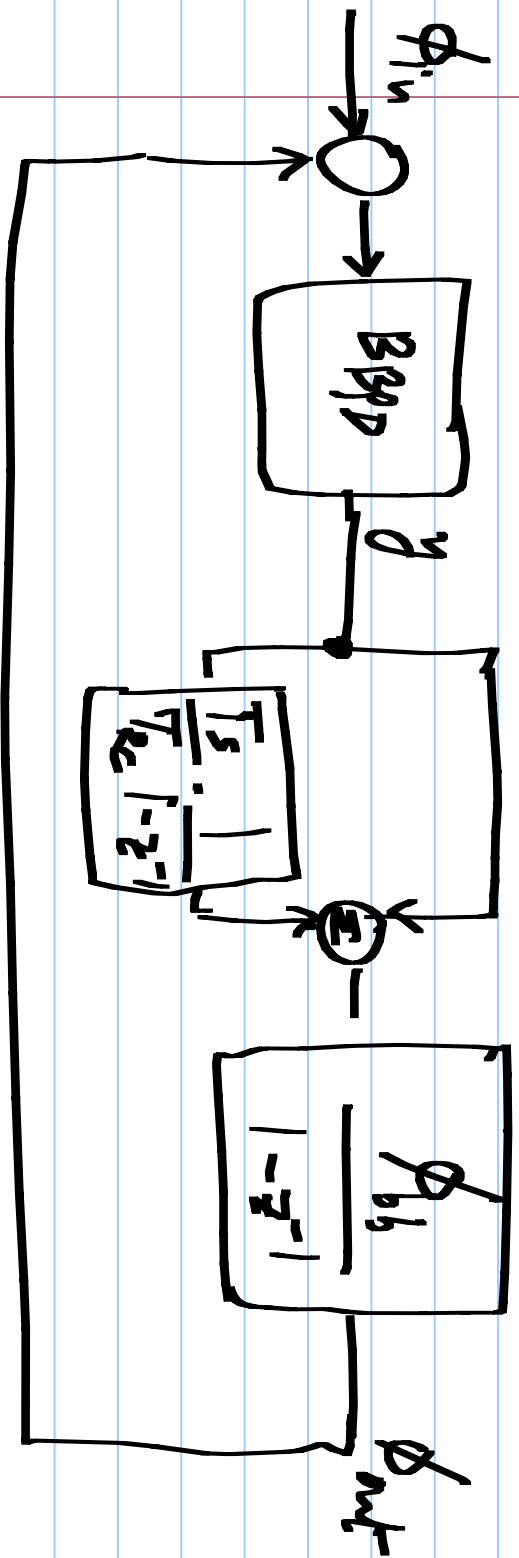



EE6322

$\pm 1, 0$




28/2/2018


$f_{TX}$   
 $D_{in}$

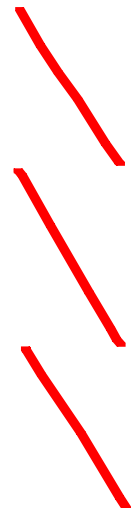


Digital accumulators

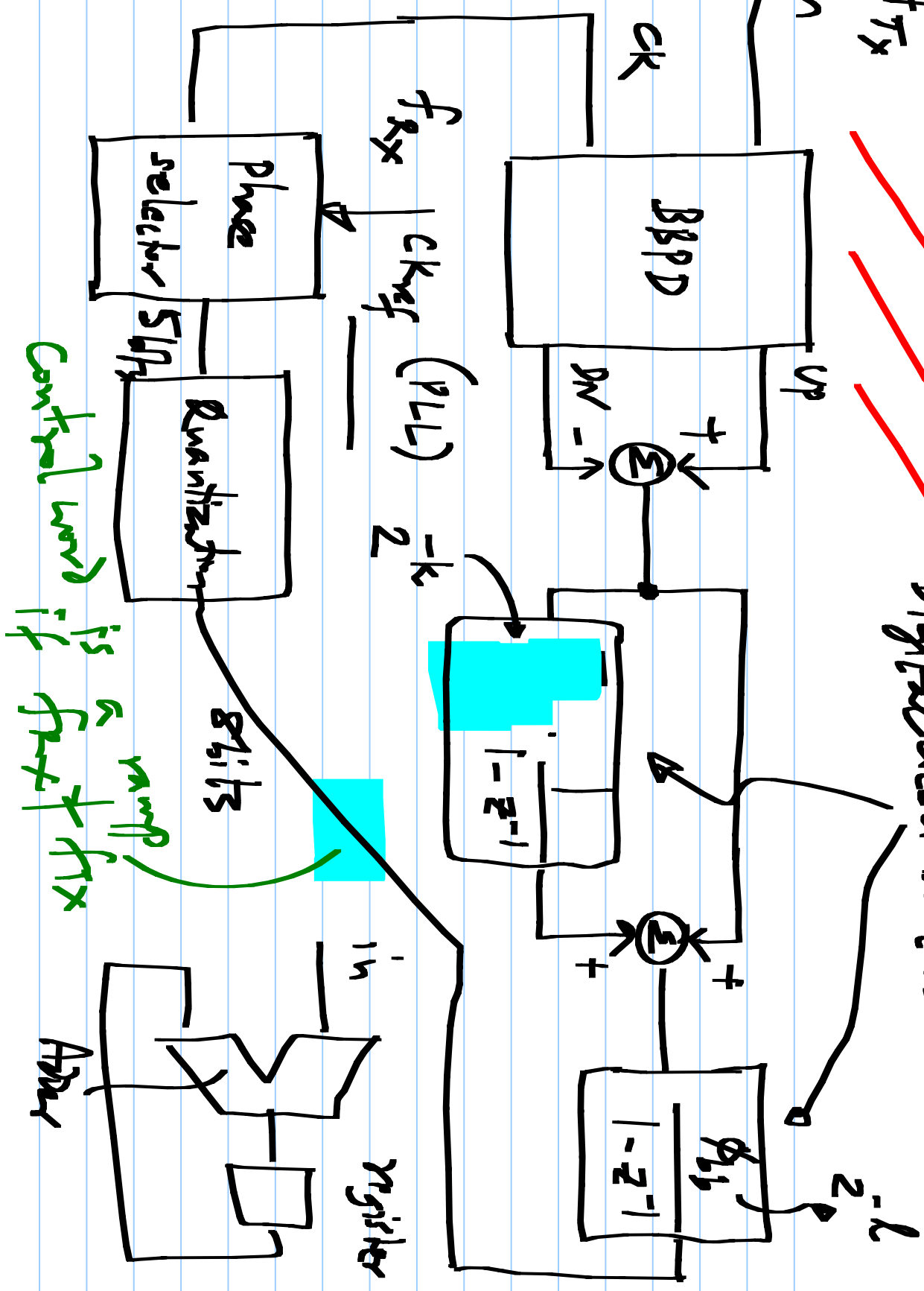



Control word is  $f_{TX} + f_{TX}$

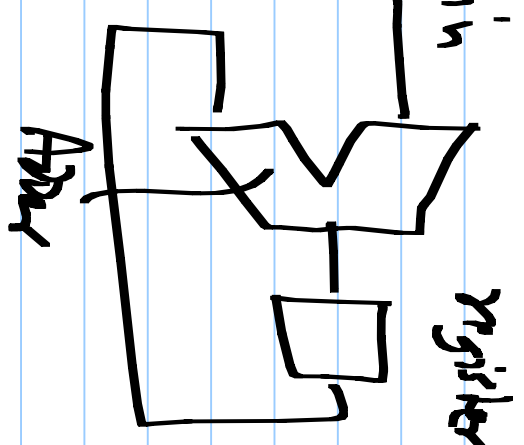

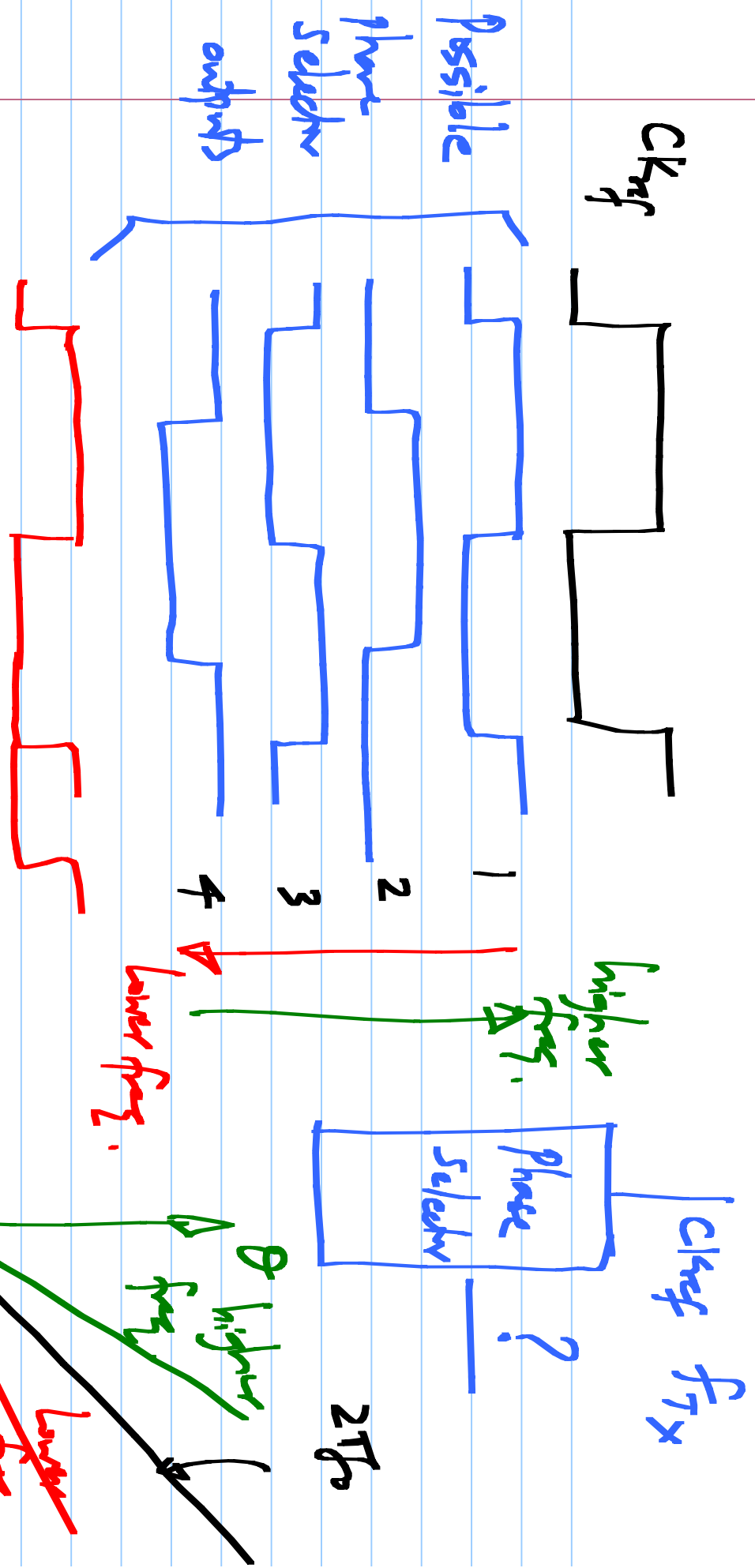

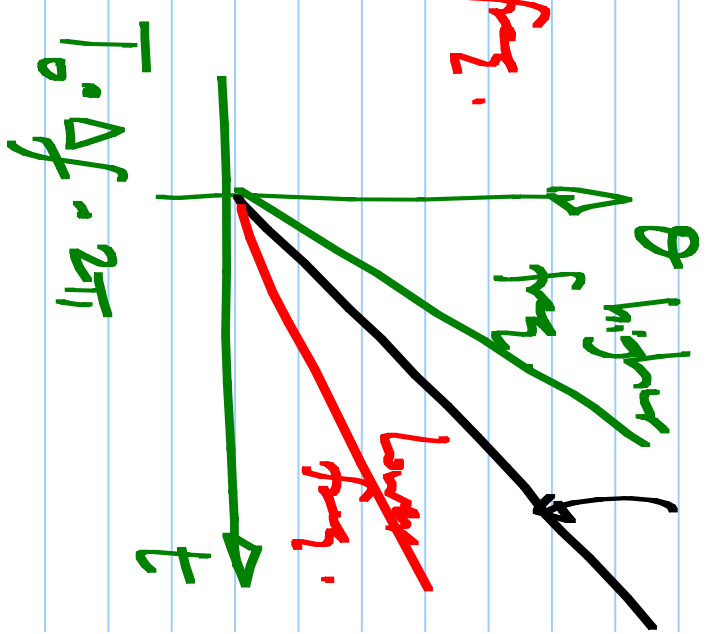
To synthesize a different frequency,  
 step through the phases.



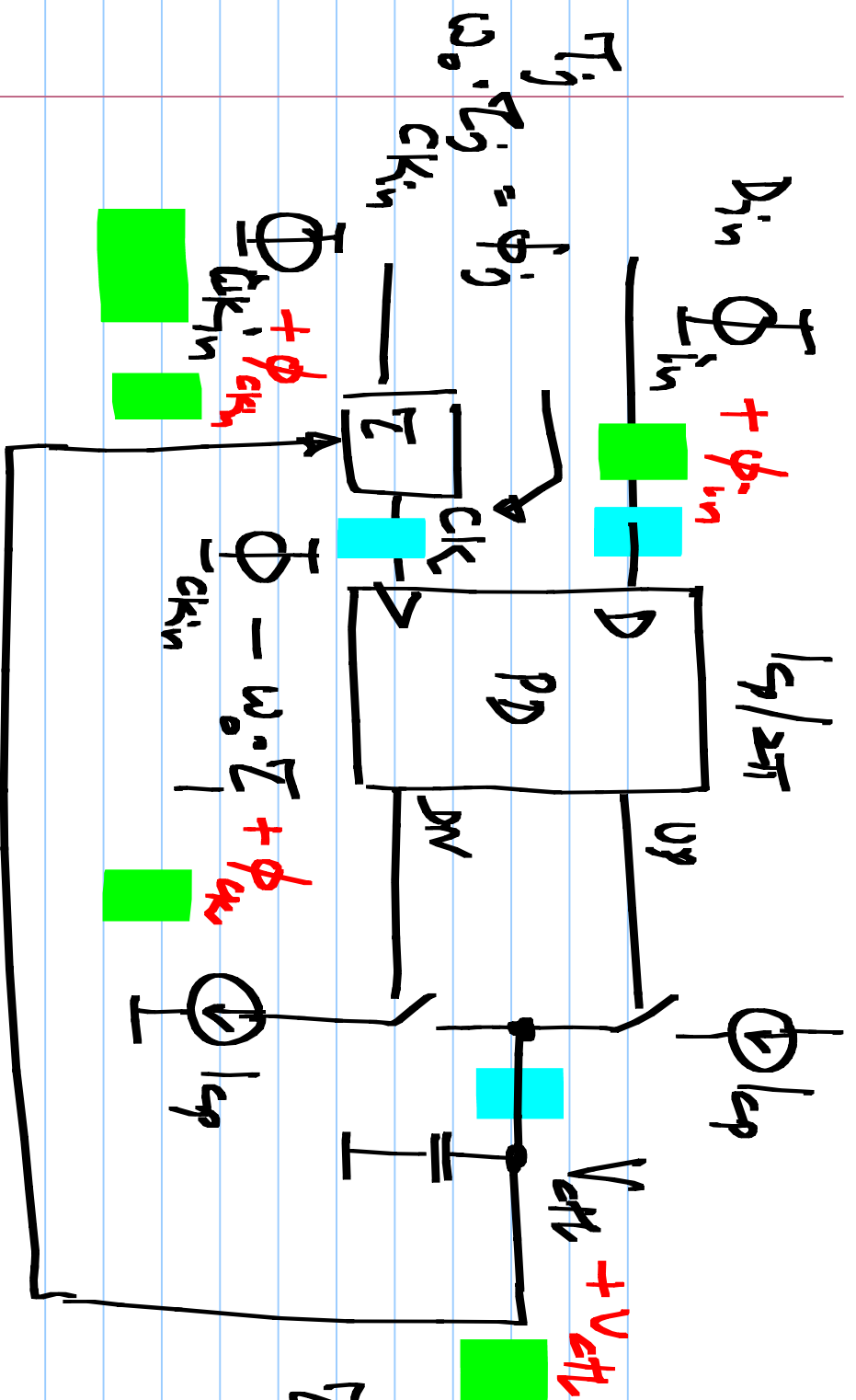

$$\underline{V = V_s - K_V \cdot V_{cth}}$$

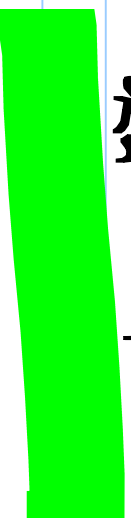② eq. point:  $\Phi_{ckin} - \omega_s T_j = \Phi_{in}$  (ck aligned to  $D_{in}$ )




$$D_{in} : \Phi_{in} + \phi_{in}$$

$$\text{Op. 9.1: } \Phi_{in} = \Phi_{ckin} - \omega_0 (T_0 - K_T \cdot V_{ch})$$

$$CK_{in} : \Phi_{ckin} + \phi_{ckin} \quad \omega_0 (T_0 - K_T \cdot V_{ch} - K_T \cdot V_{ch+1})$$

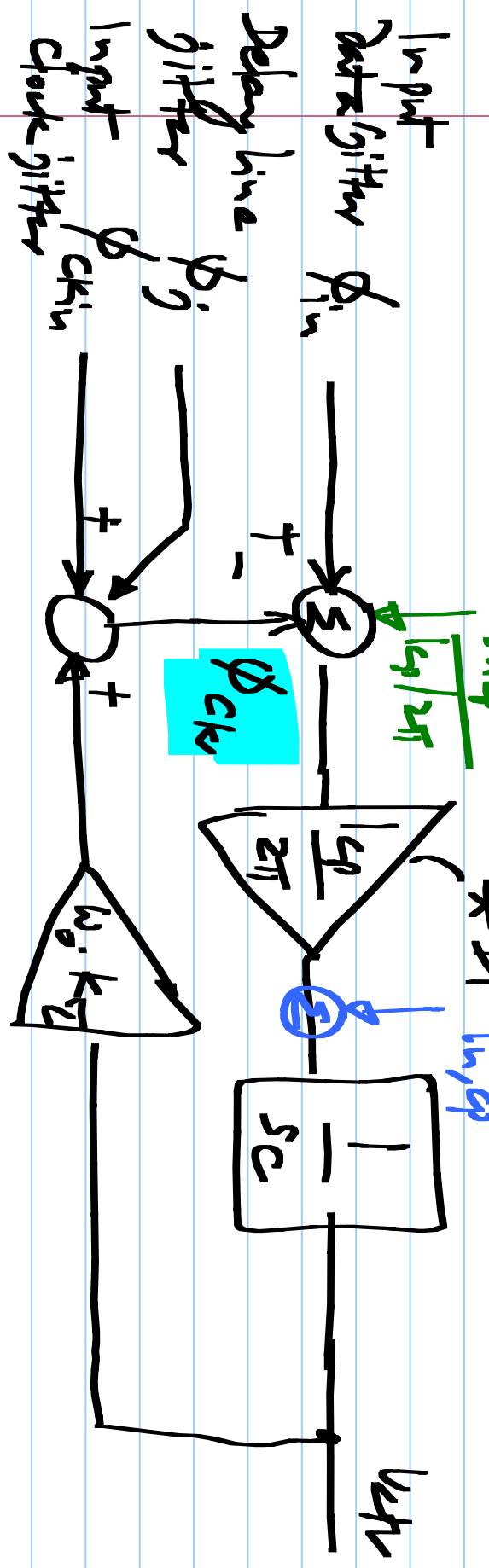
$$CK : \Phi_{ckin} + \phi_{ckin} - \omega_0 T$$



$$\underline{\text{STRAIN:}} \quad \frac{\phi_{ck}}{\phi_{in}} = \frac{L}{1+L} = \frac{1}{1 + \frac{s}{\omega_{yloop}}} \quad \omega_{yloop} = \frac{1}{2\pi} \frac{\omega_c K_c}{sC}$$

$$\underline{\text{TREN:}} \quad \left\{ \begin{array}{l} \frac{\phi_{ck}}{\phi_{cin}} = \phi_c \\ \frac{\phi_{ck}}{\phi_{ck}} = \frac{2\pi}{19} \frac{\phi_{ck}}{\phi_{in}} = \end{array} \right.$$

$$\underline{\text{JTDL:}} \quad \left| \phi_{in} - \phi_{ck} \right| < \phi_0 \quad \text{JTDL} = \frac{\phi_0}{\left| 1 - \frac{\phi_{ck}}{\phi_{in}} \right|} = \left| \phi_{in} \right| \left| 1 - \frac{\phi_{ck}}{\phi_{in}} \right| < \phi_0 \quad (\text{phase})$$

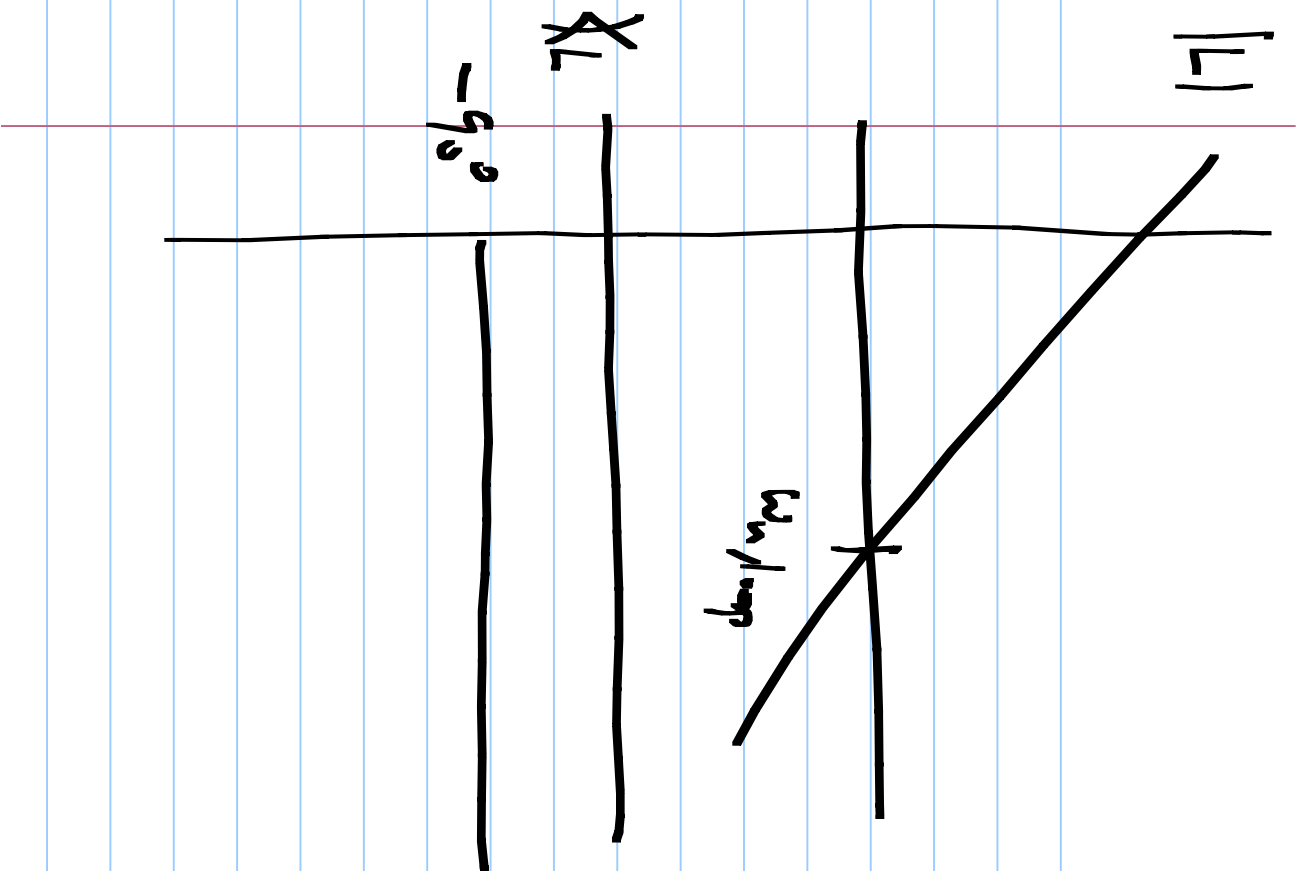

$$L(s) = \frac{1}{2\pi} \cdot \omega_0 k_T \cdot \frac{1}{sC}$$

$$\omega_{n/\text{amp}} = \frac{1}{2\pi} \frac{\omega_0 k_T}{C}$$

