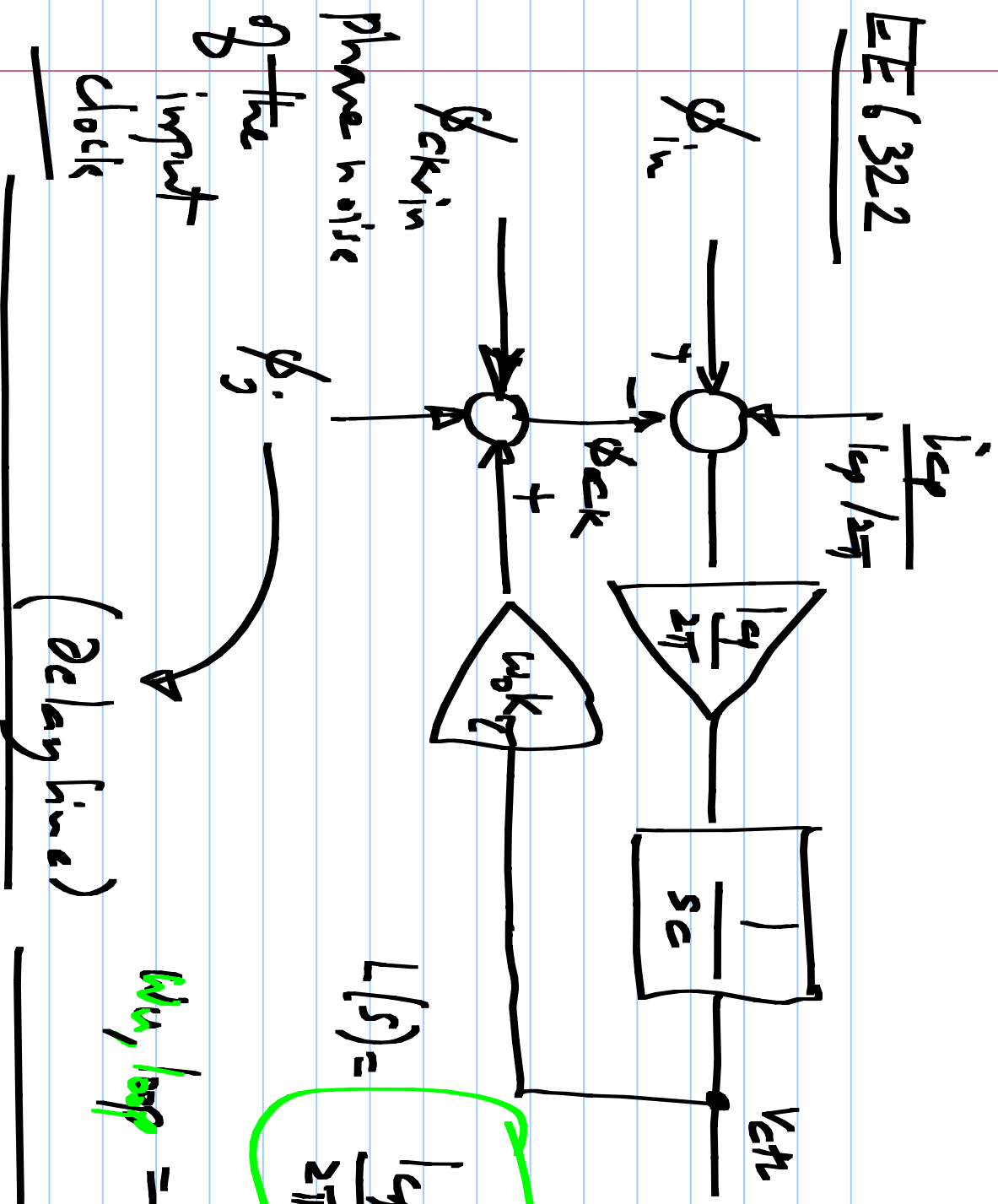


ECE 6322

5/3/2018



$$L(s) = \frac{1}{2\pi} \cdot \frac{\omega_k \tau}{s}$$

$$\omega_u, \omega_{loop} = \frac{1}{2\pi} \cdot \frac{\omega_k \tau}{c}$$

(delay line)

phase noise
of the
input
clock


$$\frac{\phi_{ck}}{\phi_{in}} = \frac{1}{1 + s/w_{n,loop}} = \frac{\phi_{ck}}{ig/(ig/2\pi)}$$

$$\frac{\phi_{ck}}{\phi_{kin}} = \frac{\phi_{ck}}{\phi_{in}} = \frac{s/w_{n,loop}}{1 + s/w_{n,loop}}$$

ТТЛ: $|\phi_{in} - \phi_{ck}| < \phi_0$ $|\phi_{in}| < \phi_0 \left(1 + \frac{w_{n,loop}}{s}\right)$

$$\left| \phi_{in} \left(1 - \frac{1}{1 + s/w_{n,loop}}\right) \right| < \phi_0$$

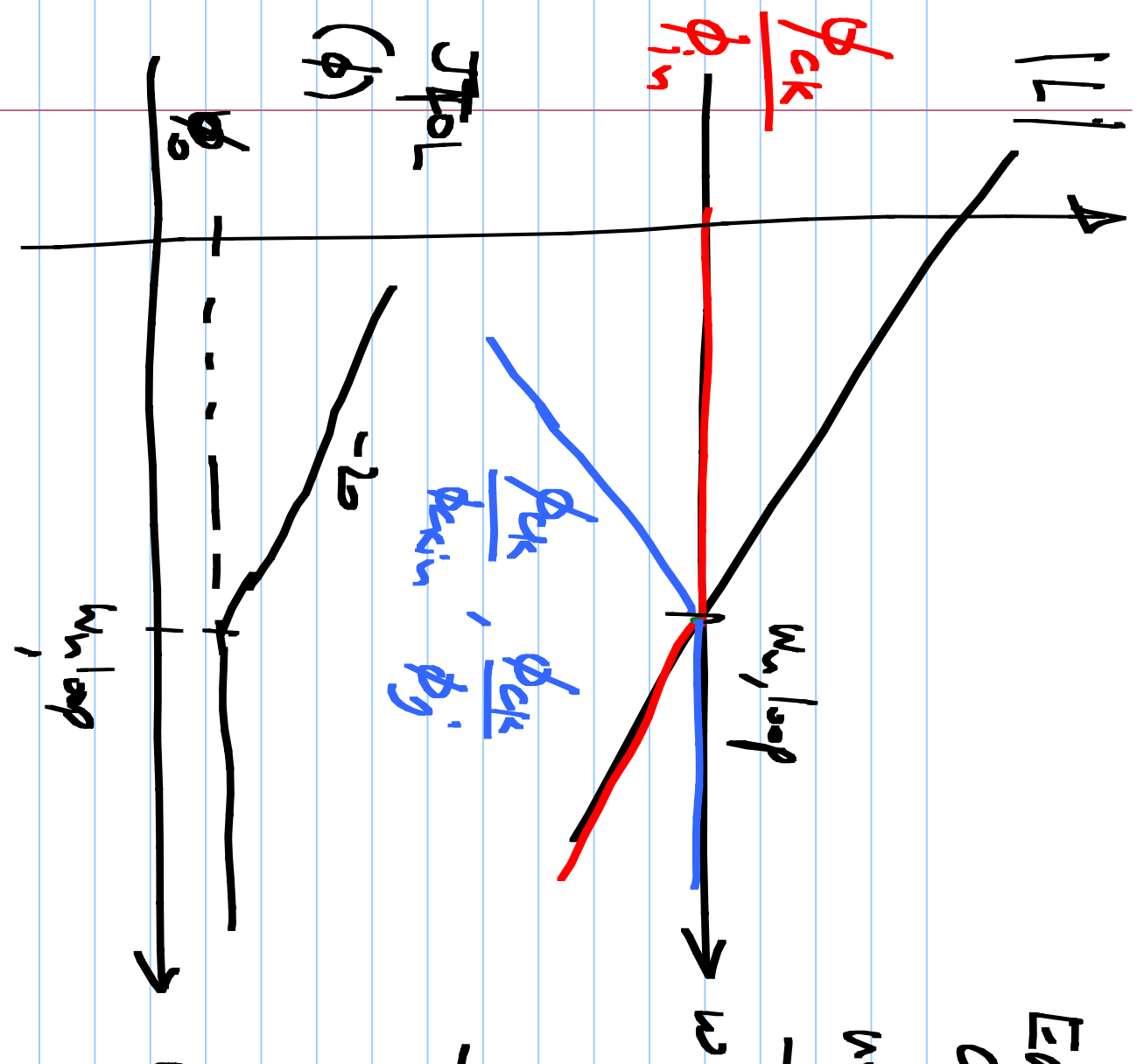Easier to satisfy stability constraint! (First order, unconditionally stable)




1/f² noise

(1/f³ @ low freq.)


1/f noise

constant (white)

(1/f @ low freq.)

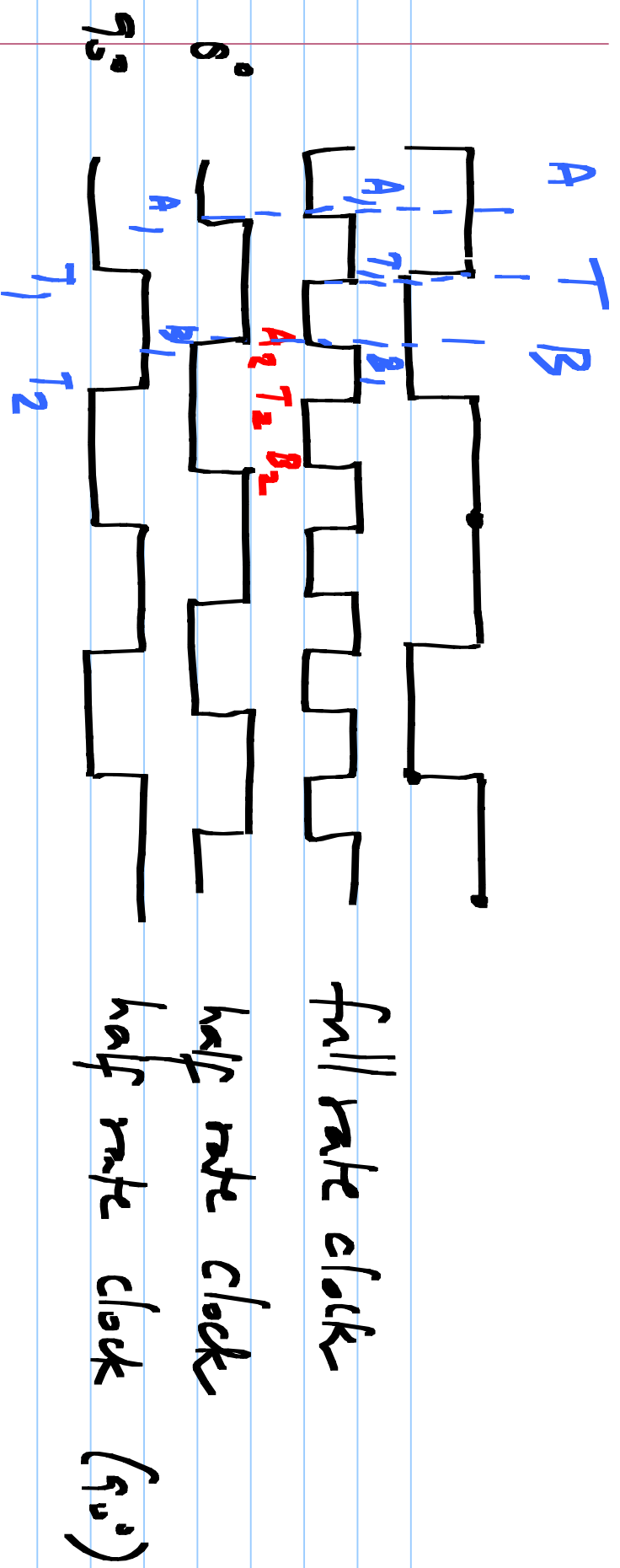

Power dissipation (FF, freq. divider)

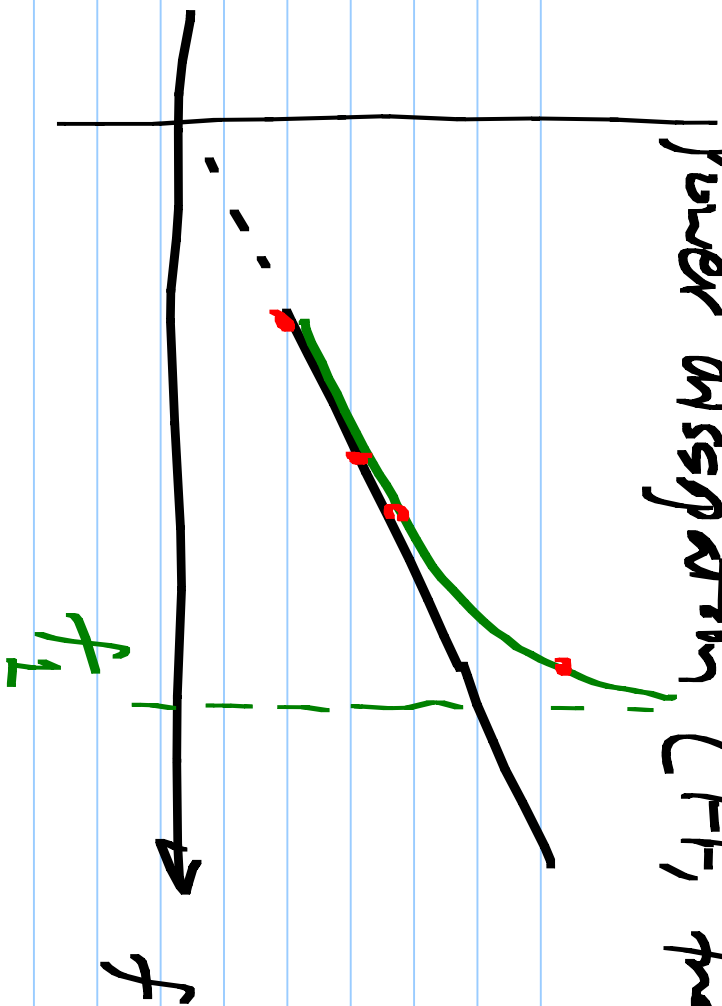


CK₉₀ Lays CK by 90° Retimes CK by 90° Retimes


A₁ & T₁ on CK₁₈₀

$$UP = A \oplus T$$

$$DN = B \oplus T$$

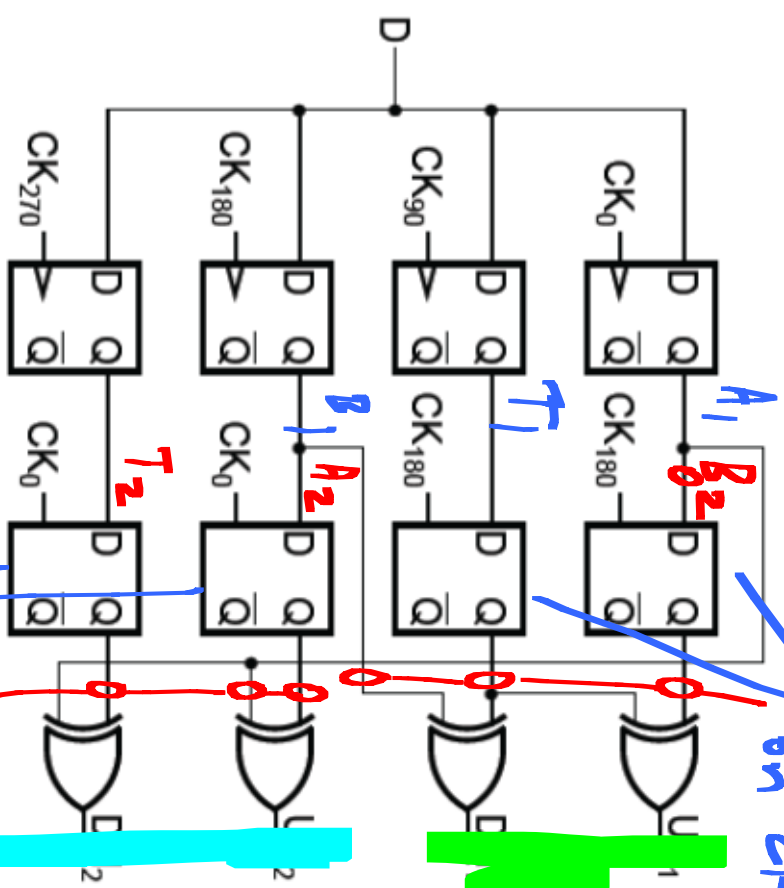

Retime A₂ & T₂ on CK₀

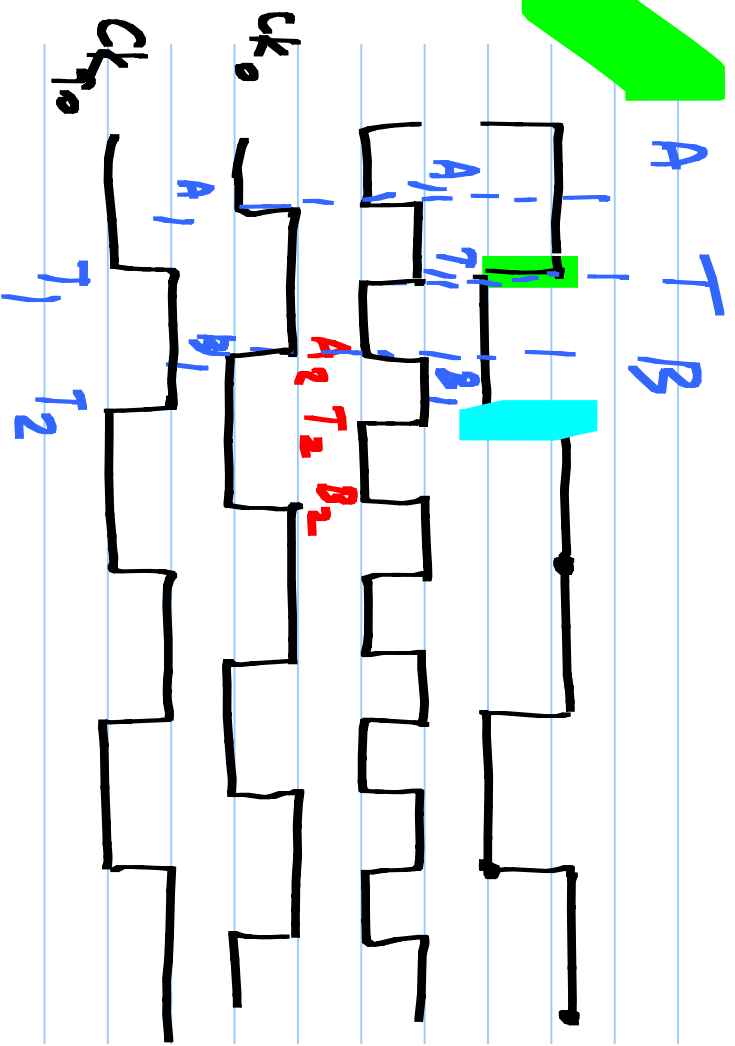

$$CK_{180} = CK_0$$

$$CK_{270} = CK_0$$

