



EE6322

Ring oscillators


To drive the

load w/o affecting the  $V_{DD}$

9/3/2018

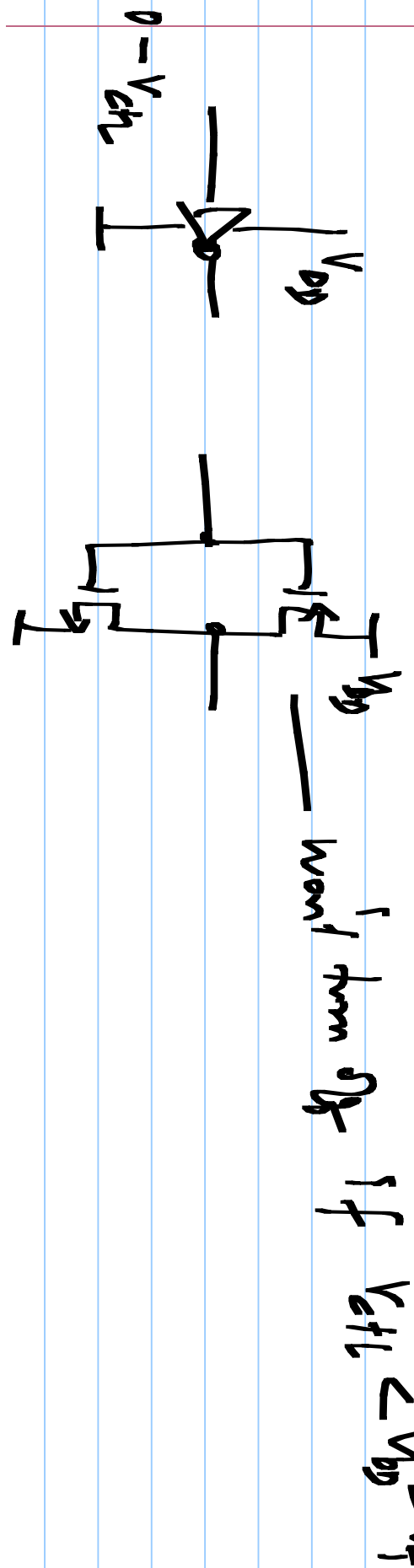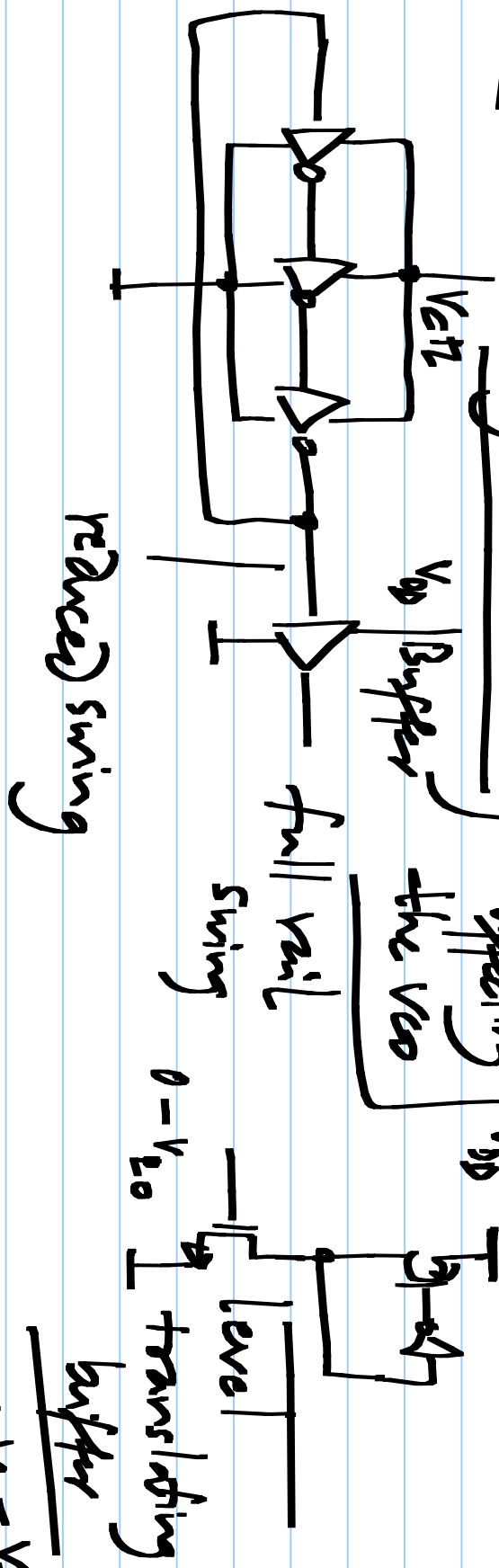

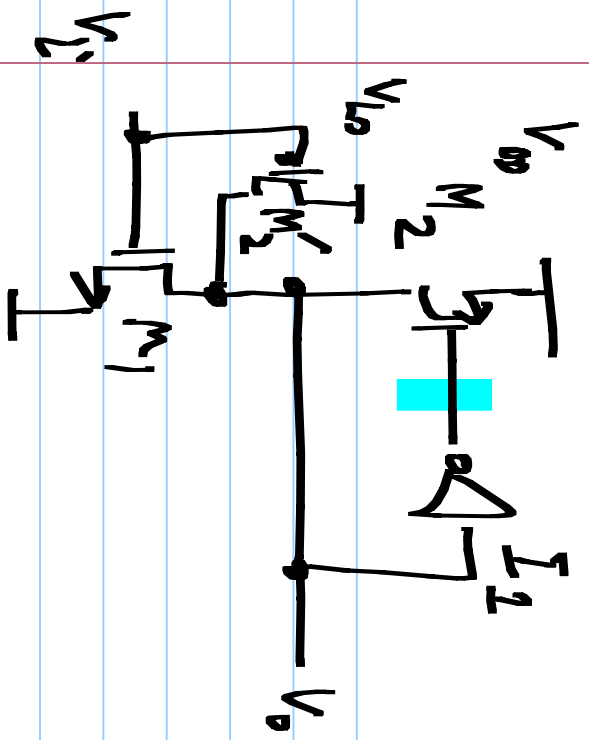won't turn off if  $V_{ch} < V_{DD} - V_T$





$V_0$  raised by  $M_2'$  to trigger  $I_1$

$V_1 = 0$  :  $M_1$  off,  $V_0 = V_{DD}$

$V_1 = V_{Ls}$  :  $V_0$  lowered sufficiently to trigger  $I_1$ ,  $M_2$  turns off

$V_1 = 0$

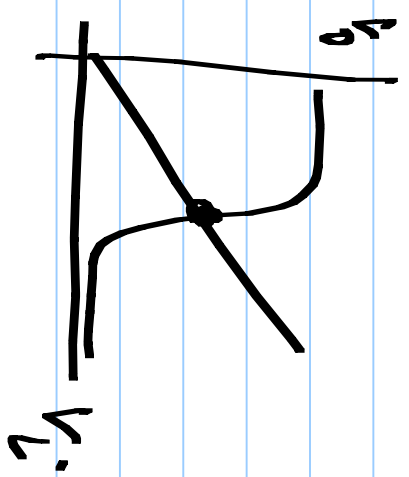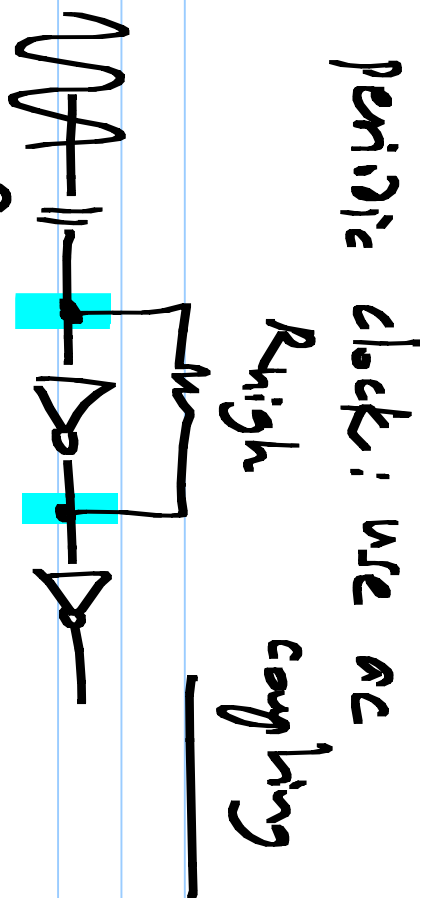


$$S_{\phi}(f) = \frac{8}{3} \frac{f_0^2}{(V_{GS} - V_T) I_p f^2}$$

$$\frac{P_d}{(S/N)(18W)} \propto kT$$

Phase noise of (an ideal model of) a ring oscillator

Figure of merit:  $10 \log$
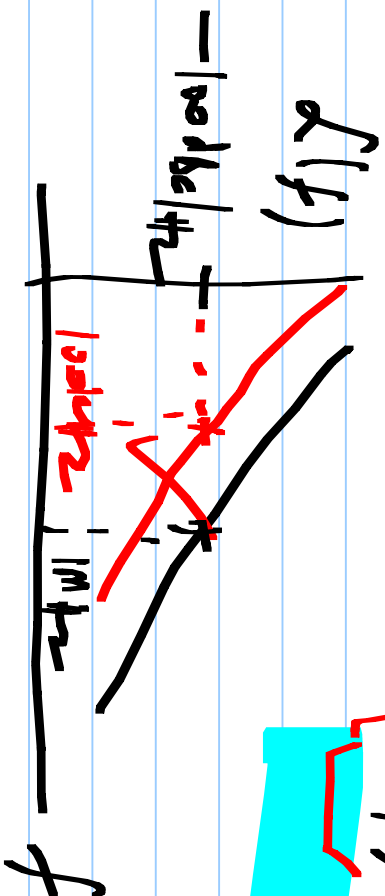
$$\left[ \frac{1}{\alpha(f)} \cdot f_0^2 \cdot \frac{1}{f^2} \cdot P_d \text{ (mW)} \right]$$



$$\checkmark \text{FOM} = \frac{3}{8} \frac{1}{kT} \frac{V_{GS} - V_T}{V_{DD}} 10^{-3}$$

10mW, 10GHz,  $\alpha(f)$  @  $f = 1\text{MHz}$  offset

$$V_{d1} = 1.2\text{V} ; V_{GS} - V_T = 0.3\text{V}$$

$$S_{\phi}(f) = \frac{8}{3} \frac{kT}{(V_{GS} - V_T) I_p} \frac{f_0^2}{f^2}$$

$$\underline{F_{0M} = 168 \text{ dB} = 10 \log \left( \frac{1}{S(f)} \left( \frac{f_0}{f} \right)^2 \cdot \frac{1}{P_d(\text{mW})} \right)}$$

$$168 \text{ dB} = 10 \log_{10} \left( \frac{1}{S(f)} \cdot \left( \frac{10^6 \text{ Hz}}{1 \text{ MHz}} \right)^2 \cdot \frac{1}{10} \right)$$

$$80 - 10$$

$$S(f) = (-168 + 70) \text{ dBc/Hz} @ f = 1 \text{ MHz}$$

$$-98 \text{ dBc/Hz} @ f = 1 \text{ MHz}$$

$$3 \quad | \quad \frac{V_{RS} - V_f}{10^{-3}}$$
$$\sqrt{\frac{32}{k_T}} \cdot \frac{V_{RS} - V_f}{V_D}$$

$$| \quad | \quad |$$
$$| \quad \frac{1}{4 \cdot 10^{-2}} \quad | \quad | \quad |$$
$$| \quad 4 \quad | \quad | \quad |$$

$$\alpha(f) \propto \underbrace{\frac{1}{f^2} \cdot \frac{f_0^2}{f^2}}_{F_{2M}} =$$

# LC oscillators:

