

EE322

12/3/2018

$$t_d = \frac{CV_{dd}}{2I_p}$$

Single stage delay

$$T_0 = \frac{MCV_{dd}}{I_p}$$

Oscillation period

$$f_0 = \frac{2I_p}{MCV_{dd}}$$

Oscillation frequency

$$P_1 = C V_{dd}^2 f_0$$

Power dissipation per stage

$$P_d = M C V_{dd}^2 f_0$$

Total power dissipation

$$I_d = M C V_{dd} f_0$$

Total current drawn from V_{dd}

$$S_0 = \frac{4}{3} kT g_m$$

$$= \frac{16}{3} kT \frac{I_p}{V_{GS} - V_T}$$

$$\sigma_{\Delta t d}^2 = \frac{8}{3} \frac{kTCV_{dd}}{(V_{GS} - V_T)I_p^2}$$

Variance of stage delay

Period jitter

$$\sigma_{\tau 0}^2 = \cancel{\frac{4}{3}} \frac{kTMCV_{dd}}{(V_{GS} - V_T)I_p^2}$$

$$S_{\tau 0}(f) = \frac{8}{3} \frac{kTMCV_{dd}}{(V_{GS} - V_T)I_p^2 f_0}$$

Spectral density of period jitter

$$S_\phi(f) = \frac{8}{3} \frac{kT}{(V_{GS} - V_T)I_p} \frac{f_0^2}{f^2}$$

Spectral density of phase
(double-sided)

g_m ill defined, but still . . .

$V_{GS} - V_T$ not fixed, but still . . .

$$S_\phi(f) = \frac{2}{3} \frac{kT}{(V_{GS} - V_T)I_p} \frac{f_0^2}{f^2}$$

Spectral density of phase

$$\mathcal{L}(f) = \frac{228}{3} \frac{kT}{(V_{GS} - V_T)I_p} \frac{f_0^2}{f^2}$$

Phase noise, $f > 0$

$14dB$

$$FOM = \frac{3}{32} \frac{1}{kT} \frac{V_{GS} - V_T}{V_{dd}} 10^{-3}$$

Figure of merit

10^{-8}

$$\frac{V_{GS} - V_T}{V_{dd}} = \frac{1}{4} \cdot \frac{3}{8} \cdot \frac{1}{4} \cdot \frac{-1}{10} = -5dB$$

$$-2 \left| \frac{d\beta}{d\delta} \right| \geq 128 \quad \left| \frac{d\beta}{d\delta} \right| \leq 64$$

Variation [capacitance depends on the fine tuning.] DC voltage across them]

connection


+ - reverse
bias on
varactor


+ - reverse
bias on
varactor


M₁ diff pair
connected on


a resistance


ρ in junction
varactor

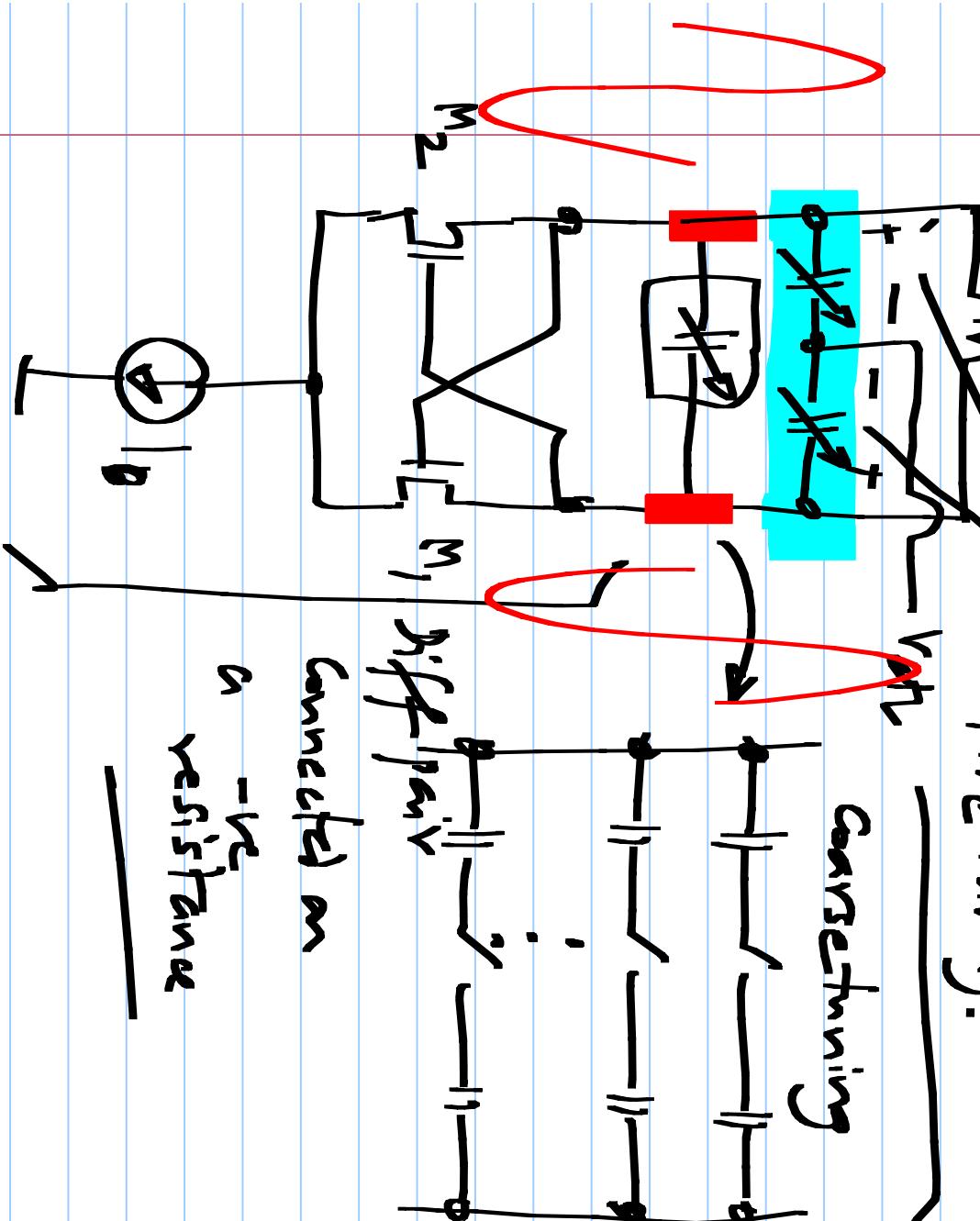


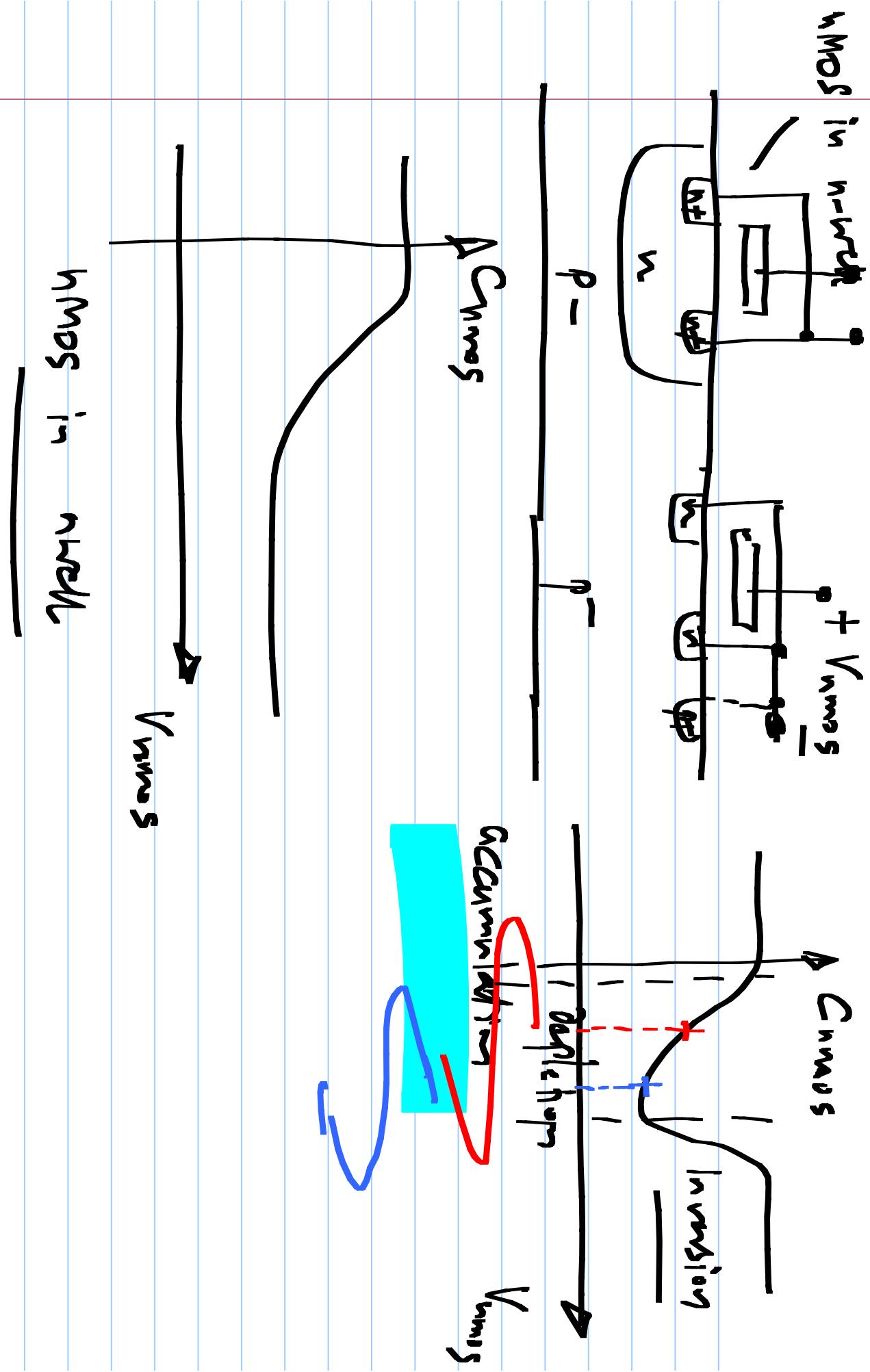


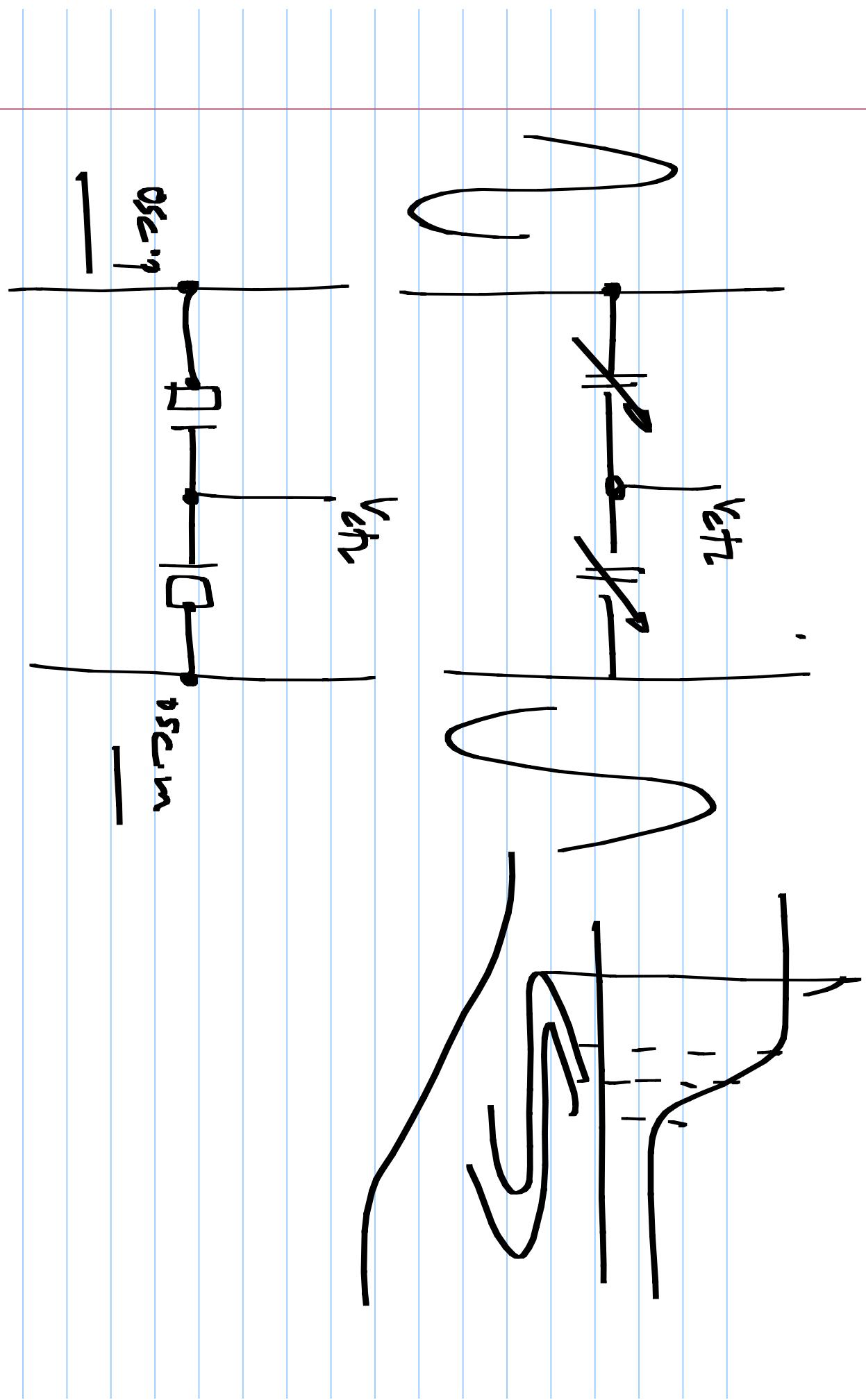

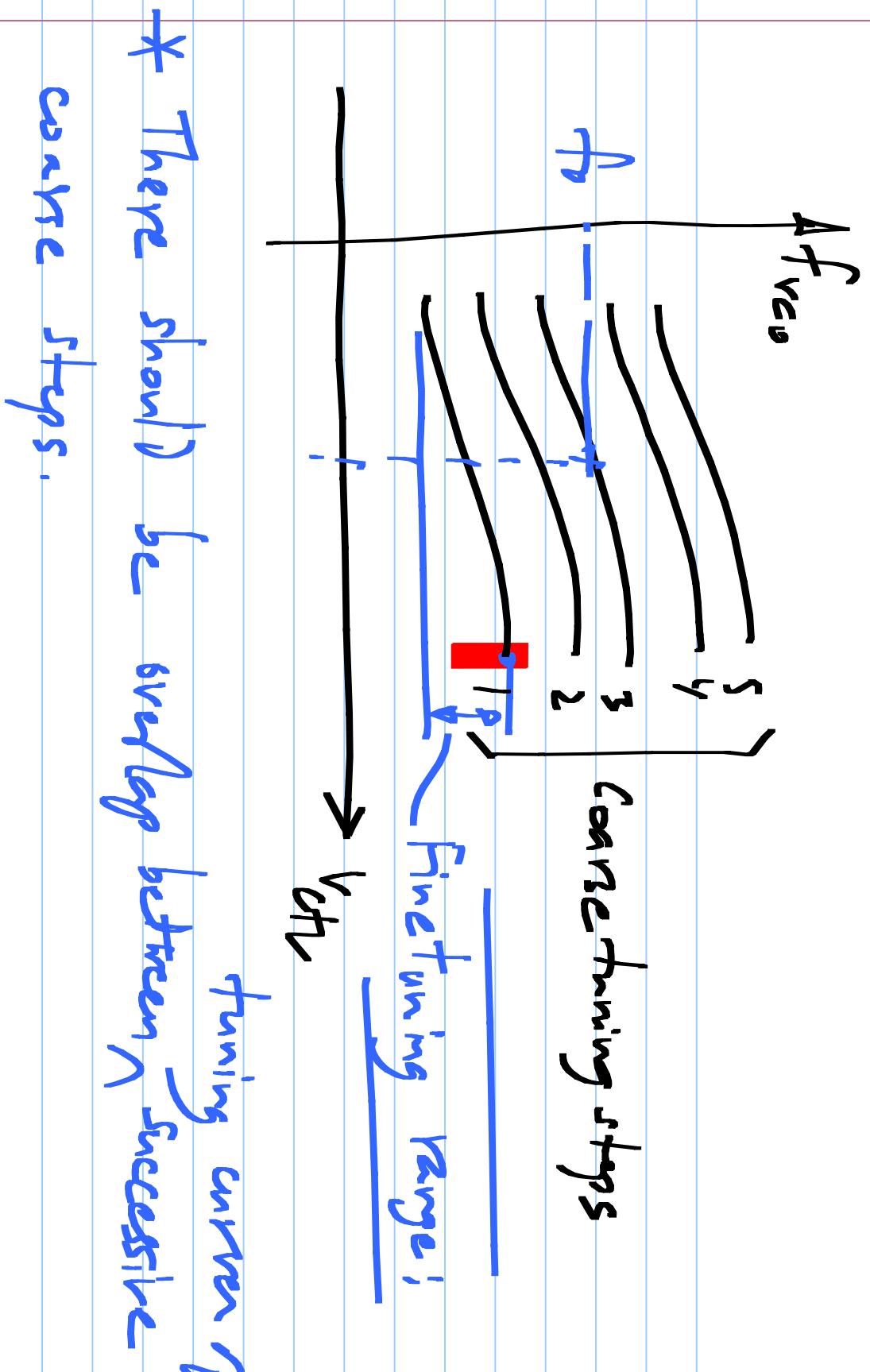


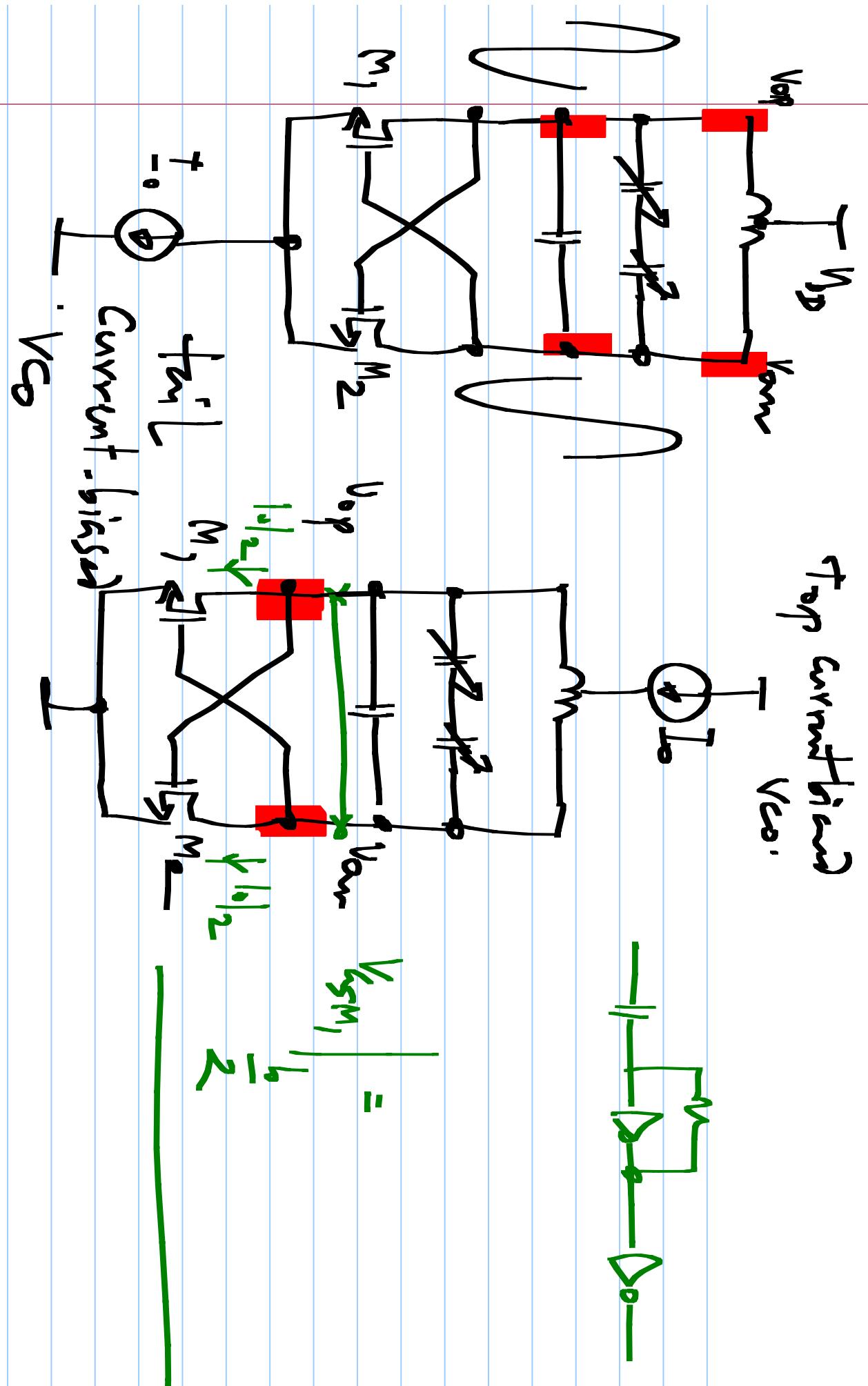

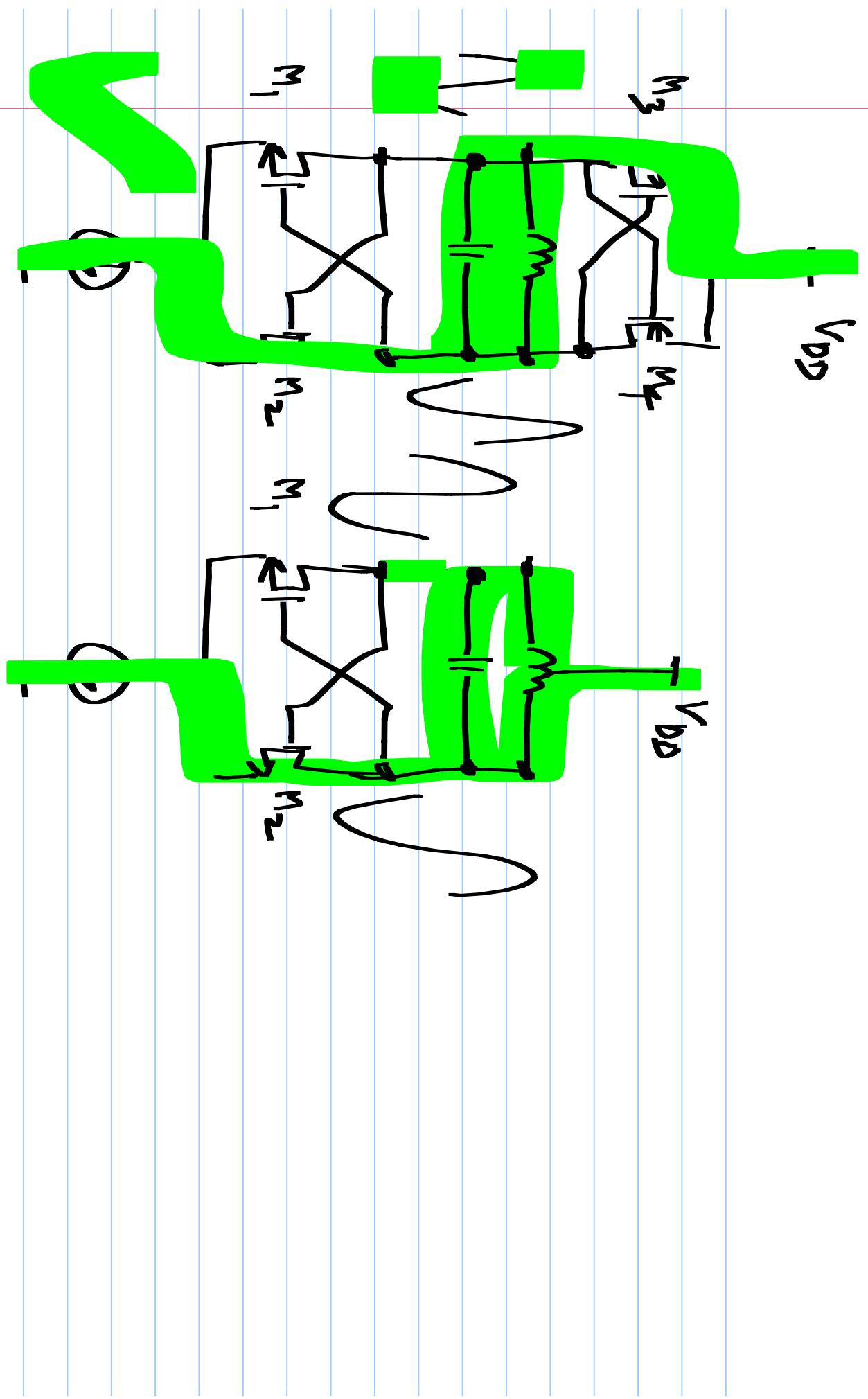

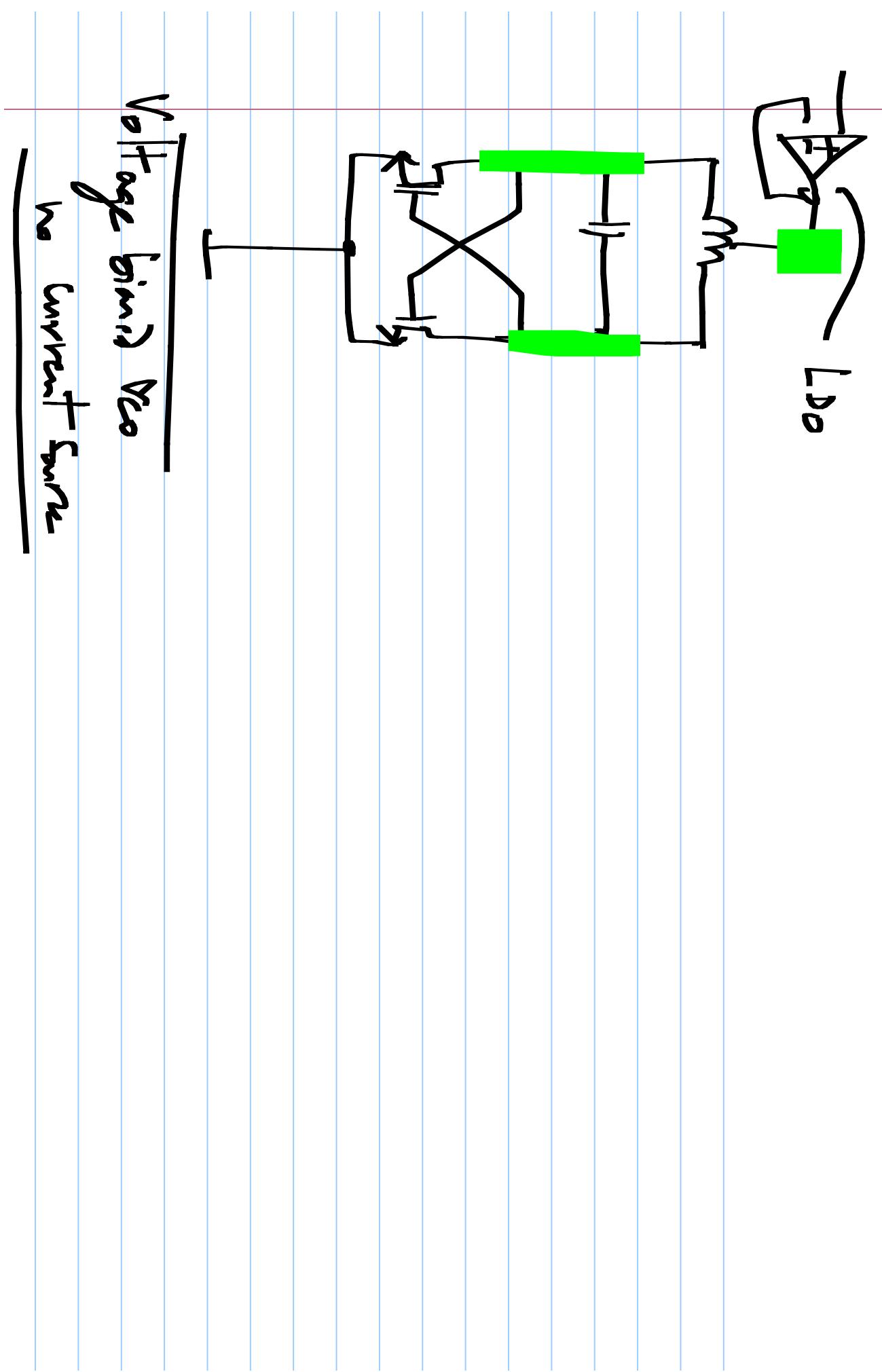

ideal linear LC oscillator

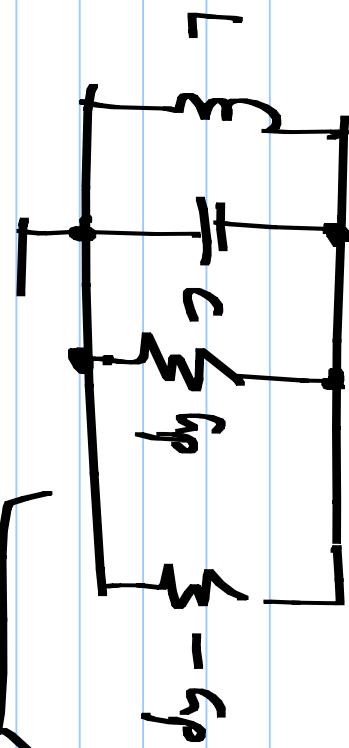

Lessons' phase model

negative less

