

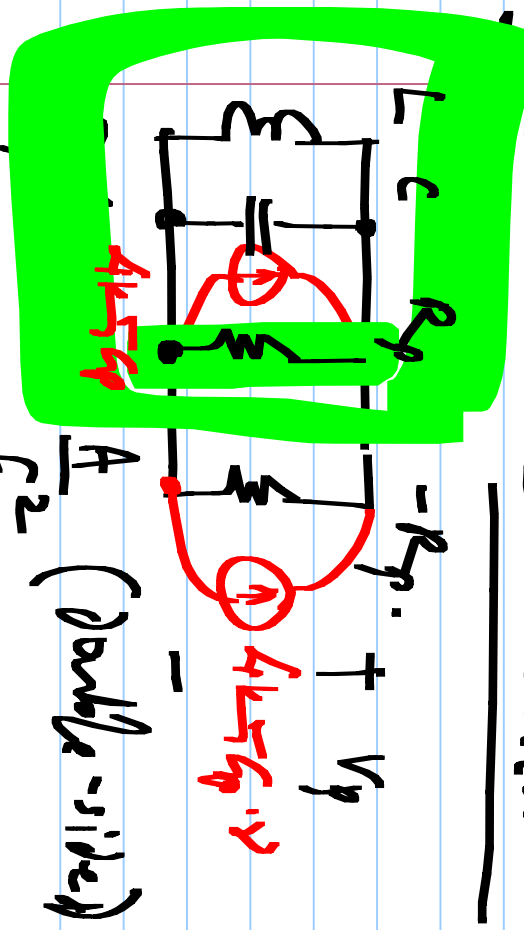
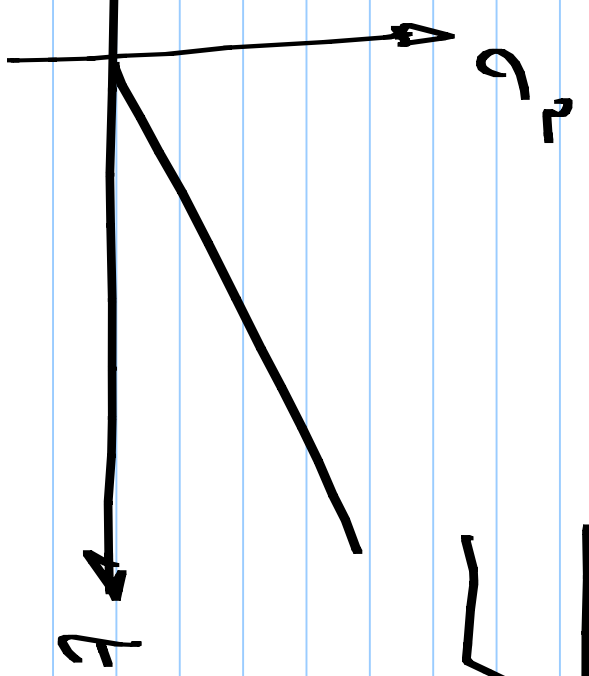


EE6322 LC oscillators

13/3/2018

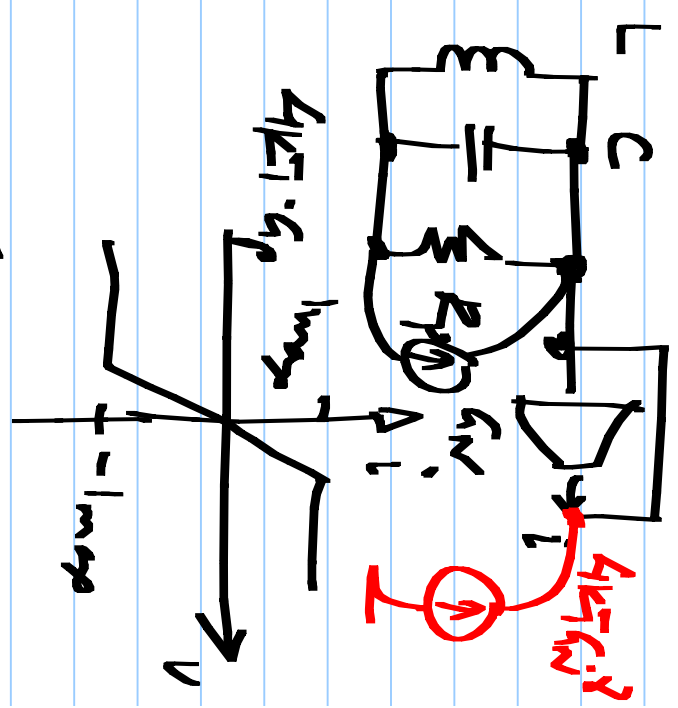

$$L(f) = \frac{A}{f^2} \quad (f > 0)$$

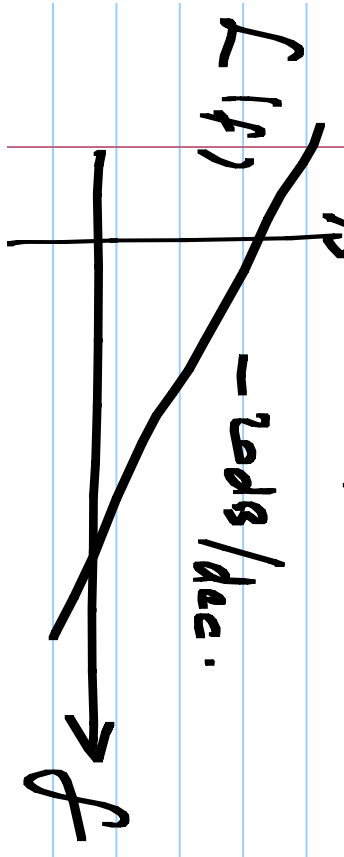

offset freq. Loss resistance (the tank which has to be compensated)

$$L(\Delta f) = \frac{KT(1+\gamma) f_0^2}{Q^2 \Delta f^2}$$

$$P_d = \frac{V_p^2}{2R_p}$$

power dissipated in the tank

$$FOM = \frac{1}{L(\Delta f) P_{d,mW} \Delta f^2} = \frac{2 Q^2}{KT(1+\gamma) 10^{-3} \Delta f^2}$$

$$L(\Delta f) = \frac{KT(1+\gamma) f_0^2}{2 Q^2 P_d \Delta f^2}$$

$$L(\Delta f) = \frac{8}{3} \frac{KT \cdot V_{DD} \cdot f_0^2}{(V_{GS} - V_T) \cdot I_{P,DD} \Delta f^2}$$

LC oscillator:

$$\frac{1}{2} \cdot kT \cdot (1+\gamma) \cdot \frac{1}{Q^2} \cdot \frac{f^2}{\Delta f^2} \quad \frac{2}{4 \cdot 10^{-2}} \cdot \frac{10^2}{2 \cdot 10^{-3}}$$

Ring oscillator:

$$\frac{8}{3} kT \cdot \frac{1}{Q^2} \cdot \frac{V_{DD}}{V_{GS} - V_T} \cdot \frac{f^2}{\Delta f^2} \quad \frac{1}{4} \cdot 10^{20} \checkmark$$

$Q=10$ $\gamma=1$


F_{oM} (LC)

$$= \frac{2}{kT} \frac{Q^2}{1+\gamma} \cdot 10^{-3} \quad \underline{194 \text{ dB}}$$

F_{oM} (Ring)

$$= \frac{3}{8} \cdot \frac{1}{kT} \cdot \frac{V_{GS} - V_T}{V_{DD}} \cdot 10^{-3}$$
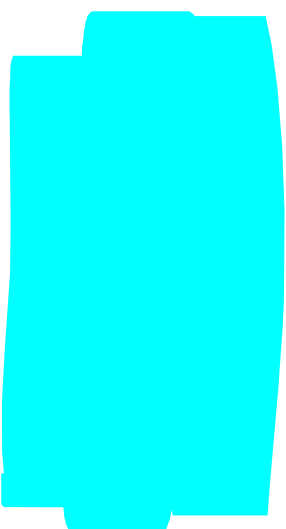
$$L(\Delta f) = \frac{kTR_p(1 + \gamma + \beta) f_0^2}{V_p^2 Q^2} \frac{f_0^2}{\Delta f^2}$$




$$P_d = \frac{P_{rank}}{\eta} \quad \eta : \text{Efficiency}$$

$$FOM = \frac{2}{kT} \frac{\eta Q^2}{1 + \gamma + \beta} 10^{-3}$$





$$4kT \cdot G_N (\gamma + \beta)$$

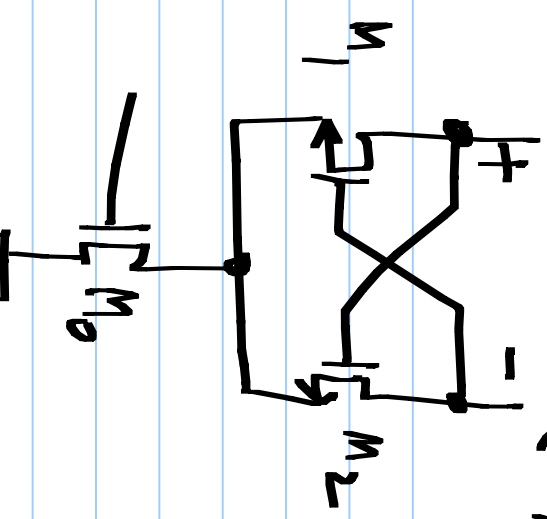

$$G_N = g_{m1} / 2$$

Quartz crystal :
Piezoelectric :

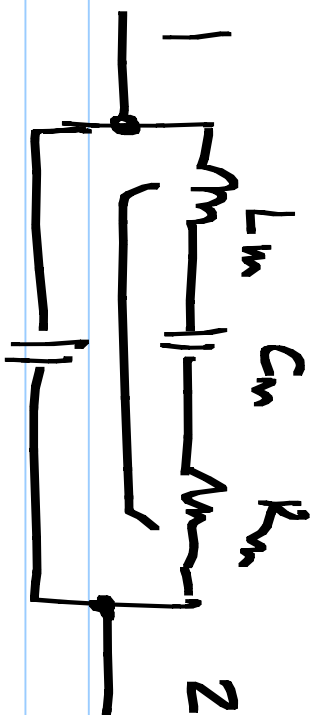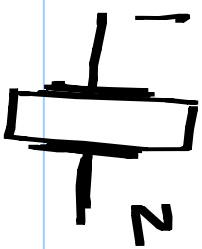

Q : Very high

Low temp. coefficient

Quartz crystal oscillator :

Low phase noise

$f_0 < 100\text{MHz}$

Accurate freq. with low temp. coefficient

Freq. multiplier


N

$N \cdot f_{\text{crystal}}$


Phase locked loop

CLK w/o forward clock:

Track D_{in} & recover its value

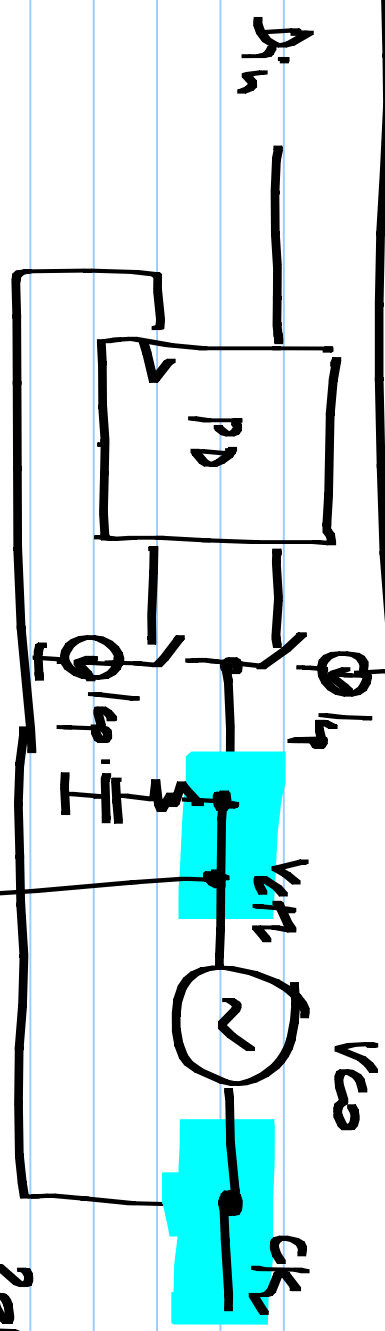

Phase-locked loop

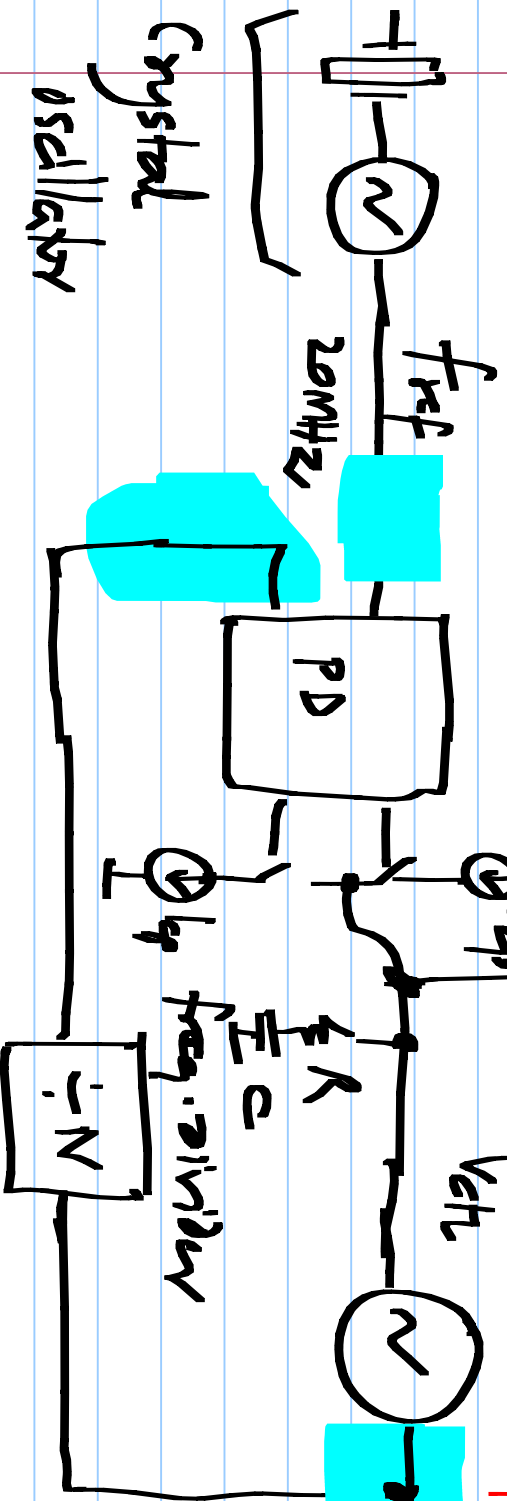

Crystal oscillator

$\frac{20\text{MHz} \times 500}{10\text{kHz}}$

generate a periodic signal
in state
for steady

