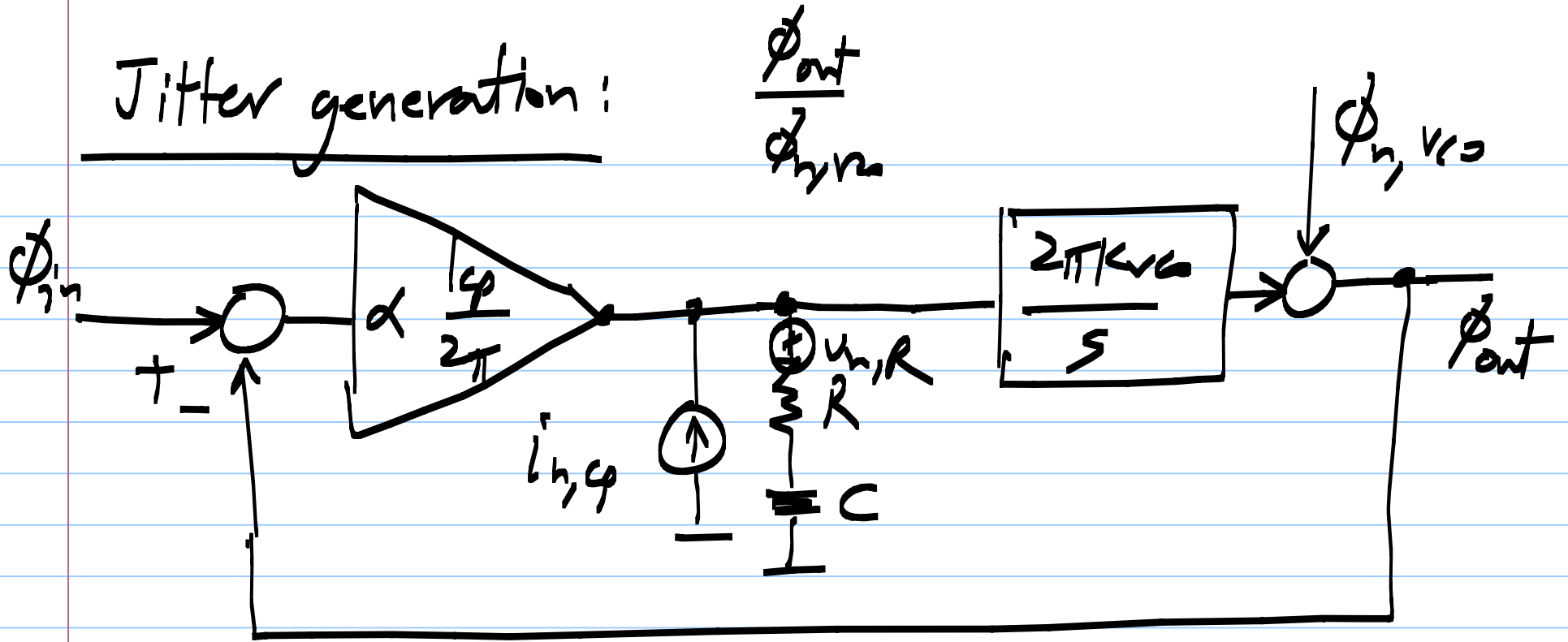


Jitter generation:



$$L(s) = \frac{\alpha \cdot I_C R K_{VCO}}{s} \left(1 + \frac{1}{sCR} \right) = \frac{\omega_n}{s} \left(1 + \frac{z_1}{s} \right)$$

ϕ_{out}

$=$

$$\frac{s^2}{\omega_n z_1}$$

$=$


$$\frac{1}{1+L}$$

$$1 + \frac{s}{z_1} + \frac{s^2}{\omega_n z_1}$$

$$1+L$$

$\phi_{n,v6}$

$|L|$

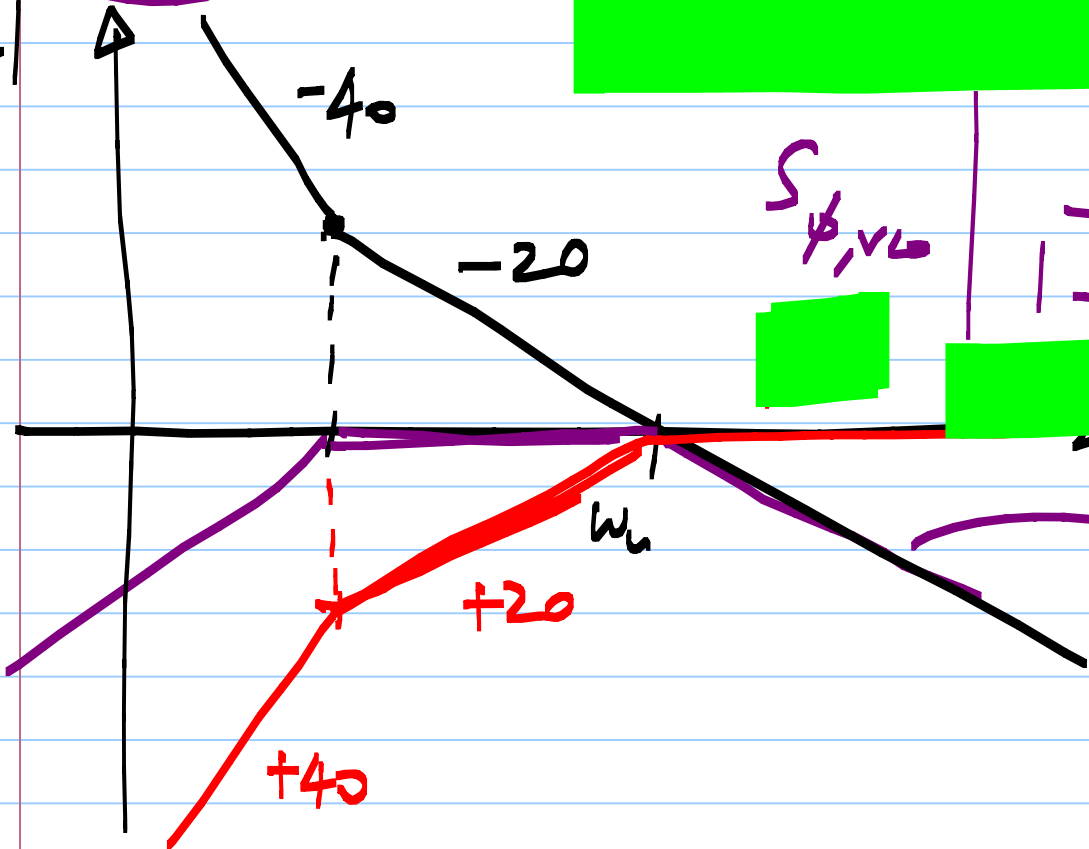

$\phi_{n,v6}$

$$\frac{s^2}{\omega_n z_1} \left(1 + \frac{s}{z_1} + \frac{s^2}{\omega_n z_1} \right)^{-2}$$

$$1 + \frac{s}{z_1} + \frac{s^2}{\omega_n z_1}$$


$$\frac{\phi_{out}}{v_{in,R}} = \frac{\phi_{out}}{\phi_{in,v_{in}}} \cdot \frac{2\pi K v_{in}}{s} =$$

$$\frac{2\pi K v_{in}}{s} \cdot \frac{2\pi}{\alpha l_{GR}} \cdot \frac{s/z_1}{1 + \frac{s}{z_1} + \frac{s^2}{\omega_n^2 z_1^2}} =$$

$$\alpha l_{GR} \cdot K v_{in}$$



$$S_{\phi, out} = 4KTR \cdot \left(\frac{2\pi}{\alpha l_{GR}} \right)^2 \cdot \left| \frac{s/z_1}{1 + s/z_1 + \frac{s^2}{\omega_n^2 z_1^2}} \right|^2$$


Oscillators:

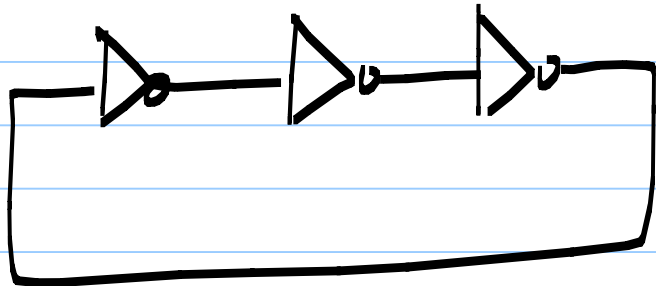


Ring oscillator

Leeson C $R_p^{(G_p)}$ $-G_N$

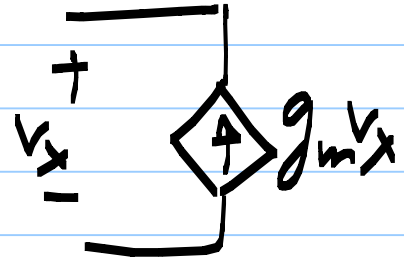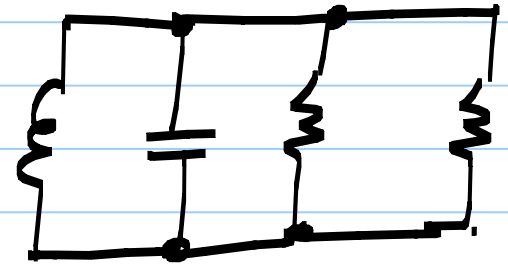

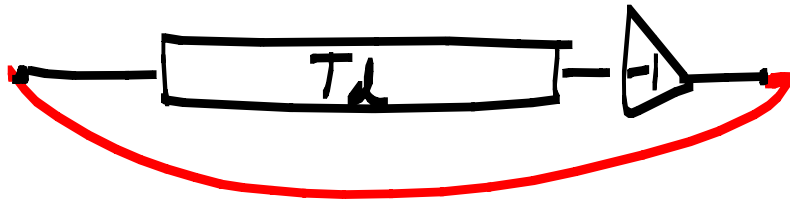


$$Z[1] = \frac{V_n[0]}{R}$$

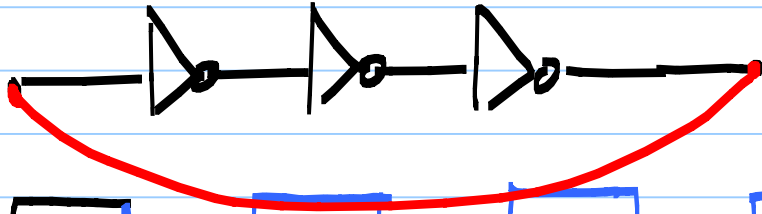

$$Z[2] = \frac{V_n[T_0/2]}{R} \quad \text{noiseless; } 2T_0$$



$$f_{osc} = 1/2T_d$$

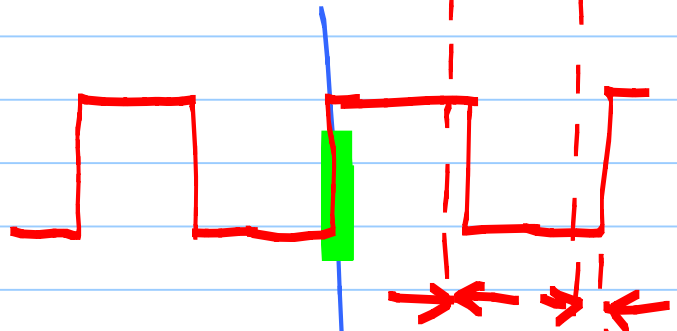


k^{th} edge will be displaced
by $\sum_{n=0}^{k-1} Z[n]$


$$Z[1] + Z[2]$$




$$= \sum_{n=0}^{k-1} \frac{V_n[k]}{R}$$

$$V_n[k]$$

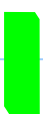

$t=0$


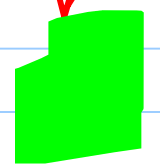


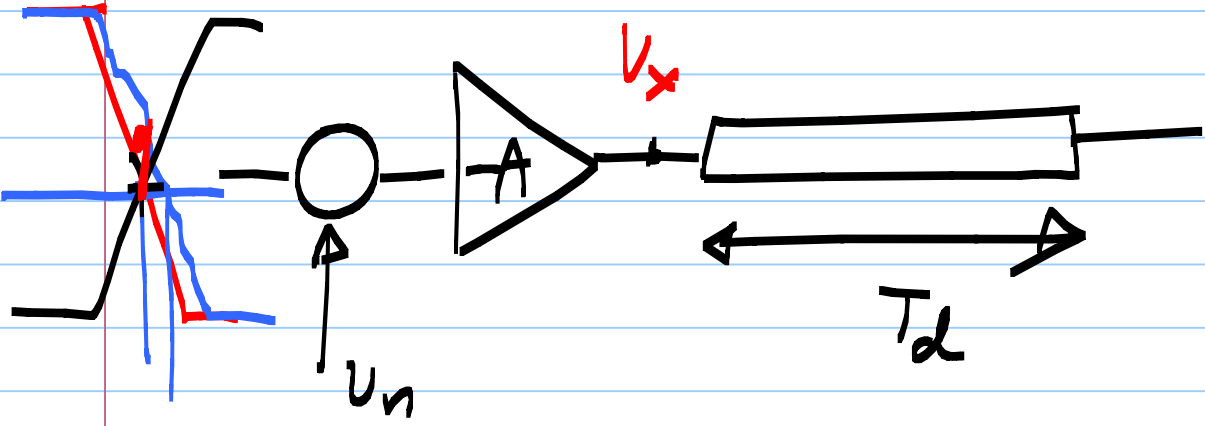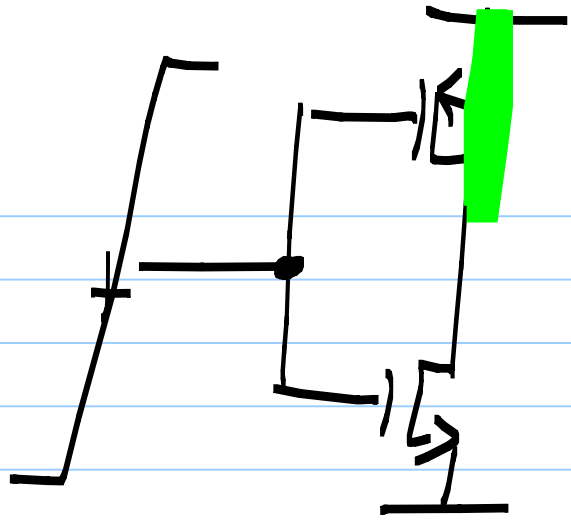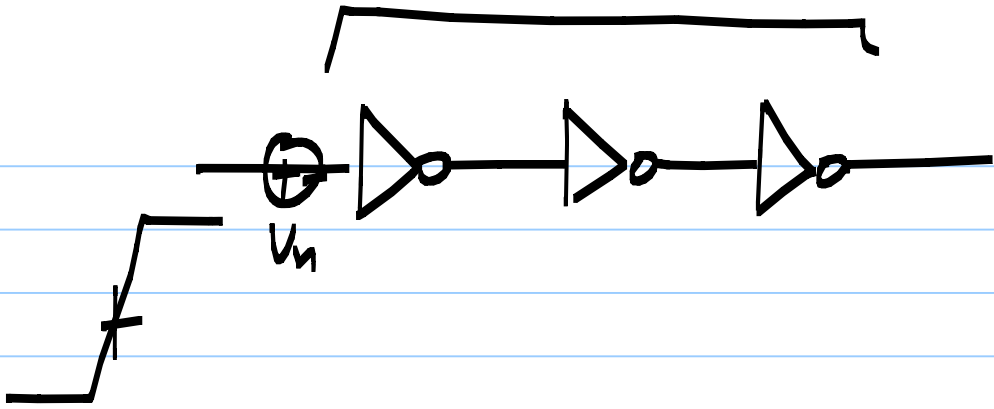

out ref noise

slope: R



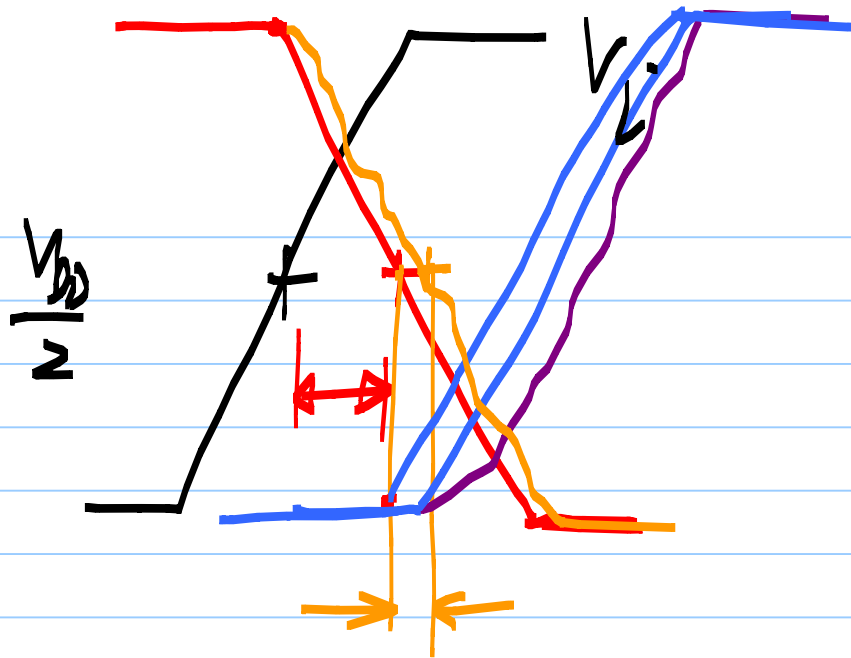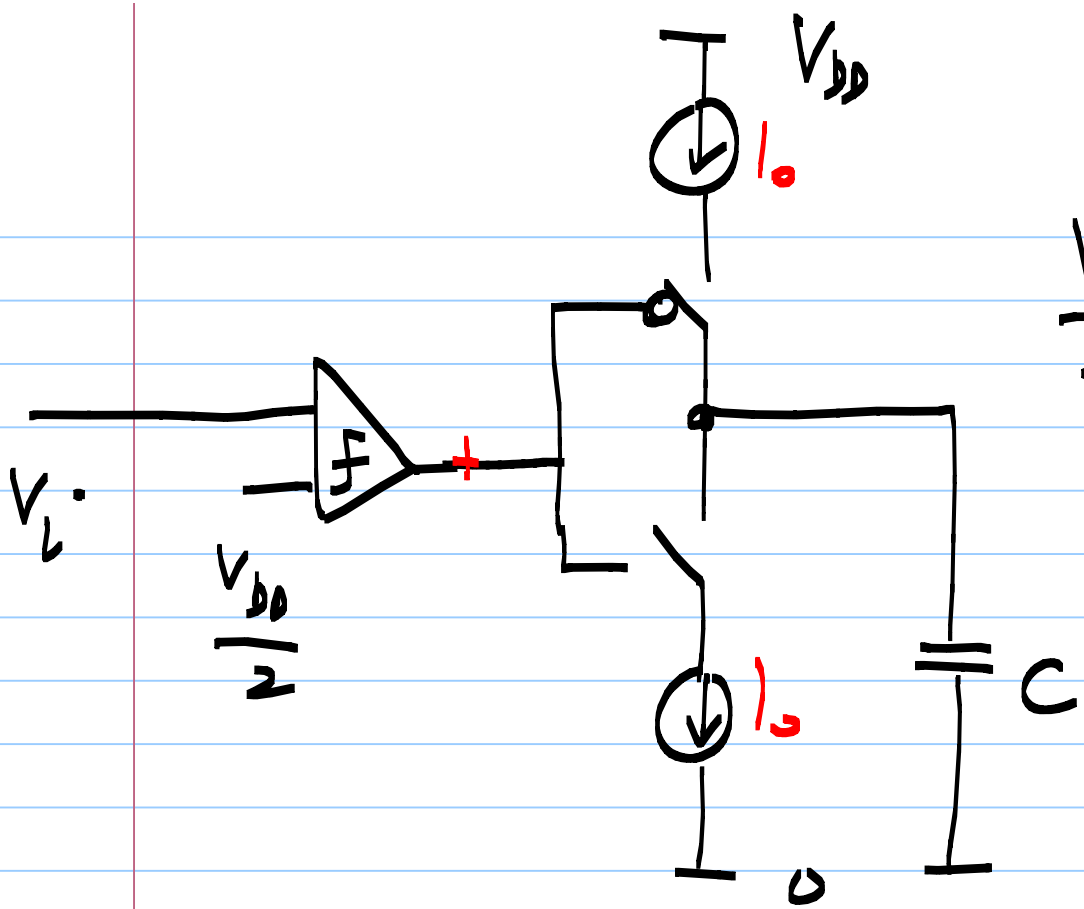

Σ
26 ops

14 ops

100°

0°

V_c

