
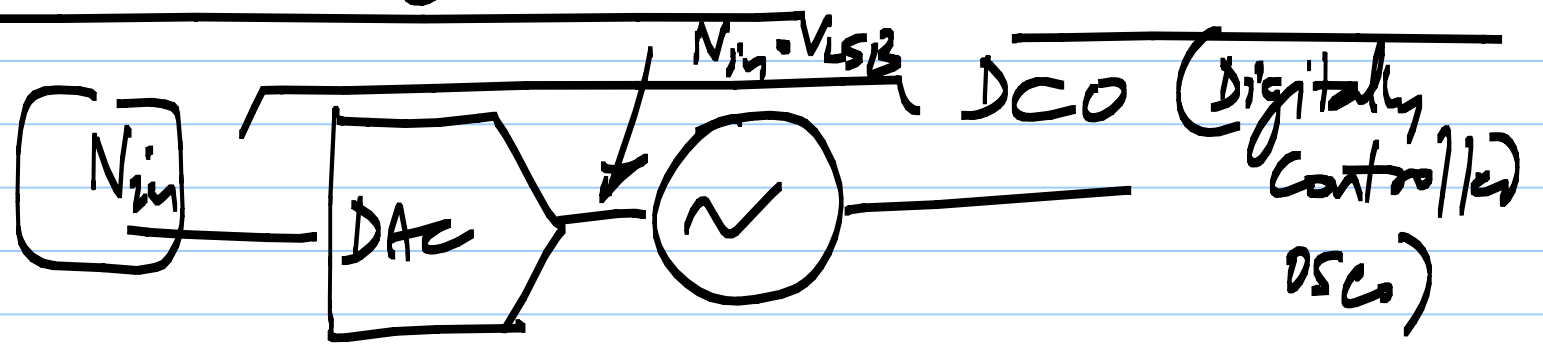


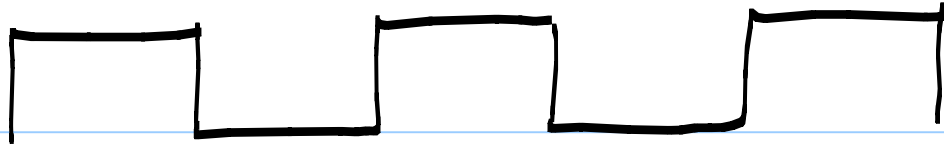Reduce the jitter generated:  $\rightarrow R \downarrow I_{cp} \uparrow C \uparrow$




Data




CK




UP

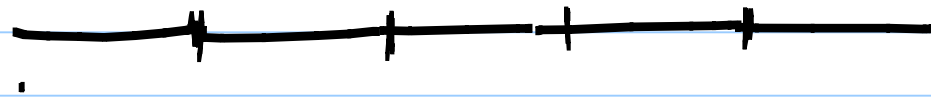

$V_R$

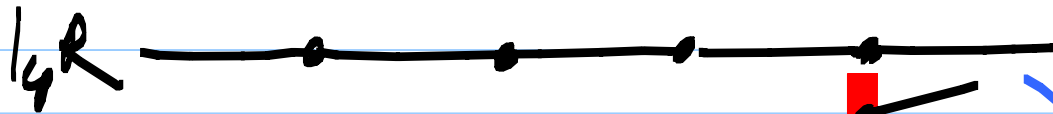

$V_C$

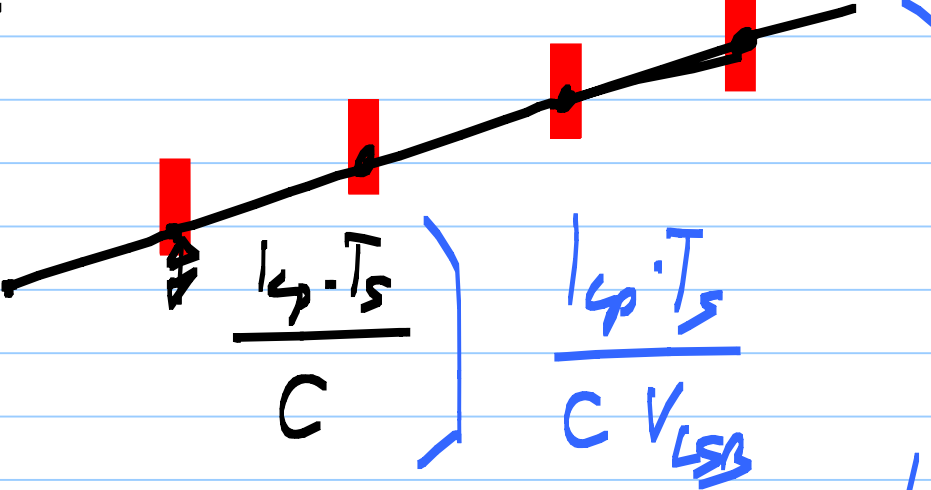

UP=1  
DN=0.

$$V_R = 0, \pm \frac{1}{4}R$$

$V_C$  change in every cycle:

$$0, \pm \frac{1/4 Ts}{C}$$

Dig. output


$$\frac{1/4 R}{V_{LSB}}$$

Input  $N_{in}$  of the digitally controlled oscillator:

$$\begin{aligned}
 & \overset{w}{N_{in}}(z) \underbrace{\left( \text{UP-DN} \right)}_{\pm 1, 0} \underbrace{\left[ \frac{1_{\mu} R}{V_{LSB}} \right]}_{\text{Integer } N_R} + \underbrace{\left( \text{UP-DN} \right)}_{\text{Integer } N_C} \underbrace{\left[ \frac{1_{\mu} T_s}{C V_{LSB}} \right]}_{\text{Integer } N_C} \frac{z^{-1}}{1-z^{-1}} \\
 & \underbrace{\hspace{10em}}_{\text{Resistor}} \qquad \qquad \qquad \underbrace{\hspace{10em}}_{\text{Capacitor}}
 \end{aligned}$$

$$V_{CH}(s) = I_{CP}(s) \cdot \left( R + \frac{1}{sC} \right)$$

---

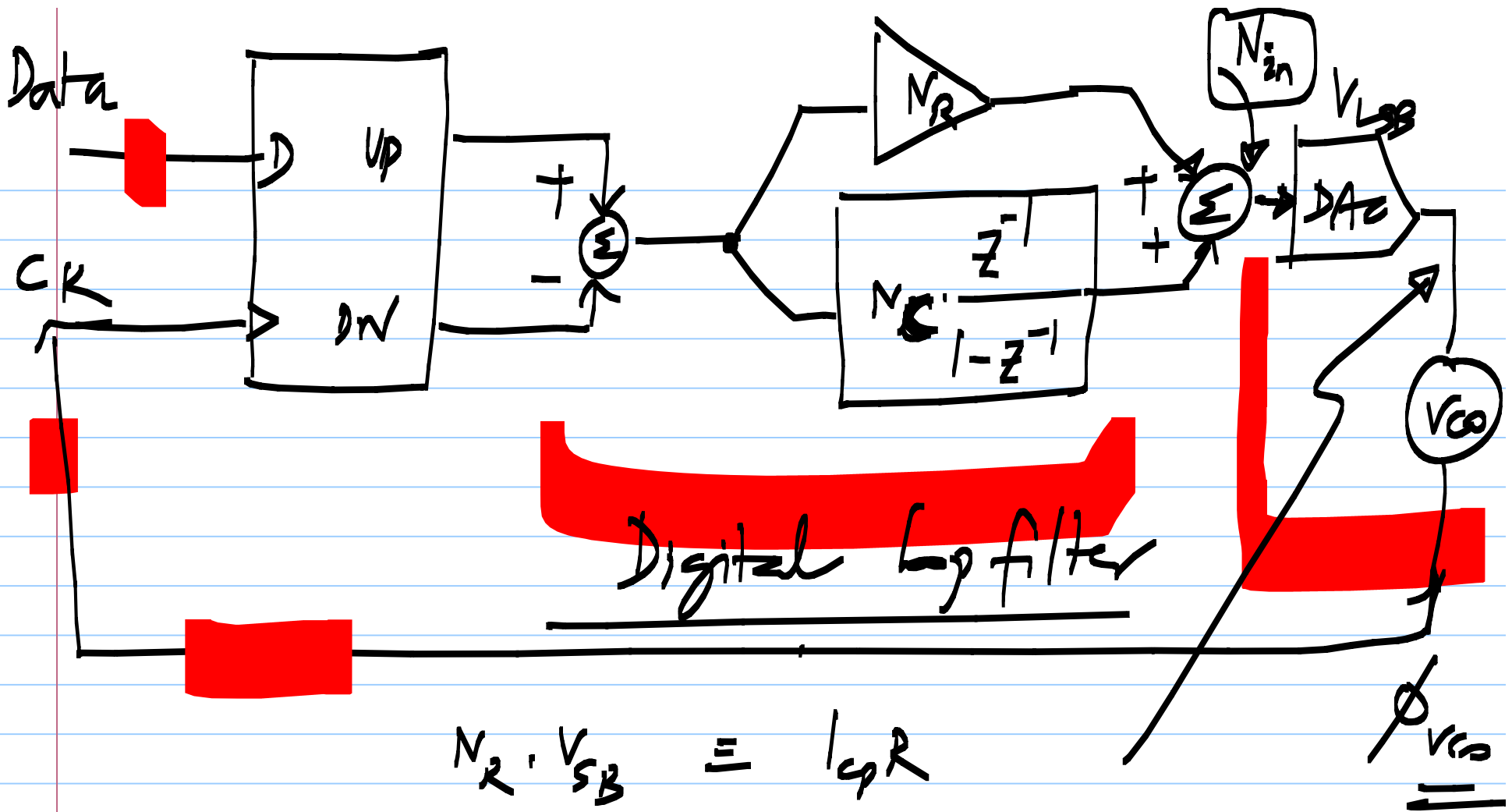



$$N_R \cdot V_{LSB} \equiv I_{cp} R$$

$$N_C \cdot V_{LSB} \equiv \frac{I_{cp} \cdot T_s}{C}$$

$$Y(z) = U(z) \cdot \frac{z^{-1}}{1 - z^{-1}}$$




$$y[n] - y[n-1] = u[n-1]$$


$$y[n] = y[n-1] + u[n-1]$$

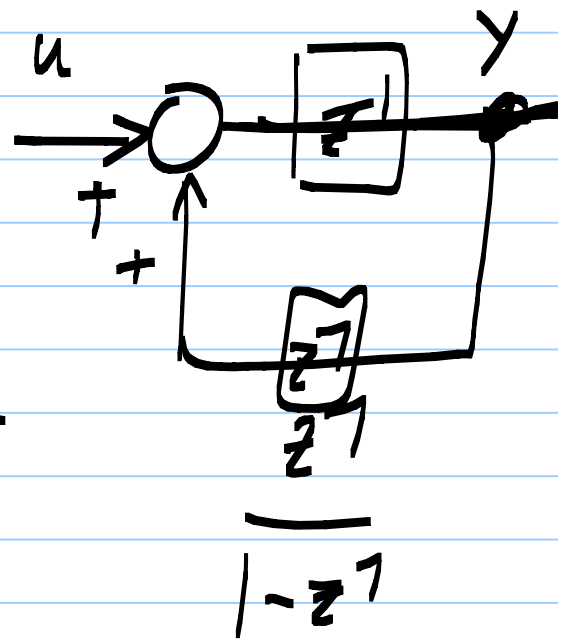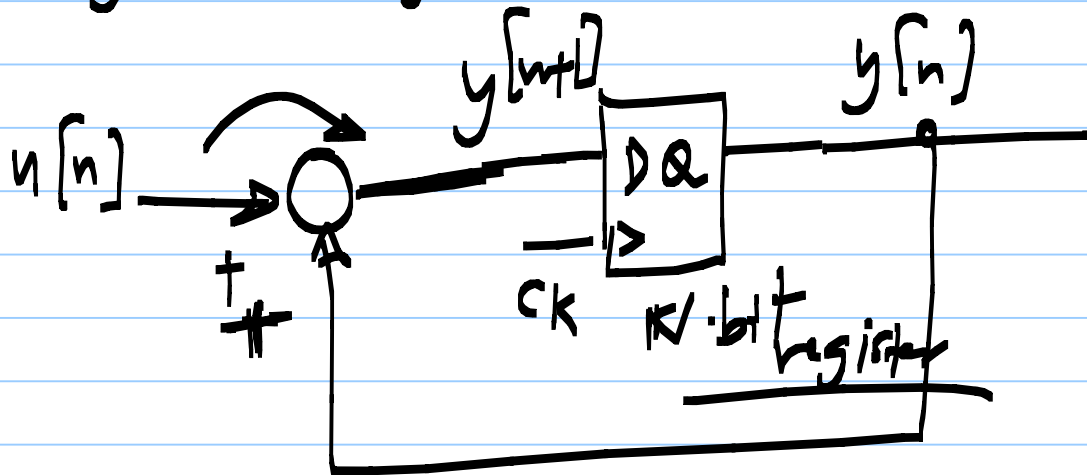

$1 \text{ nH}, 1 \text{ pF} \sim 5 \text{ GHz}$

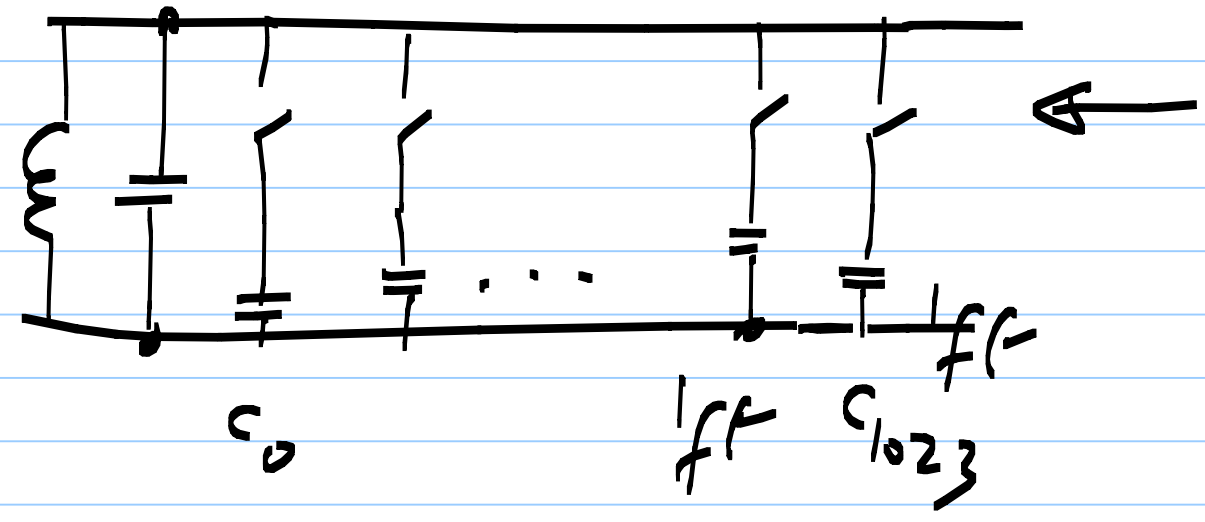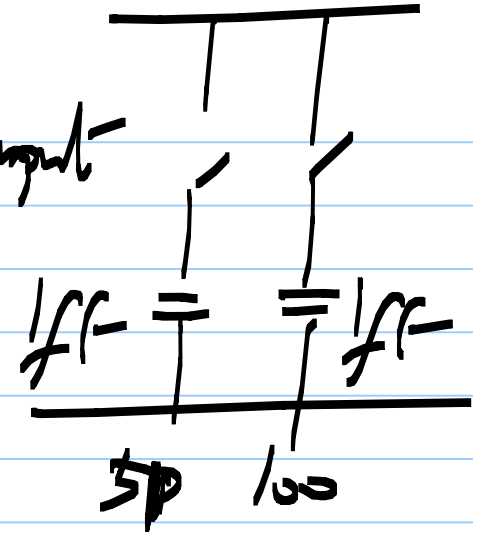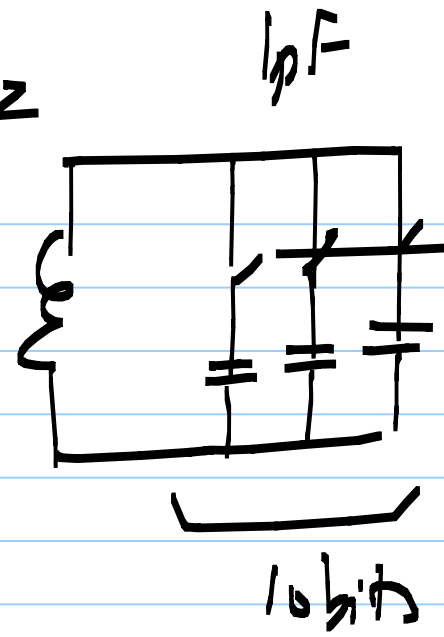$200 \text{ pF} \times 200 \text{ fF} = 25 \text{ GHz}^2$



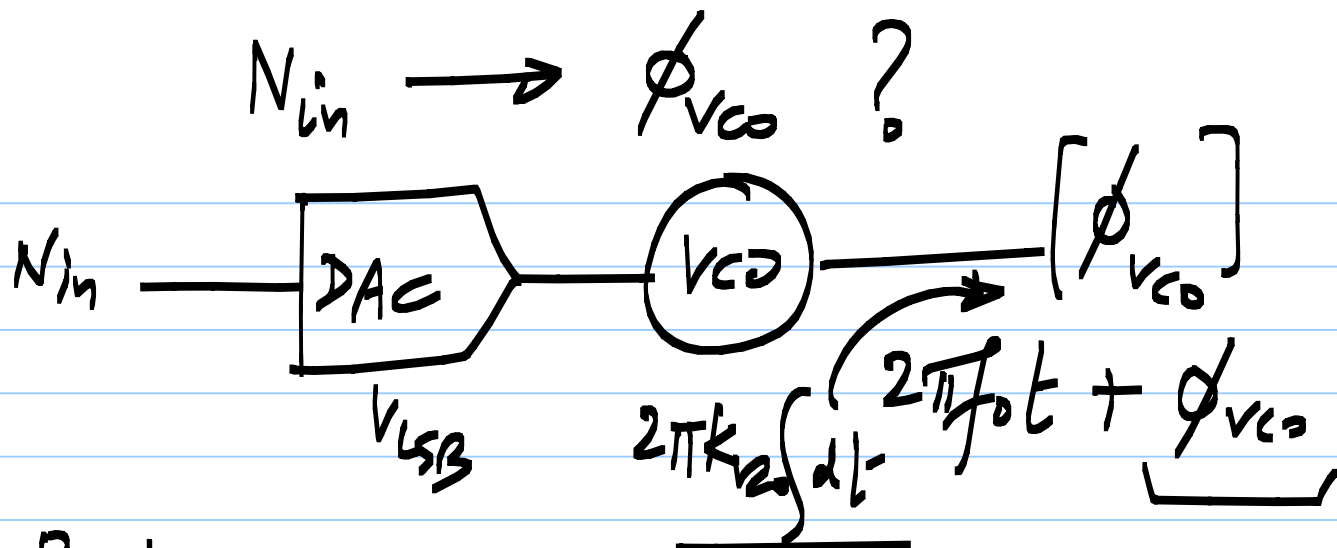


$N_{in} = 0 :$



$N_{in} = 1 :$


$2\pi k_v \cdot V_{LSB} \cdot T_s$


phase increment  
 in every cycle

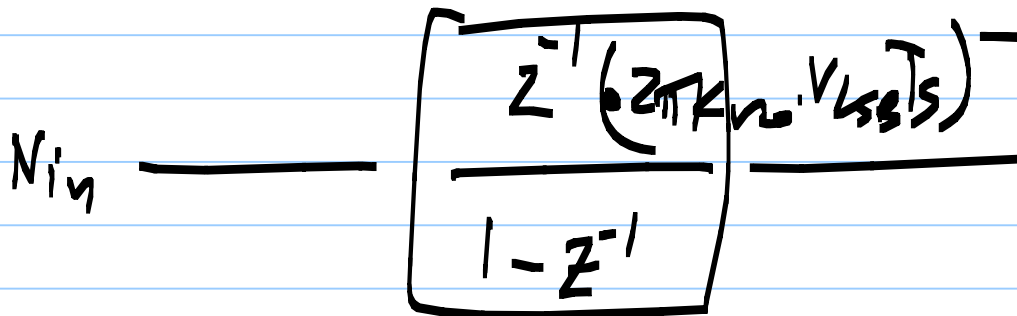



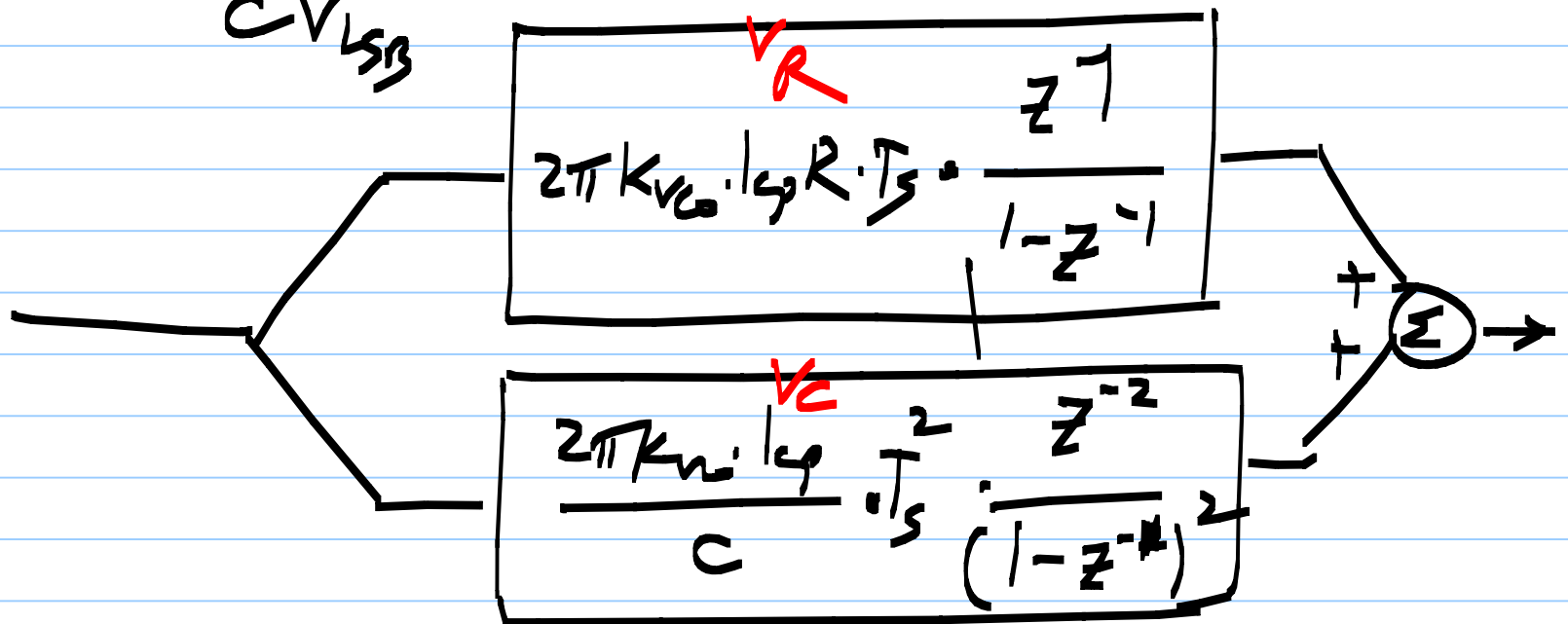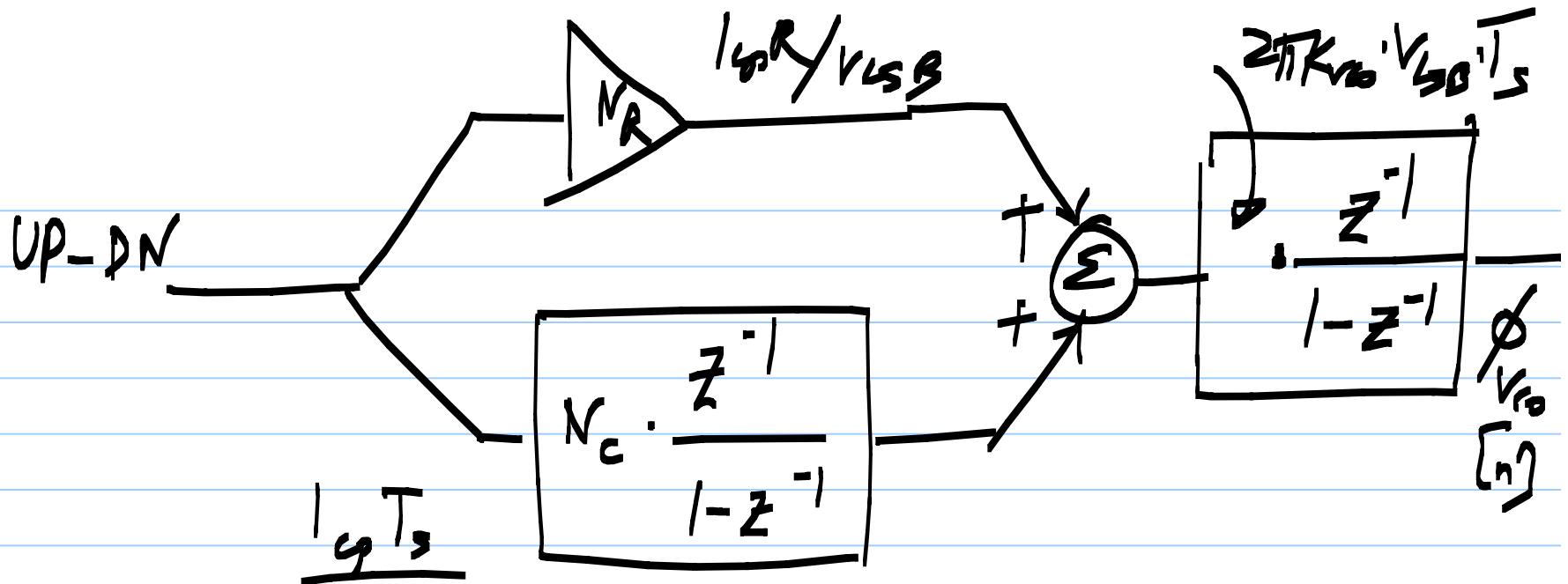

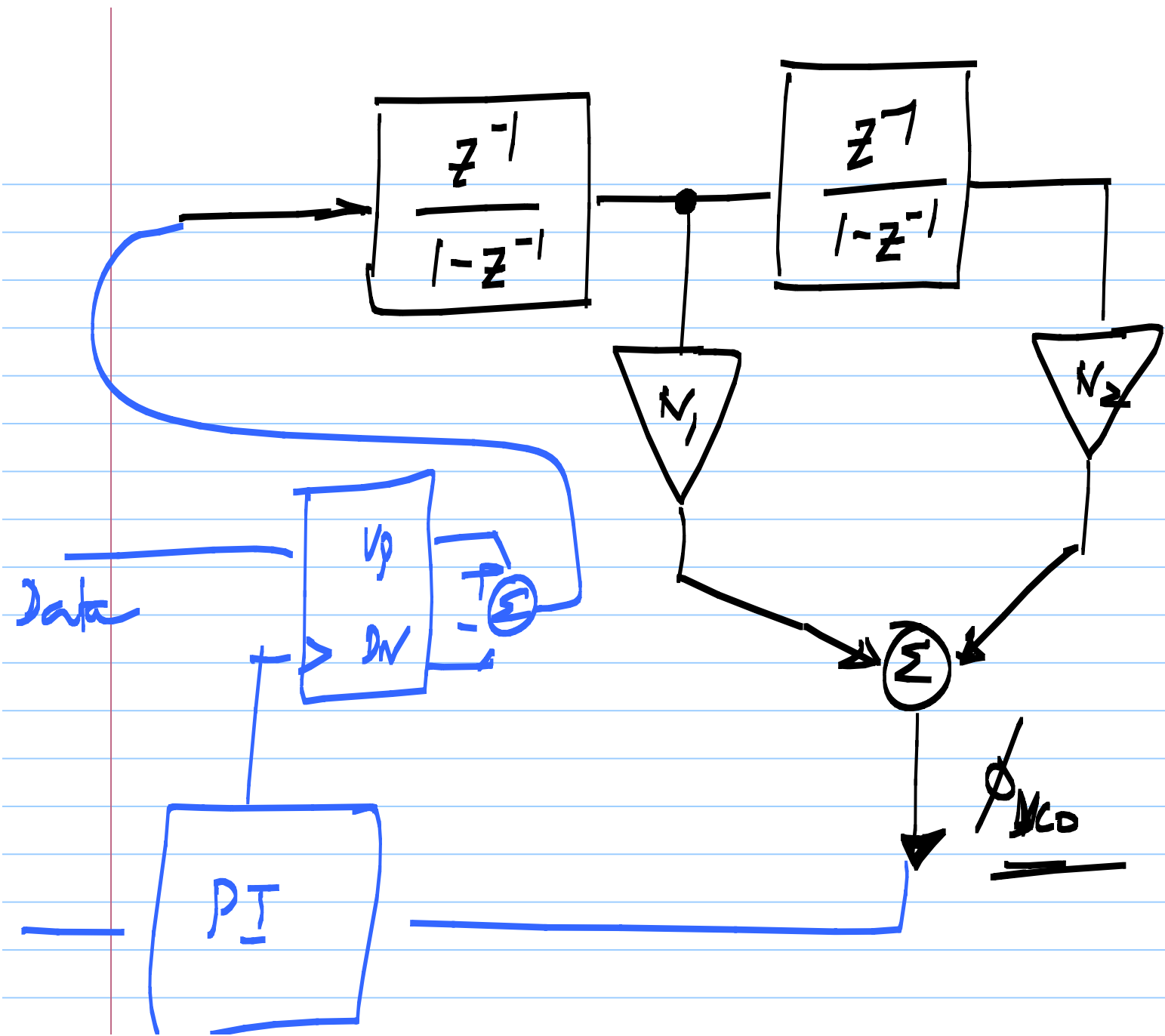

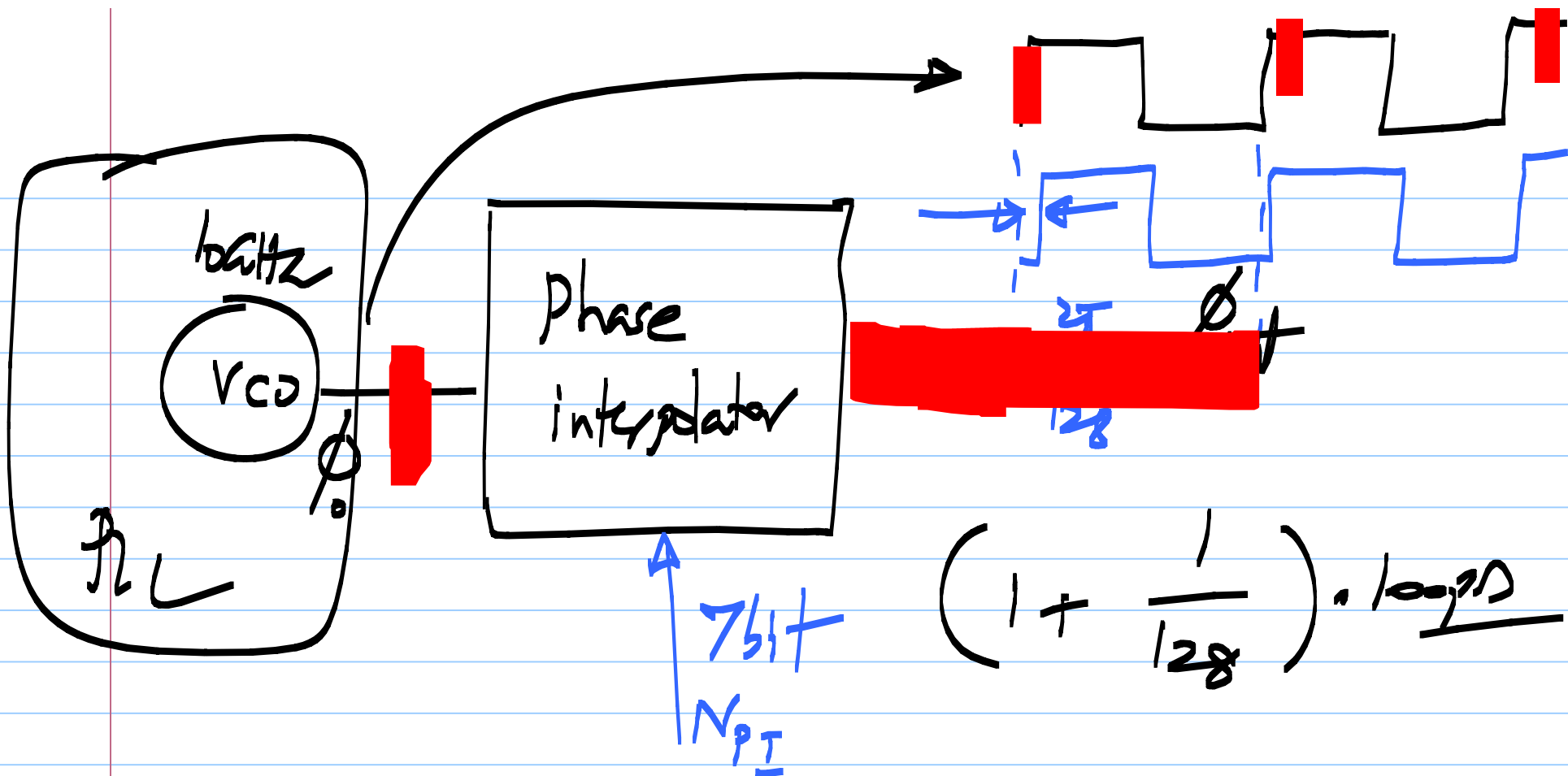

$$\left(1 + \frac{1}{128}\right) \cdot 100\text{kHz}$$

$$\phi_0 - \phi_{\text{out}} = N_{PI} \cdot \phi_{\text{LSB}}$$