
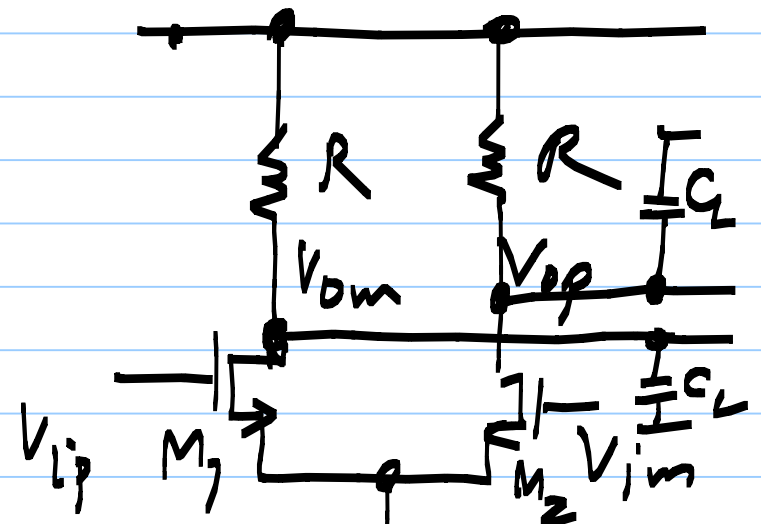




linear (CTLE)
 Continuous-time equalizer



$$H_{eq}(s) = \frac{1 + s/z_1}{(1 + s/p_1)(1 + s/p_2)}$$

In the Rx, before sampling

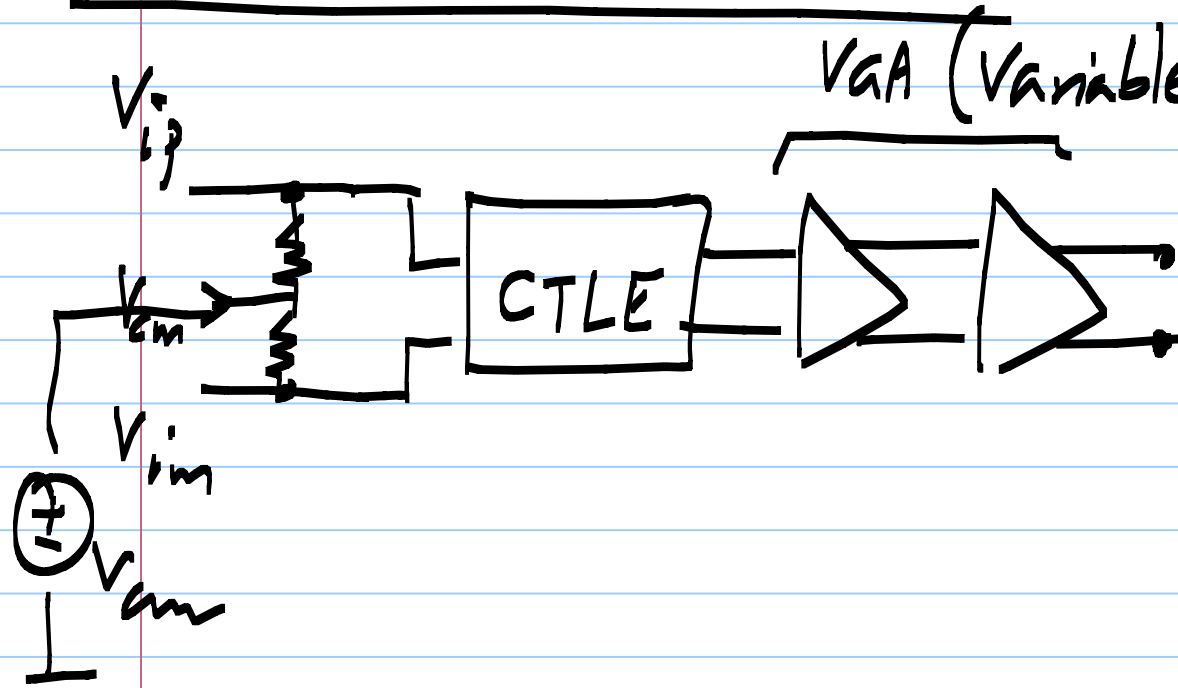

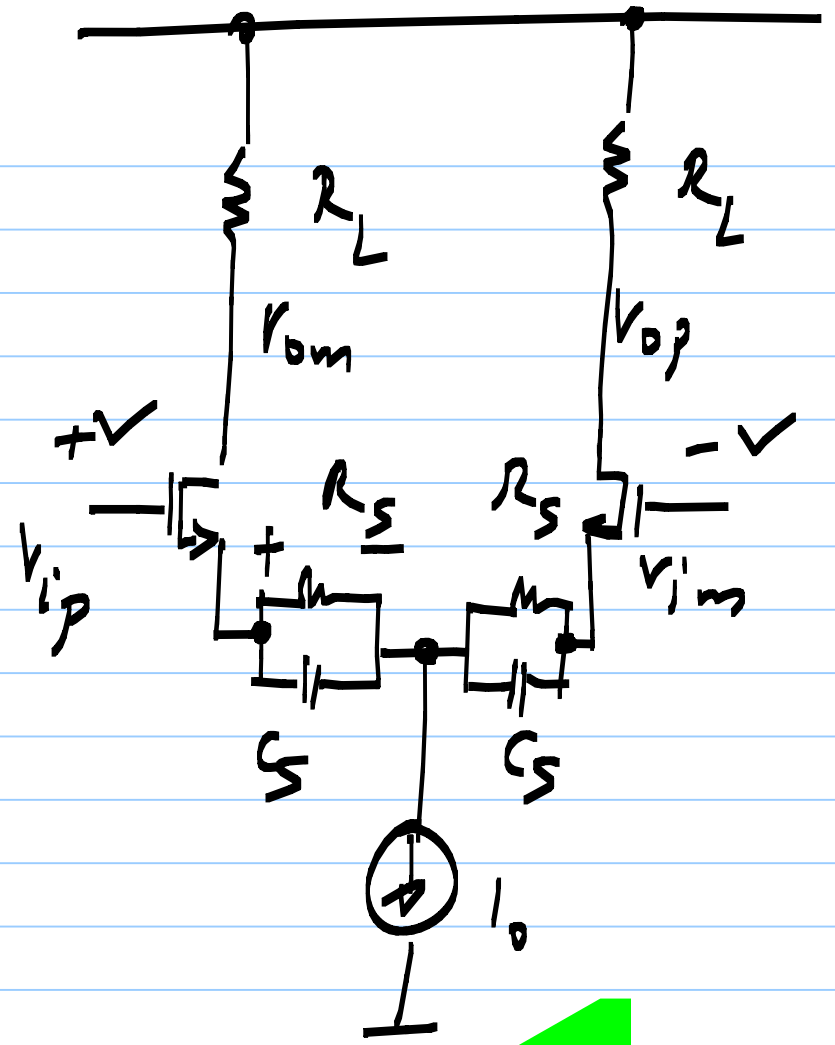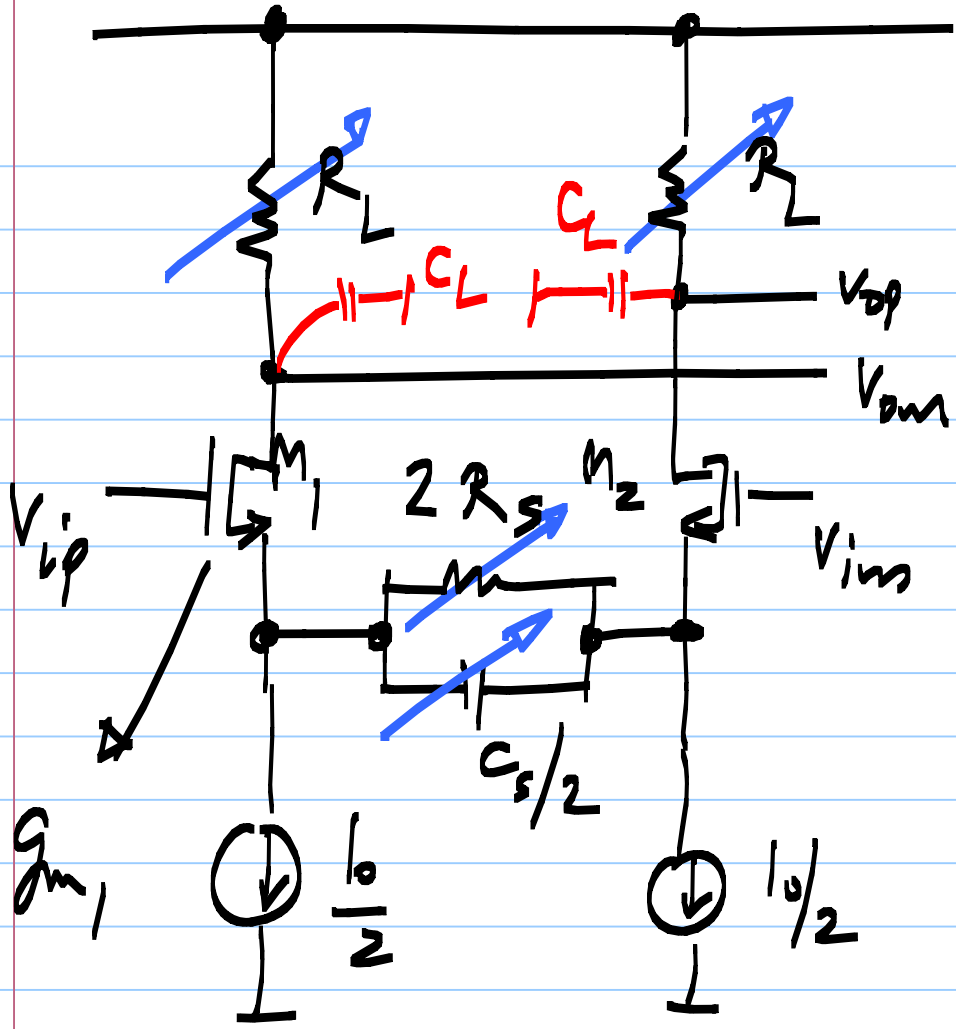dc gain: $g_{m1} R$
 BW: $1/\tau_{CL}$ rad/s




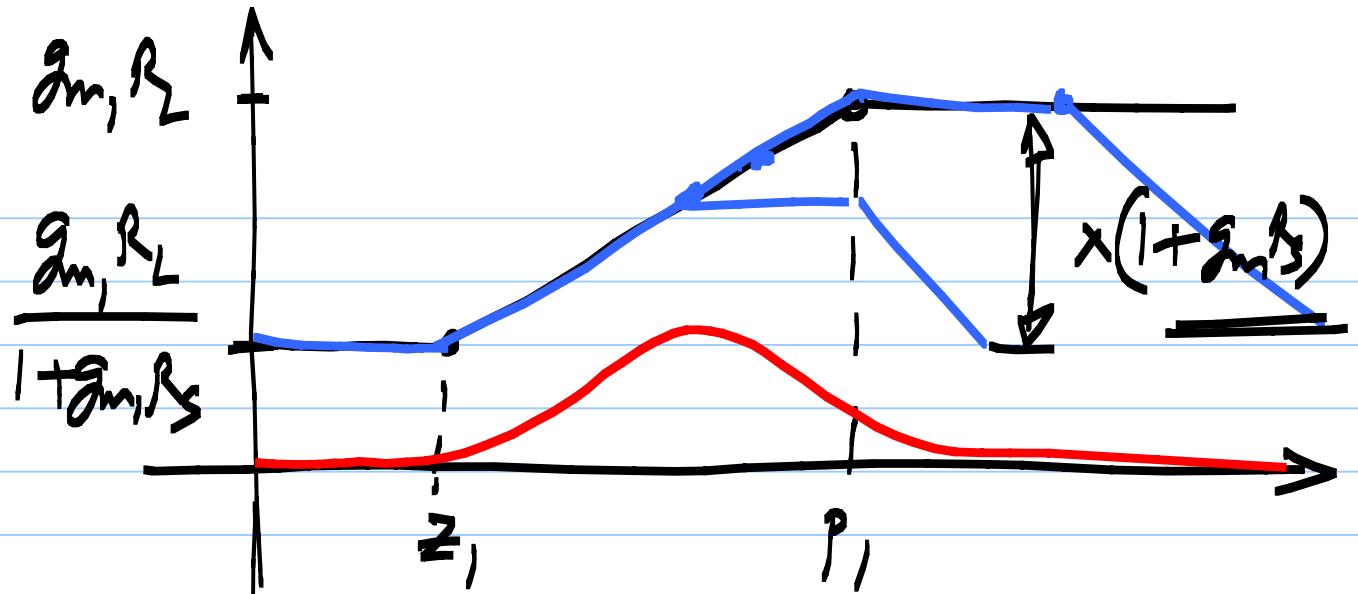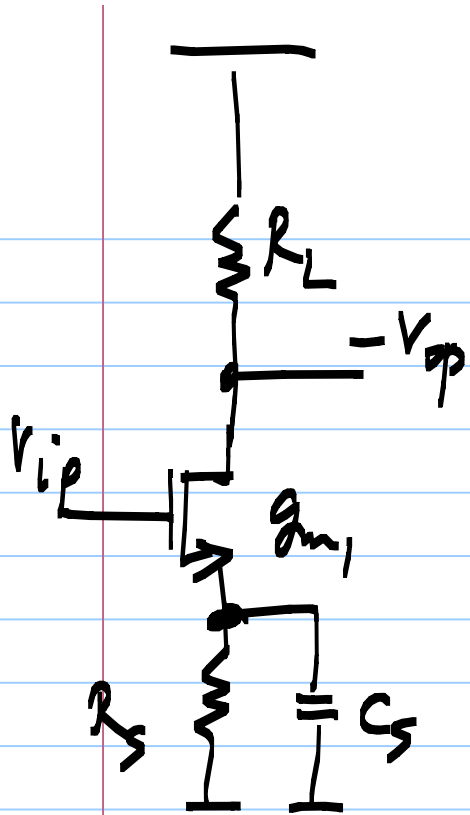

$$\frac{1}{R_S C_S} = \frac{g_S + g_m}{C_S}$$


$$p_2 = \frac{1}{R_L C_L}$$
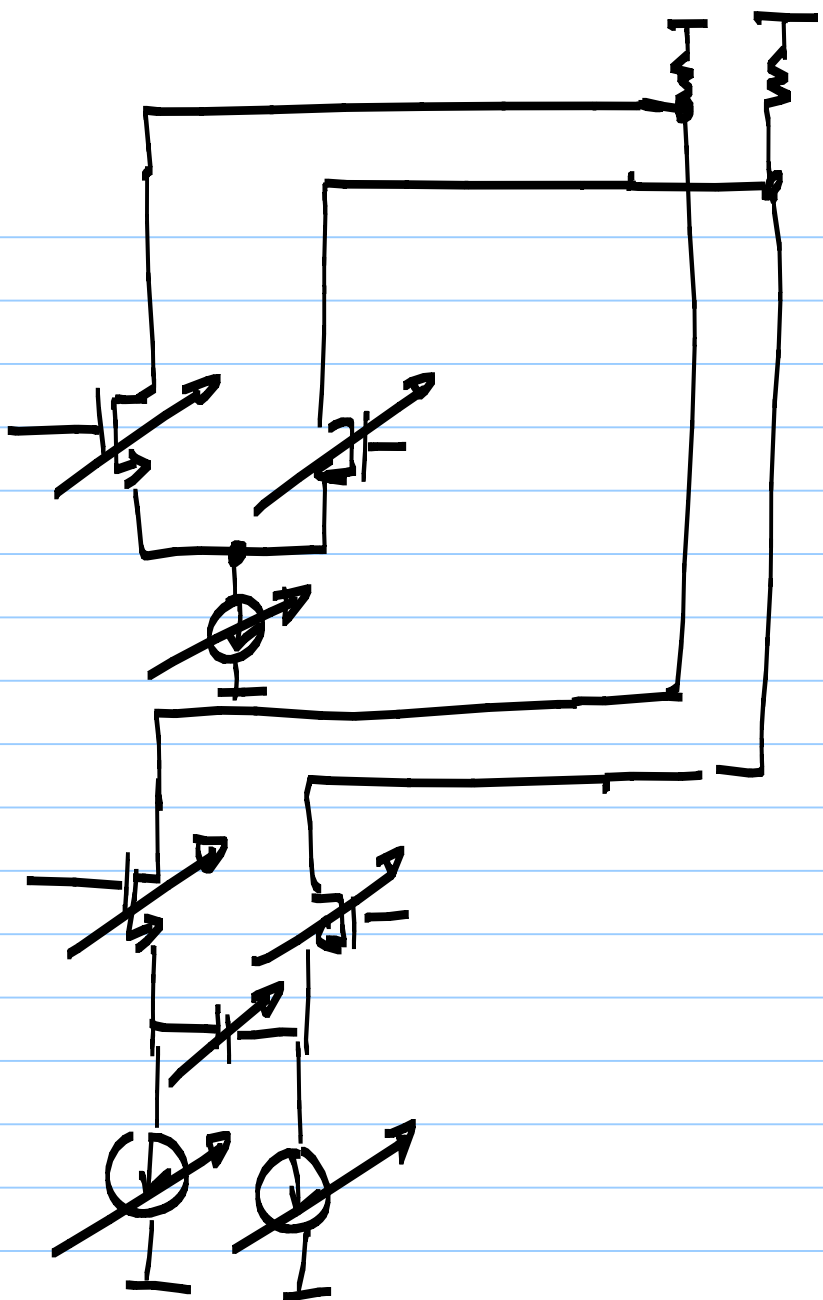
$$H(s) = \frac{g_m R_L}{1 + g_m R_S} \cdot \frac{1 + s/z_1}{1 + s/p_1} \cdot \frac{1}{1 + s C_L R_L}$$




Heaviside

Pupin

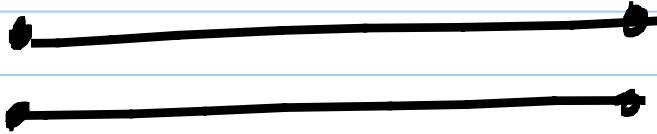


Loading coil

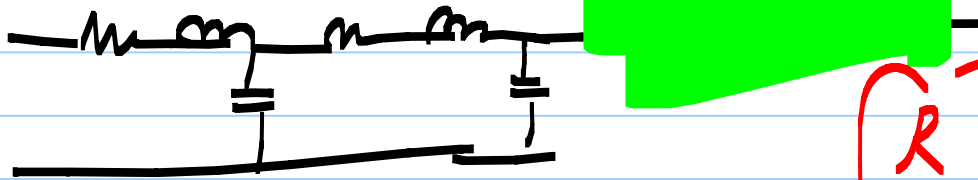


$$\frac{R}{L} = \frac{G}{C}$$

$R \cdot \Delta x$ $L \cdot \Delta x$

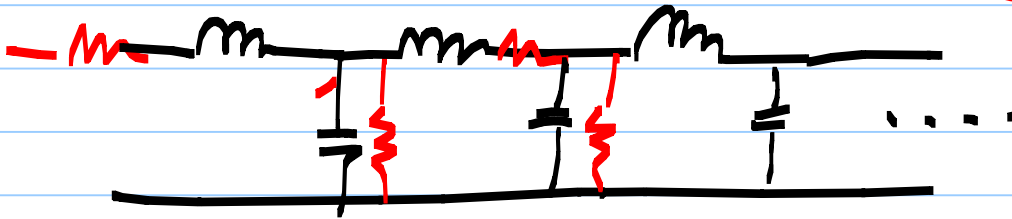


$C \cdot \Delta x$ $G \cdot \Delta x$

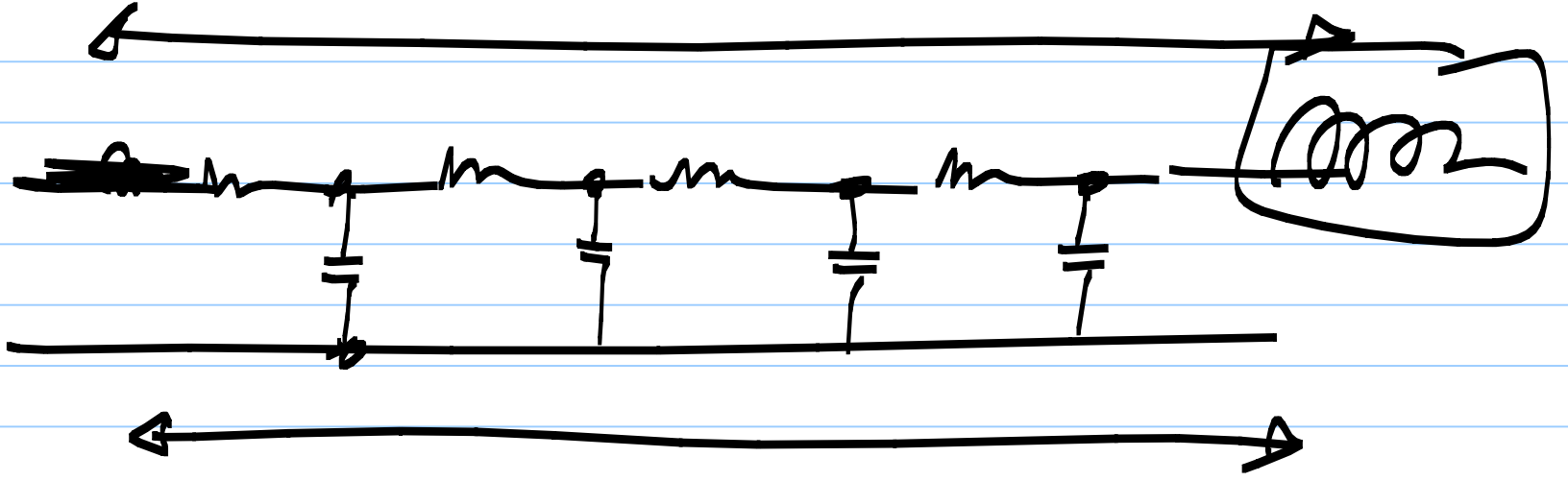

l

$$T \sim l^2$$

$$\frac{T}{l}$$

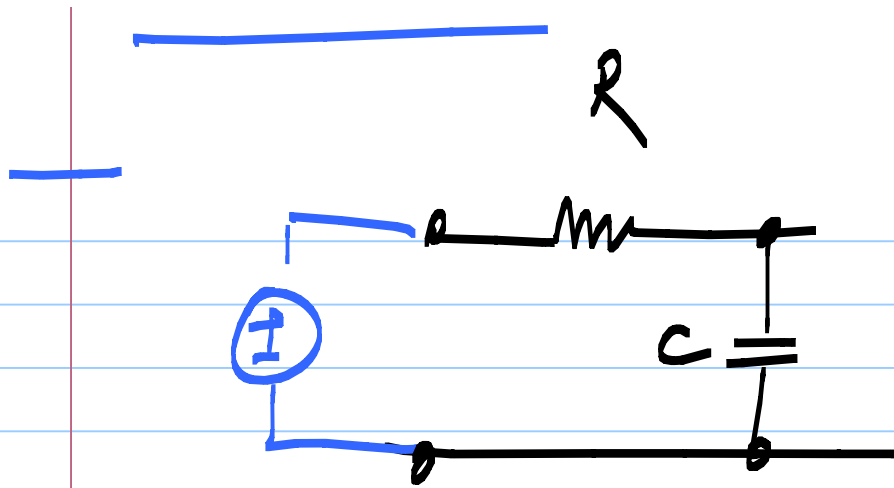

$$1 + az^{-1}$$

$$1 - az^{-1}$$

~~channel~~

1
0

