
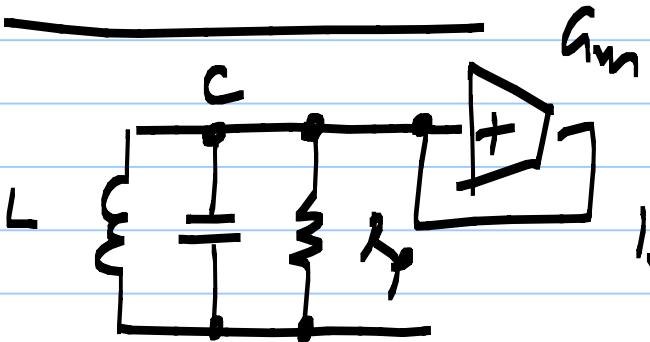


LC oscillator.

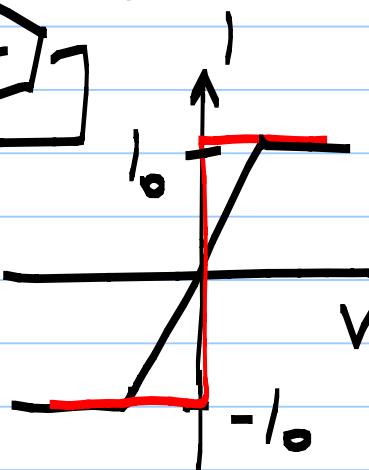



$V_p \cos(\omega t)$

$$V_p = \frac{4}{\pi} I_0 R_p$$



$\mathcal{L}(f)$

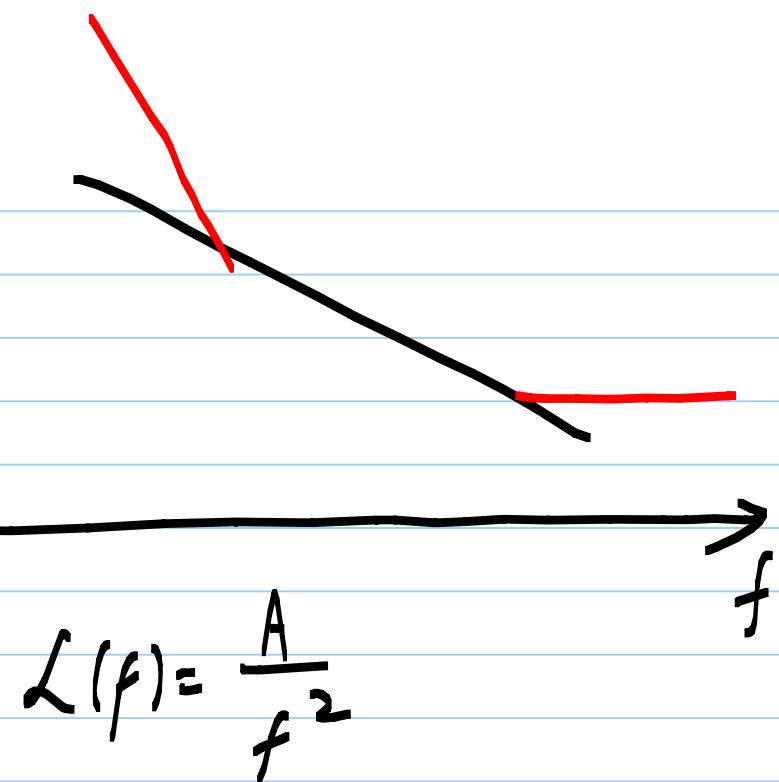


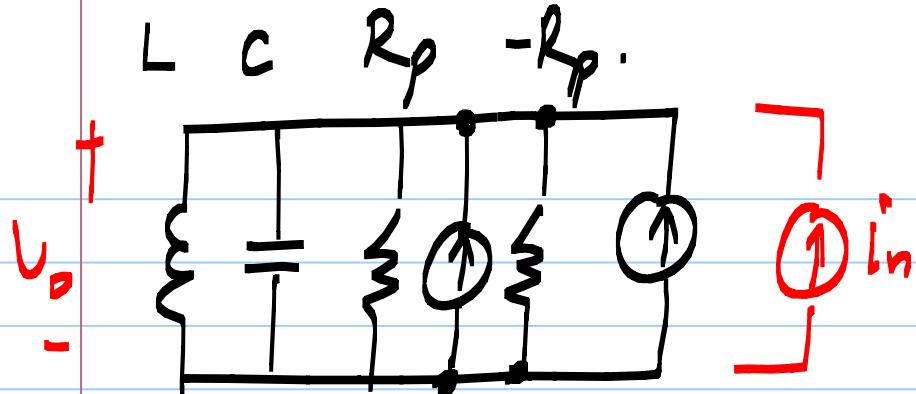

$$\left[\frac{4k_r}{R_p} \quad \frac{4k_i}{R_p} \right]$$

$$\left| \frac{V_o}{I_n} \right| = \frac{1}{\left| j\omega C + \frac{1}{j\omega L} \right|}$$

$$= \left| \frac{\left[j\omega L \right]}{-\omega^2 LC + 1} \right|$$

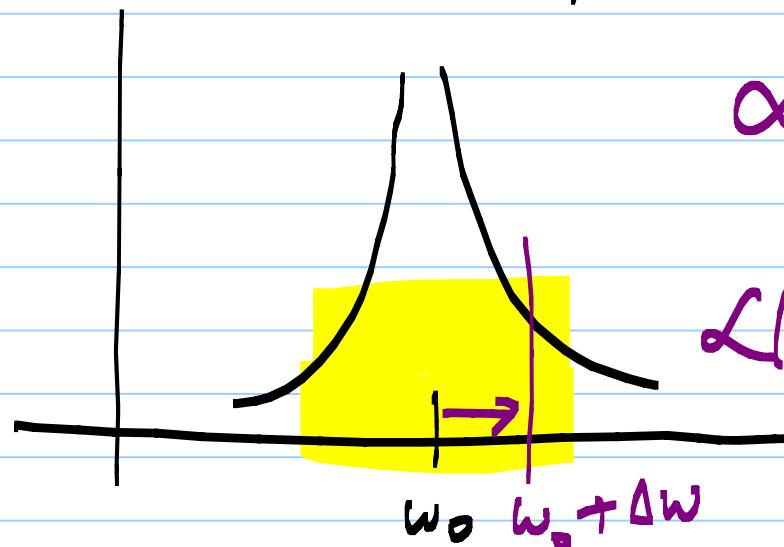

$$\propto \frac{1}{\Delta\omega^2}$$

$$\mathcal{L}(f) \propto \frac{1}{f^2}$$

$$\propto$$


$$\frac{1}{(\omega + \omega_0)(\omega - \omega_0)}$$

$$1 - \frac{\omega^2}{\omega_0^2}$$

$$= \frac{1}{\omega_0^2 - \omega^2} = \frac{1}{2\omega_0(\Delta\omega)}$$


- * Phase noise $L(f) \propto \frac{1}{f^2}$ due to thermal noise $[L(f) = \frac{A}{f^2}]^f$

- * Can have $\frac{1}{f^3}$, f^α terms

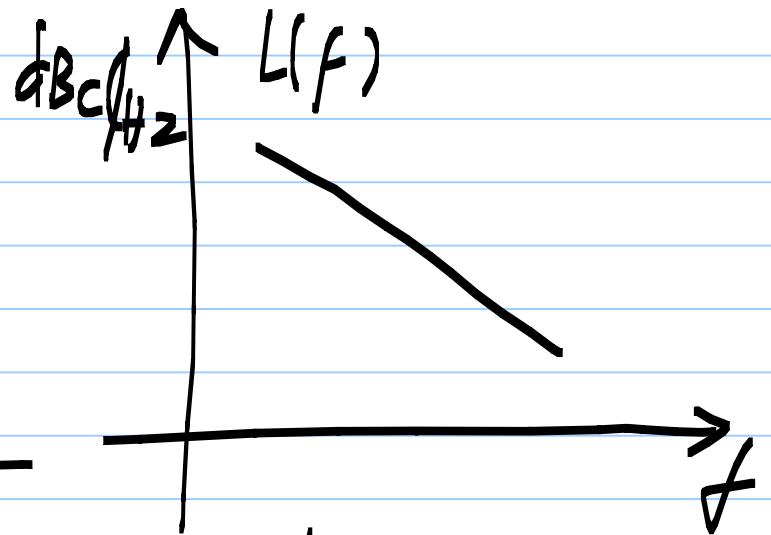


Ring oscillator has a higher phase noise than LC oscillator

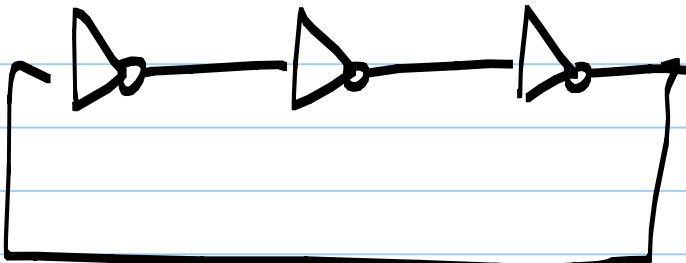- * Phase noise inversely proportional to power dissipation




P_d , $L(f)$

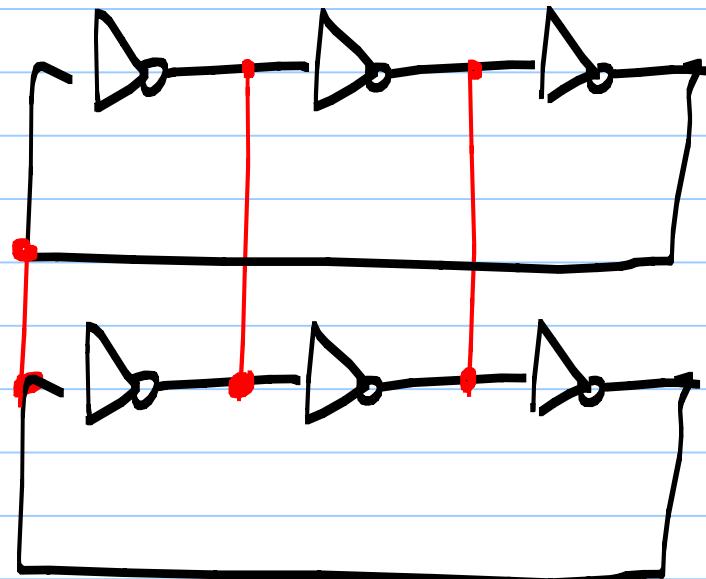

$2P_d$, $\frac{L(f)}{2}$

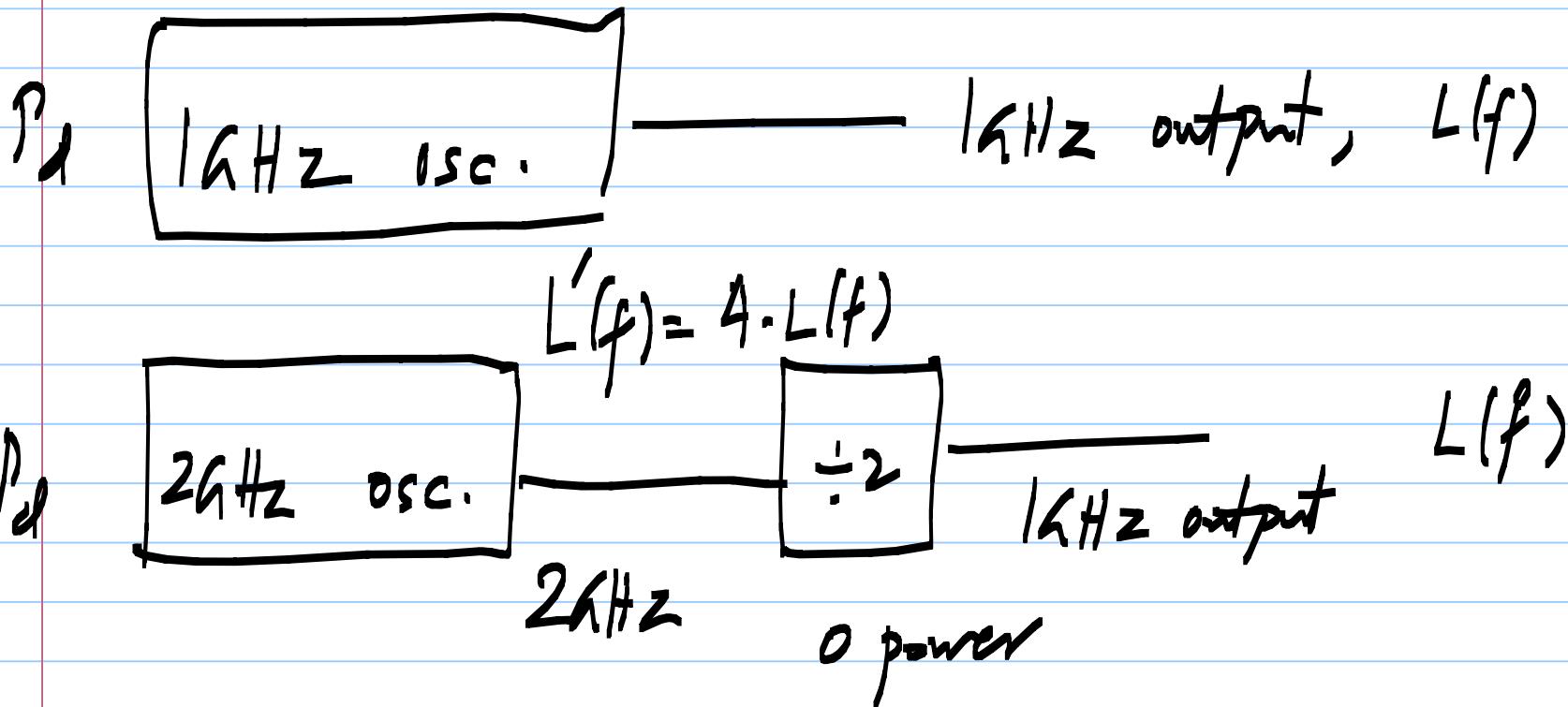For the same power dissipation, $L(f) \propto f_0^2$
 f_0 : oscillation frequency



Phase noise figure of merit.

$$L(f) = \alpha \cdot \frac{1}{f^2} \cdot f_0^2 \cdot \frac{1}{P_d}$$

$$\alpha = L(f) \cdot \frac{f^2}{f_0^2} \cdot P_d$$

CMOS oscillations

The lower, the better

$$\alpha = \frac{1}{L(f)} \cdot \frac{f^2}{f_0^2} \cdot \frac{1}{P_d}$$

The higher, the better

Oscillator PN

FOM =

$$\log_{10} \left[\frac{1}{L(f)} \cdot \frac{f^2}{f_0^2} \cdot \frac{1}{P_d, \text{mW}} \right]$$

$\sim 165 \text{ dB}$ for

Ring osc.

$\sim 185 \text{ dB}$ for

LC osc.

Calculate the Phase noise of ring & LC VCOs
(FOM = 165dB 185dB)

10MHz oscillator, 10mW power dissipation

Phase noise @ 1MHz offset

$$165 \text{ dB} = 10 \log_{10} \left[\frac{1}{L(f)} \right]$$

$$FoM = \log_{10} \left[\frac{1}{L(f)} \cdot \left(\frac{f}{f_0} \right)^2 \cdot \frac{1}{P_{d, \text{mw}}} \right]$$

$$= -\log_{10}(L(f)) + 2\log_{10}\left(\frac{f}{f_0}\right) - \log_{10}(P_{d, \text{mw}})$$

~~100Hz~~

~~Phase noise~~
in dBc/Hz

$$165 \text{ dB} = -L_{dB}(f) + 80 \text{ dB} - 10 \text{ dB}$$

$$L_{dB}(f) = (-165 + 70) = -95 \text{ dBc/Hz}$$

$$185 \text{ dB} : L_{dB}(f) = -115 \text{ dBc/Hz}$$

$$\omega_n = 10 \text{ MHz}$$



$$\phi_{rms} =$$

$$\Gamma_{rms} =$$

JEN due to the V_{C_0} :

$$\left\{ \frac{2\pi^2 A}{\omega_n} \right\}$$

