
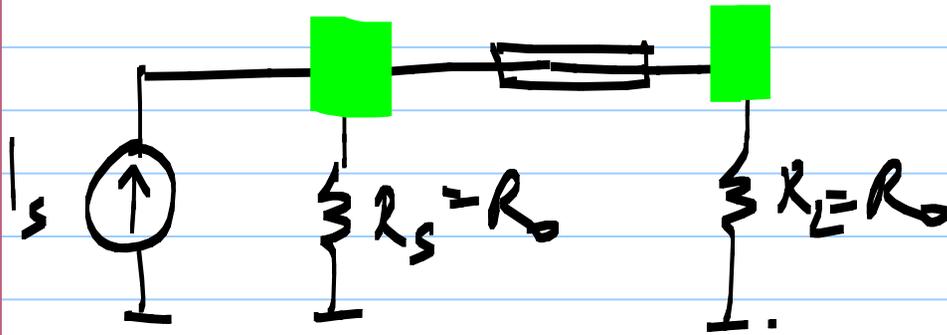


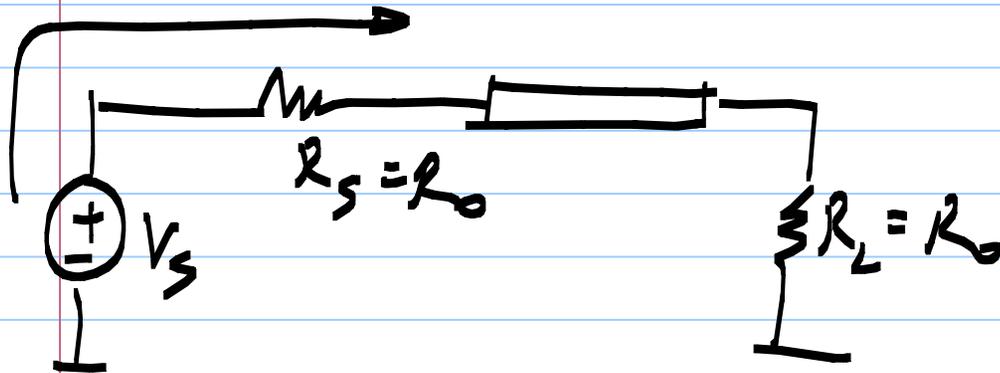Small swings $\sim 100\text{ s mV}$ Voltage mode Tx is more efficient
Current and voltage mode transmit drivers





Current driver
 \Rightarrow current division
 $V_{Rx} = V_{Tx}$





Voltage driver
 All of Tx current goes to the receiver
 Voltage division

Smaller Tx current

Current mode driver

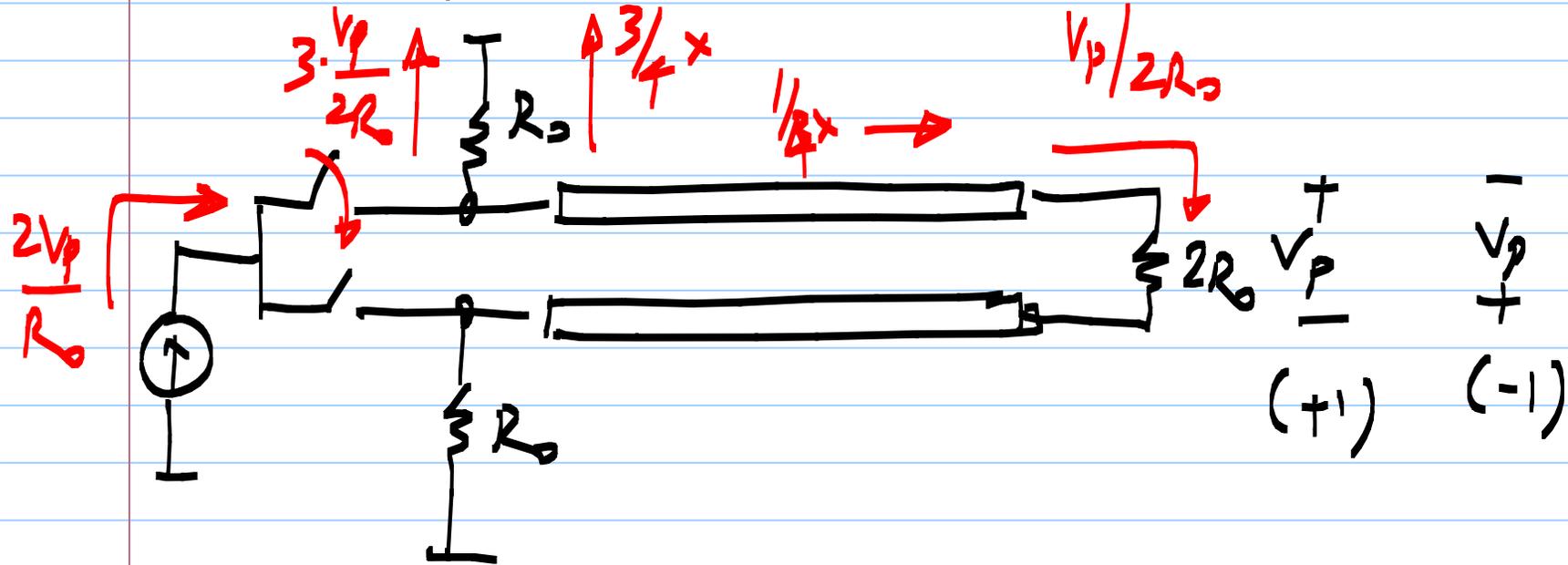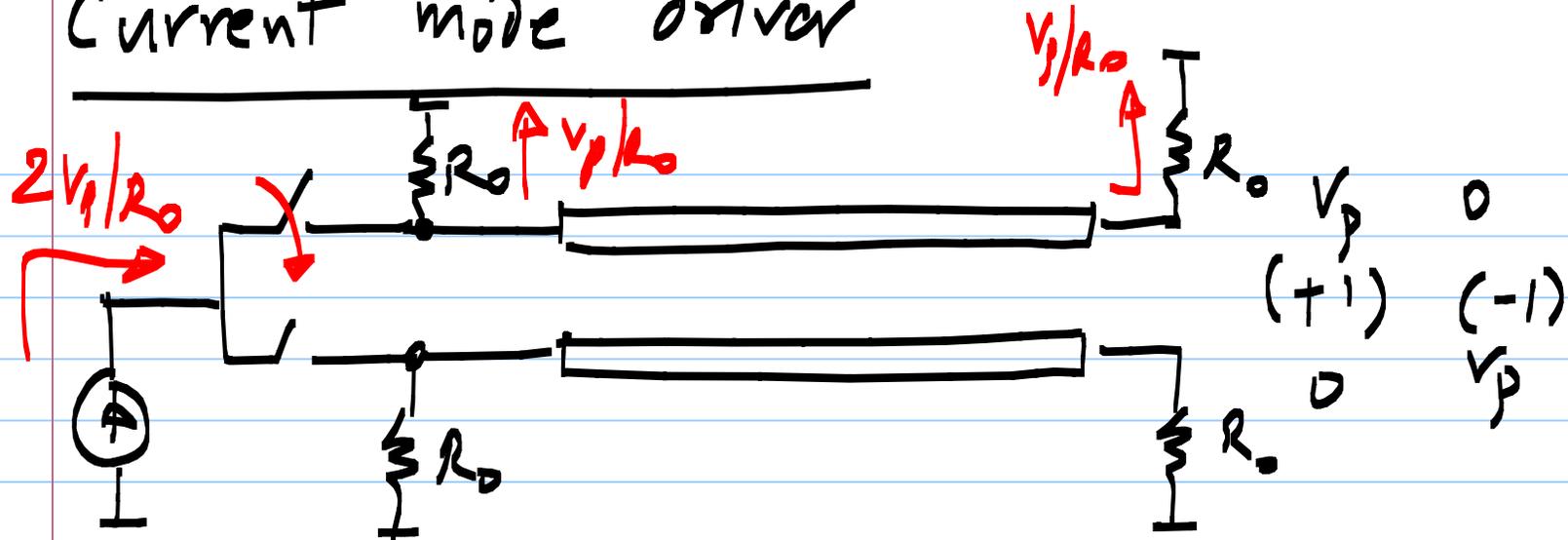

Voltage mode driver:

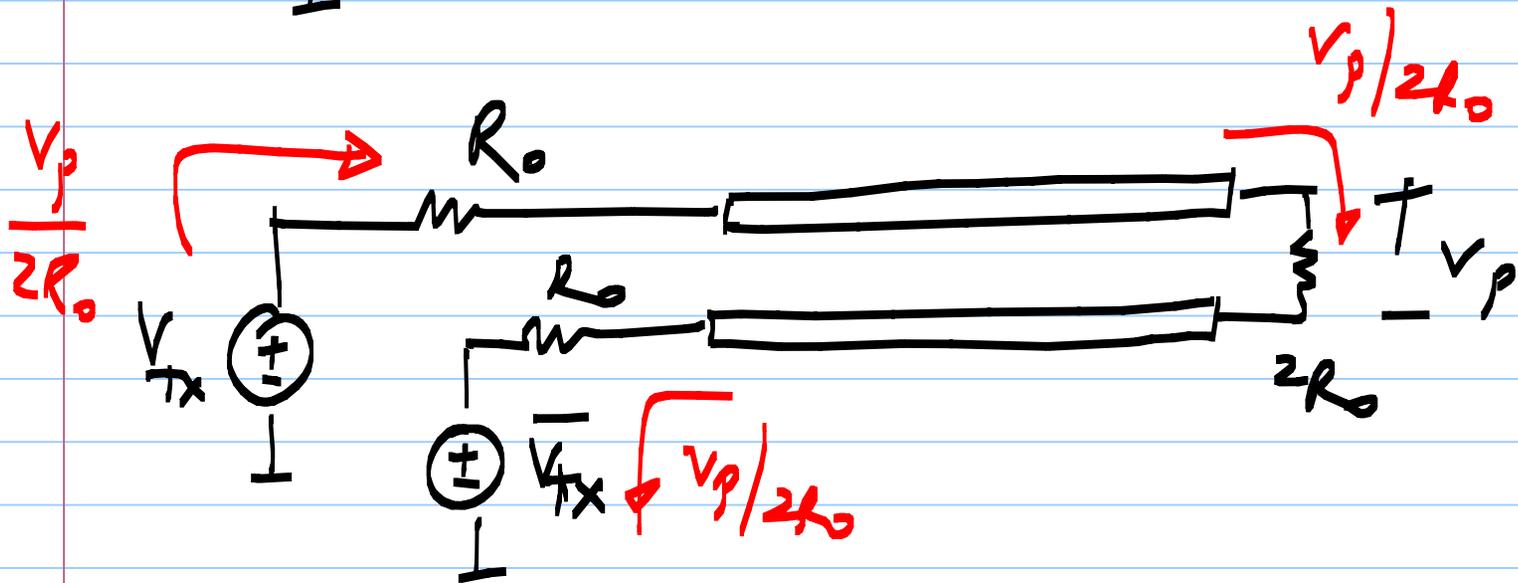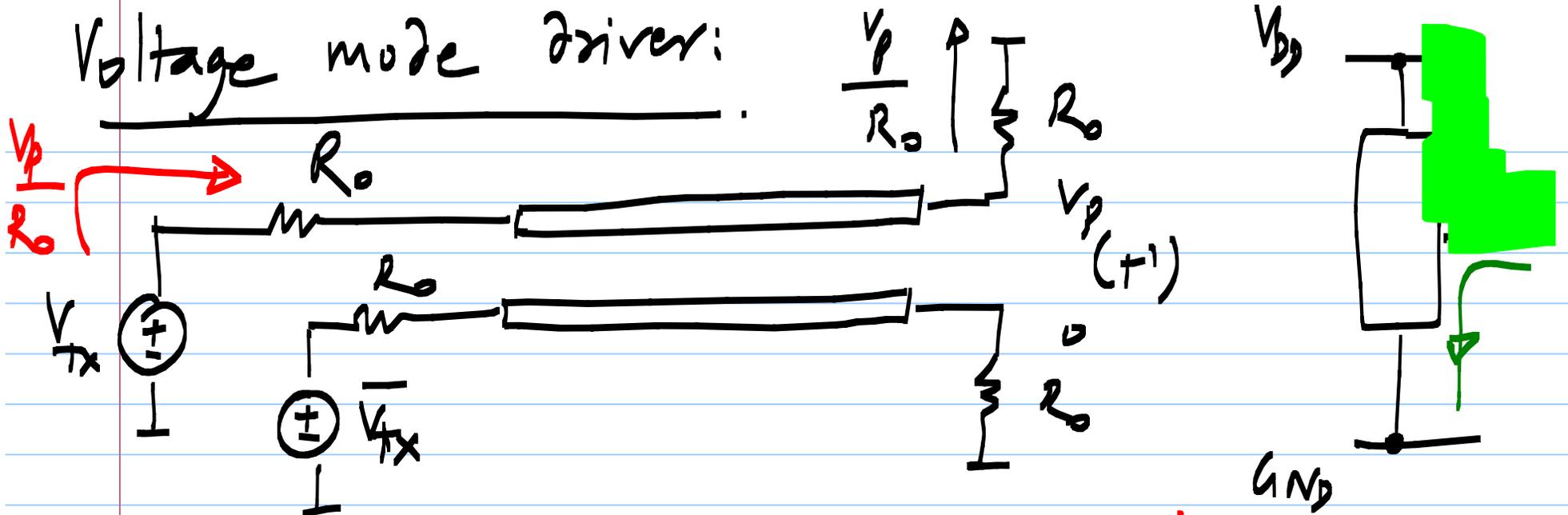

Pseudo-diff
termination

Diff
termination

V. mode



$$V_p/2$$

$$V_p/2$$

I. mode

$$2V_p/2$$

$$2V_p/2$$

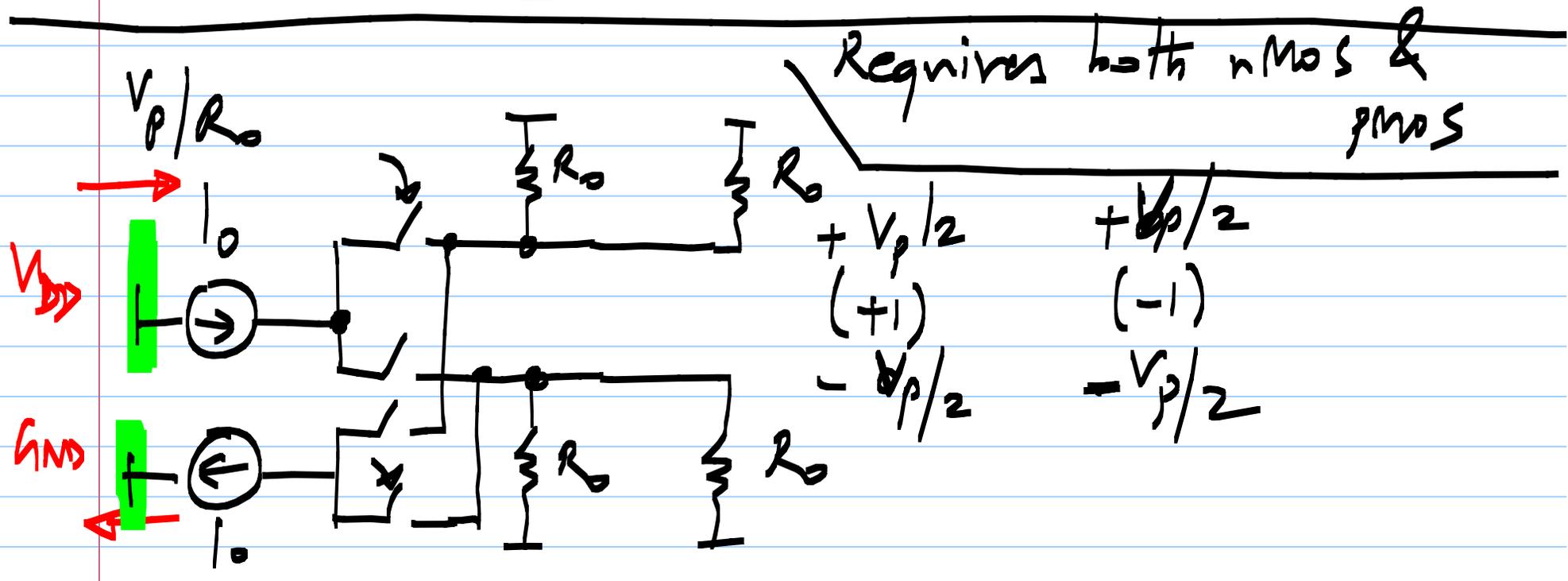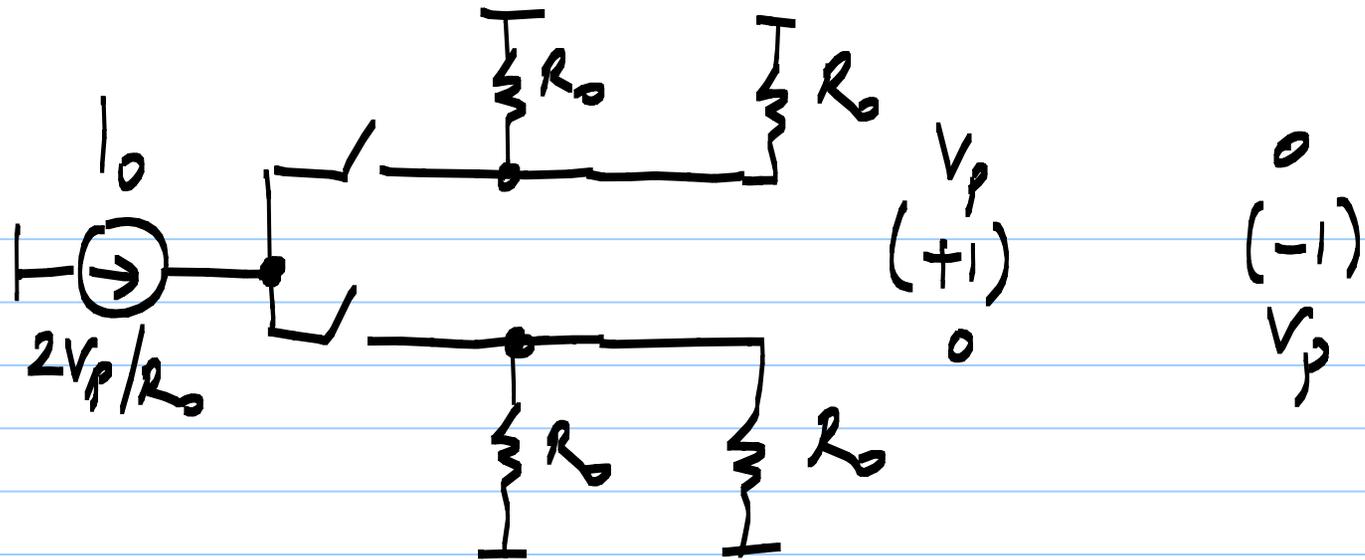


$$\text{Power efficiency} : \frac{\text{Power dissipated (TR}_x\text{)} (W)}{\text{Data rate (b/s)}}$$

$$: \frac{\text{Energy}}{\text{bit}}$$




State of the art : $< 4 \text{ pJ/bit}$

$$\underline{1 \text{ pJ/bit} = \frac{1 \text{ mW}}{\text{GHz}}}$$

Current mode driver: (No equalization)

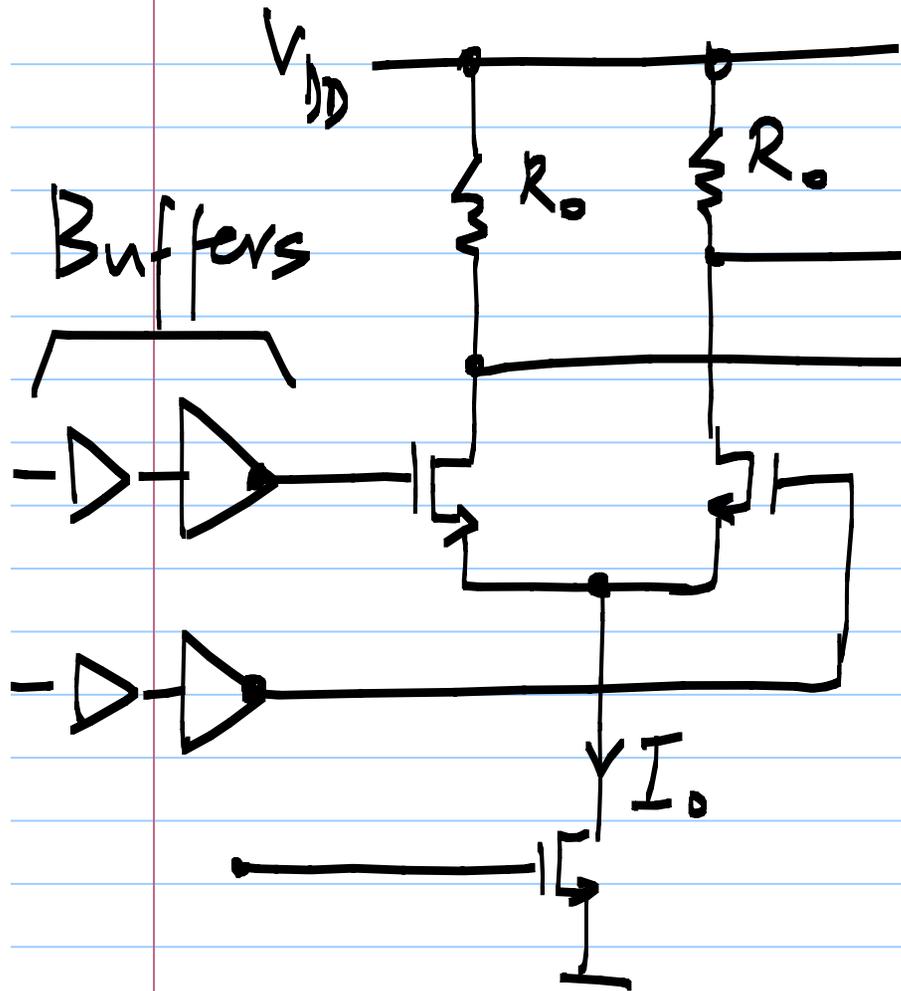


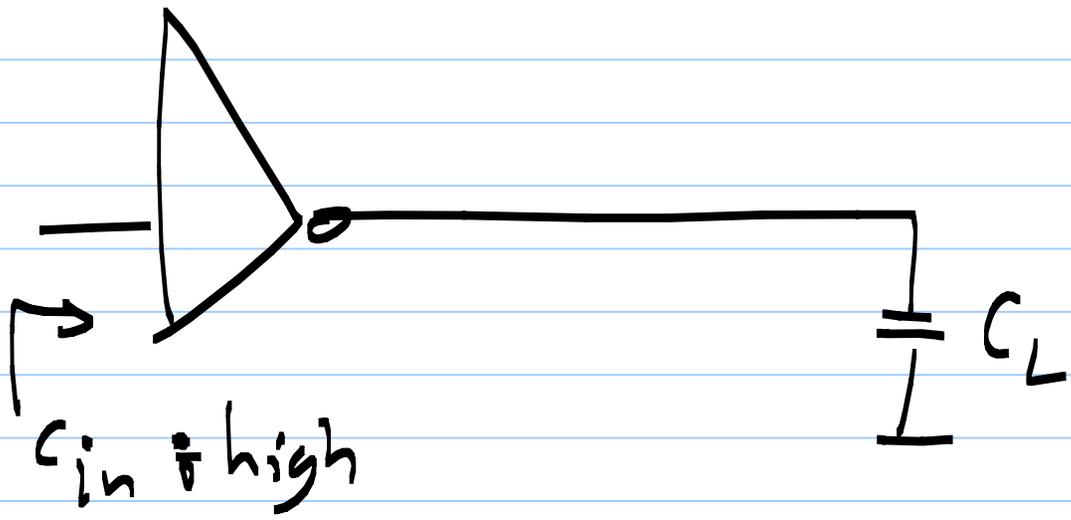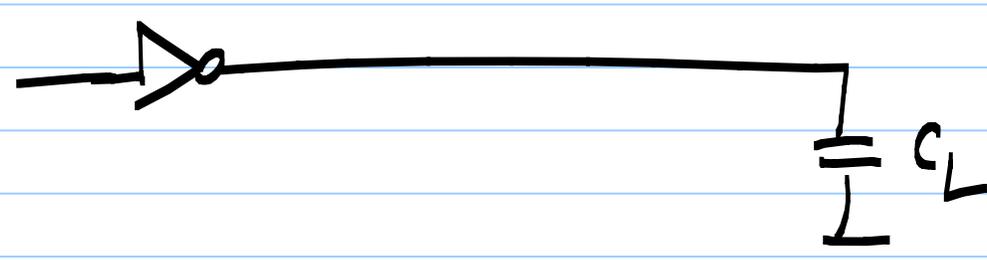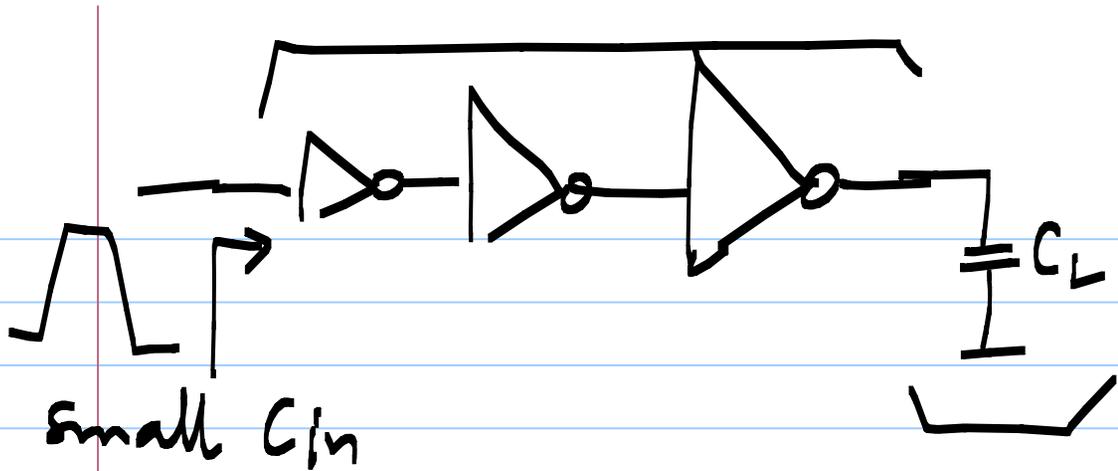Diff pair: has to switch current from one side to another $\Rightarrow \frac{W}{L}$ (Lmin)



Use $R_T > R_0$

R_0
 $R_T > R_0$

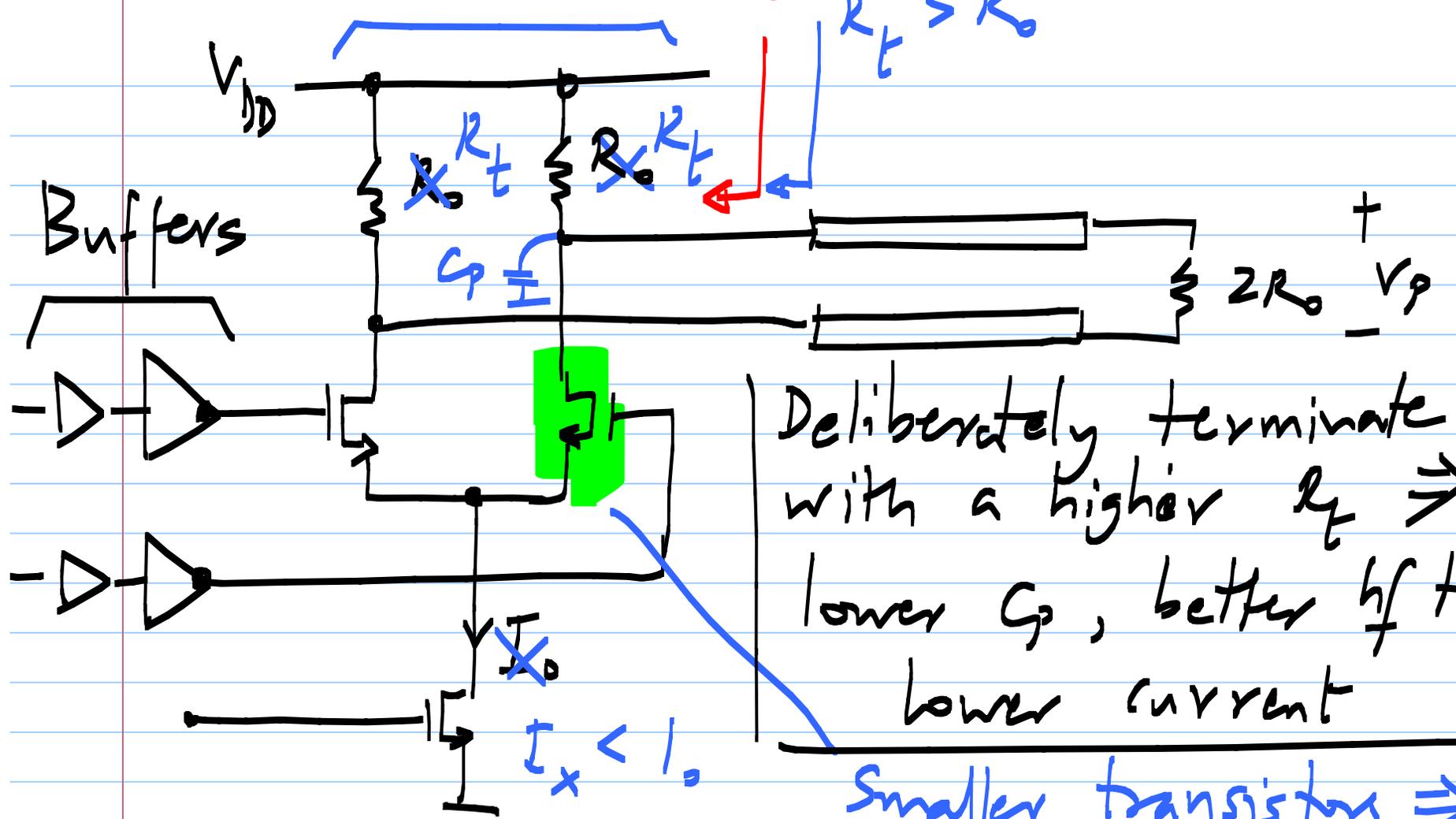

Deliberately terminate with a higher $R_T \Rightarrow$ lower C_p , better hf term, lower current

Smaller transistors \Rightarrow Smaller C_p .


Equalization:

Peak: $h_0 + \sum_{k \neq 0} |h_k|$

Cursor: h_0



DC gain: $\sum_k h_k$

Common-mode current sources

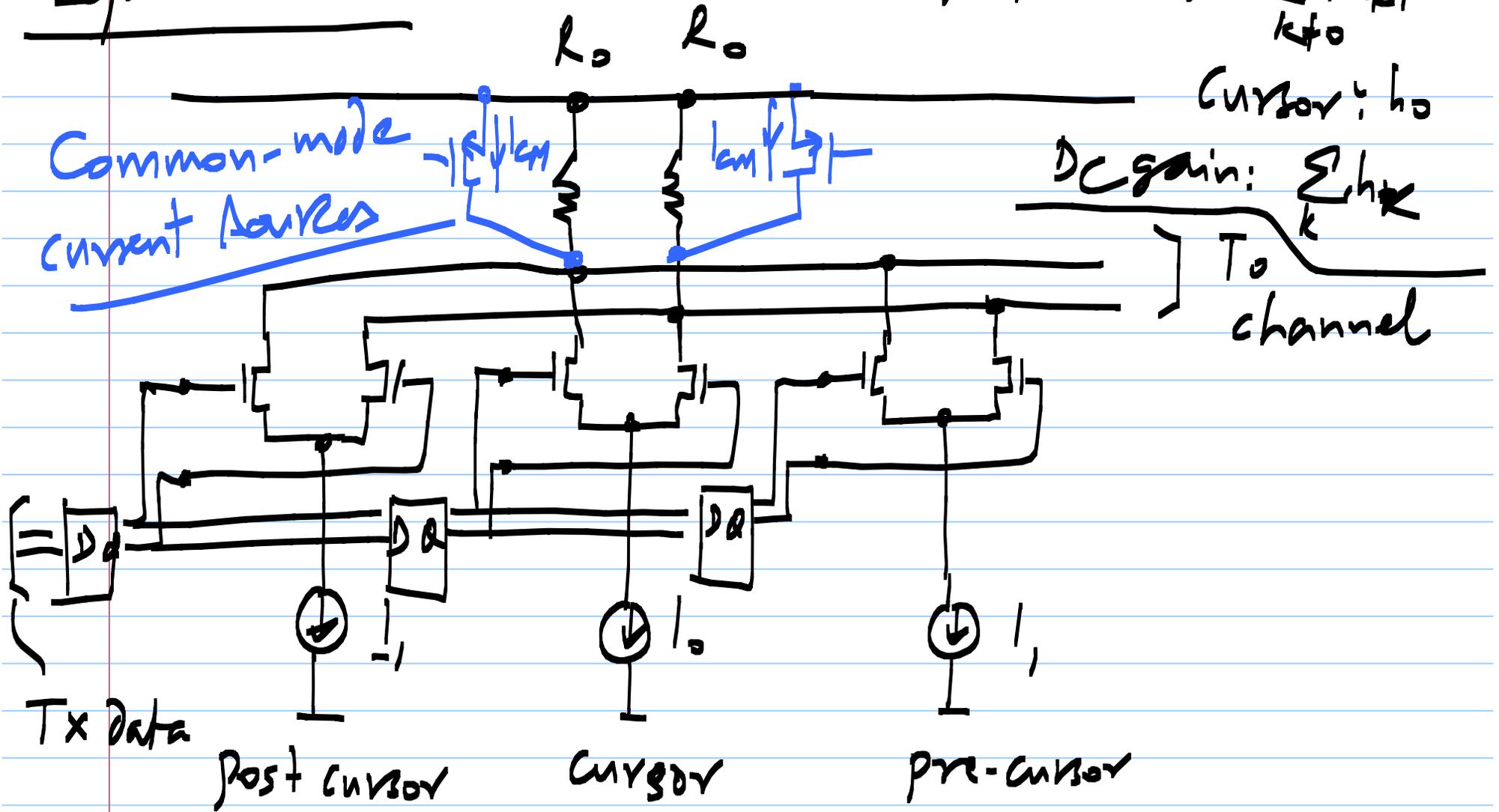


DAC based Tx


$$\underline{[b_1 \dots b_N] = x}$$

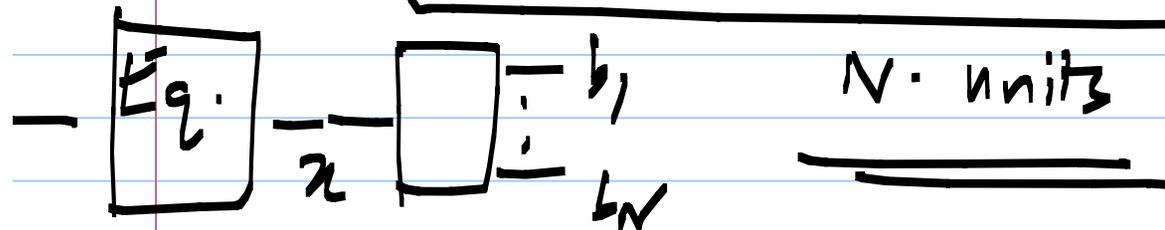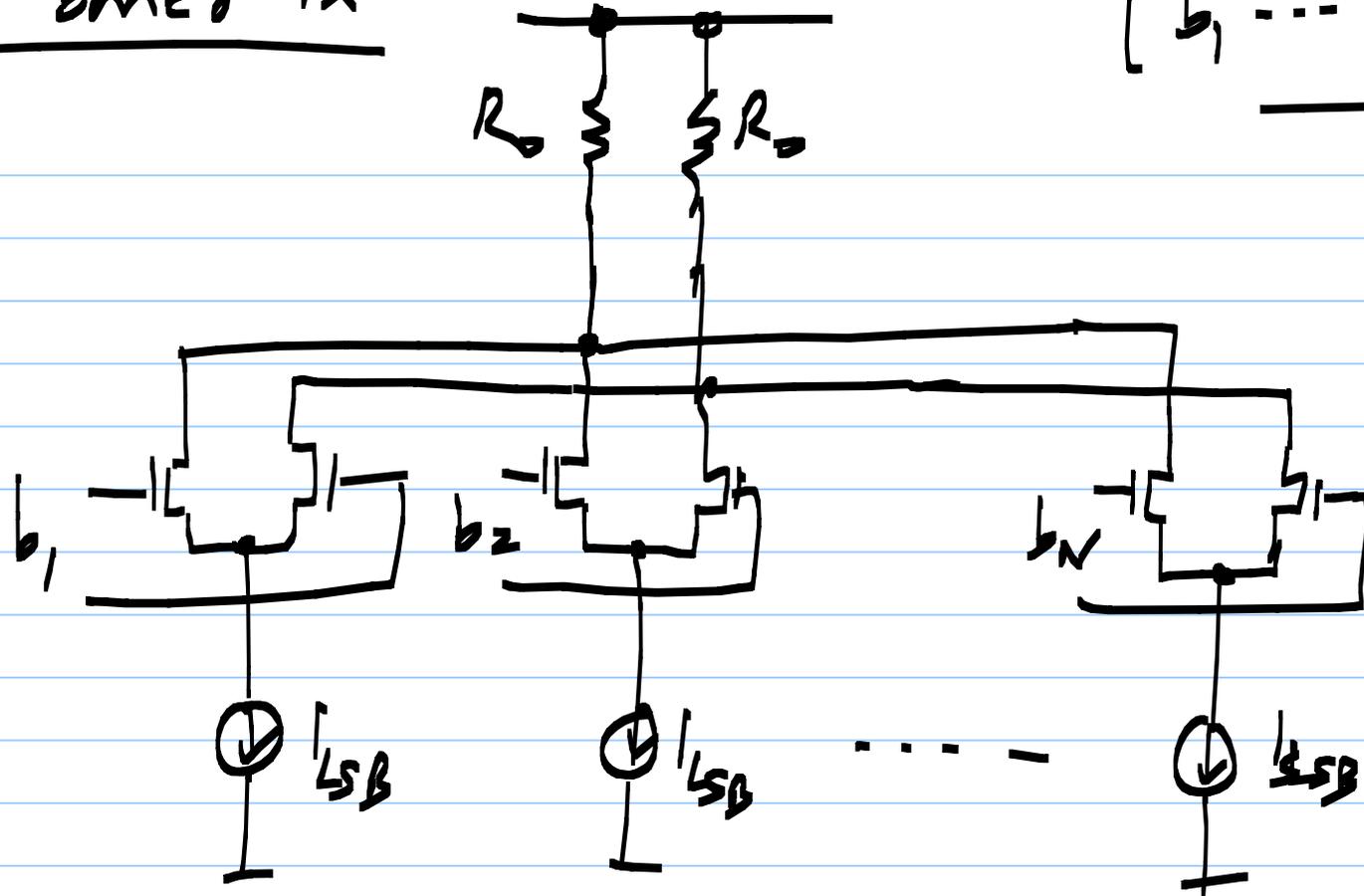



No equalization:

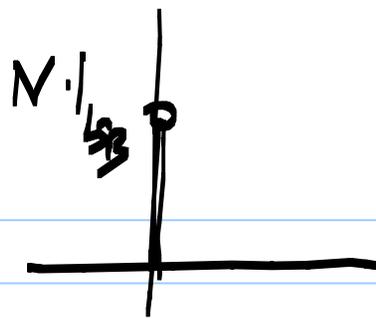


|||

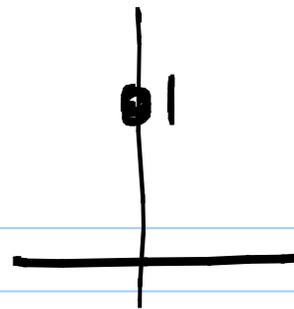


1 tap equalization:

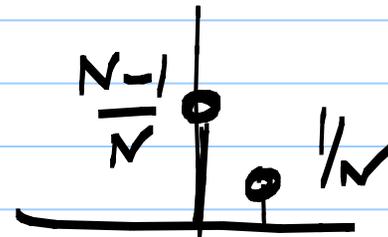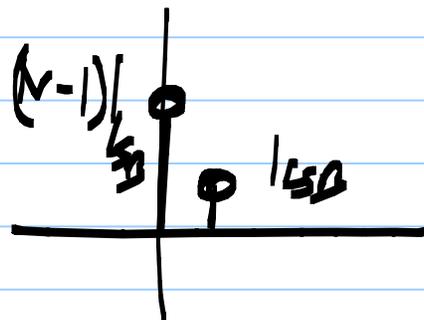

Semi-digital :

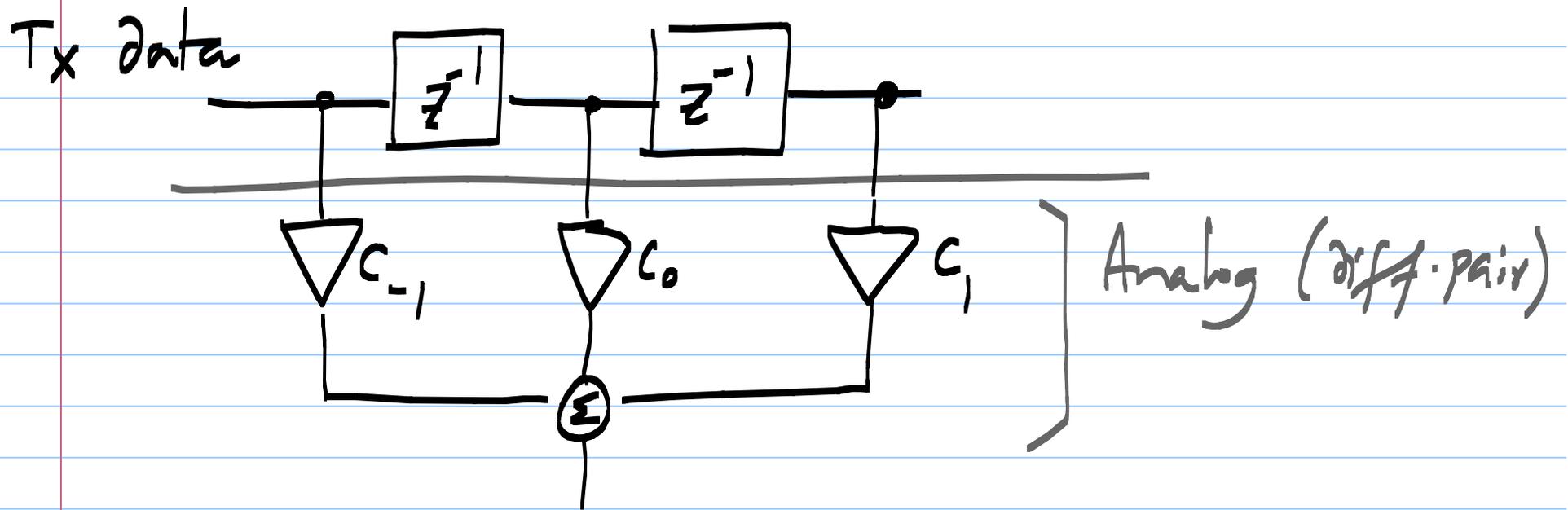

Digital

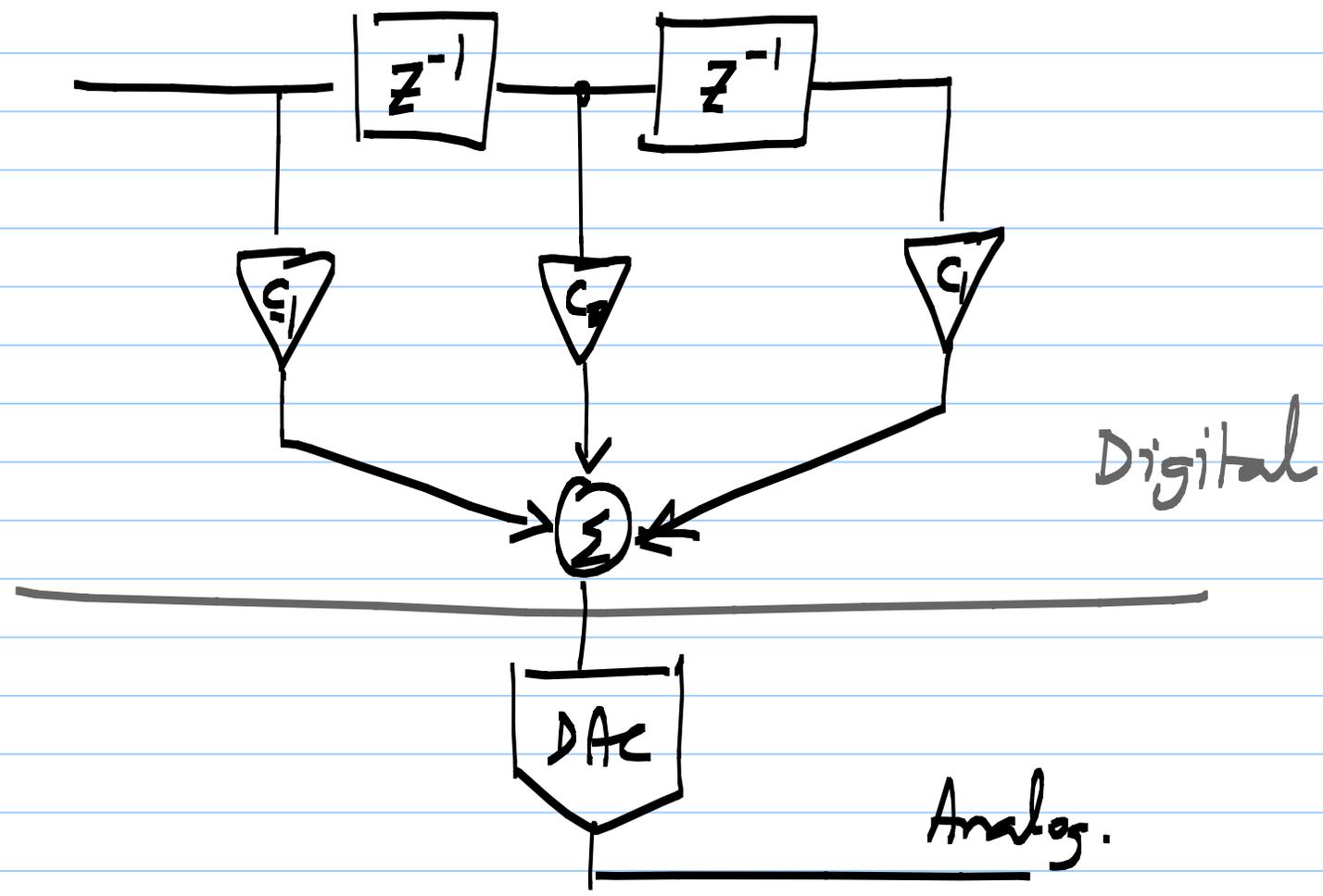

Digital

Analog.