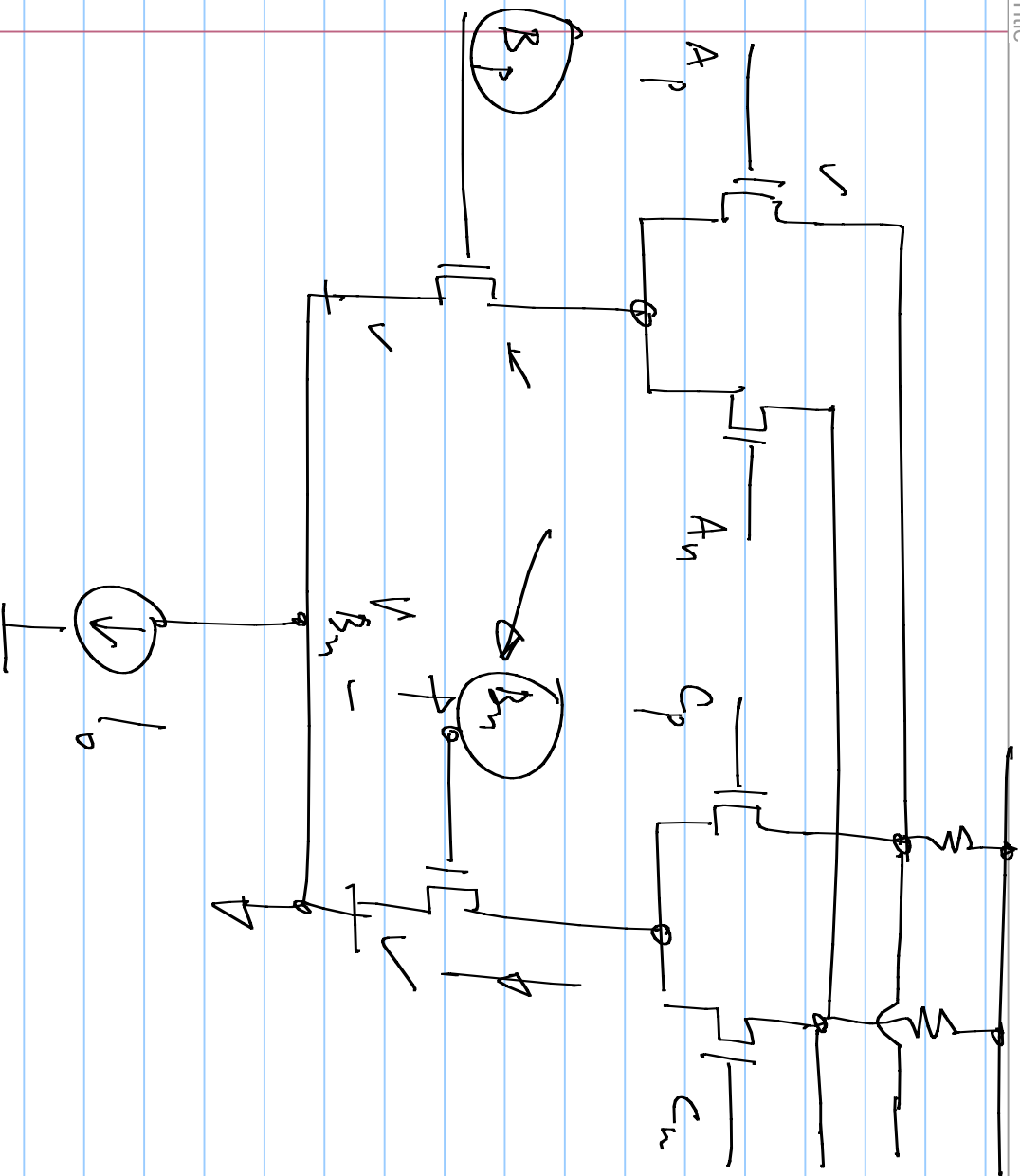


Current mode logic V_{DD} V_{SS}




$$Y = A \cdot B + C \cdot B$$

$$V_{over} = V_{DD} - \frac{I_D R}{2}$$

$$V_T + \sqrt{\frac{2I_D}{\mu C_{ox} W/L}}$$



" " " " " "


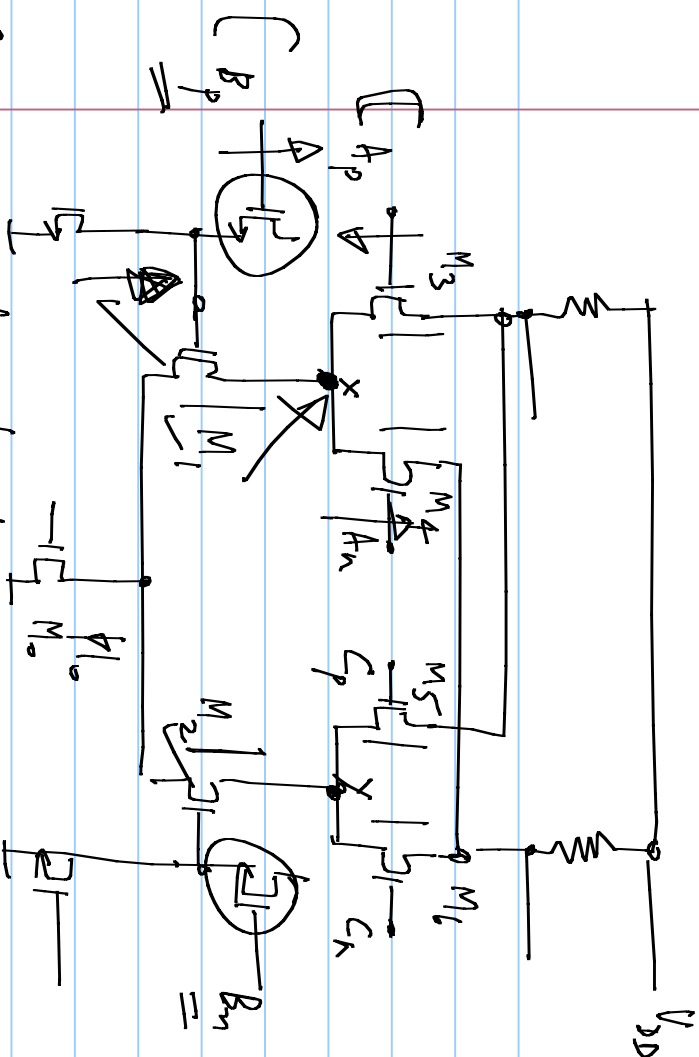


$$V_{DD} - I_{DQ} R_D - V_{DSAT, M4} + V_{T, M1}$$

Common mode limits

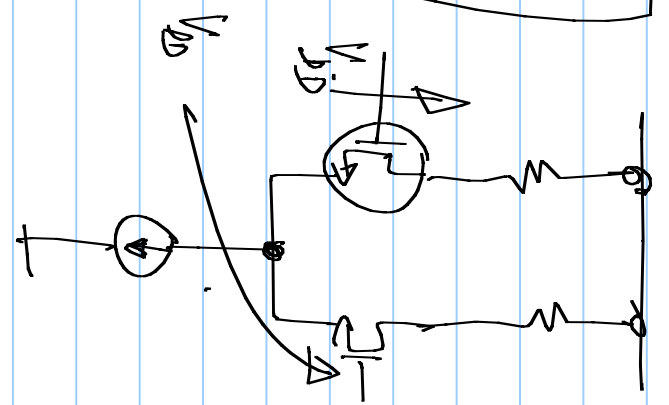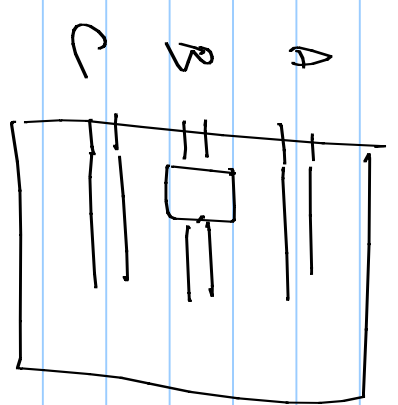
$$V_{B, cm} : V_{T1} + V_{DSAT1} + V_{DSAT2} < V_{B, cm} < V_{A, cm} = V_{DSAT3} - V_{T3} + V_{T1}$$



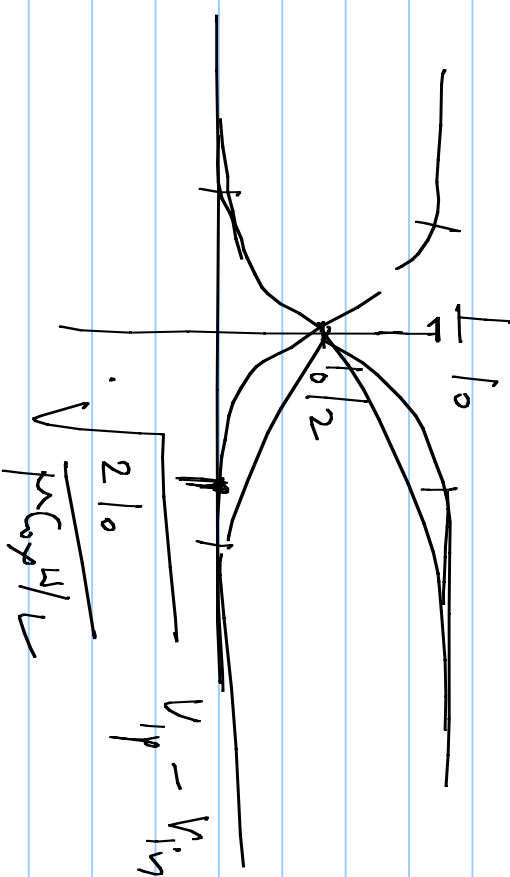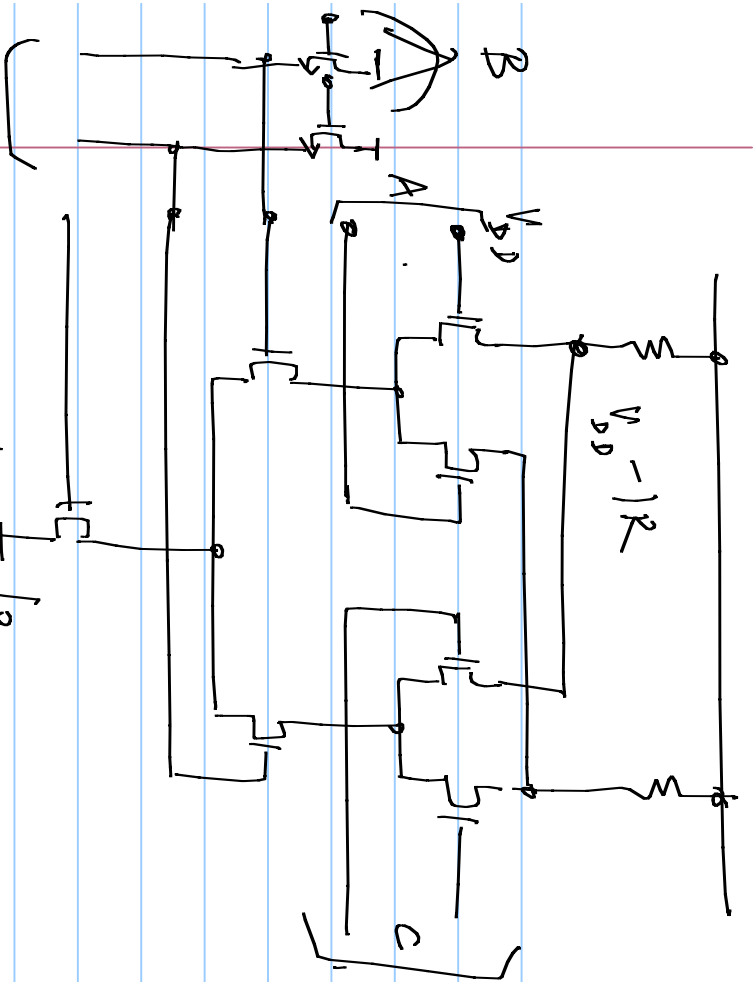

$$IR < V_T$$





$$Y = A \cdot B + C \cdot B$$

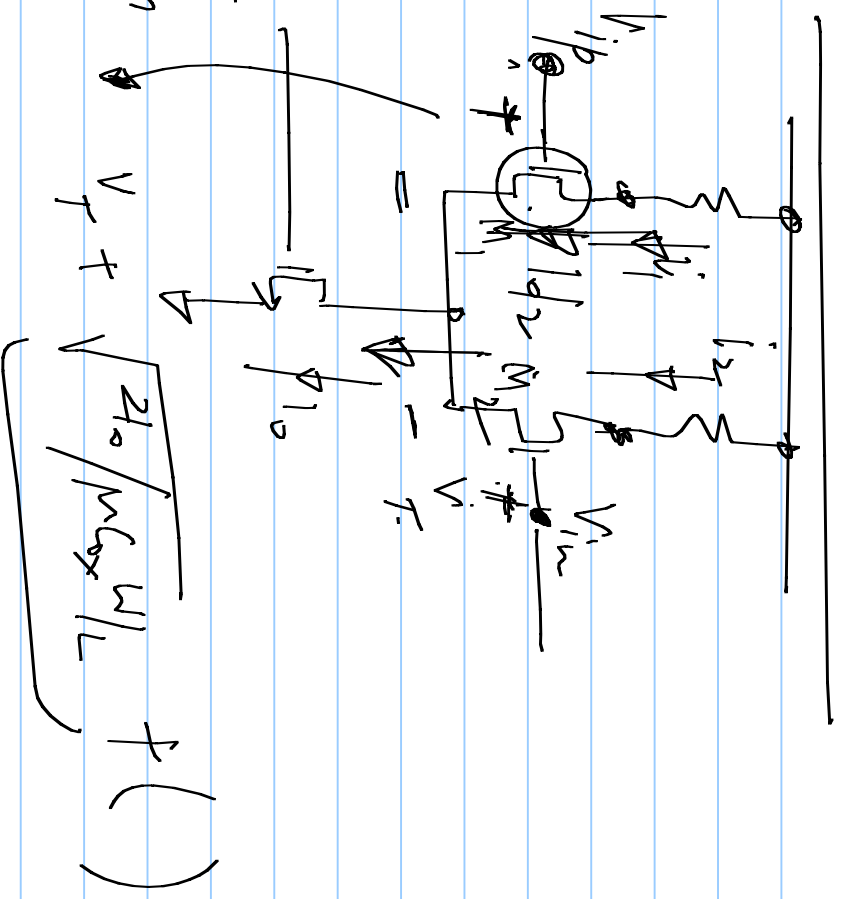

$$Y = A \cdot B + C \cdot \bar{B}$$

D_0 —

$$C = A \bar{A}$$

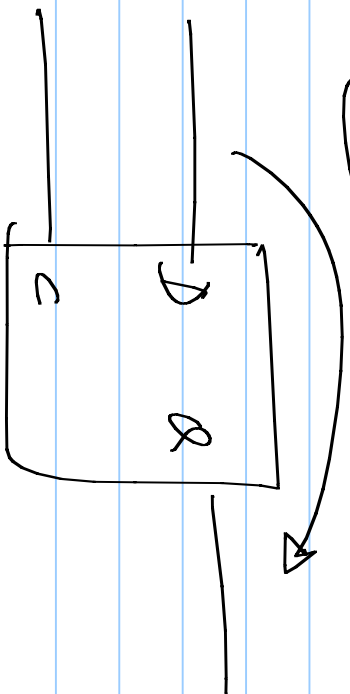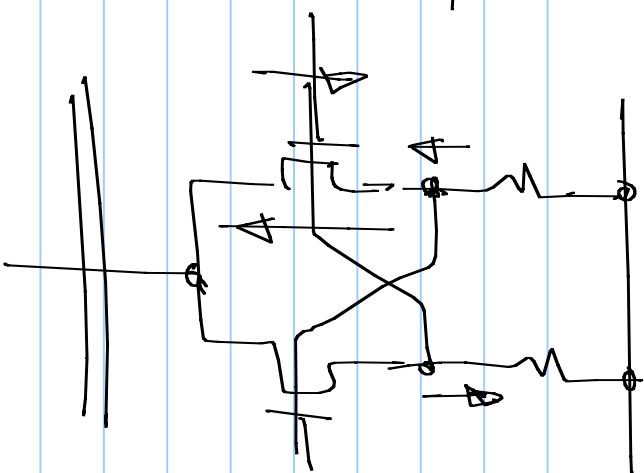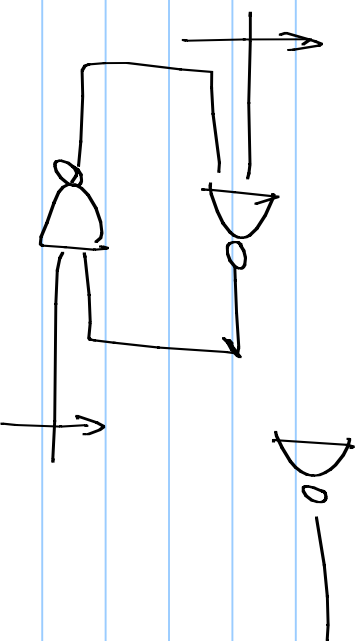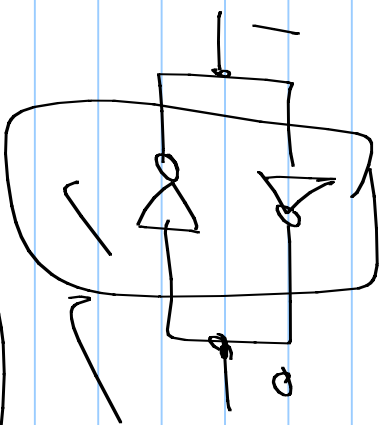

Latch

