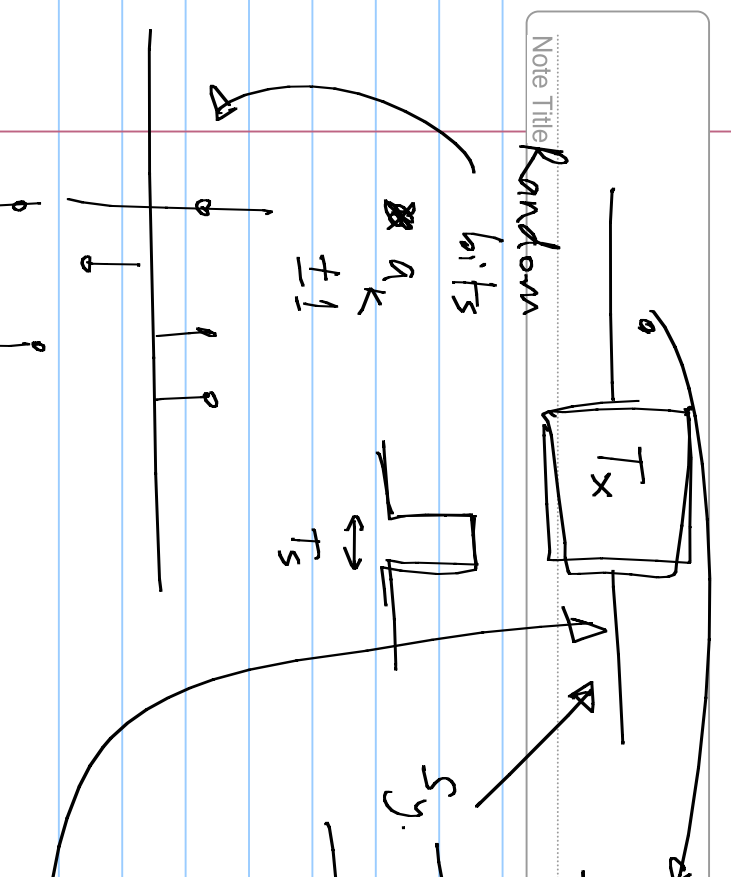



Random

Sinc²


$\frac{f_s}{2}$: Highest frequency periodic signal that can be generated.



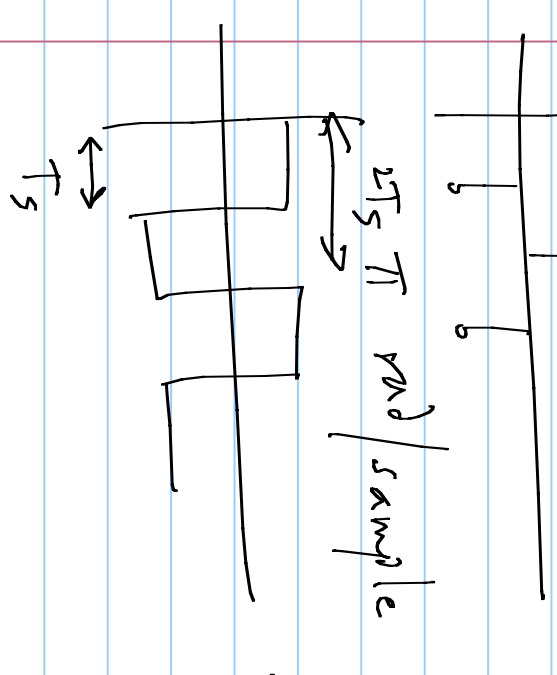frequency
 periodic signal
 that can be
 generated.



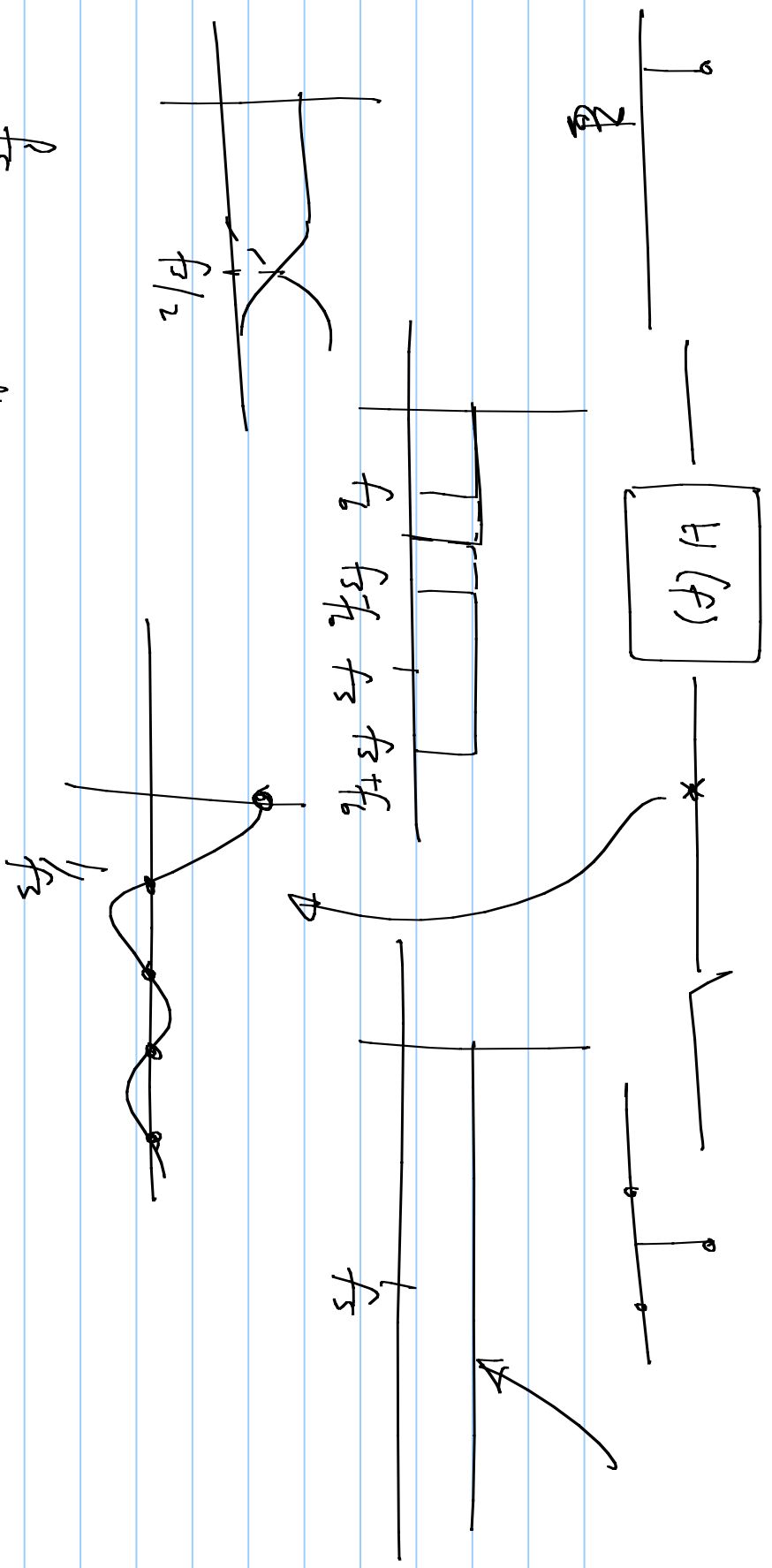
f_s BW required to transmit
 f_s without ISI?
 Sinc(1/2)
 $\frac{2}{f_s}$ -4dB





$\frac{f_s}{2}$: Smallest BW required to have zero ISI

② data rate f_s .

Data transmission over a channel

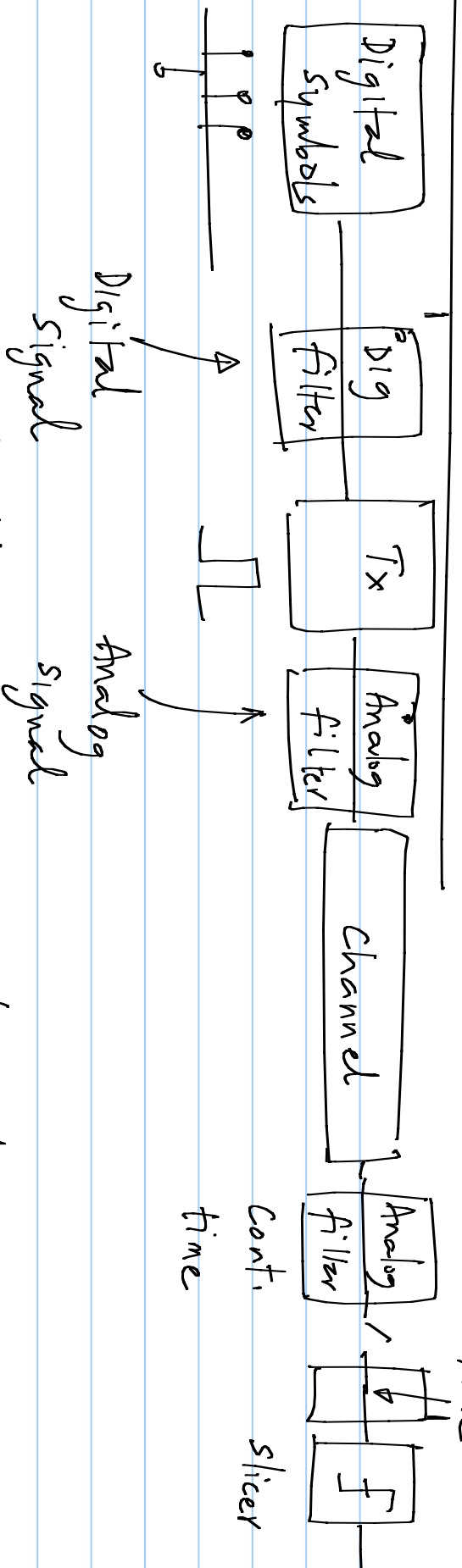

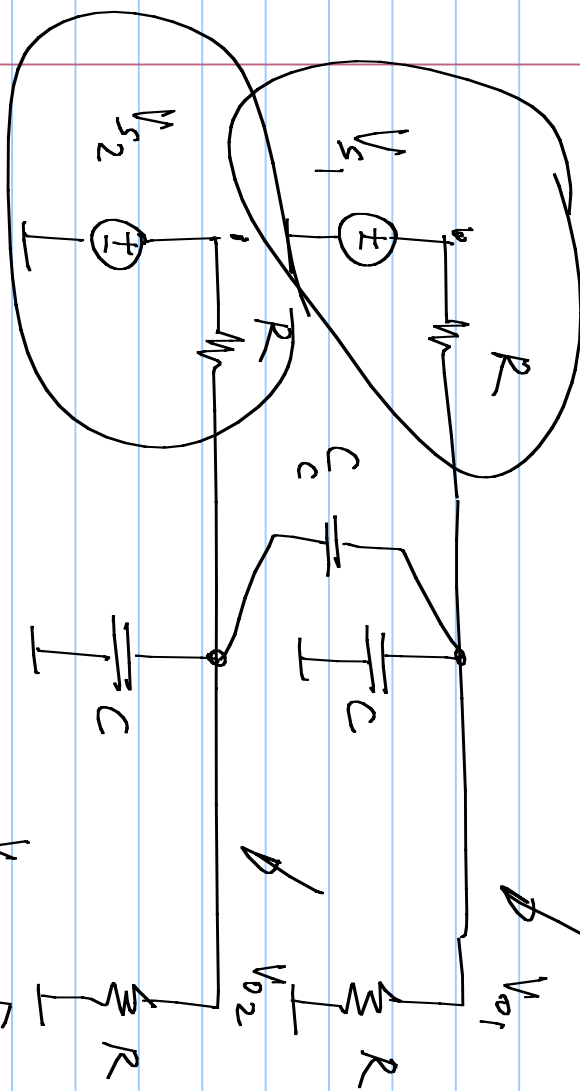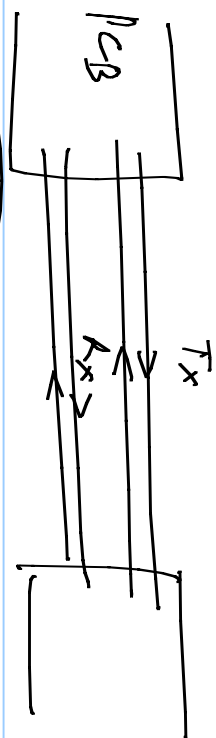* Filter can be placed anywhere along the signal path before the slicer.




$$V_{o1} = \frac{1/2}{1 + s \frac{R C_e}{2}}$$

($C_c = 0$) single pole @ $\frac{2}{R C_e}$

$$\frac{V_{o1}}{V_{s1}}$$
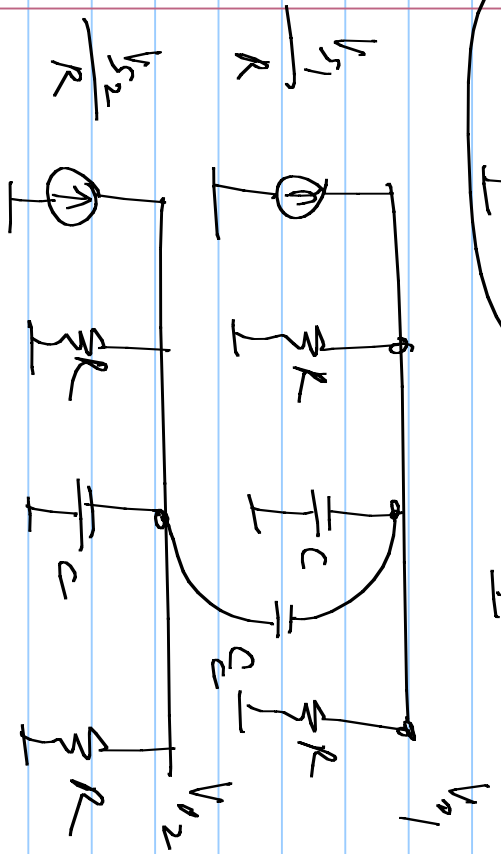
$$\begin{bmatrix} 2q + s(C+C_c) & -sC_c \\ -sC_c & 2q + s(C+C_c) \end{bmatrix} \begin{bmatrix} V_{o1} \\ V_{o2} \end{bmatrix} = \begin{bmatrix} V_{s1}/R \\ V_{s2}/R \end{bmatrix}$$




$$V_0 = \frac{V_{s1} R (sC + C) + 2R)}{(s(C_c + C) + 2R)^2} + \frac{sC_c - V_{s2} - R}{sC_c^2}$$

$$= \frac{V_{s1} \cdot R (2R + s(C + C_c)) + R \cdot sC_c - V_{s2}}{(2R + s(2C_c + C)) (2R + s - C)}$$

Crossfallk

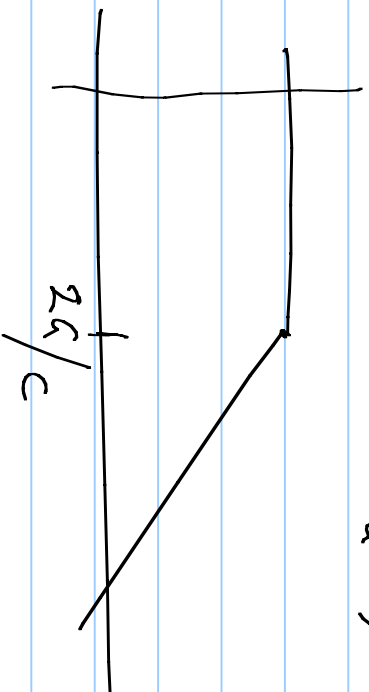
$$= V_{s1} \cdot \frac{1}{2} \left[\frac{1 + \frac{s \cdot C + C}{2R}}{\left(1 + \frac{s(2C_c + C)}{2R}\right) \left(1 + \frac{s - C}{2R}\right)} + \frac{V_{s2} \cdot 1}{sC_c/2R} \right] (s)$$



pole @ $\frac{2R}{C}$

poles @ $\frac{2R}{2C_c + C}$, $\frac{2R}{C}$

$\frac{C + C_c}{2R}$

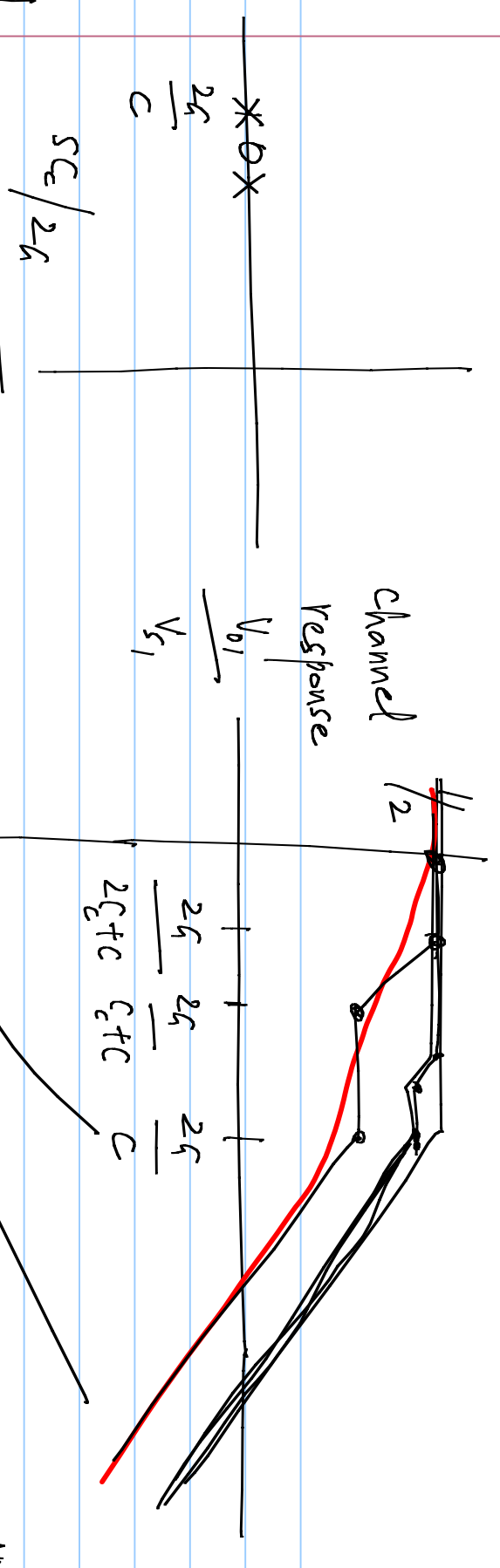

$$\frac{1}{\sqrt{2}} \cdot \frac{1}{\left(1 + \frac{s_c}{2f}\right)^2}$$

$$\frac{\frac{2f}{c} \cdot \frac{2f}{c}}{\left(1 + j1\right)^2}$$

$$\left[V_{s2} \cdot \frac{1}{2} \right] \left(\frac{c/c}{2} \right)$$

Crosstalk

$\frac{V_{o1}}{V_{s2}}$

high pass

- * Crosstalk because of coupling to other lines
 - highpass behavior
- * Equalizer - highpass
 - Amplifies high components of the signal
 - amplifies crosstalk

