

① * large C

* R_x input

Common mode
voltage is indep
-endent of T_x

① ac coupled T_x output

* $V_{com} = V_{DD} - I_{tail} R/2$

* signal swing $I_{tail} R$ (pp)

* T_x s/p common mode
is independent of the R_x


② R_x : large common
mode resistance

* $V_{com} = V_{DD} - I_{tail} R/2$

* signal swing $I_{tail} R$

* T_x o/p common mode
is independent of the R_x

* dc Coupled

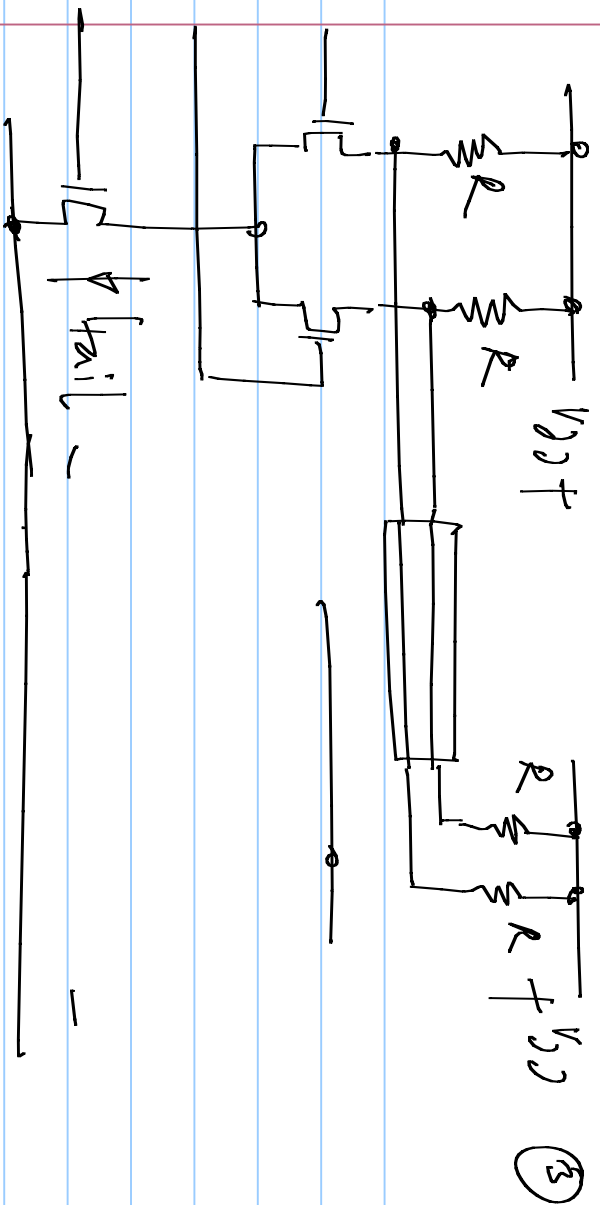

$$V_{oem} = V_{DD} - I_{tail} \frac{R}{4} \quad (3)$$

Swing: $I_{tail} R \cdot (pp)$

larger V_{oem} . so

Can accommodate

a larger swing

* Cannot expect


same supply & ground



on T_x , R_x sides

Useful only when

T_x , R_x are on




the same board.

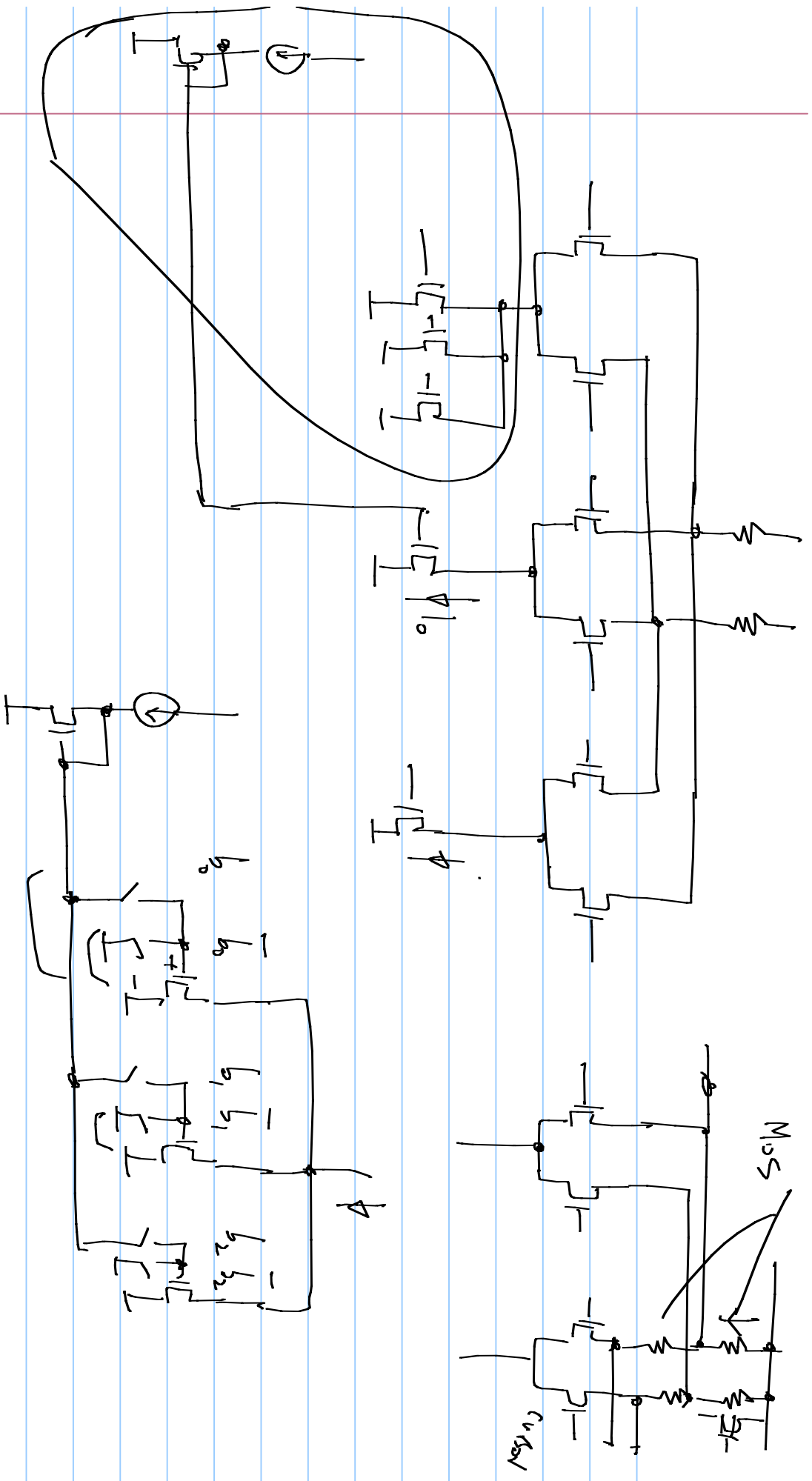

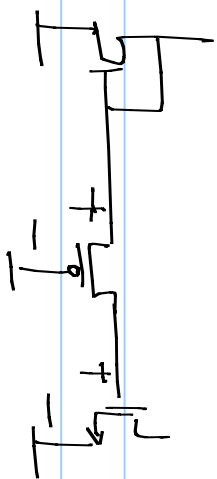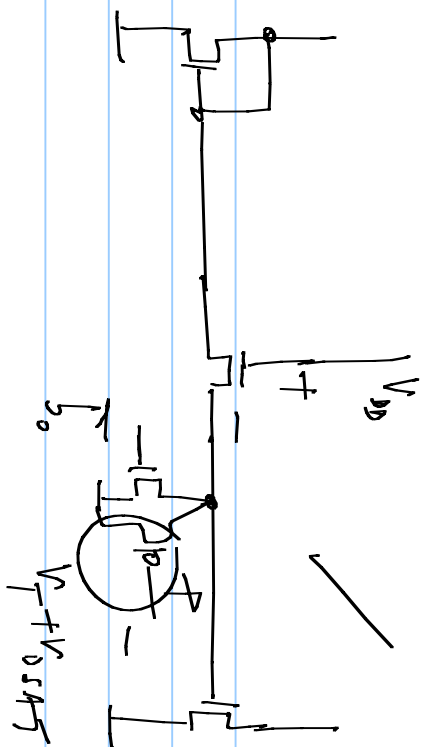


$V_{DD} > 2V_{DSAT}$

NMOS.

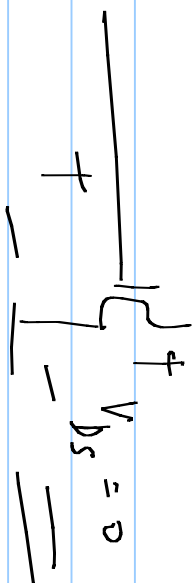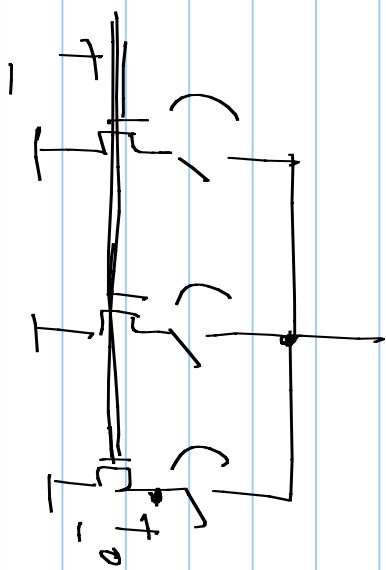
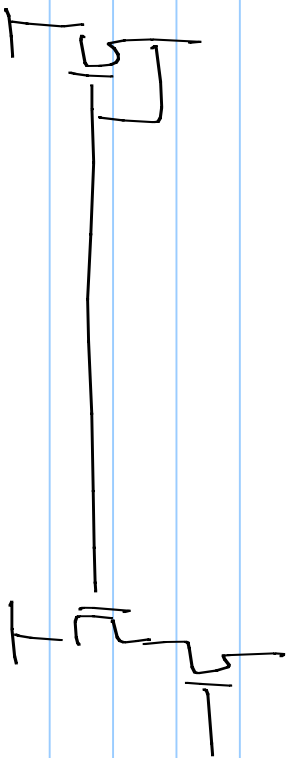



Use an nMOS
switch @ drain

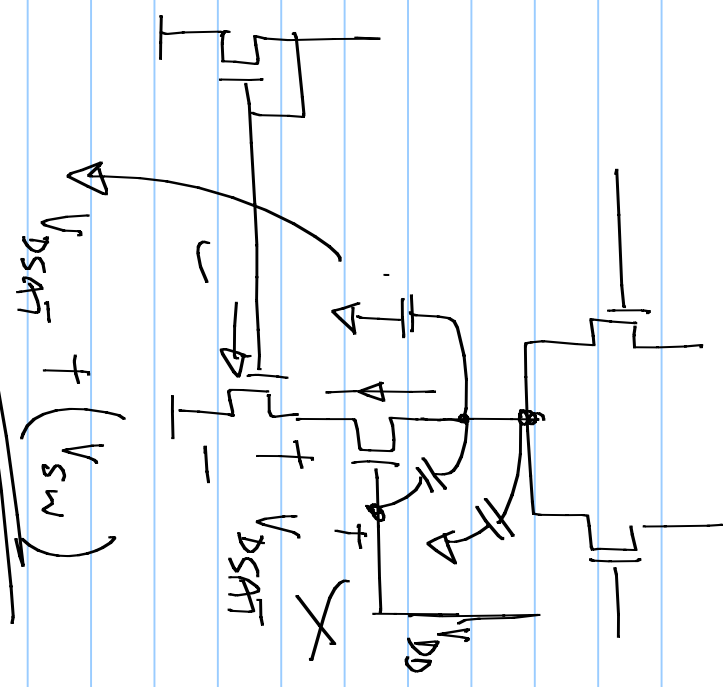



Switch: large to reduce V_{SW}


$$V_{DSAT} - V_T < 0$$

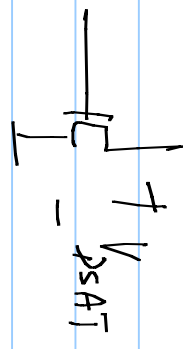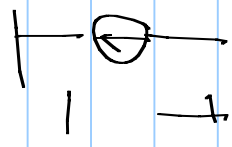

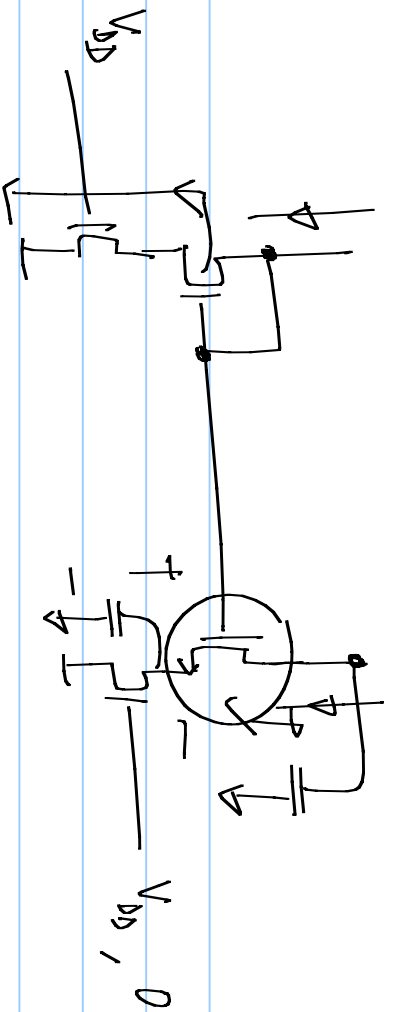
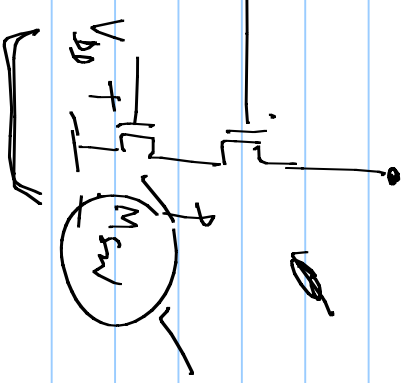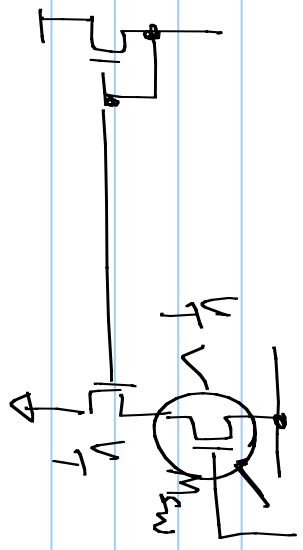
$$\frac{V_{DSAT}}{V_{5V}} = \frac{150 \mu V}{V_{5V}}$$




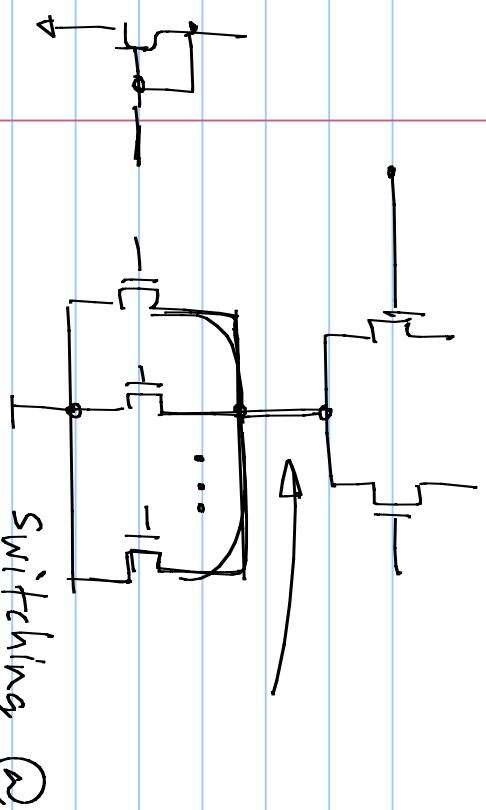

Switching @ source / gate

Source

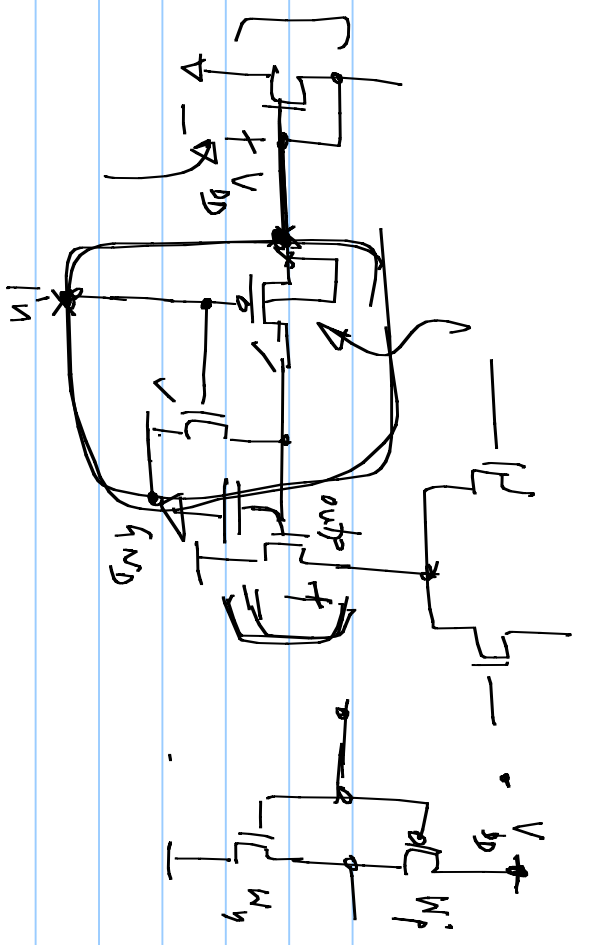- larger switch size
- Drop across the switch
- + Don't need complementary controls



gate

- + smaller switch size
- + No extra drop across the current source
- Complementary controls