
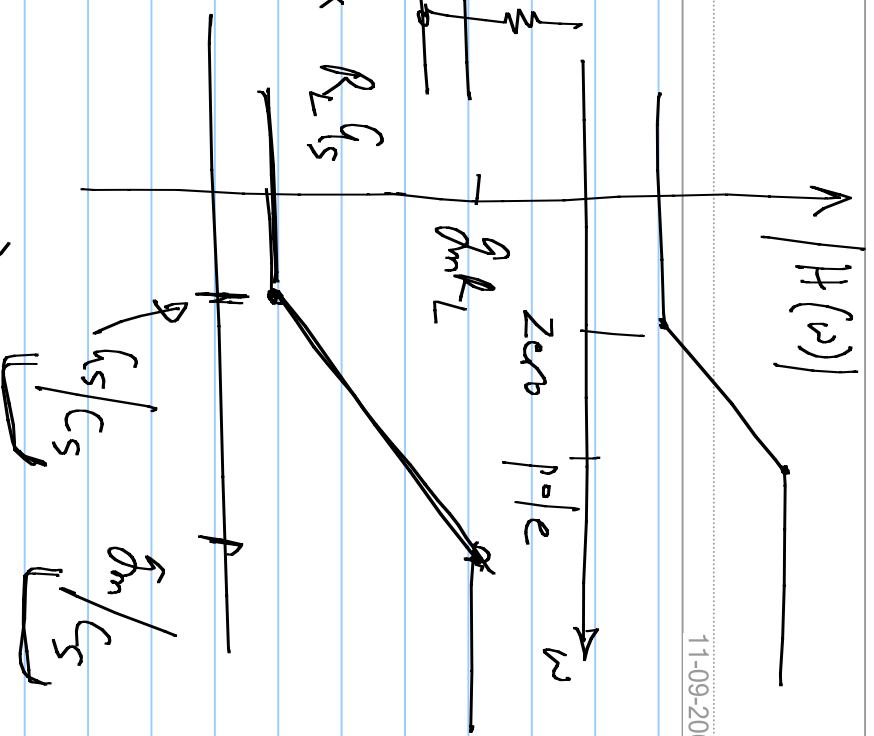
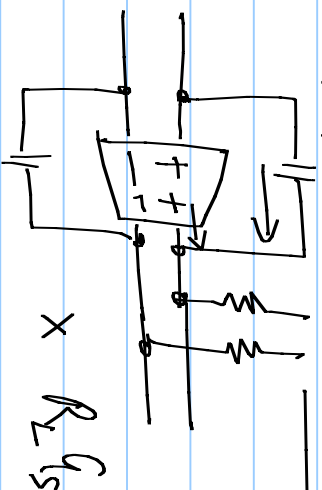


CT Equalizer:

Note Title

11-09-2007

Response With a zero & a pole.

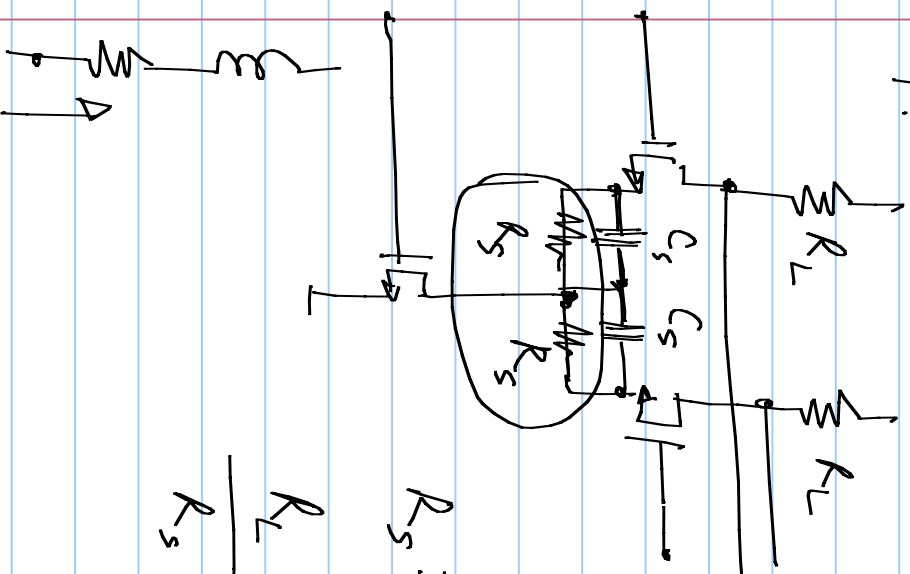



$$R_s \gg \frac{1}{g_m} \rightarrow \frac{R_L}{R_s} \rightarrow R_L (G_s + s C_s)$$




$$\frac{g_m R_L}{1 + g_m \cdot Z_s} = \frac{g_m R_L}{1 + g_m \left(\frac{R_s}{1 + s C_s R_s} \right)} = g_m R_L \cdot \frac{1 + s C_s R_s}{1 + g_m R_s + s C_s R_s}$$

$$= \frac{g_m R_L}{1 + g_m R_s} \cdot \frac{1 + s C_s R_s}{1 + \frac{s/\omega_0}{Q} + (s/\omega_0)^2}$$



20 dB/dec

$|H(\omega)|$ Equalizer response



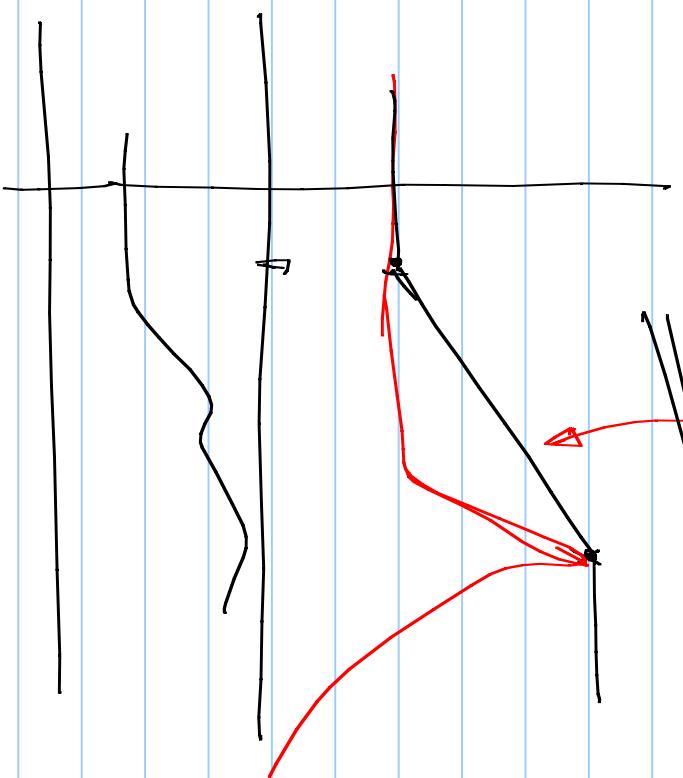
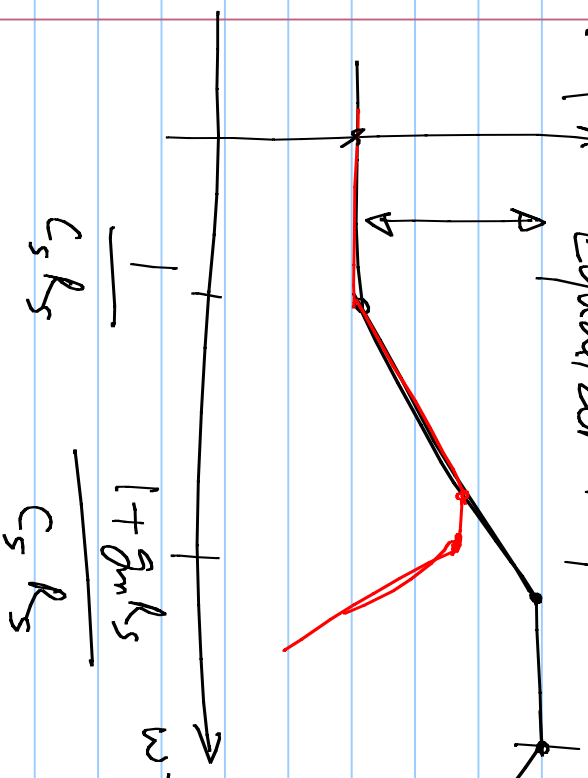


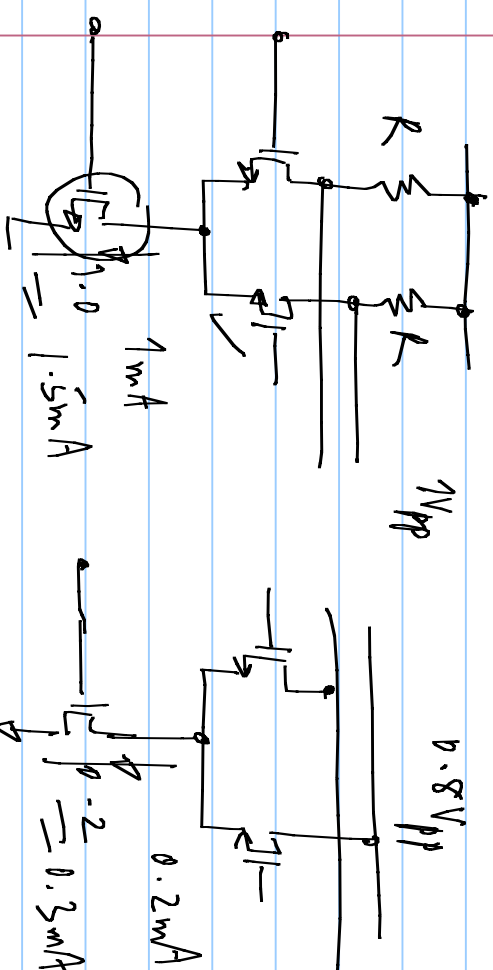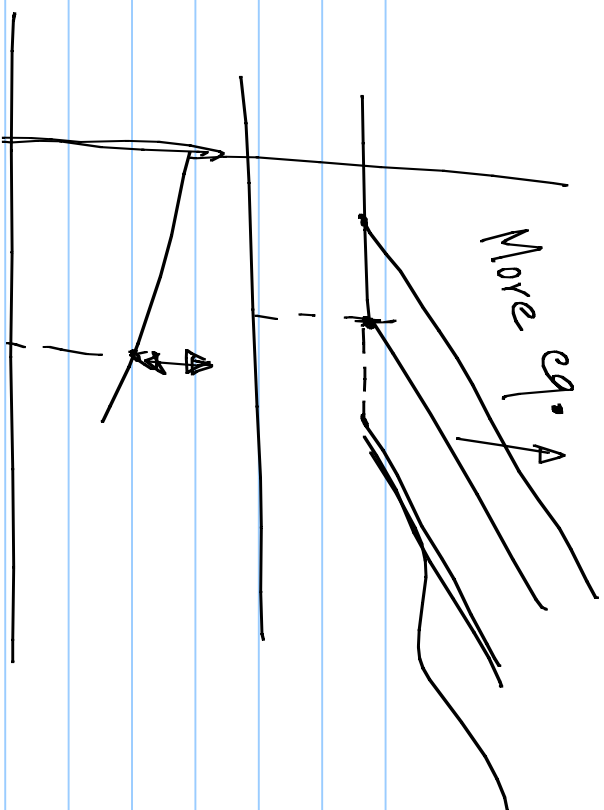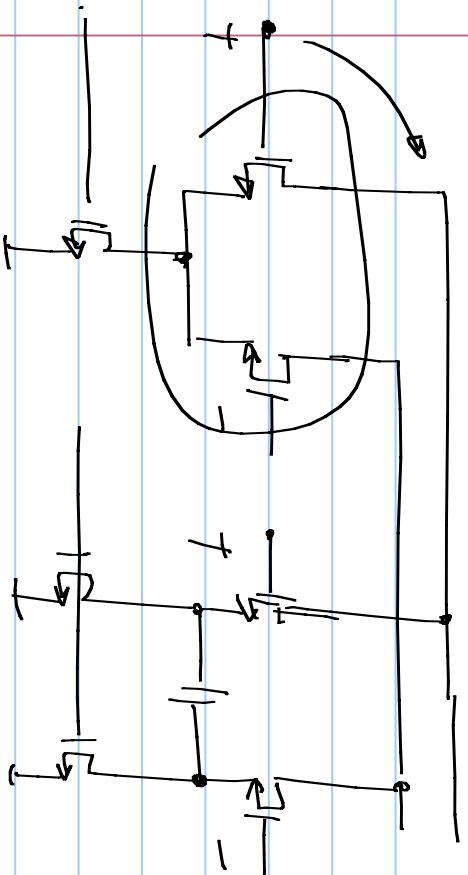


$(1, -0.8)$

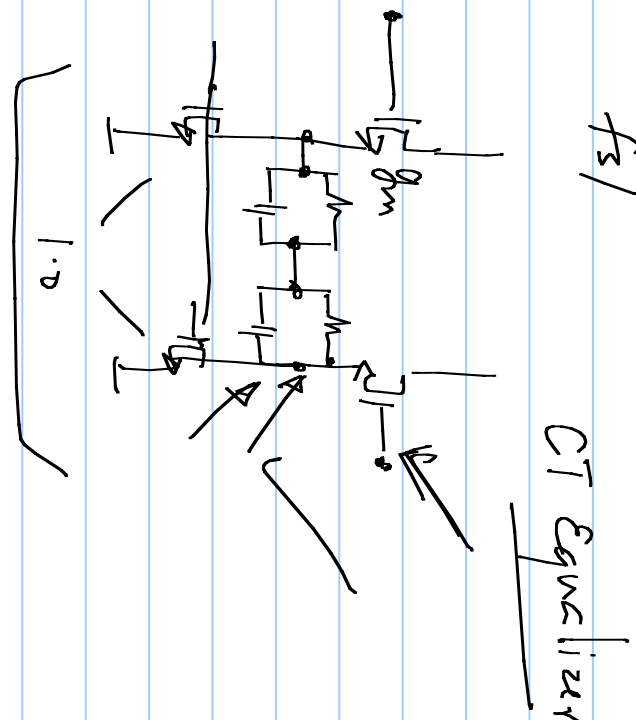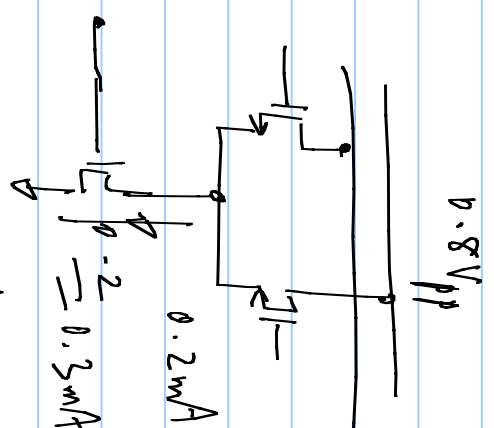

CT Equalizer

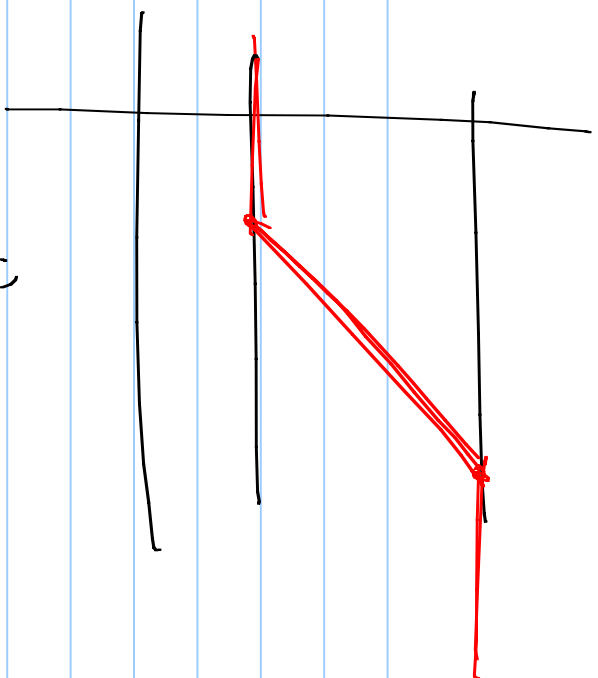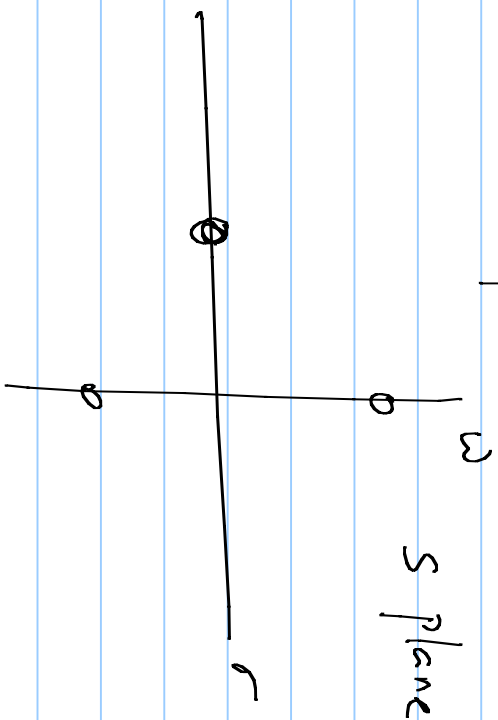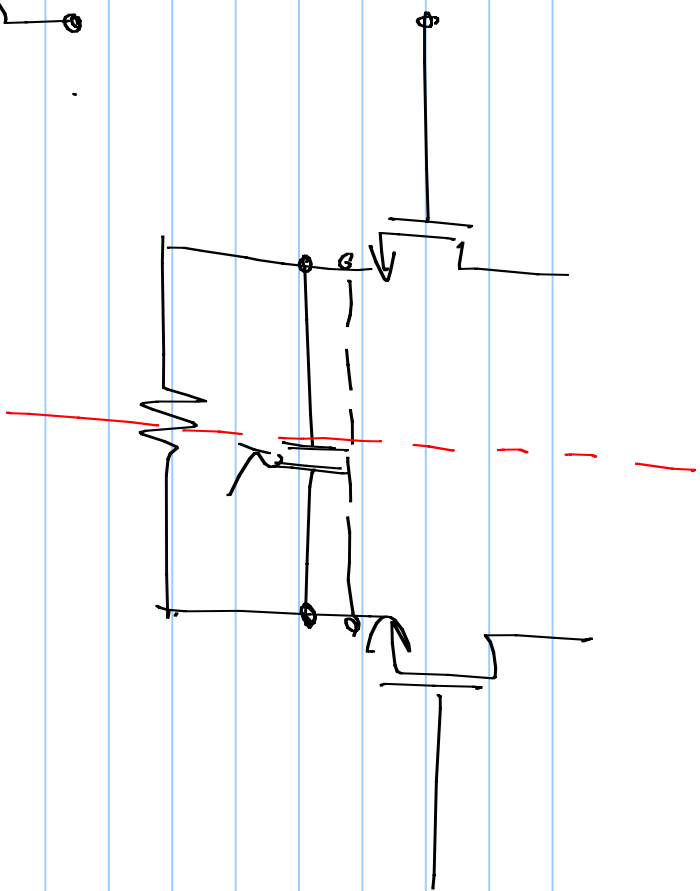
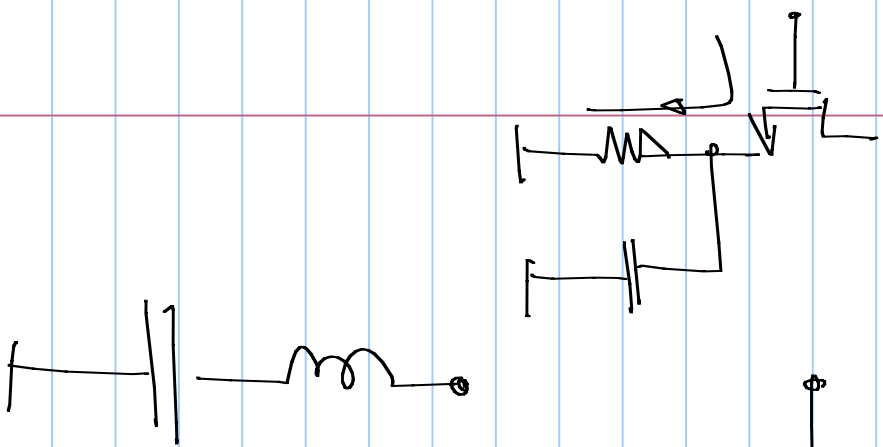


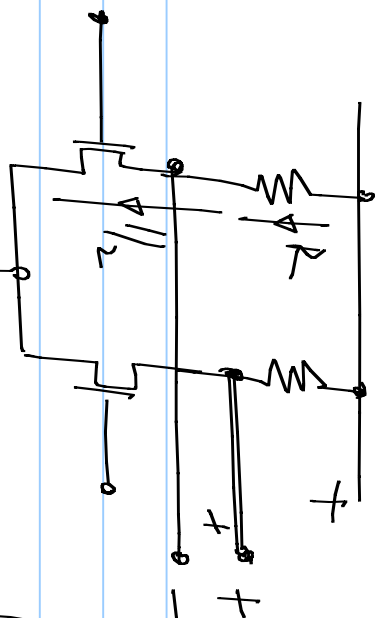

R (onchip) $\pm 25\%$

$$1/R: \frac{225\text{mV}}{300\text{mV}}$$

$$375\text{mV}$$

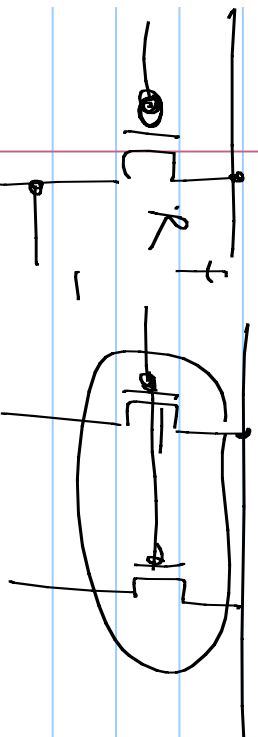
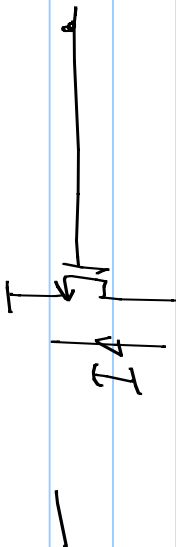


- ① Measure the o/p, adjust I
- ② Make a tunable resistor (pMOS) - adjust that



Measure the o/p cm voltage

& adjust the resistance
current



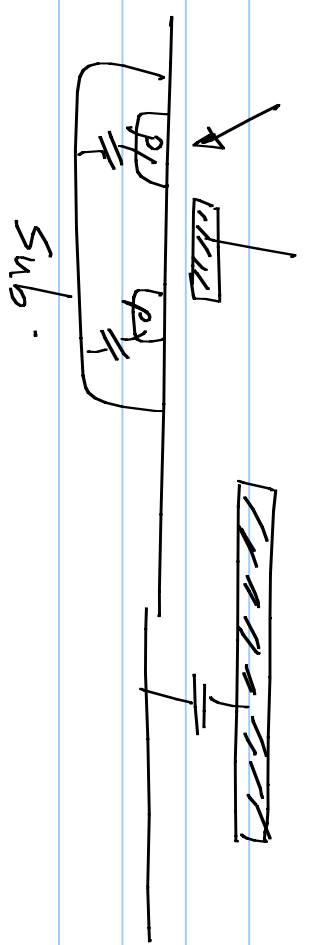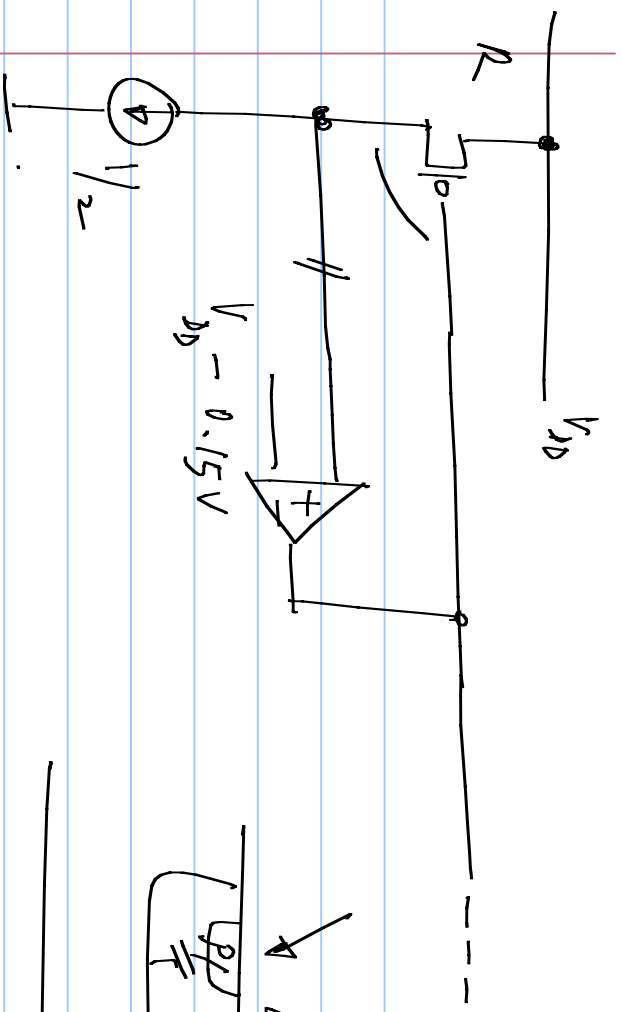
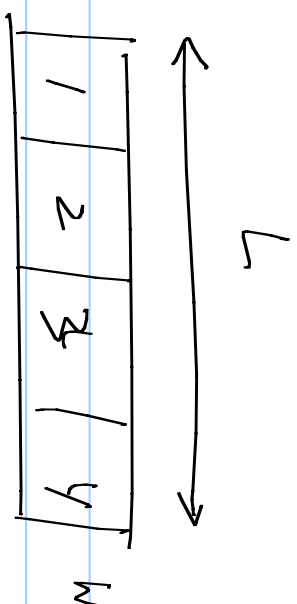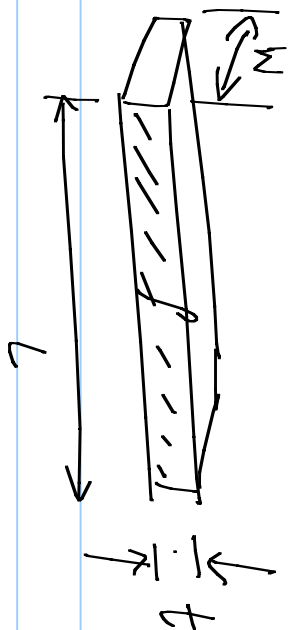
$$I_{bias} = \frac{V_{ref}}{R} = \frac{V_{ref}}{R_{sh} \cdot \frac{L_1}{W_1}} = \frac{V_{ref}}{R_{sh} \cdot \frac{L_1}{W_1}} = I_{bias}$$



$$\int \cdot \frac{L}{W(t)}$$

$$\left(\frac{1}{t}\right) \cdot \left(\frac{L}{W}\right)$$

$$\frac{L}{W}$$

R_{sk}

$$\frac{E \cdot A}{d}$$

$$\frac{L}{sq.}$$