

Receiver equalizer


Note Title

19-09-2007


FIR equalizer

- Transmission line / L.C transmission line (lumped approximation)
- Sample & Holds to implement delays
- A/D conversion + Digital filter implementation

Delay using RC

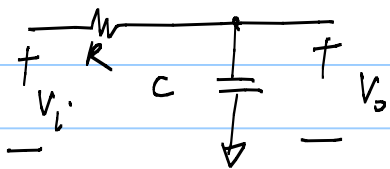

$$\frac{V_o}{V_i} = \frac{1}{1 + sCR}$$

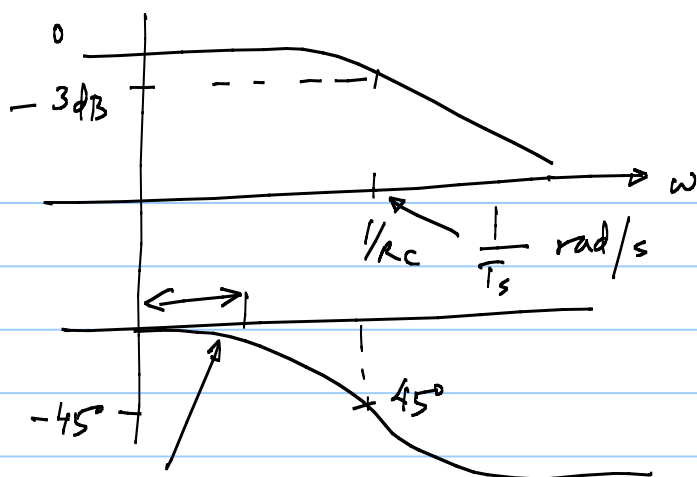

$$\phi = -\tan^{-1}(\omega CR)$$

1 GHz



$$\frac{1 \text{ GHz}}{2\pi \cdot 1 \text{ ns}}$$


$$= 159 \text{ MHz}$$

$$\frac{\partial \phi}{\partial \omega} = \frac{CR}{1 + (\omega CR)^2}$$


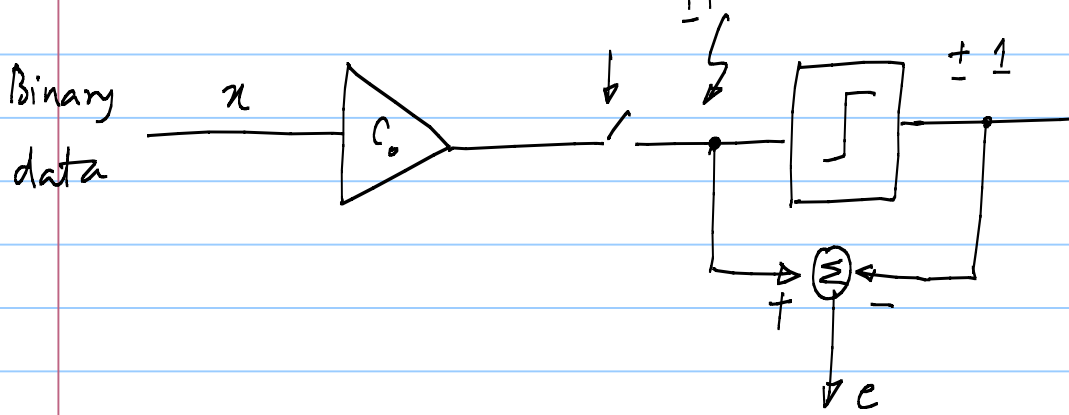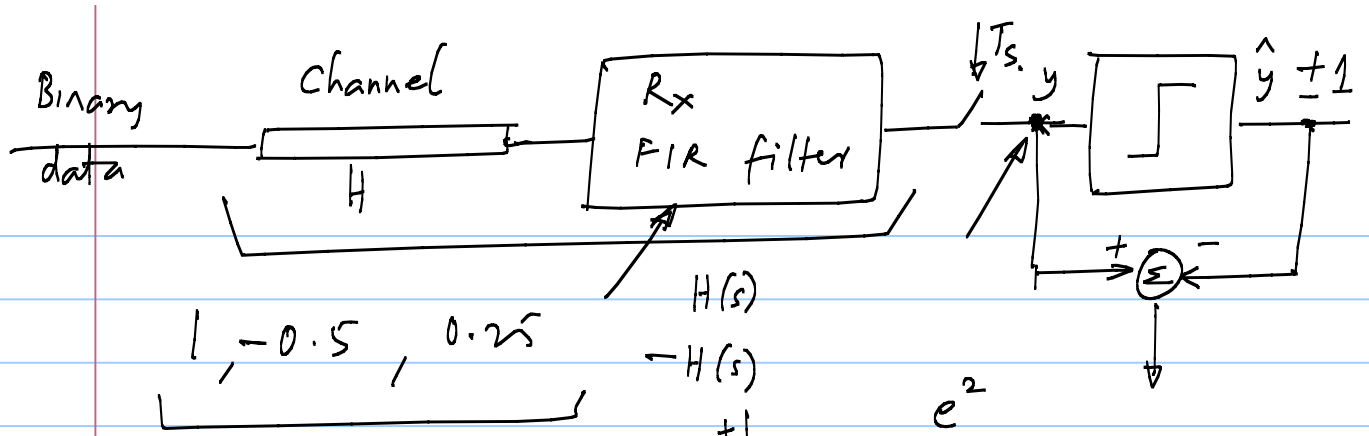
$$\text{Delay} = CR = T_s = 1 \text{ ns}$$




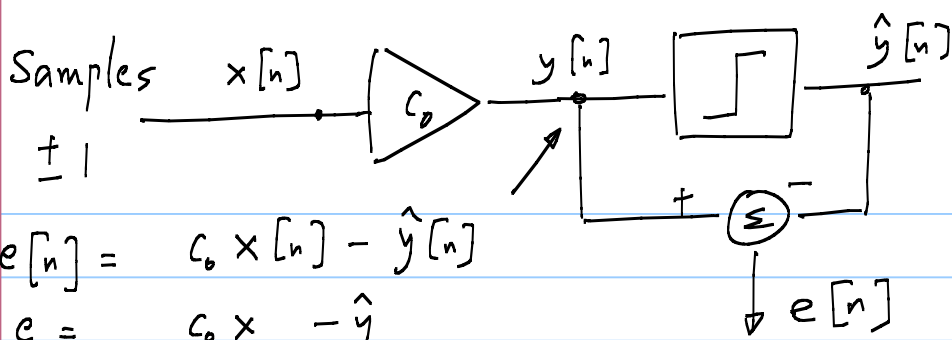

$$e[n] = c_0 x[n] - \hat{y}[n]$$

$$e = c_0 x - \hat{y}$$
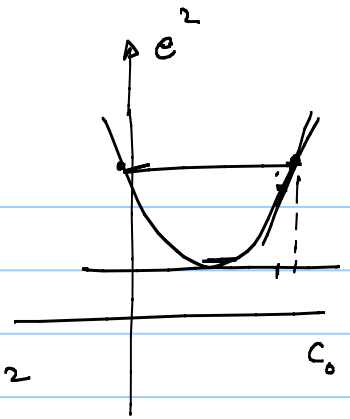
$$e^2 = (c_0 x - \hat{y})^2 = c_0^2 x^2 - 2c_0 x \hat{y} + (\hat{y})^2$$



$$\frac{d}{dc_0} \cdot e^2$$

$$c_0[k] = c_0[k-1] - \frac{\mu}{2} \frac{d}{dc_0} (e^2)$$

$$= 2 \cdot e \cdot \left(\frac{de}{dc_0} \right)$$

$$c_0[k] = c_0[k-1] - \mu \cdot e[k-1] \cdot x[k-1]$$

$$= 2 \cdot e \cdot x$$

