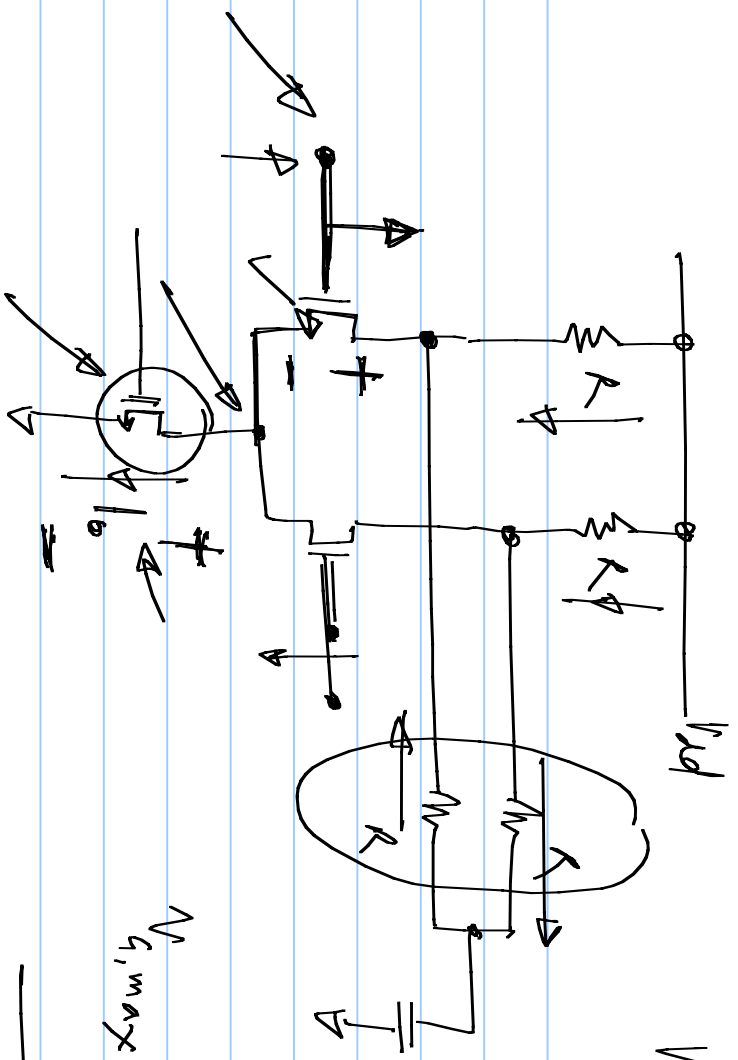


$$I_o = \frac{V_{dd} - V_{o,cm}}{R}$$

$$I_o = \frac{V_{dd} - V_{o,cm}}{R_1} + \frac{V_{dc} - V_{o,cm}}{R_2}$$



$$V_{g,max} = V_{dd} - \frac{3 \cdot I_o \cdot R}{4} + V_T$$

$$V_{o,2m} = \left(V_{dd} - \frac{I_o \cdot R}{2} \right) - \frac{I_o \cdot R}{4}$$

$$V_{o,min} = \left(V_{dd} - \frac{3 \cdot I_o \cdot R}{4} \right)$$

Tail source: min V_{DS} @ zero diff. input $\underbrace{\hspace{2cm}} = V_{icm} + \frac{V_{in,ppd}}{4}$


$$\left[V_{g,max} - V_T - \sqrt{\frac{2I_o}{\mu C_{ox} \frac{W}{L}}} \right]$$

$$V_{a,cm} = V_{DSAT} + V_{DSAT} + V_T = (0.9V)$$



Switching voltage = $\sqrt{2} \cdot V_{DSAT} = 280mV$

diff. voltage

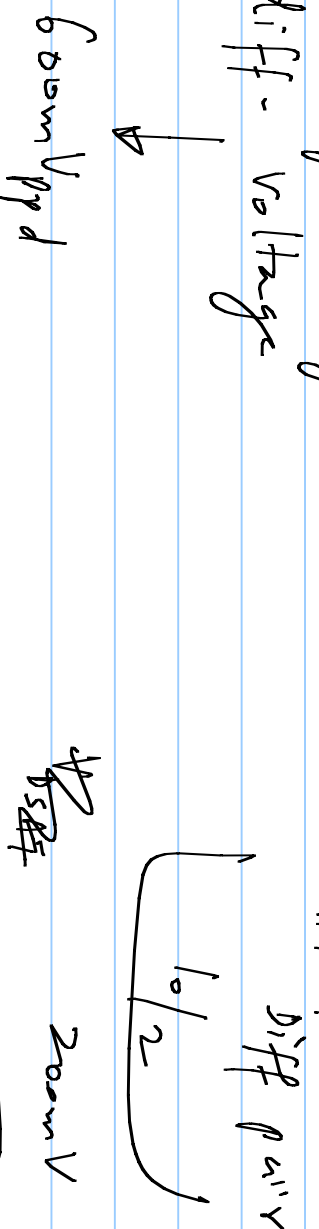




$$V_{G,max} = 1.05V = 0.55V = V_{DQ} - \frac{3}{4} R$$

1.8V


Diff pp. o/p swing = $I_{OR} = \frac{5}{3} V = 1.67V$

$I_b R = 1.5V_{pp}$ differential o/p. $32mA \times 50\Omega$

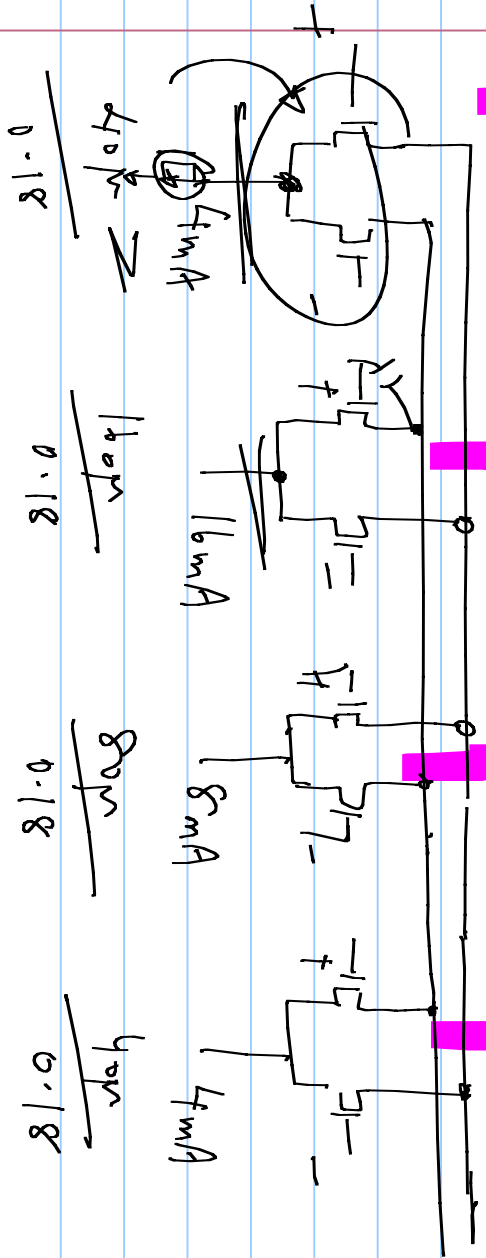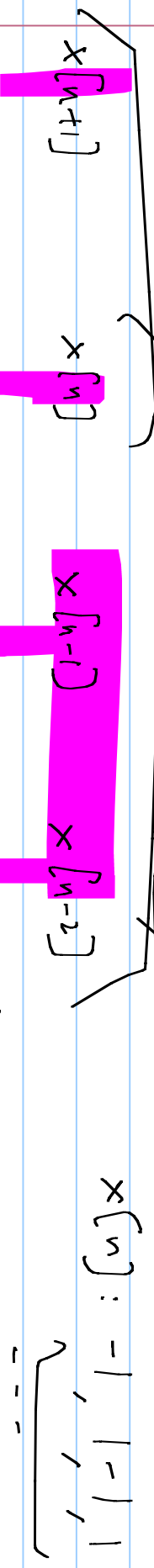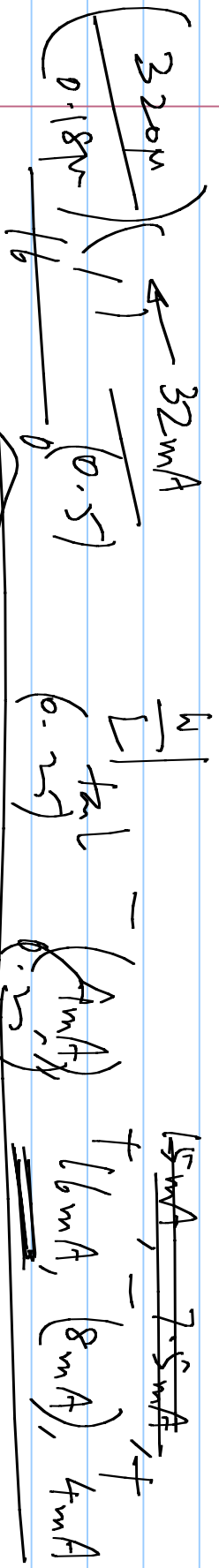
$I_b = 30mA$ $\left[\begin{matrix} \left(\frac{-0.25}{1} \right) \left(\frac{1}{0.5} \right), 0.25 \end{matrix} \right] = 1.6V_{pp}$



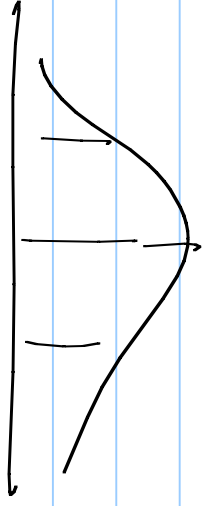$\frac{40pF}{0.18} \approx 10ps$ $\frac{8ps}{0.18} \approx 44ps$ $\frac{4ps}{0.18} \approx 22ps$ $\frac{4ps}{0.18} \approx 22ps$




0.11

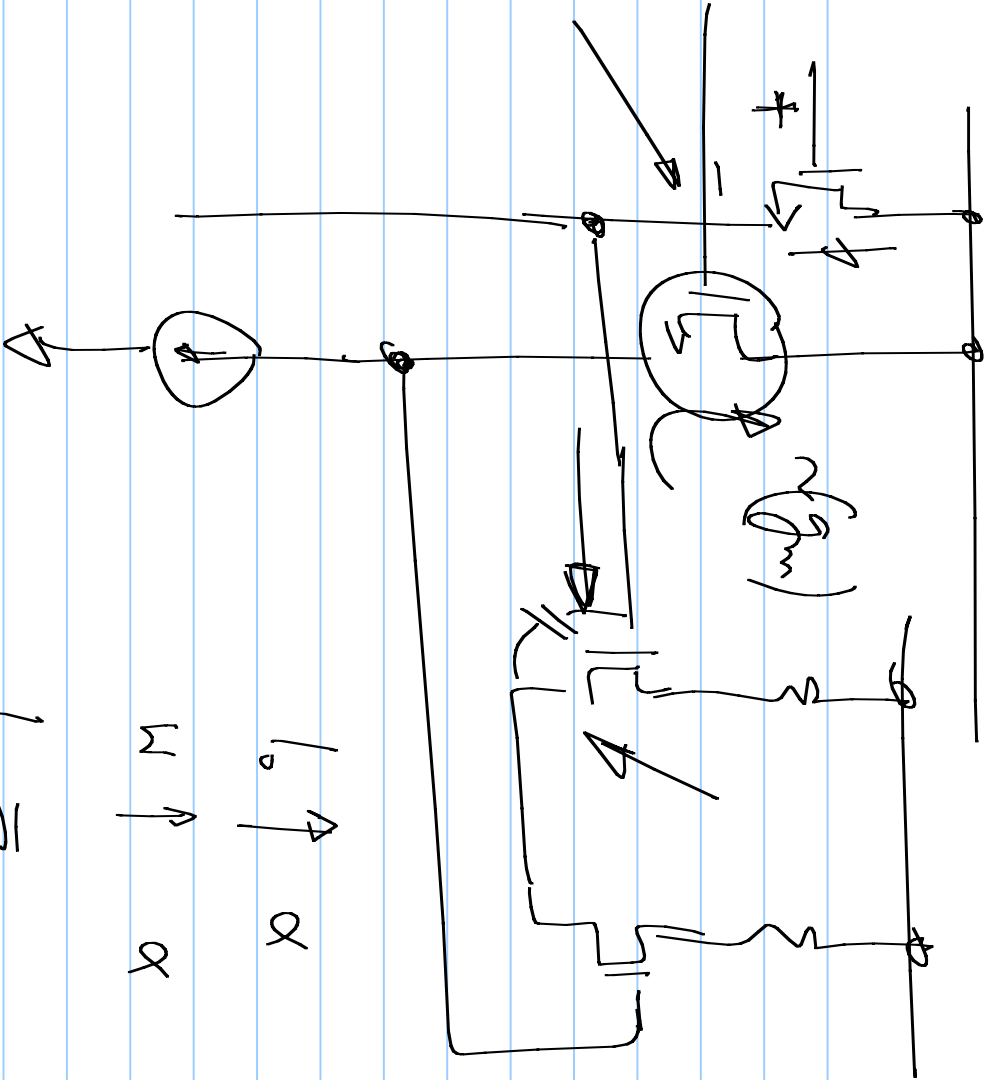

$I_b \uparrow \alpha$
 $I_c \uparrow \alpha$


$L \equiv III$

$R \uparrow \alpha$

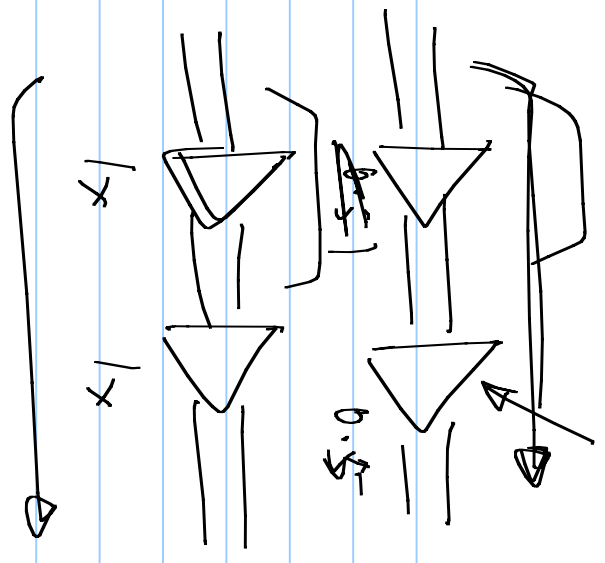



$I_c \uparrow \alpha$

0.5

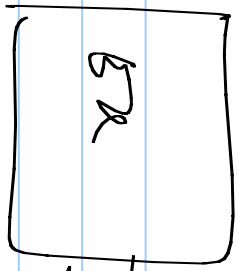

$-0.25, 1, -0.5, 0.25$




(2^1)

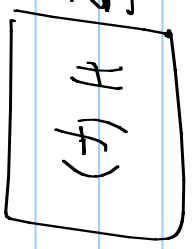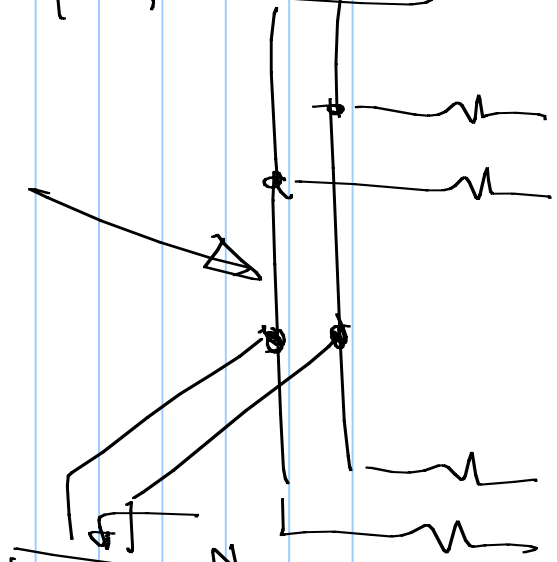


$z^{-1} = \infty$

0.67

$$\frac{1}{8(1 + s/w_p)}$$

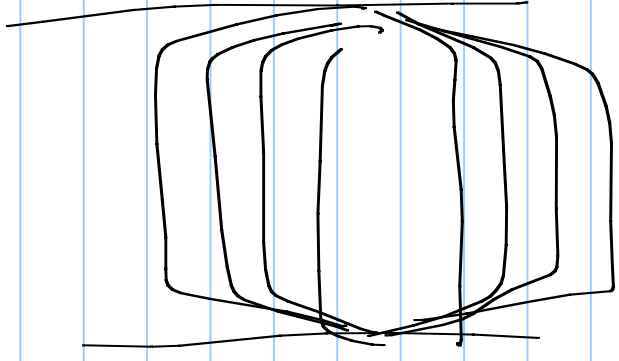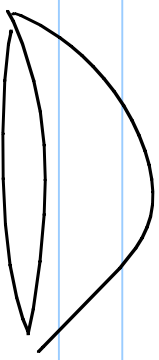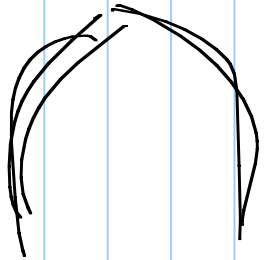

PAMY

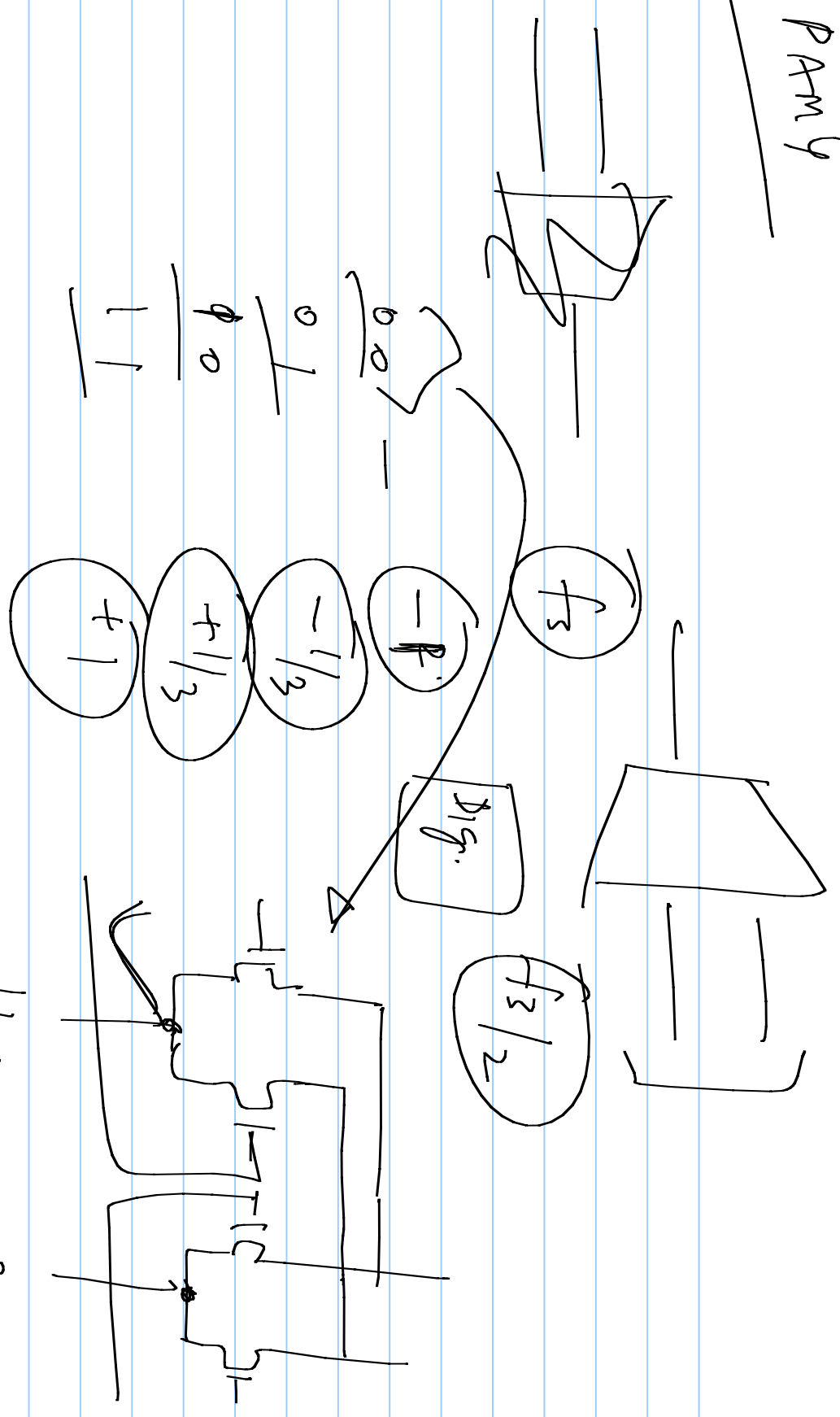

$$1/3 \times$$

$$2/3 \times$$