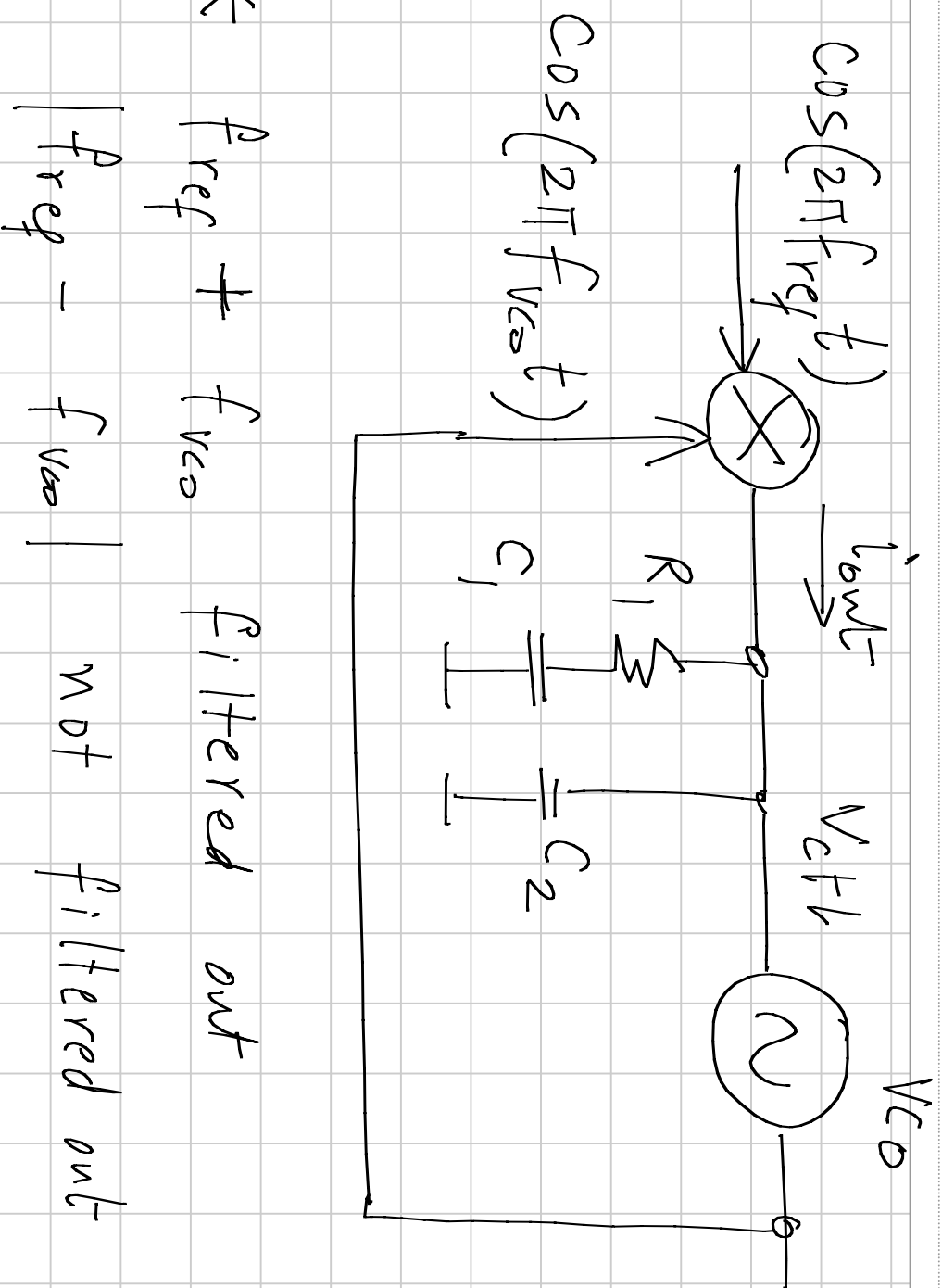



PLL capture process

Note Title

15-11-2007




 V_{ctl} (Filtered to remove $f_{ref} + f_{vco}$)




* $f_{ref} > f_{vco}$: V_{ctl} must increase

* If V_{ctl} increases, it results in a progressively lower $|f_{ref} - f_{vco}|$ and a wider positive pulse

 


- * $f_{ref} > f_{co}$: V_{ctL} must increase
- * If V_{ctL} decreases, $|f_{ref} - f_{co}|$ progressively increases and results in a narrower negative pulse.

 

* Average V_{ct1} increases progressively, resulting in a higher average frequency, eventually resulting in capture

* If $|f_{req} - f_{osc}|$ is also attenuated by the loop filter, capture may not occur (or occur very slowly)

 Hogge phase detector with frequency difference between clock and data



* Pattern repeats after $5T_c$

$$* 5T_c = 4T_d$$

$$* f_c - f_d = \frac{1}{T_c} - \frac{1}{T_d}$$

$$= \frac{1}{T_c} - \frac{4}{5T_c} = \frac{1}{5T_c}$$

* UP-DN has a component at the difference frequency