

# *Introducing Negative Feedback with an Integrator as the Central Element*

*2012 International Symposium on Circuits and Systems  
Seoul, Korea*

**Nagendra Krishnapura**

Department of Electrical Engineering  
Indian Institute of Technology, Madras  
Chennai, 600036, India

**23 May 2012**


## *Motivation*

- Intuition before full blown analysis
- Synthesis instead of ad-hoc introduction
- Time domain reasoning/analysis
  - More intuitive
  - Exact analysis difficult for complex systems
- Frequency domain analysis
  - More abstract
  - Can handle complex systems easily

## *Outline*


- Traditional introduction to negative feedback systems
- Integrator as controller in a negative feedback system
- Intuition and analysis in the time domain
- Pedagogical advantages of the proposed introduction
- Conclusions
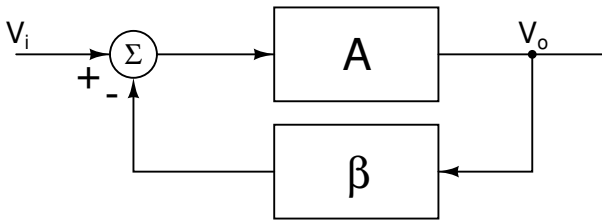
## *Traditional introduction to negative feedback systems*






- Algebraic system—cannot explain evolution over time
- Unstable with arbitrarily small loop delay
  - Ideal delay  $T_d$  in the loop  $\Rightarrow$  oscillations with a period  $2T_d$
- Real systems have non-zero delay and don't respond instantaneously
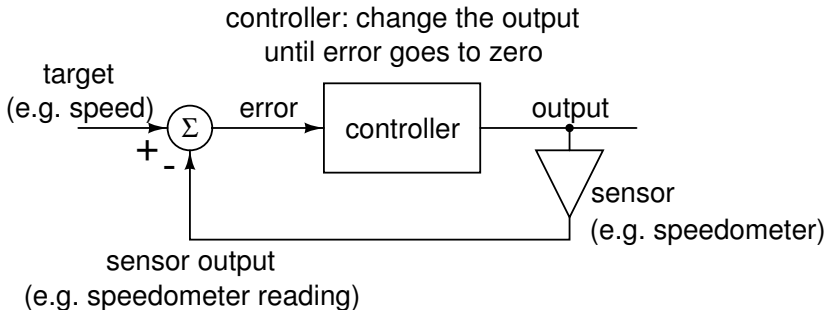
## Intuitive understanding of negative feedback systems




- Compare the sensed output to the target (desired output)
- *Continuously* change the output until the output approaches the target

## Nature of the controller

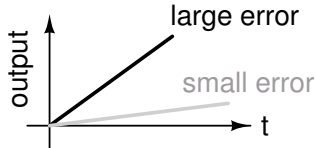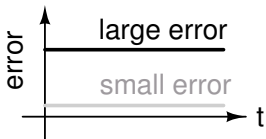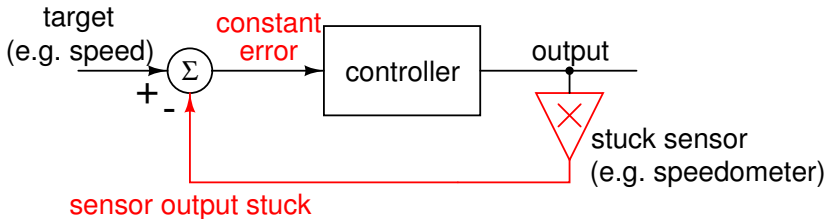


- Controller integrates the error
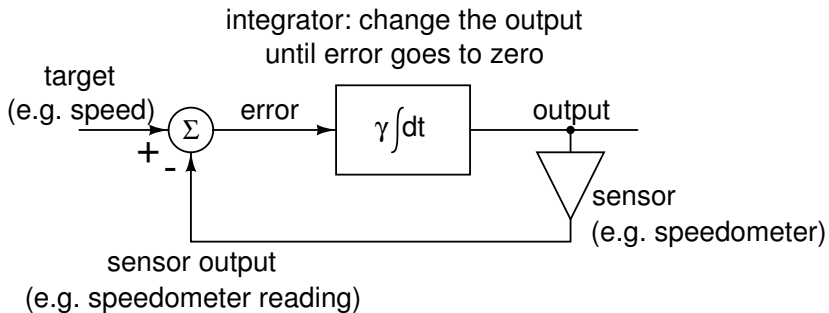
## *Negative feedback system with an integrator*




## Negative feedback amplifier

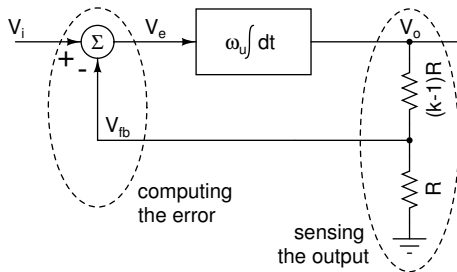


- Need the output  $V_o$  to be gain  $k$  times the input  $V_i$
- Compare  $V_o/k$  to  $V_i$  and integrate the error
- Steady state when  $V_o = kV_i$  for constant  $V_i$


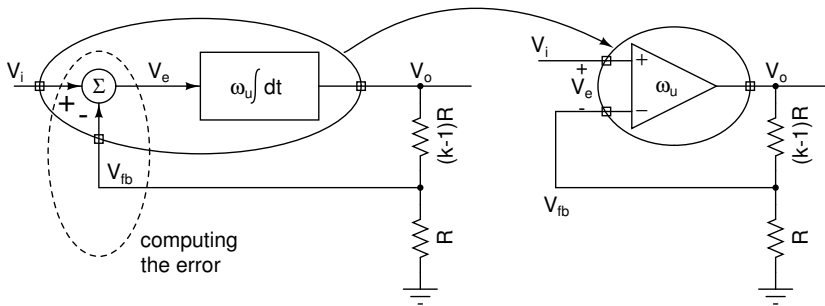
# Opamp for implementing a negative feedback amplifier


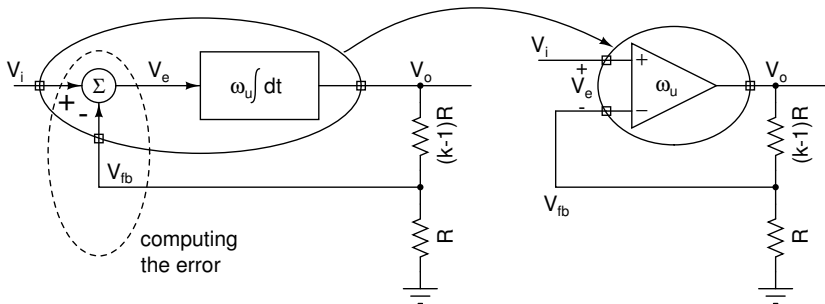
## Time domain behavior with constant/step inputs



$$\frac{1}{\omega_u} \frac{dV_o}{dt} = V_i - \frac{V_o}{k}$$

$$V_o(t) = kV_p \left( 1 - \exp\left(-\frac{\omega_u}{k} t\right) \right)$$

- Time constant  $k/\omega_u$
- Asymptotically reaches  $V_o = kV_i$  or  $V_{fb} = V_i$

## *Relation to frequency domain analysis*

$$\text{Loop gain } L(s) = \frac{\omega_u}{ks} = \frac{\omega_{u,loop}}{s}$$

Frequency domain:


- Unity loop gain frequency  $\omega_{u,loop}$
- Significant negative feedback up to  $\omega_{u,loop} \Rightarrow$  nearly ideal behavior up to  $\omega_{u,loop}$  (Closed loop Bandwidth)

$$\tau_{loop} = \frac{1}{\omega_{u,loop}}$$

Time domain:


- Unit step response of the loop gain  
 $= t / (1 / \omega_{u,loop}) = t / \tau_{loop}$
- Closed loop response time constant  $= 1 / \omega_{u,loop} = \tau_{loop}$
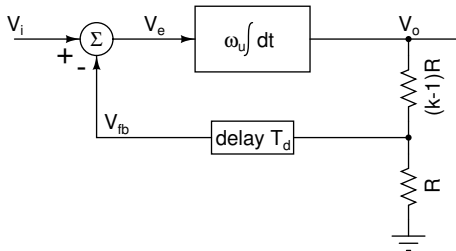
## Negative feedback amplifier with delay in the loop



- Reacts to past output  $\Rightarrow$  Don't know target has been reached
- Possibility of overshoots or unbounded oscillation
- Unaffected if the integrator's output doesn't change significantly over  $T_d$

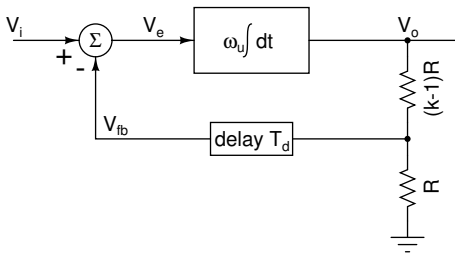
## Negative feedback amplifier with delay in the loop



$$\frac{1}{\omega_u} \frac{dV_o(t)}{dt} = V_i - \frac{V_o(t - T_d)}{k}$$

Delay differential equation

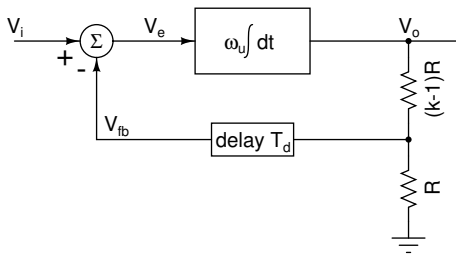
## Negative feedback amplifier with delay in the loop



- $T_d/\tau_{loop} \leq 1/e (= 0.367)$ : No overshoot
- $1/e < T_d/\tau_{loop} < \pi/2$ : Overshoot + ringing
- $\pi/2 < T_d/\tau_{loop}$ : Unstable

In practice we need a “well behaved” response (limited overshoot)
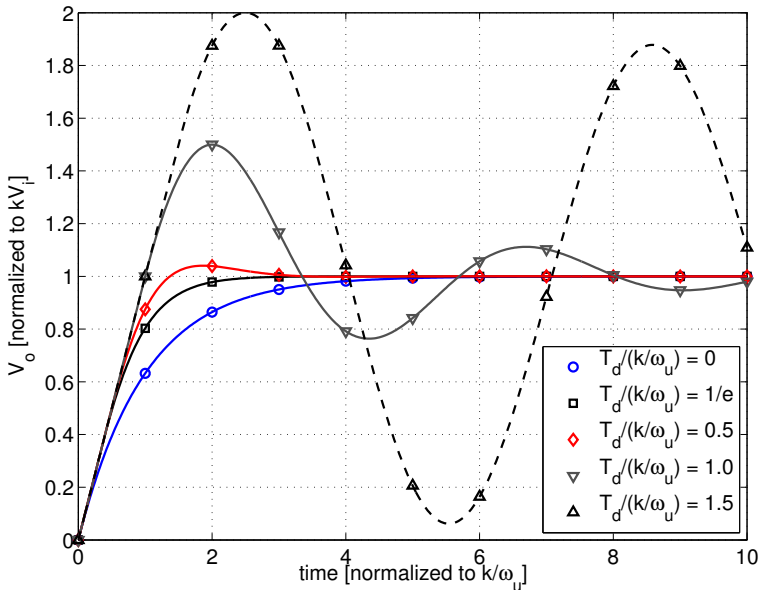
## Negative feedback amplifier with delay in the loop



## *Negative feedback amplifier with delay in the loop*

% Overshoot	0	1	2	4	10	20
$T_d/\tau_{loop}$	$\leq 1/e$ (0.367)	0.445	0.465	0.5	0.585	0.695




## *Fixing the stability problem in presence of delay*

- Stability governed by the ratio of  $T_d$  to  $\tau_{loop}$
- Reduce  $T_d$ : Faster circuit/technology
- Increase  $\tau_{loop} \Rightarrow$  Decrease  $\omega_{u,loop}$ : Slower integration
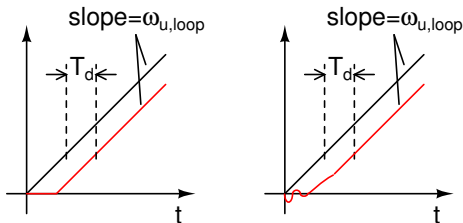
## Delays in circuit implementation—parasitic poles and zeros


$$\text{Loop gain } L(s) = \underbrace{\frac{\omega_{u,\text{loop}}}{s}}_{\text{Ideal}} \cdot \underbrace{\frac{\prod_{k=1}^M (1 + s/z_k)}{\prod_{k=2}^N (1 + s/p_k)}}_{\text{Parasitic}}$$



Unit step response of  $L(s)$  is a ramp of slope  $\omega_{u,\text{loop}}$  (same as ideal) with a delay  $T_d = \sum_{k=1}^N 1/p_k - \sum_{k=1}^M 1/z_k$

# Closed loop response with equivalent delay

Transient Response

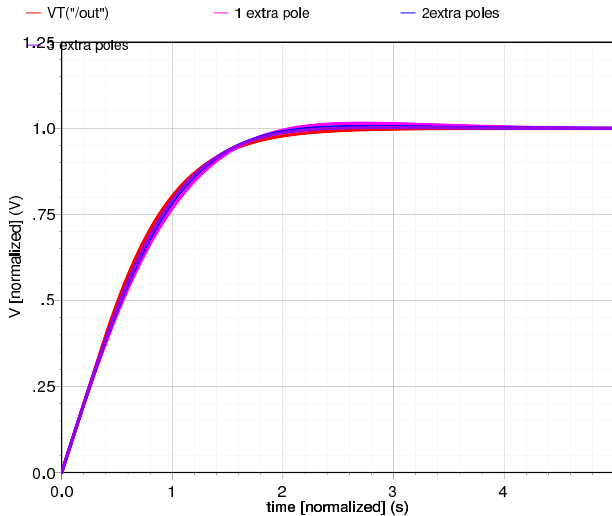

## *Advantages of this formulation*

- Synthesis from common experience of negative feedback based adjustment in the time domain
- Intuition and key results obtained from time domain reasoning
  - Exponential settling
  - Possibility of ringing, overshoot, and instability

## *Advantages of this formulation*

- Traditional viewpoint
  - Memoryless amplifier (loop gain) in the ideal case
  - Frequency dependence as non-ideal feature
- Proposed viewpoint
  - Integrator in the ideal case ( $\infty$  dc gain)
  - Finite dc gain due to non-ideal implementation
- $\omega_{U,loop}$  more fundamental characteristic of the negative feedback loop than dc loop gain
  - Increasing  $\omega_{U,loop}$  requires higher power
  - Increasing dc loop gain indirectly influences power
- Loop gain of all feedback systems has integrator-like behavior over some frequency range
  - Nyquist plot should enter the unity circle near the negative imaginary axis
  - Bode plot should have  $-20$  dB/decade slope near the unity gain frequency

## *Advantages of this formulation*

- Clear why fastest negative feedback systems are slower than fastest open loop systems
- Leads to commonly used opamp and phase locked loop topologies

## *Suggested course outline*

- **Negative feedback with integrating controller**
- **Opamp for computing and integrating error**
- **Time domain analysis with delay**
- Laplace transform stability analysis, Nyquist criteria
- **Relation to time domain analysis results**
- Synthesis of opamp, PLL topologies

# References



Adel S. Sedra and Kenneth C. Smith, *Microelectronic Circuits*, 6th ed., Oxford University Press 2009.



Paul R. Gray, Paul J. Hurst, Stephen H. Lewis, Robert G. Meyer, *Analysis and Design of Analog Integrated Circuits*, 5th ed., Wiley 2009.



Nagendra Krishnapura, "Synthesis Based Introduction to Opamps and Phase Locked Loops," *Proc. 2012 IEEE ISCAS*, May 2012.



Karl J. Astrom and Richard M. Murray, "Feedback Systems: An Introduction for Scientists and Engineers," Available:  
[http://www.cds.caltech.edu/~murray/amwiki/index.php/Main\\_Page](http://www.cds.caltech.edu/~murray/amwiki/index.php/Main_Page)



Barrie Gilbert, "Opamp myths," Available: <http://pe2bz.philpem.me.uk/Parts-Active/IC-Analog/OpAmps/OpAmpMyths/c007-OpAmpMyths.htm>



Hal Smith, *An Introduction to Delay Differential Equations with Applications to the Life Sciences*, 1st ed., Springer 2010.



Nagendra Krishnapura, "EE5390: Analog Integrated Circuit Design," Available:  
<http://www.ee.iitm.ac.in/~nagendra/videolectures>