

*Synthesis Based Introduction to Opamps and
Phase Locked Loops*

*2012 International Symposium on Circuits and Systems
Seoul, Korea*

Nagendra Krishnapura


Department of Electrical Engineering
Indian Institute of Technology, Madras
Chennai, 600036, India

23 May 2012

Outline


- Negative feedback amplifier
 - Integrate the error to drive the output
- Opamp to compute and integrate the error
 - G_m loaded by a capacitor—Single stage opamp
 - Better I-V conversion—Two stage opamp
 - Further refinement—Three stage opamp
- PLL as negative feedback frequency multiplier
 - Integrate frequency error to drive the output—Type I PLL
 - Static phase error causes reference spurs
 - Additional integrator to null phase error—Type II PLL
- Conclusions

Negative feedback system

 


- Controller: Continuously changes the input until error goes to zero

Negative feedback system

 


- Controller: Continuously changes the input until error goes to zero

Negative feedback amplifier

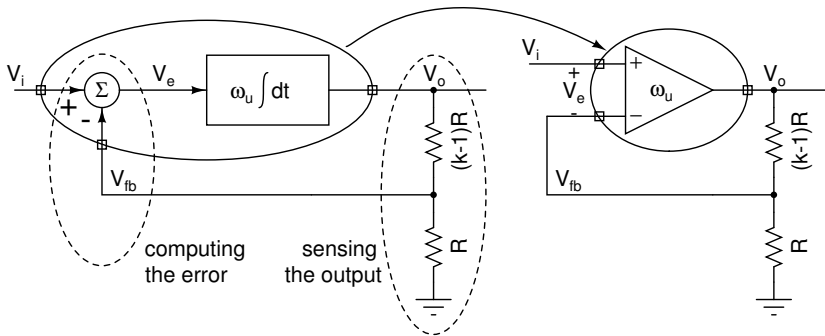


- Integrate the error $V_i - V_o/k$ to drive the output
- Opamp computes the error and integrates it

Opamp (integrator) realization

 


- $G_m - C$ integrator
- Finite $R_{o1} \Rightarrow$ Finite dc gain \Rightarrow Steady state error

 Transimpedance amplifier for better I-V conversion



- Use negative feedback to realize a CCVS
- $V_o \approx I_{Gm}Z_c$ within the unity loop gain frequency

Improved I-V conversion—Two stage opamp

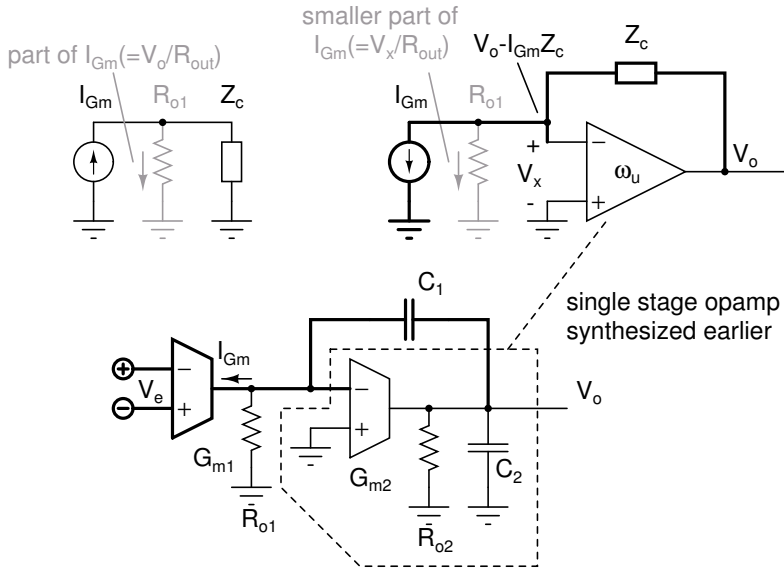


Intuition about two stage opamp

I-V conversion bandwidth \approx unity loop gain frequency

$$\omega_{u,desired} < \omega_{u,inner}$$

$$\frac{G_{m1}}{C} < \frac{G_{m2}}{C_2}$$

Further improvement—Three stage opamp

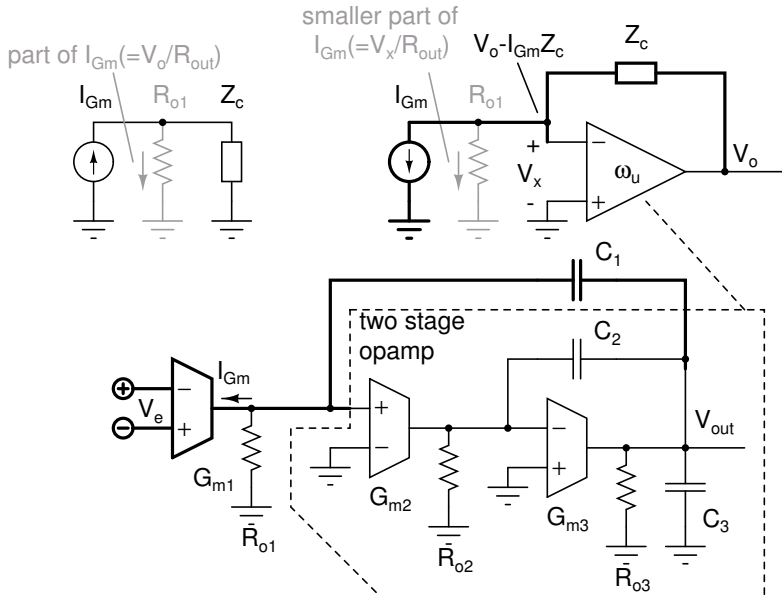

Intuition about three stage opamp

I-V conversion bandwidth \approx unity loop gain frequency



$$\omega_{u,desired} < \omega_{u,inner}$$

$$\frac{G_{m1}}{C} < \frac{G_{m2}}{C_2} < \frac{G_{m3}}{C_3}$$


Analysis of two and three stage opamps

- Two stage opamp
 - DC gain
 - Pole locations, pole splitting
 - Stability constraints
 - RHP zero and its cancellation
- Three stage opamp
 - DC gain
 - Pole locations
 - Stability constraints
 - Zero pair and their optimization

  
Frequency multiplication analogous to voltage amplification




Frequency multiplication

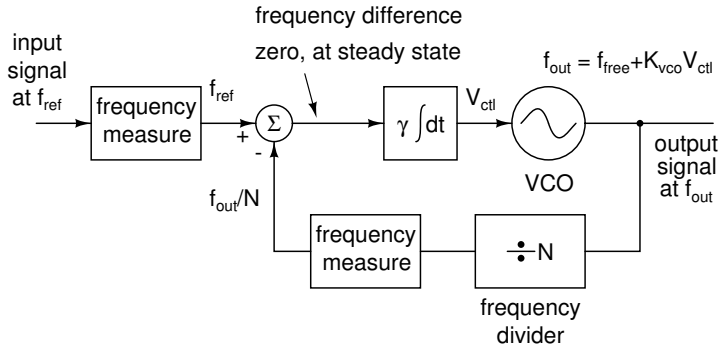

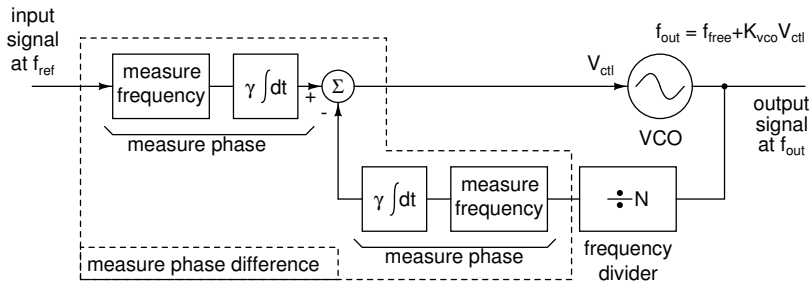Integrate frequency difference \Rightarrow Phase difference




Type I phase locked loop

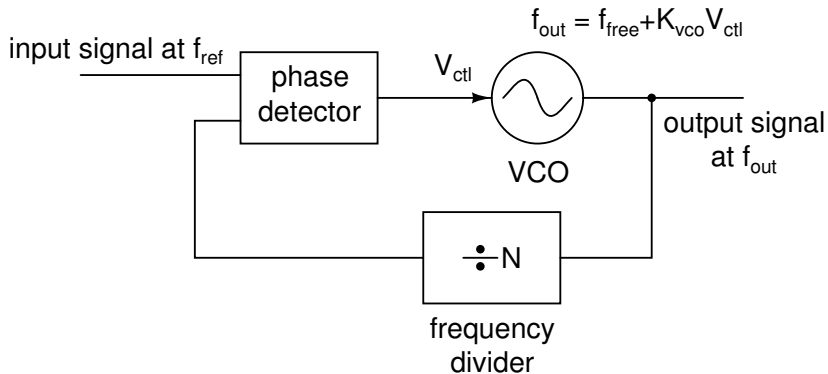


- Phase detector and VCO in a loop

Type I phase locked loop

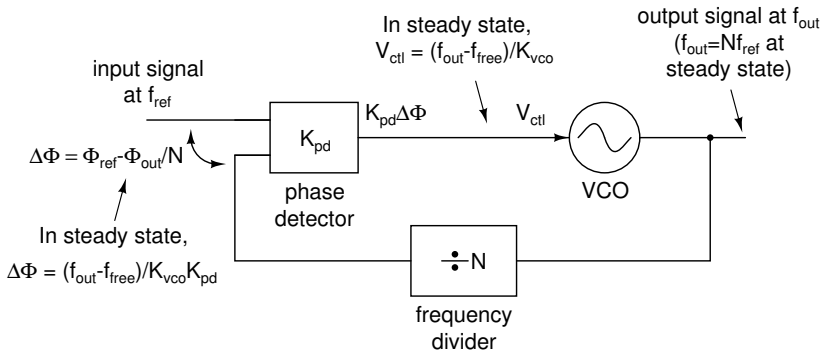

- Phase offset $\Delta\Phi = (f_{out} - f_{free})/K_{vco}K_{pd}$ between input and feedback signals
- $|\Delta\Phi|$ limited to $\pm n\pi$ due to periodic nature of phase
- Limited lock range $|f_{out} - f_{free}|$

Tri state phase detector example

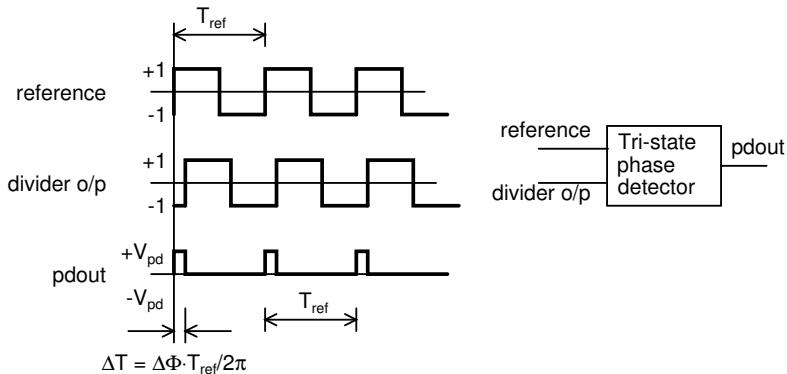


$$\frac{V_{out}(t)}{V_{pd}} = \underbrace{\frac{\Delta\Phi}{2\pi}}_{\text{Average}} + \underbrace{\frac{\Delta\Phi}{\pi} \sum_{n=1}^{\infty} \text{sinc}\left(\frac{n\Delta\Phi}{\pi}\right) \cos(2\pi n f_{ref} t - n\Delta\Phi/2)}_{\text{Periodic error at } f_{ref} \propto \Delta\Phi}$$

Type I PLL with a practical phase detector

- Output average value $\propto \Delta\Phi$
- Periodic signal at f_{ref}
- Periodic signal magnitude proportional to $\Delta\Phi$
- VCO modulated at f_{ref} and its harmonics
- PLL output has sidebands at integer multiples of f_{ref}


For a modest sideband level of -40 dB, PLL lock range $\approx 10^{-4} f_{ref}$. Cannot change N at all!

Type I phase locked loop

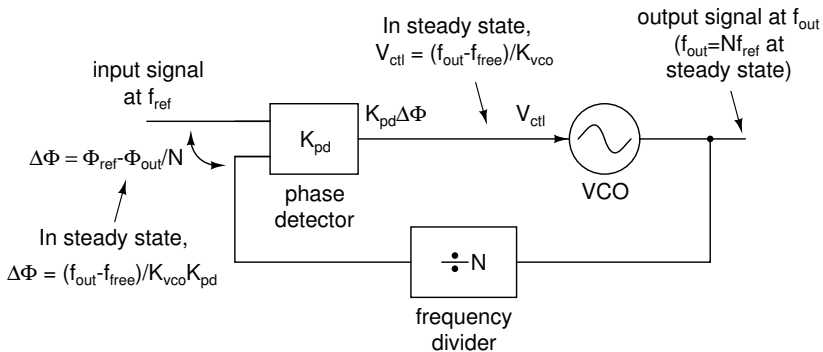


$\Delta\Phi = 0$ if f_{out} happens to be equal to f_{ref} . Zero spurs!

 Changing the free running frequency of a VCO




- Add a bias to the input to change the free running frequency

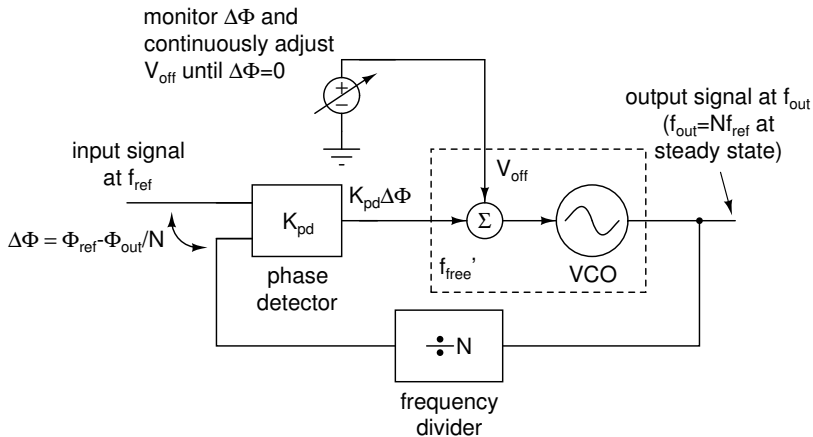Slowly change the bias until $\Delta\phi = 0$




- Slowly change the bias V_{off} until $\Delta\phi = 0$

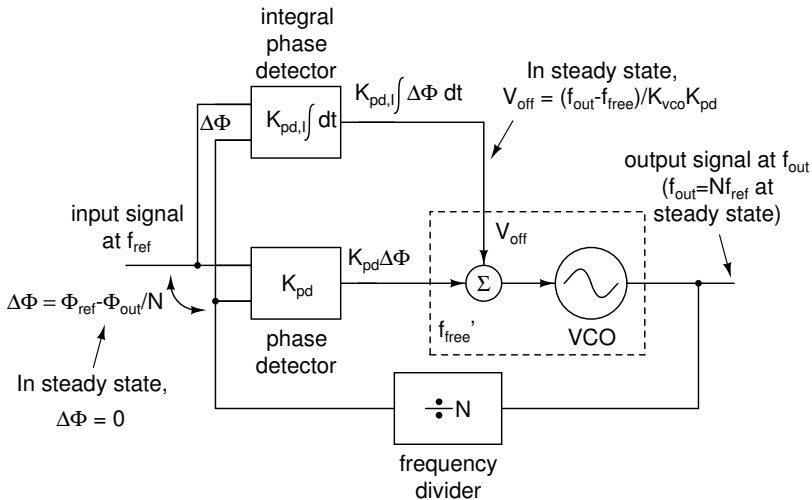Slowly change the bias until $\Delta\phi = 0$




- Measure $\Delta\phi$ and integrate it to control V_{off}

Type II Phase locked loop

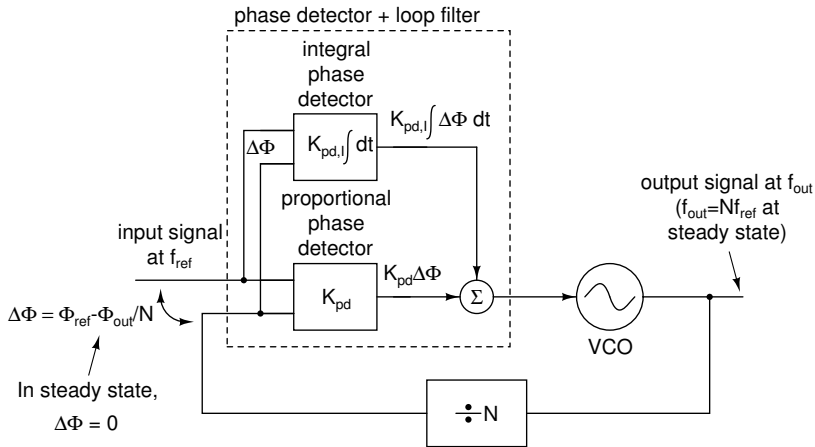

- Proportional + integral loop filter

Type II Phase locked loop implementation

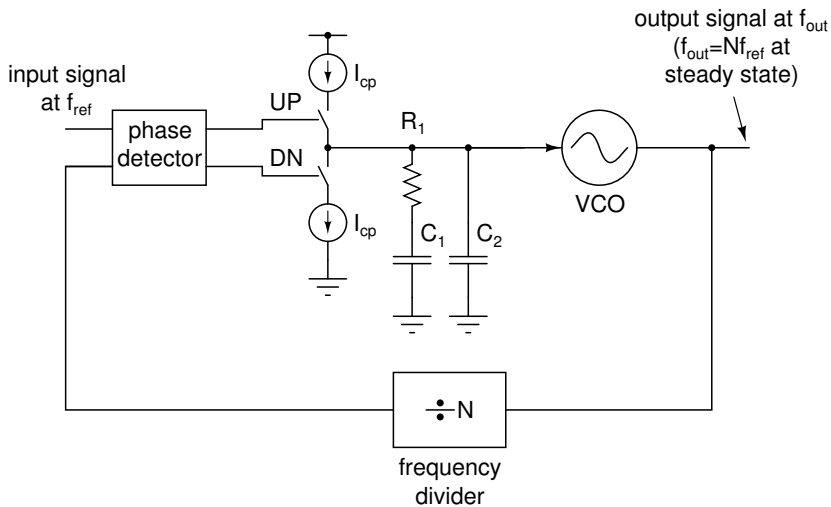

Intuition about the Phase locked loop

- Reason for using a phase detector for frequency synthesis
- Reason for an additional integrator in the loop filter
- Integral path for adjusting V_{off} slower than the main path (type I)
 - PLL bandwidth (unity loop gain frequency) is the same as in the type I loop
 - Presence of a zero before the PLL bandwidth (unity loop gain frequency)
 - Integral path influences the phase transfer functions only well below the PLL bandwidth

Analysis of type II Phase locked loop

- Pole zero locations
- Phase (jitter) transfer functions
- Higher order loop filter for higher spur suppression

Suggested course outline

- Negative feedback circuits
- Stability analysis
- **Opamp topologies using controlled sources (G_m)**
- Opamp topologies at the transistor level
- **Phase locked loop at the system level**

Conclusions

- Negative feedback: *Continuous* adjustment to reduce error
- Integrator is the key element of the negative feedback loop
- Implementing a voltage integrator and seeking to improve its performance leads to commonly used opamp topologies
- Implementing a negative feedback frequency multiplier and seeking to improve its performance leads to type I and II phase locked loops
- Valuable intuition gained before embarking on analysis

References



Paul R. Gray, Paul J. Hurst, Stephen H. Lewis, Robert G. Meyer, *Analysis and Design of Analog Integrated Circuits*, 5th ed., Wiley 2009.



R. D. Middlebrook, "Methods of design-oriented analysis: Low-entropy expressions," *New Approaches to Undergraduate Education IV*, Santa Barbara, 26-31 July 1992.



Nagendra Krishnapura, "Introducing negative feedback with an integrator as the central element," *Proc. 2012 IEEE ISCAS*, May 2012.



Shanthi Pavan, "EC201: Analog Circuits," Available:
<http://www.ee.iitm.ac.in/~nagendra/videolectures>



Floyd M. Gardner, *Phaselock Techniques*, 3rd ed., Wiley-Interscience 2005.



Roland Best, *Phase Locked Loops: Design, Simulation and Applications*, 5th ed., McGraw-Hill 2007.



Stanley Goldman, *Phase Locked Loop Engineering Handbook for Integrated Circuits*, Artech House 2007.



Behzad Razavi, *Design of Analog CMOS Integrated Circuits*, 1st edition, McGraw-Hill, 2000.



Nagendra Krishnapura, "EE5390: Analog Integrated Circuit Design," Available:
<http://www.ee.iitm.ac.in/~nagendra/videolectures>