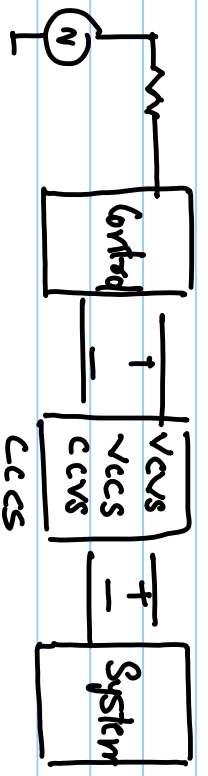



Lecture #2

Controlled Sources



$$P_{in} = P_{out}$$

$$(P_{in} > 0) < (P_{out} = 0)$$

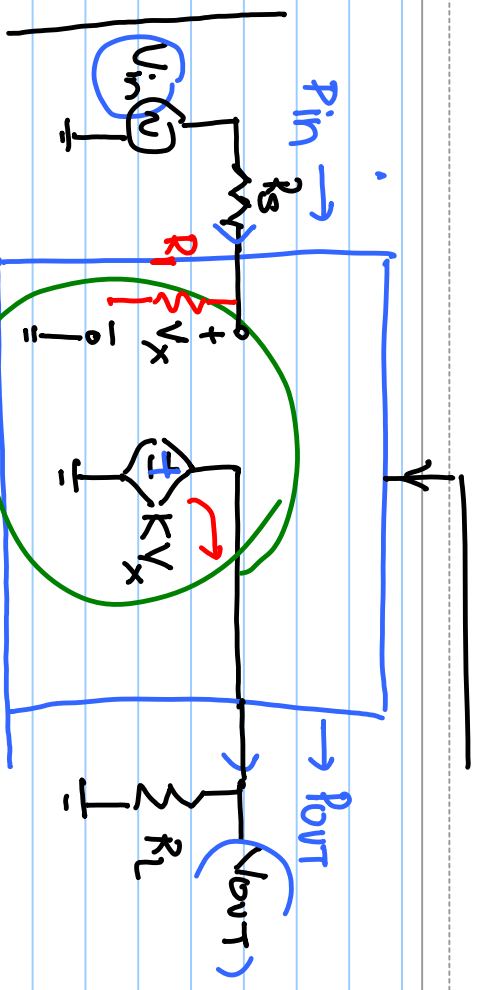




$$P_{out} = \frac{V_{out}^2}{R_L} = \frac{(K V_x)^2}{R_L}$$

$$P_{in} = \frac{V_{in}^2}{R_1 + R_s}$$

$$\text{Power Gain} = \frac{P_{out}}{P_{in}} > 1$$

$$= \frac{K^2}{R_L} \times \left(\frac{R_1}{R_1 + R_s} \right)^2 \frac{V_{in}^2}{V_{in}^2} \frac{(R_1 + R_s)}{V_{in}^2}$$



$\propto K^2$

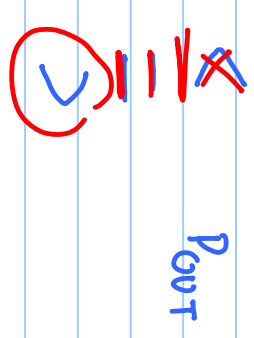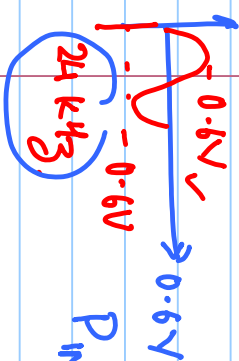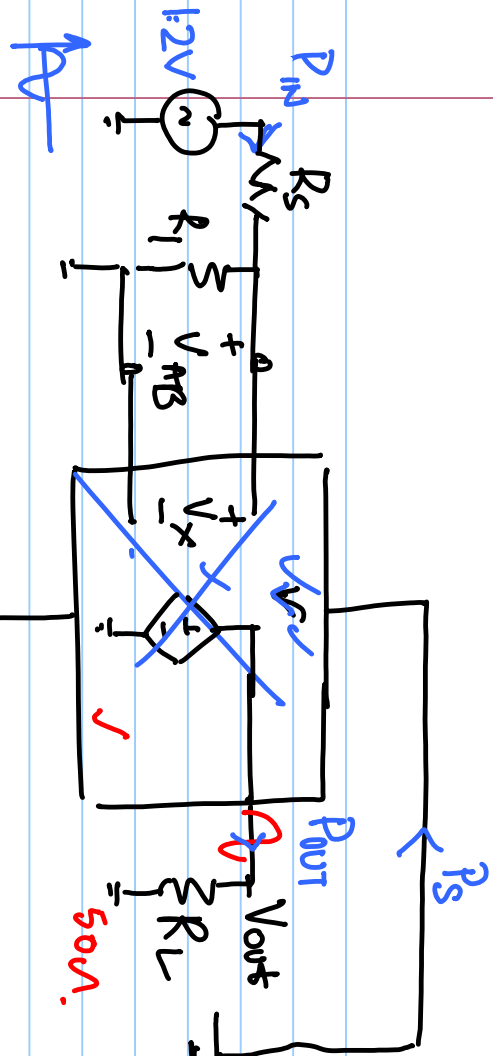

$P_{out} < P_{in} + P_s$


$v_i(t) = A \sin(\omega t)$

$\omega = 2\pi \times 24 \mu\text{S}$

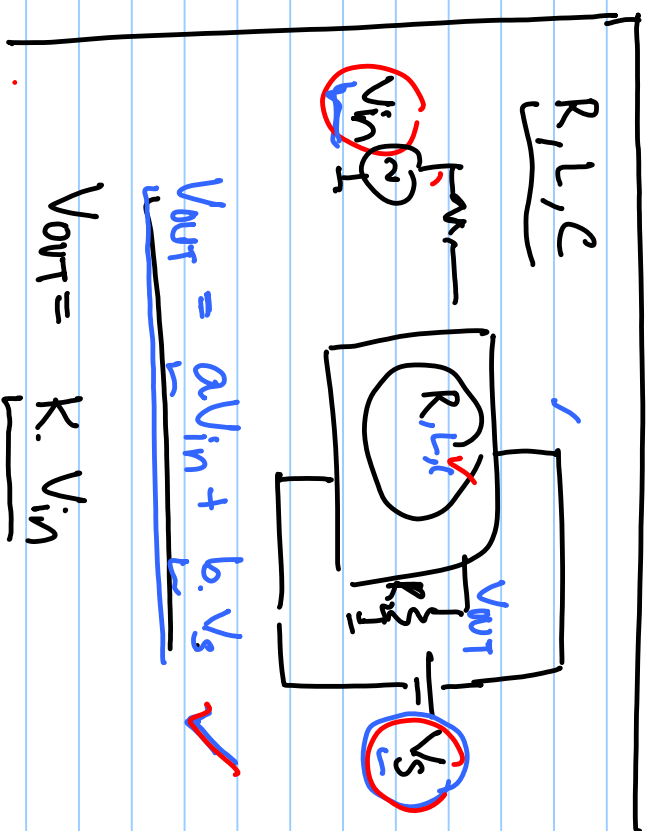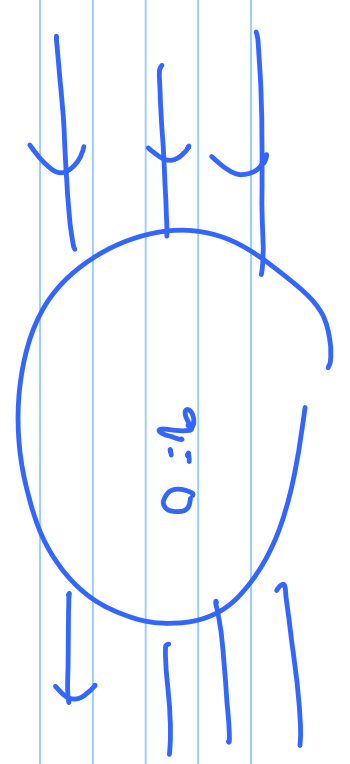

$V_{out} = a V_{in} + b \cdot V_s$


$V_{out} = K \cdot V_{in}$

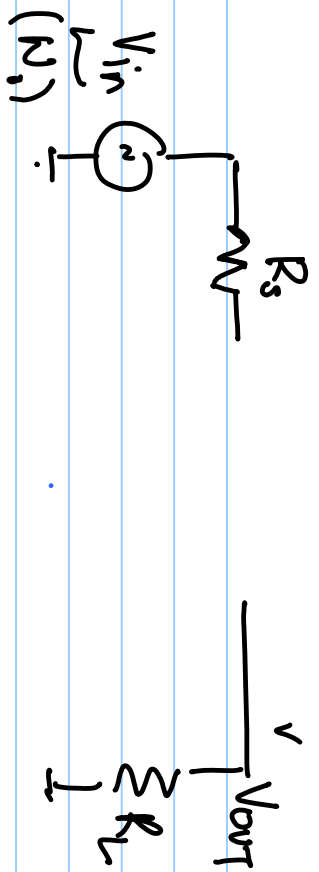

$$\frac{V_{out}}{V_{in}} = k > 1$$

$$V_{out} = \frac{R_L}{R_s + R_L} V_{in}$$


$$V_{out} = aV_{in} + b \cdot V_s$$

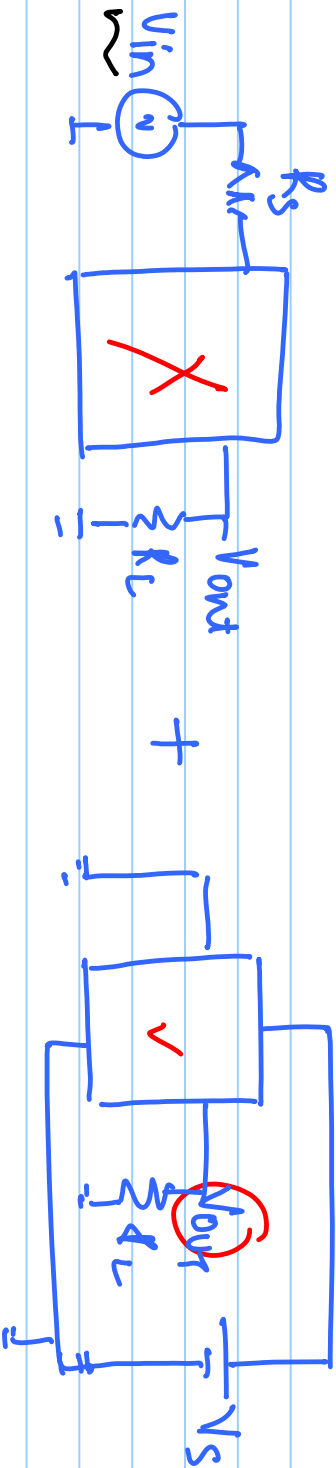

$$V_{out} = a_0 (aV_{in} + bV_s) + a_1 (aV_{in} + bV_s)^2 + a_2 (aV_{in} + bV_s)^3 + \dots$$



$$a_0 (\sin(\omega t) + 12) + a_1 (\sin(\omega t) + 12)^2 + \dots \rightarrow 2 \cdot 12 \cdot \sin(\omega t)$$

$\omega_0 = \frac{1}{\sqrt{LC}}$

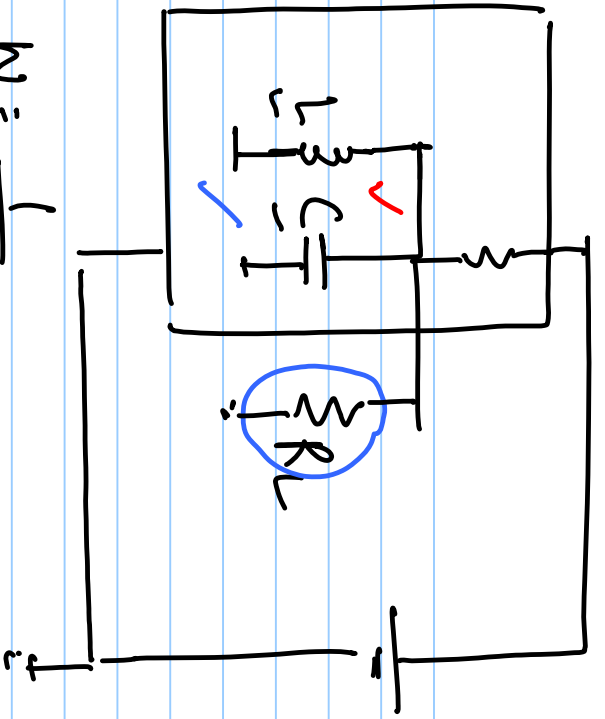


$$W = \frac{1}{\sqrt{LC}}$$

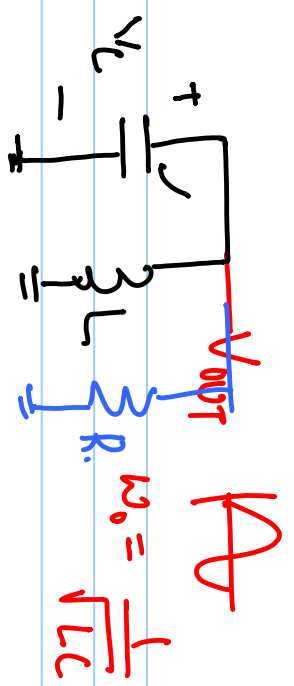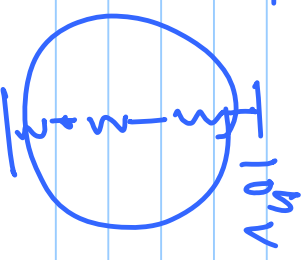- Power derived from supply by a non-linear system
- input-to-output control has to be linear.




$t=0, V_L(t) = V_{CC}$

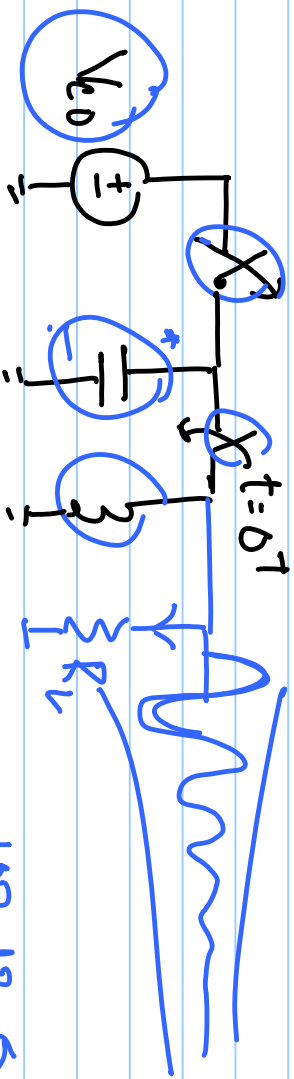

$$V_{out} = f(V_s, V_{in})$$

$$\left(-102 \frac{dBm}{s} \right) = 10 \log_{10} \left(\frac{V^2}{4 \times 50} \right)$$


-25 dBm

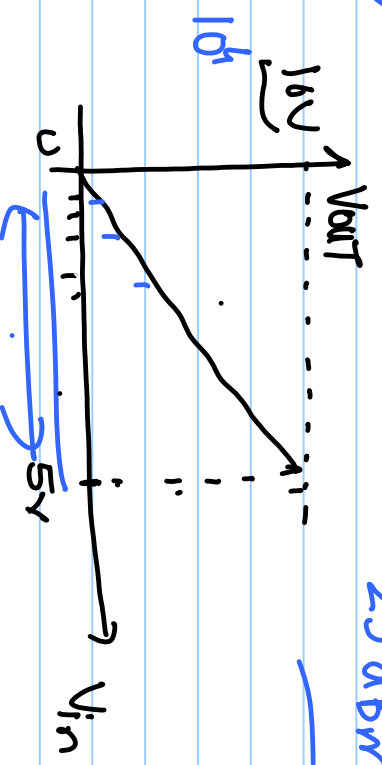

✓ (M) MOSFET :

$$V_{out} = f(V_{in}, V_s) \quad \checkmark$$

✓ (B) BJT :

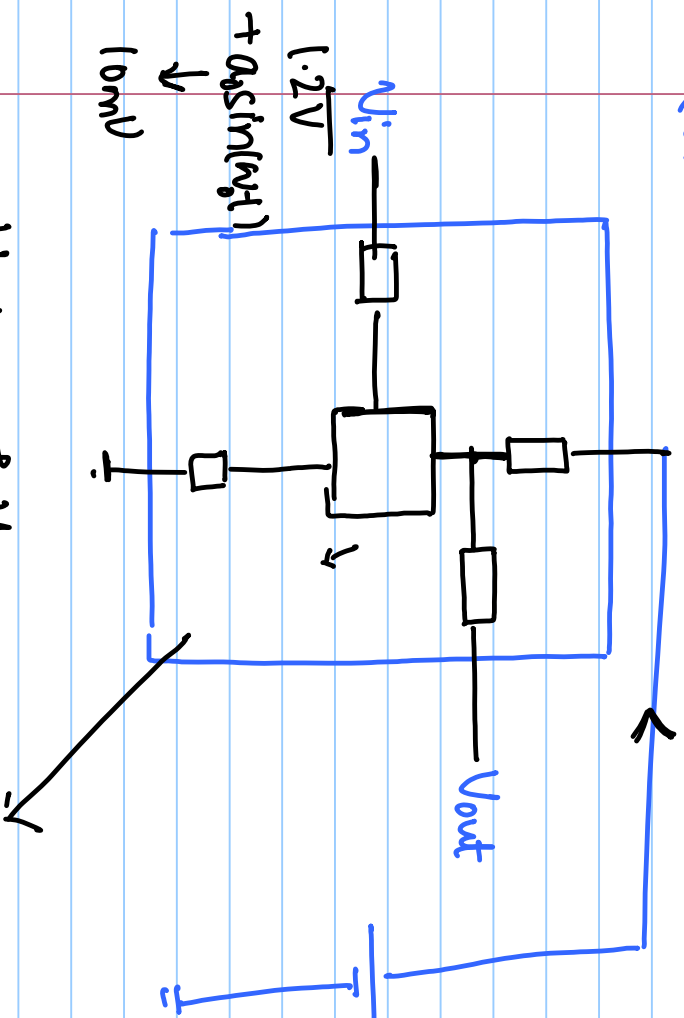

non-linear.

$$V_{out} = R V_{in} = \text{limited.}$$

$$\Delta V_{out} = 100 \cdot \Delta V_{in} \quad \checkmark$$

NCVS, NCVS, - .