
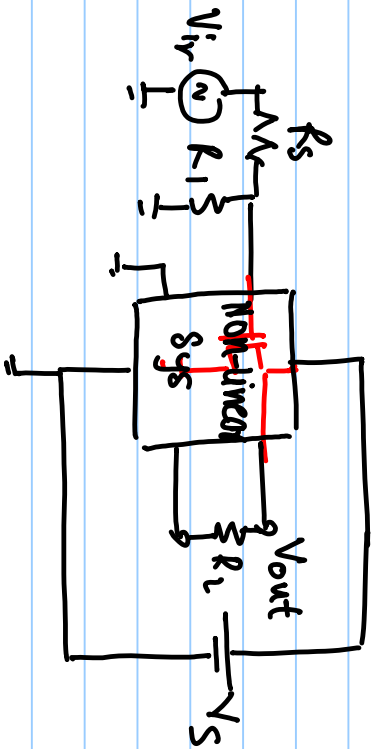



Lecture #4

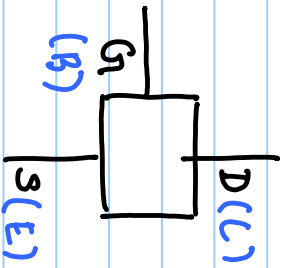


- Non-linear system to deliver large power
- input-to-output as linear control
- MOSFETs (MOS) BJT's



MOS

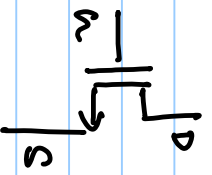


MOS

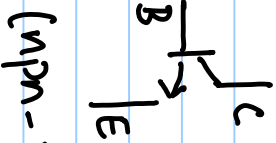

(NPN-BJT)


(NMOS)

linear approximate model of MOS

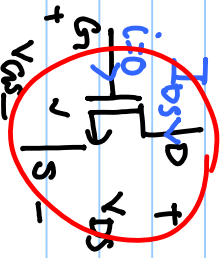


$I_{DS} = f(V_{GS}, V_{DS})$

≡

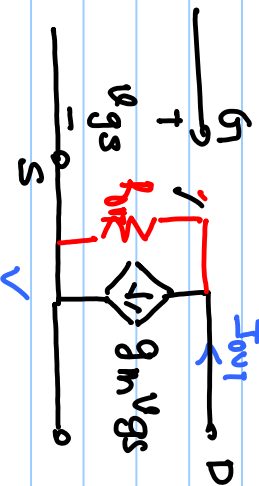


Voltage controlled current source (VCCS)

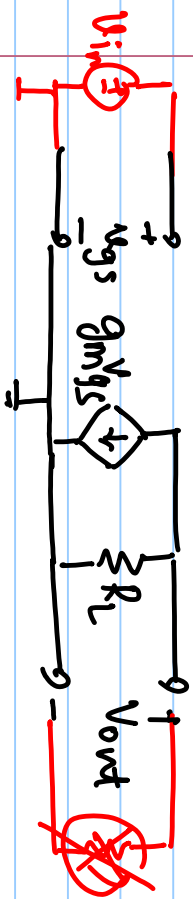

$$\frac{V_{out}}{V_{in}} = -g_m R_L = K$$


(VCVS)

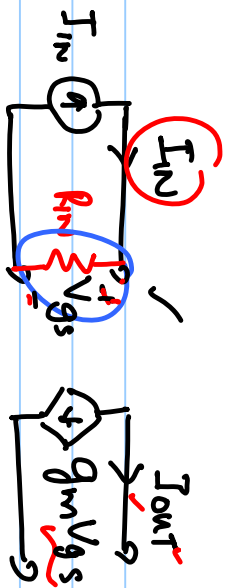

$$I_{out} = g_m R_{in} I_{in}$$




$$\frac{I_{out}}{I_{in}} = -g_m R_{in}$$

$v_{gs} = I_{in} \cdot R_{in}$

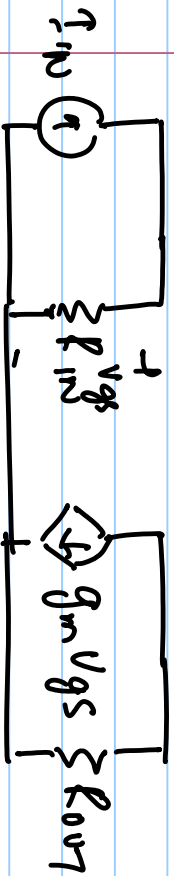

$$V_{out} = g_m (R_{in} \cdot I_{in}) R_{out} \Rightarrow \frac{V_{out}}{I_{in}} = \dots (g_m R_{in}) R_{out}$$

CCVS

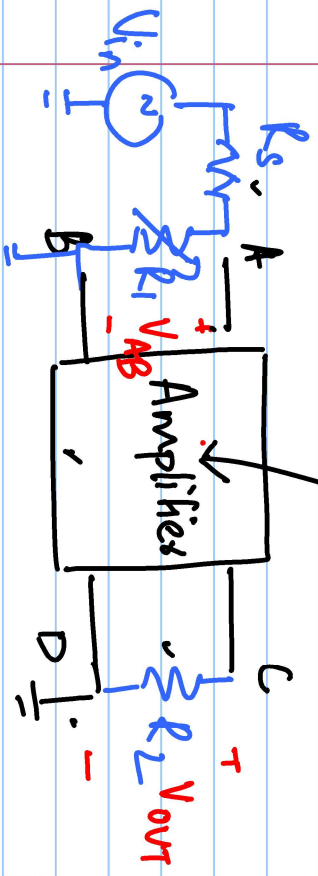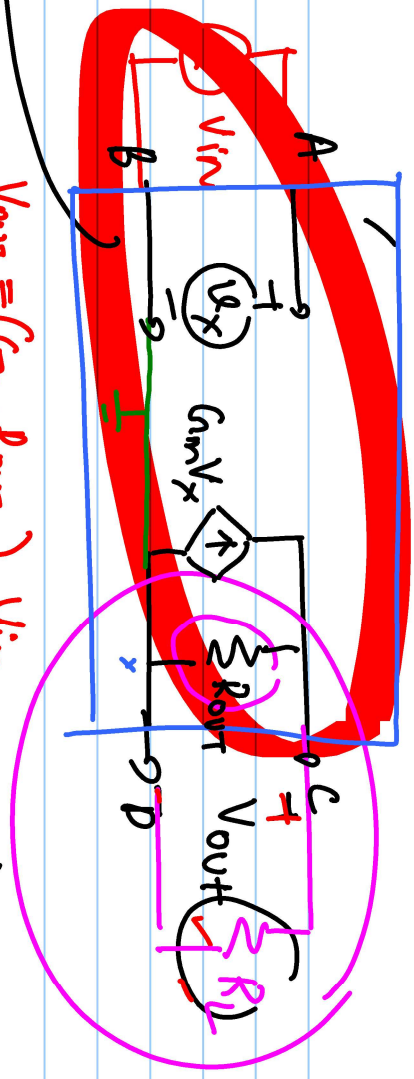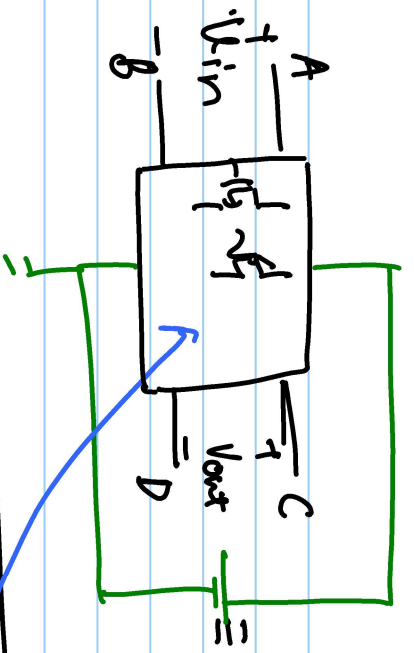

$$V_{out} = (G_m R_{out}) V_{in}$$

$$\frac{V_{out}}{V_{in}} = G_m R_{out}$$


$$G_m = 10 \text{ mA/V} \pm 10\%$$


$$R_{out} = 16 \text{ k}\Omega \pm 20\%$$

$$V_{out} = G_m (R_L || R_{out}) V_{AB}$$

$$V_{AB} = \frac{R_1}{R_1 + R_s} V_{in}$$

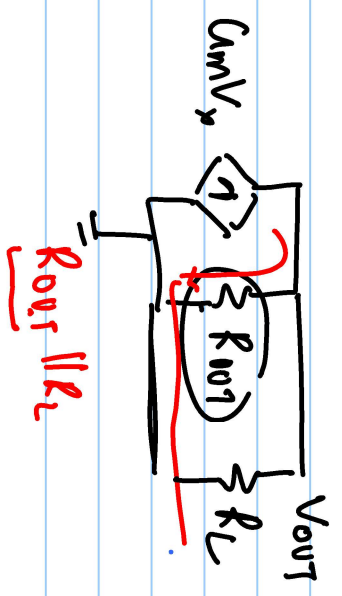
$$V_{out} = \frac{G_m}{\frac{1}{R_L} + \frac{1}{R_{out}}} \times \frac{R_1}{R_1 + R_s} V_{in}$$



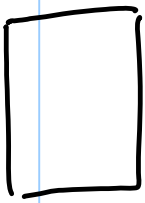

PVT variations.

Process, voltage, temperature

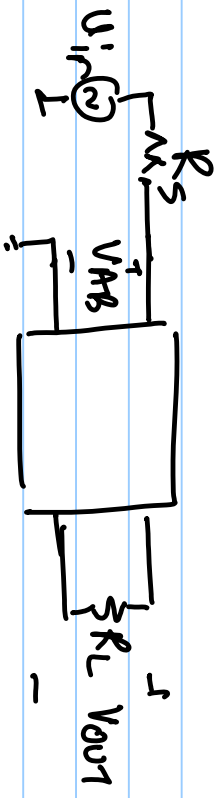


$$V_{out} = 150 V_{in} = \underbrace{C_{gm}}_{= 150} (R_L || R_{out}) V_{in}$$

$$V_{out} = 100 V_{in}$$

0
0 → 60 miles/hr.

Example.

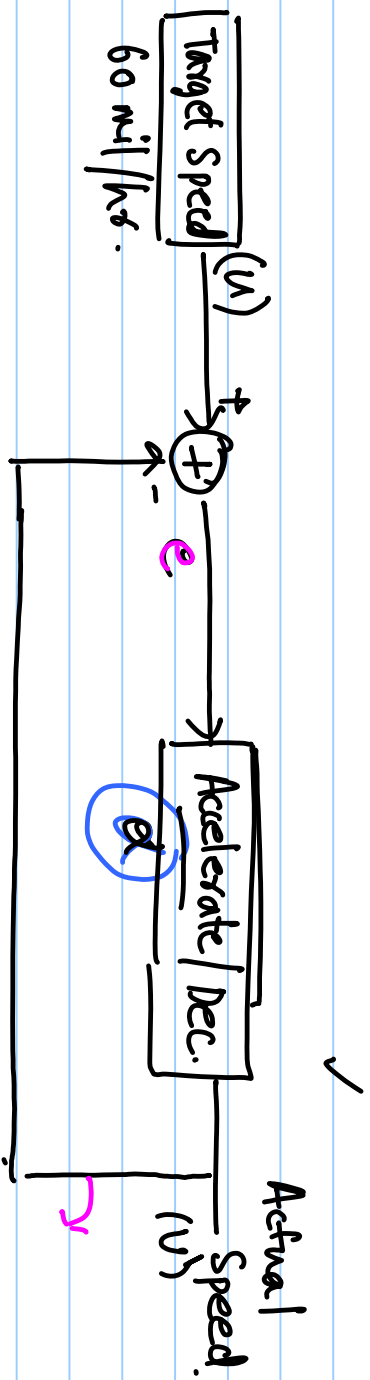

— $v(0) = 0$, $v(t) = \underline{\alpha} \cdot t$

— α varies with time.

— α is proportional to $(u-v)$

