

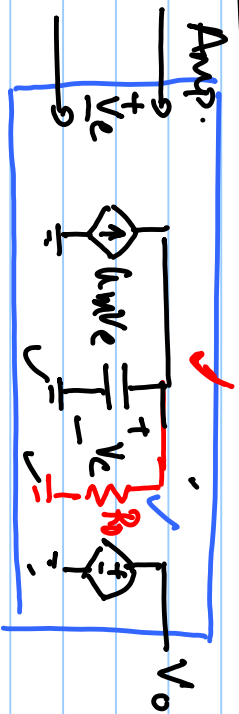


# Lecture #7.

Ideal Amp.

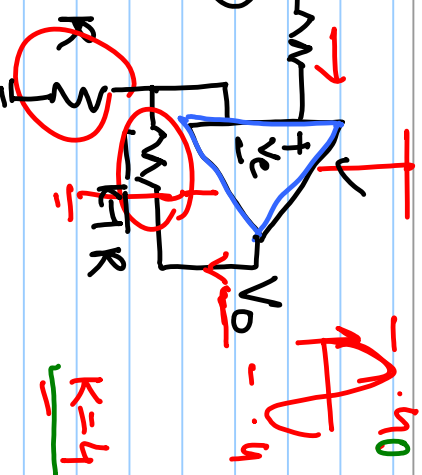
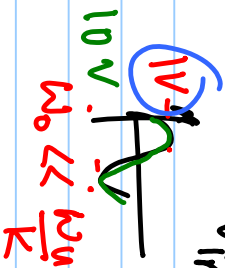
$$\frac{V_o(s)}{V_e(s)} = \frac{G_m}{sC}$$



$$\frac{V_o}{V_{in}} = 4$$

$$\frac{V_o(s)}{V_e(s)} =$$

$$V_o(s) = G_m V_e \times (R_o || \frac{1}{sC})$$

$$\frac{V_o}{V_e} = \frac{G_m R_o}{1 + sR_o C} = \frac{1}{\frac{1}{G_m R_o} + \frac{sC}{G_m}}$$

$$= \frac{1}{\frac{1}{A_o} + \frac{s}{\omega_w}}$$

$$\frac{V_o}{V_{in}} =$$

$$V_e = V_{in} - \frac{V_o}{K}$$

$$V_o = \frac{1}{\frac{1}{A_o} + \frac{s}{\omega_w}} \cdot V_e$$



$$\frac{V_o}{V_{in}} = \frac{1}{1 + \frac{1}{A_o} + \frac{s}{\omega_w}}$$

$$H(s) = \frac{V_o}{V_{in}} = \frac{1}{1 + \frac{1}{A_0} + \frac{\Delta}{\omega_n}}$$

$$\left. \frac{V_o}{V_{in}} \right|_{s=0} = \frac{K_v}{1 + \frac{1}{A_0}}$$

$$s = -\omega_n \left( \frac{1}{K} + \frac{1}{A_0} \right)$$

$$\approx -\frac{\omega_n}{K}$$

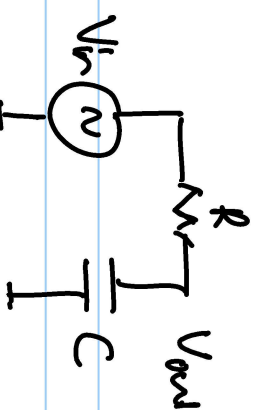
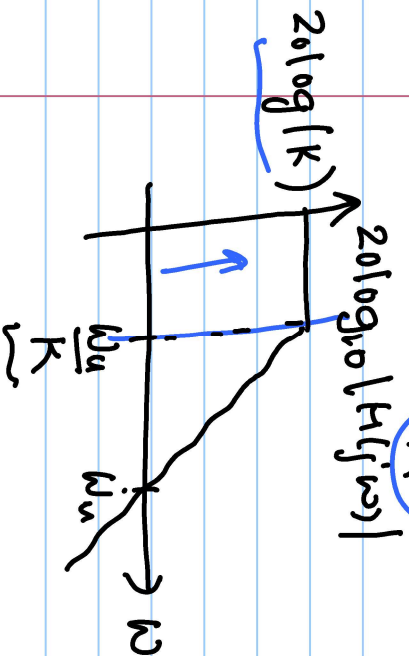


$$\frac{V_o}{V_{in}} = \frac{1}{1 + sRC}$$




$$\frac{N(s)}{D(s)} = H(s)$$

$$D(s) = 0$$

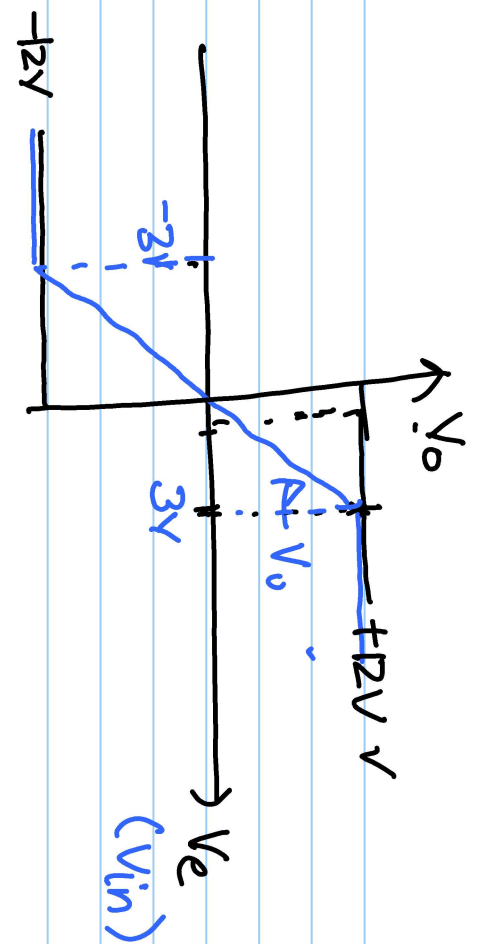
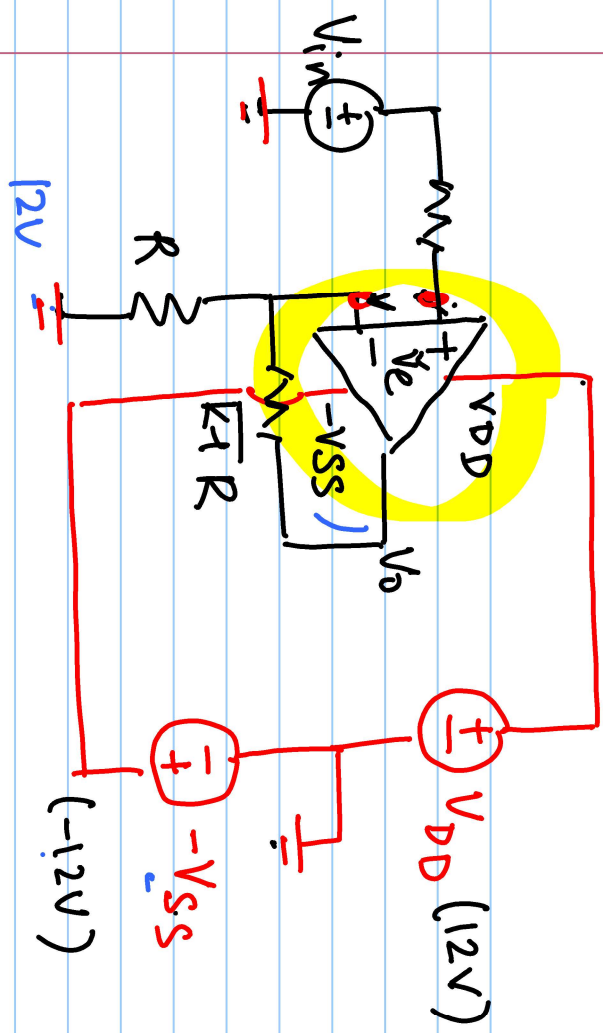


$\rightarrow V_o = A_o V_e$  if  $A_o \rightarrow \infty, V_e = +\Delta \Rightarrow V_o \rightarrow +\infty$   
 $V_e = -\Delta \Rightarrow V_o \rightarrow -\infty$

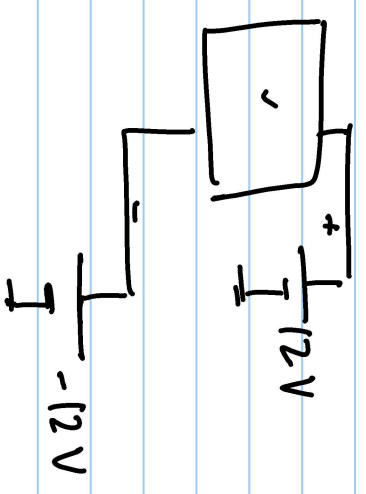$\checkmark V_e = V_{in} - \frac{V_o}{K}$



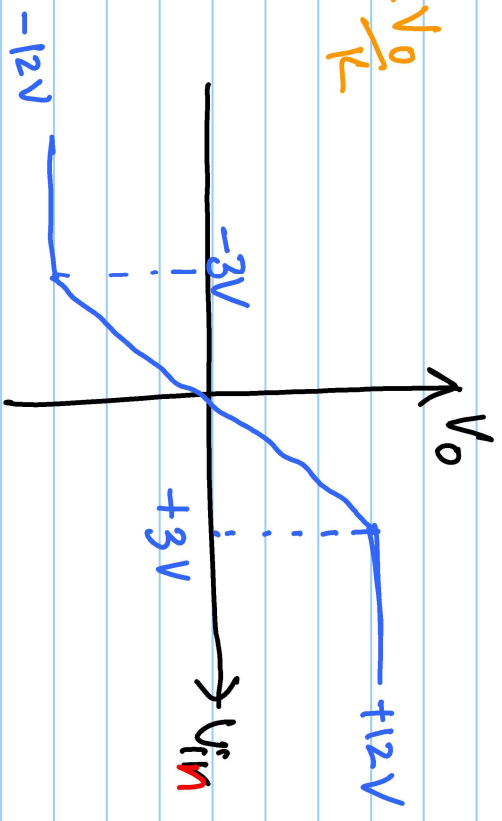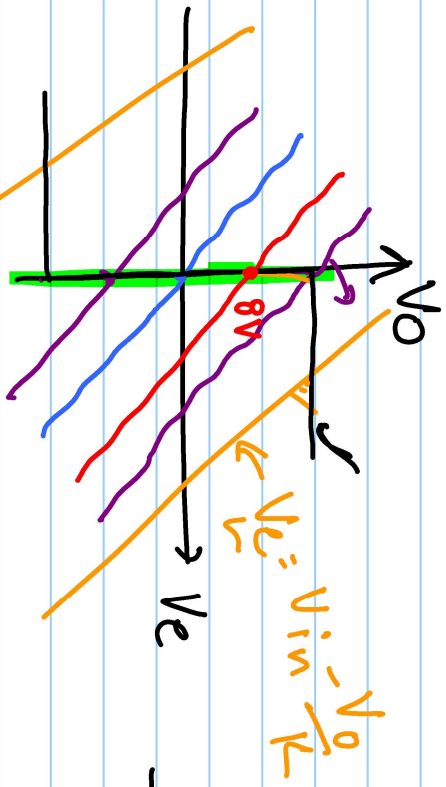$A_o \rightarrow \infty$   
 $V_o = K V_{in}$   
 $V_{in} ? \rightarrow V_o = +12V$




$$V_0 = A_0 V_e$$

$$V_e = V_{in} - \frac{V_0}{K}$$

$$V_e = -\frac{V_0}{K}$$

$$V_{in} = +2V$$

$$V_e = 2 - \frac{V_0}{K}$$

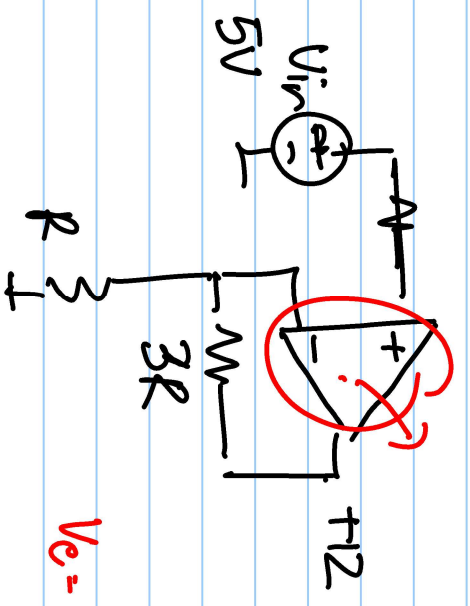


$$V_e = 5 - \frac{12}{K}$$

$$V_0 = A_0 V_e$$

$$V_e = V_{in} - \frac{V_0}{K}$$

$$V_e = \frac{V_{in}}{(1 + \frac{A_0}{K})}$$

$$V_o = A_o V_e$$

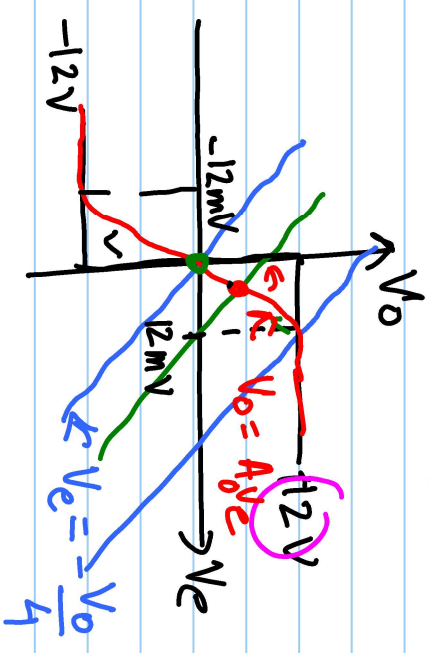

$$\begin{cases} V_o = A_o V_e \\ V_e = V_{in} - \frac{V_o}{K} \\ \neq 0 \\ = V_{in} - \frac{V_o}{4} \end{cases}$$

