
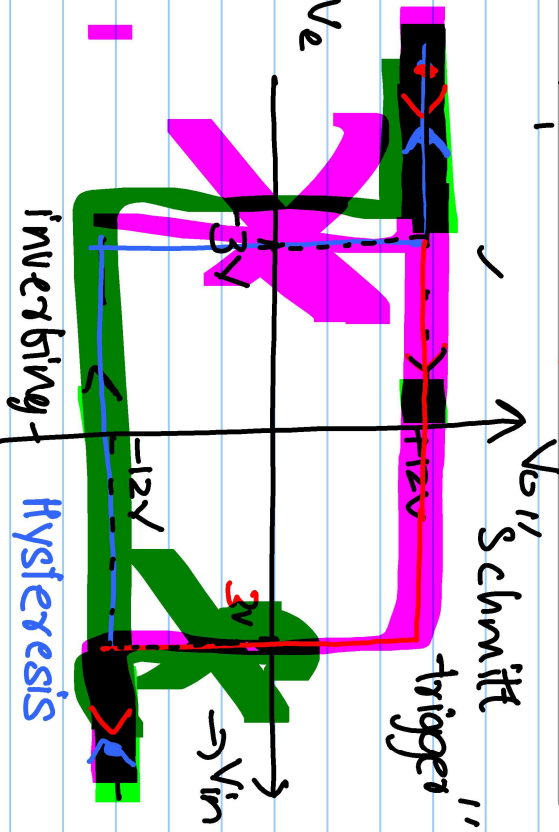
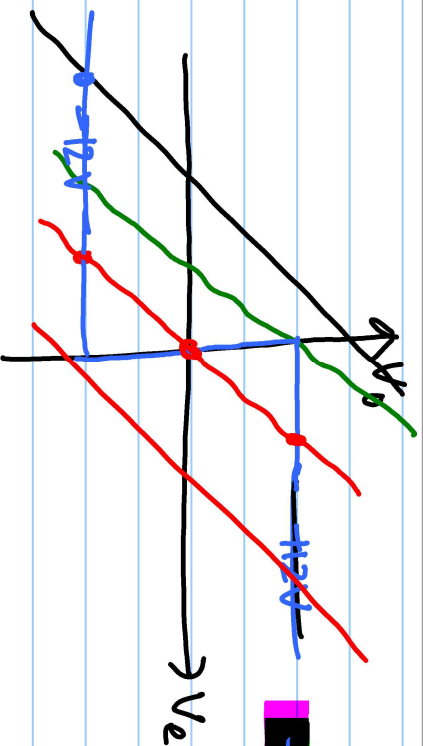


lecture #9

$$\frac{dy}{dx} = 0$$

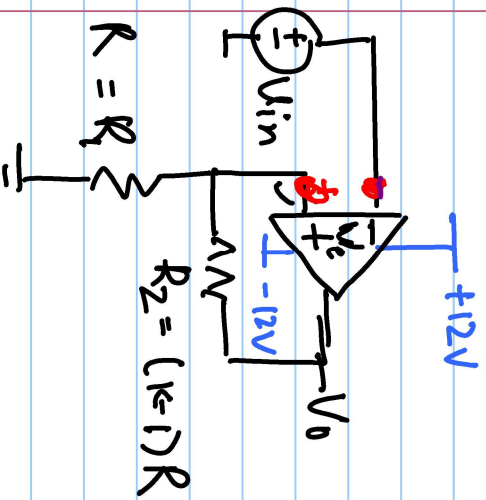

$$V_e = \frac{V_0}{k} - V_{in}$$

✓

$$V_0 = A_0 V_e \text{ where } A_0 \rightarrow \infty$$

$$V_{in} = 0 \Rightarrow V_e = \frac{V_0}{k}$$

$$V_{in} = +$$

$$V_{in} > 3V \Rightarrow V_0 = -12V$$

$$V_{in} < -3V, \Rightarrow V_0 = +12V$$


$$V_e = \frac{V_0}{k} - V_{in}$$


$$\text{if } V_{in} > 3V \Rightarrow V_0 = -12V$$

$$V_e = \frac{-12}{4} - V_{in} = -3 - V_{in}$$

$$V_{in} < -3V$$




$$V_e = \frac{12}{4} - V_{in}$$

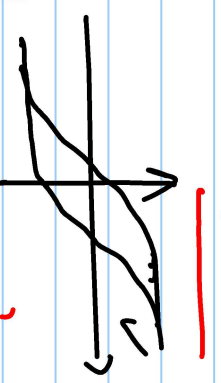

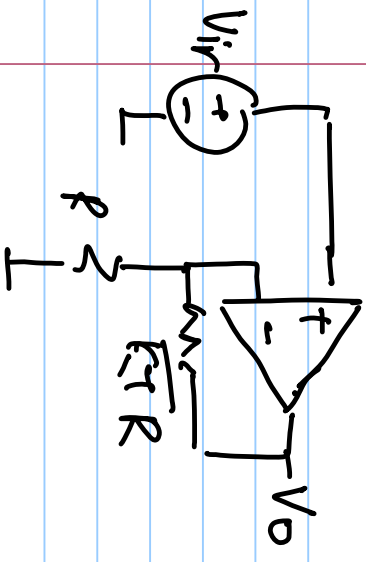

$$\frac{V_o}{V_{in}} = K_{(FV)}$$

non-inverting amplifier

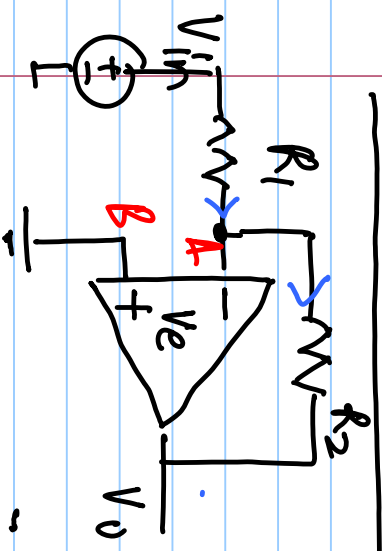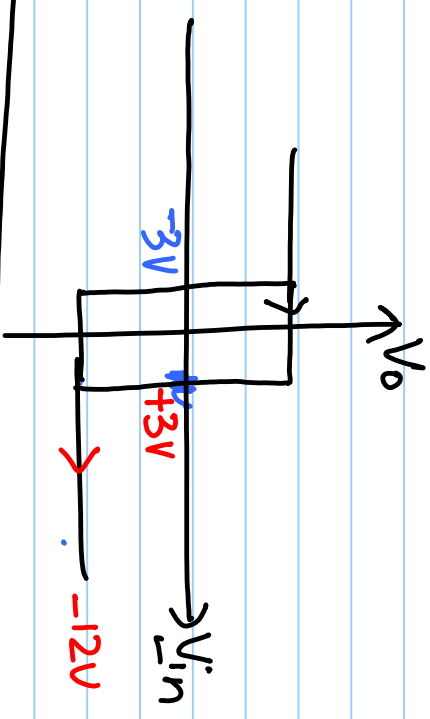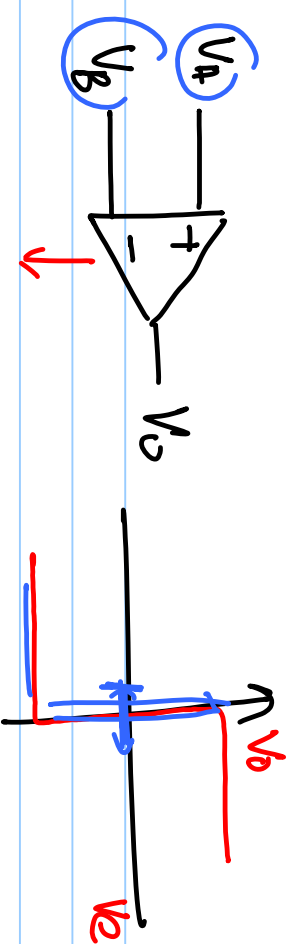

$$V_e = 0$$

$$V_A = 0$$

$$\frac{V_{in}}{R_1} = -\frac{V_o}{R_2}$$

$$\frac{V_o}{V_{in}} = -\frac{R_2}{R_1}$$



inverting amplifiers

$$V_e = 0 \Rightarrow \frac{R_1}{R_1 + R_2} V_o + V_{in}$$

$$V_e = - \frac{V_o}{-R_2}$$


$$V_e = 0 - \frac{R_1}{R_1 + R_2} V_o - \frac{V_{in} R_2}{R_1 + R_2} \left(V_{in} \frac{R_1}{R_1 + R_2} \right)$$
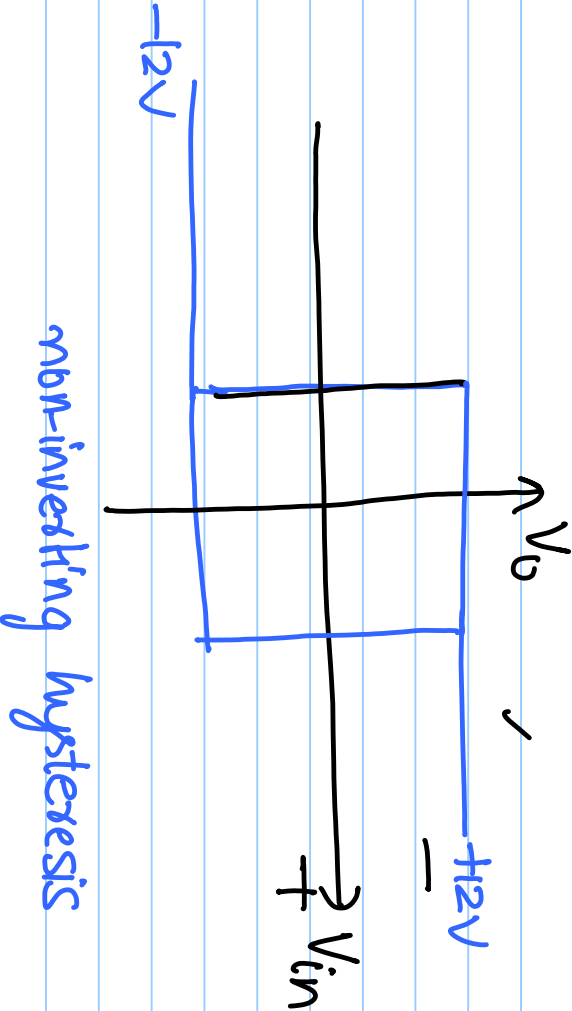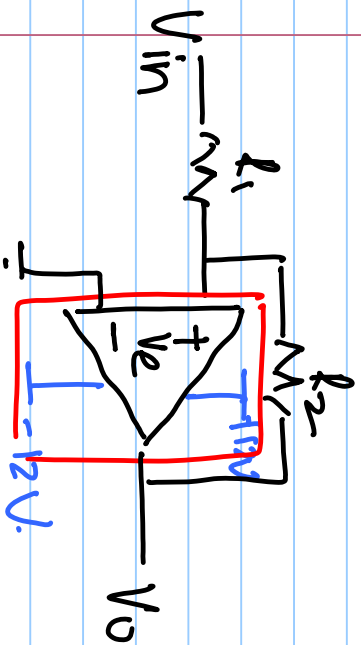
$$V_e = V_b - V_a = 0 - \left(\frac{R_1}{R_1 + R_2} V_o + \frac{R_2}{R_1 + R_2} V_{in} \right)$$




$$V_e = \frac{R_1}{R_1 + R_2} V_o$$

> 0

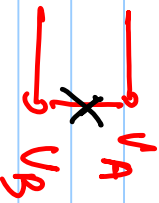


$V_A = V_B$
virtually short

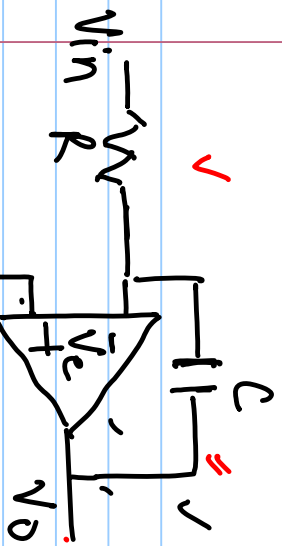


$$V_0 = A_{v_c} V_c$$
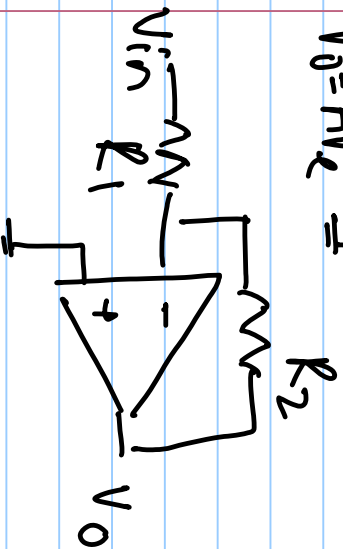
$$\frac{V_0}{V_{in}} = - \frac{(V_{s_c})}{R_1} = \frac{-1}{\cancel{2CR_1}}$$




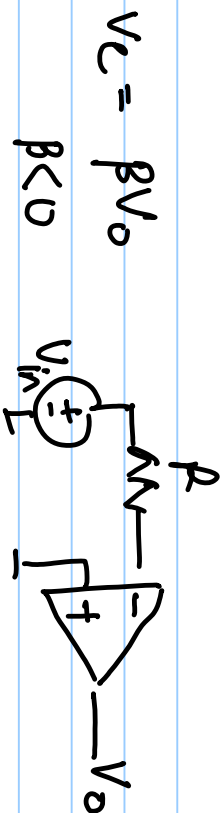
$$\frac{V_0}{V_{in}} = - \frac{R_2}{R_1}$$



$$V_c = BV_0$$



$$B < 1$$

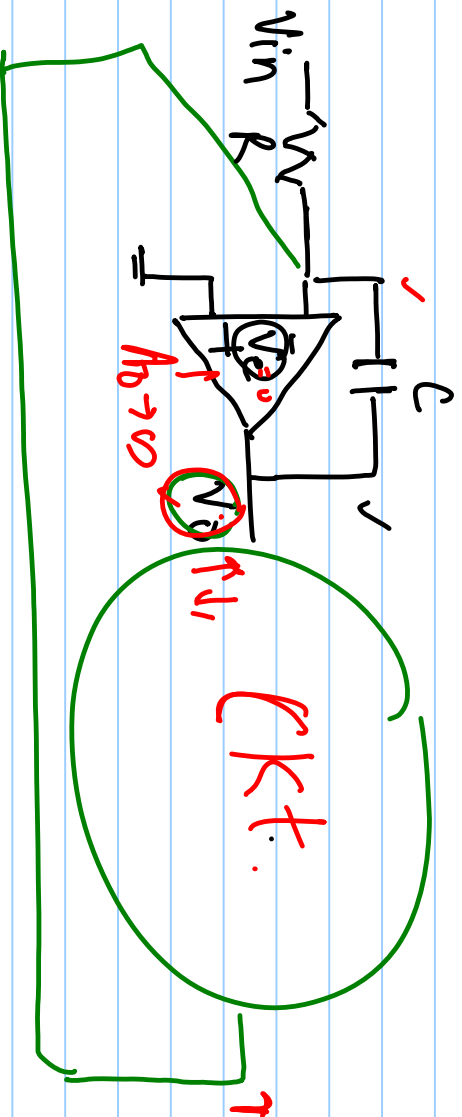

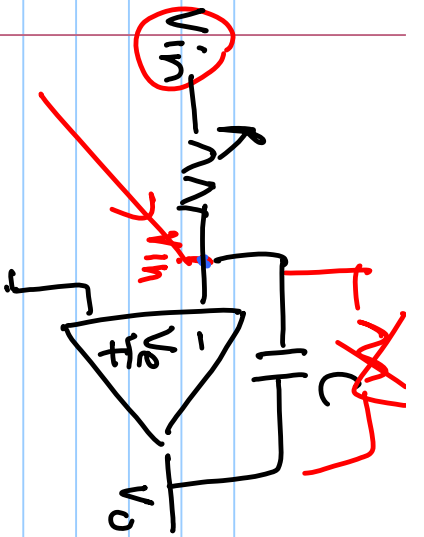

$$\frac{V_{in}}{R} = -C \frac{dV_o}{dt}$$
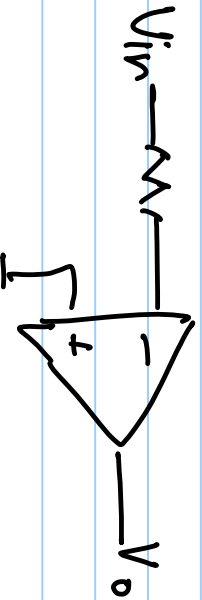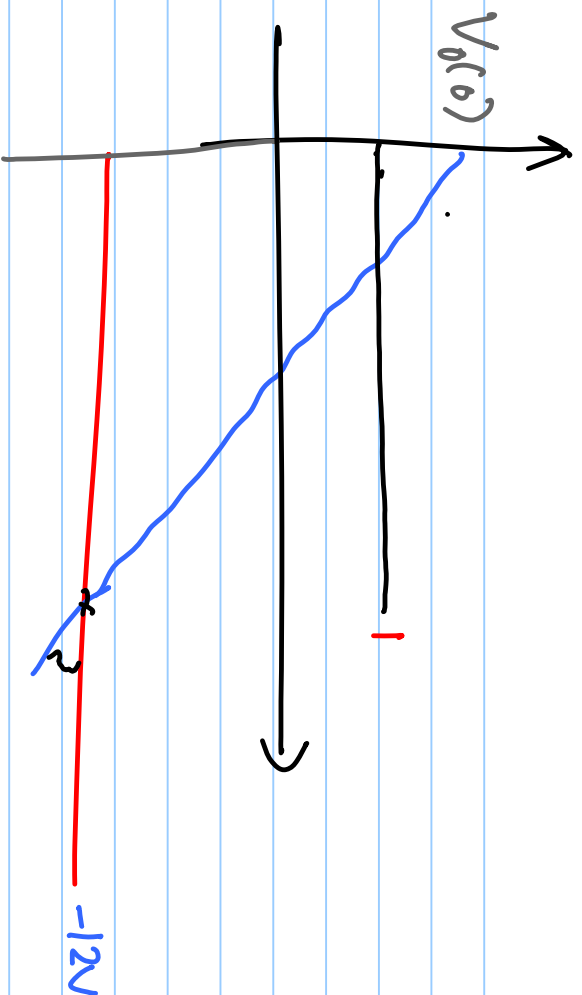
$$\frac{dV_o}{dt} = -\frac{1}{RC} V_{in}$$



Under approx. that dc negative feedback exists around integrator

$$V_e = 0 \Rightarrow \frac{dV_o}{dt} = -\frac{1}{RC} V_{in}$$

$$\frac{V_o(s)}{V_{in}(s)} = \frac{-1}{RCs}$$