

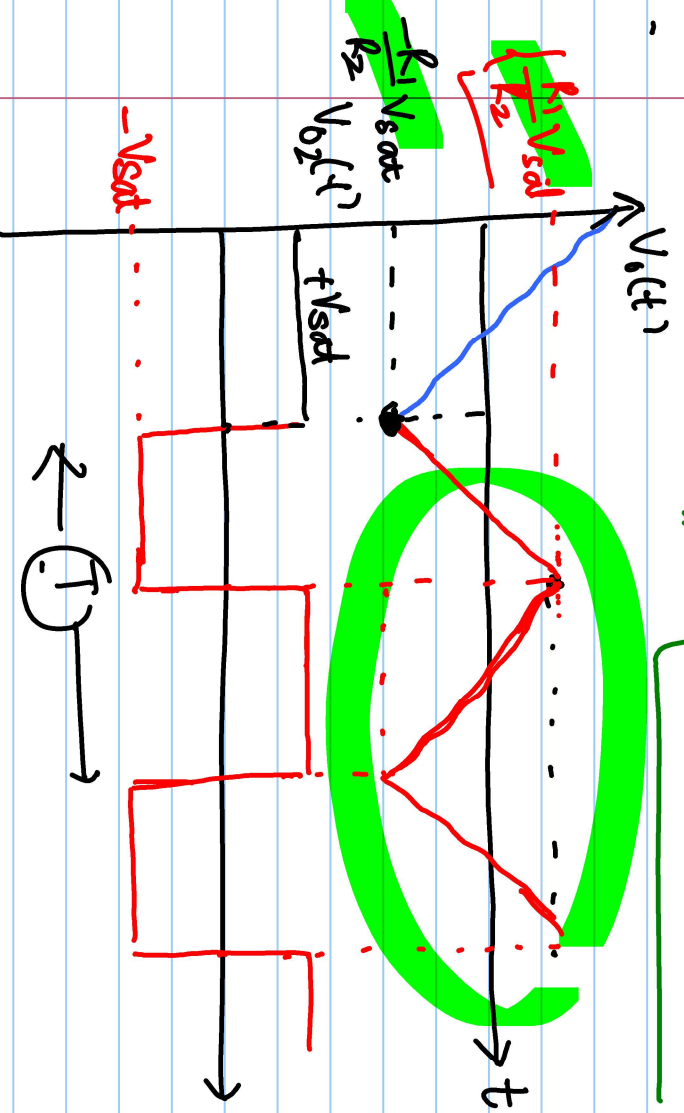


Lecture # 10

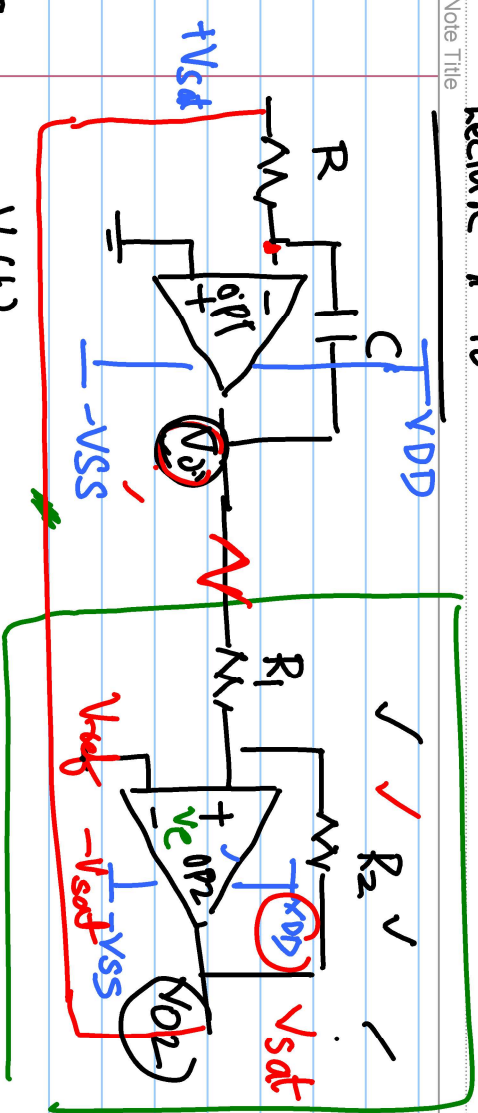

At $t=0$. $V_o(0)$

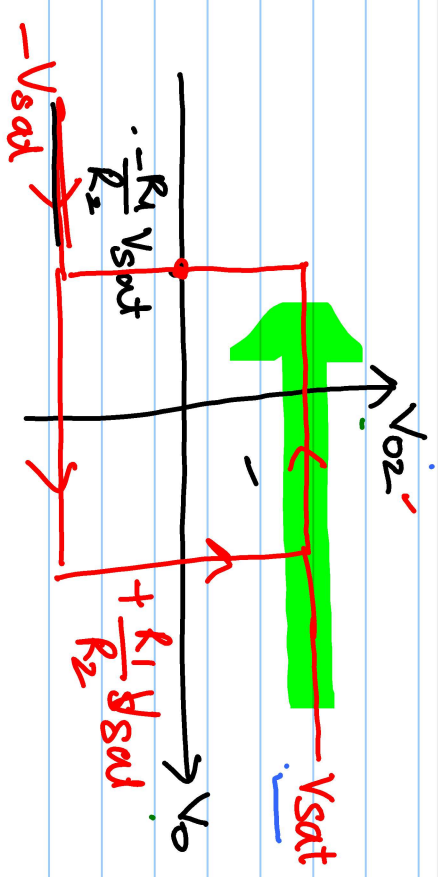


$$V_e = \frac{R_2}{R_1 + R_2} V_o + \frac{R_1}{R_1 + R_2} V_{o2}$$

$$V_o = \frac{R_1}{R_1 + R_2} V_e + \frac{R_2}{R_1 + R_2} V_{o2}$$

$$V_e = \frac{R_2}{R_1 + R_2} V_o + \frac{R_1}{R_1 + R_2} V_{sat}$$
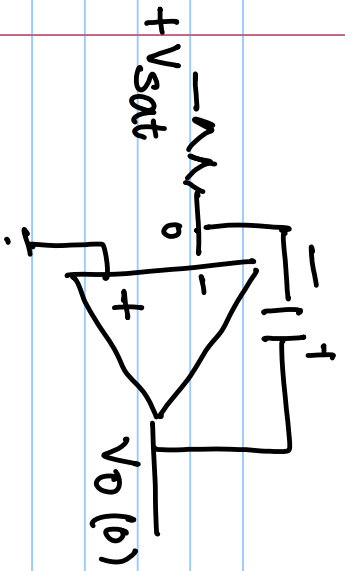
$$V_e = 0 \Rightarrow V_o = \frac{-R_1}{R_2} V_{sat}$$



$$\frac{V_{sat}}{R} = -C \frac{dV_o(t)}{dt}$$


$$\frac{dV_o}{dt} = + \frac{V_{sat}}{RC}$$


$$\frac{T}{2} = \frac{2 \cdot R_1 \cdot V_{sat}}{R_2} = \frac{2 R_1 R C}{R_2}$$

$$T = \frac{4 R_1 R C}{R_2}$$



$$f_{osc} = \frac{1}{T} = \frac{R_2}{R_1} \times \frac{1}{4RC} \quad \checkmark$$

$$f_{osc} = 10 \text{ M}$$

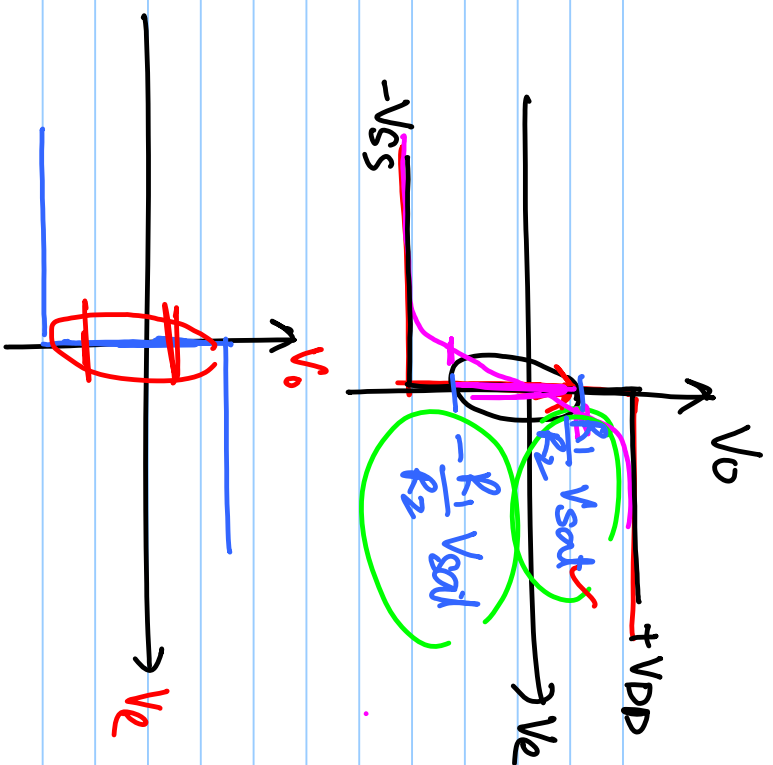


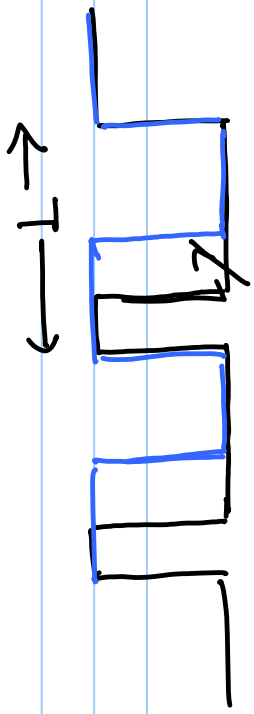

Duty Cycle = $\frac{T_{high}}{T}$

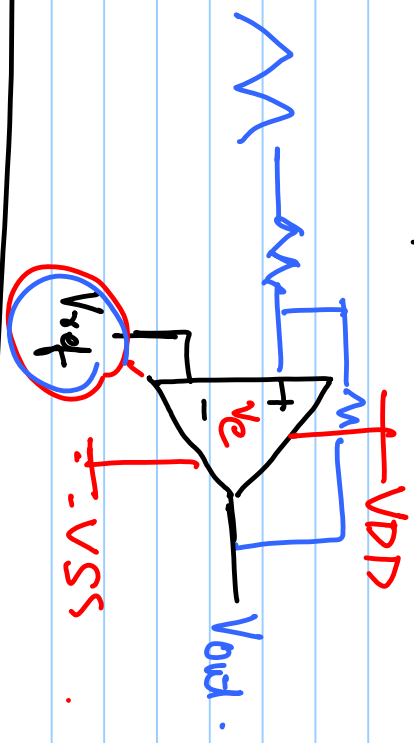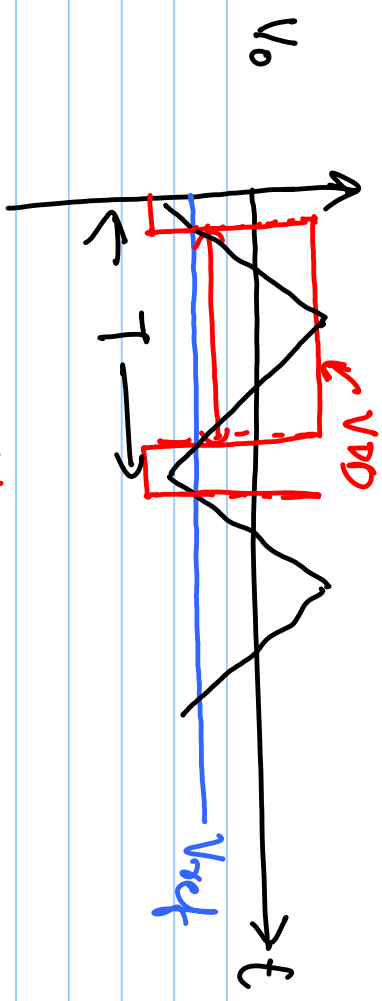

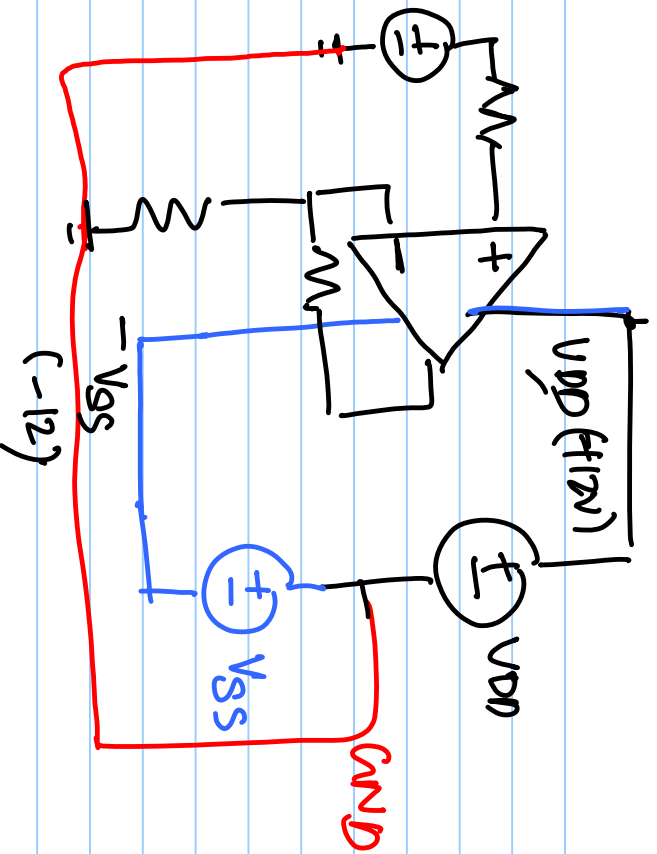-
- Non-inverting amp. / Schmitt trigger
 - inverting amp. / Schmitt trigger
 - Comparators
 - Integrators



Bipolar (BJT's) $V_{DD} / -V_{SS}$
 CMOS $V_{DD} / 0$

