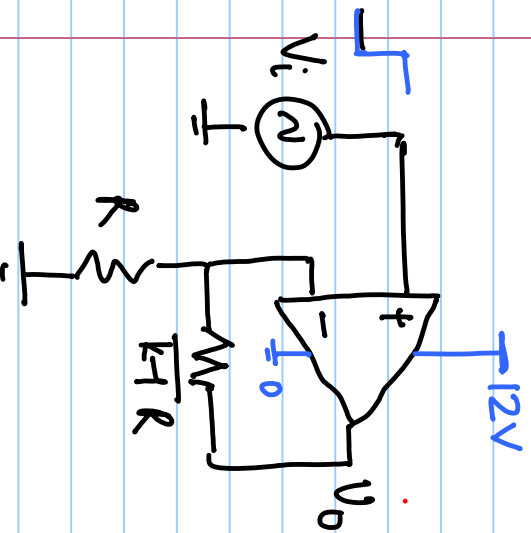


Lecture #15




$$\frac{V_o}{V_i} = K$$


$$V_o = V_e \times G_m \left(\text{roll } \frac{1}{s} \right)$$

$$= V_e \cdot$$
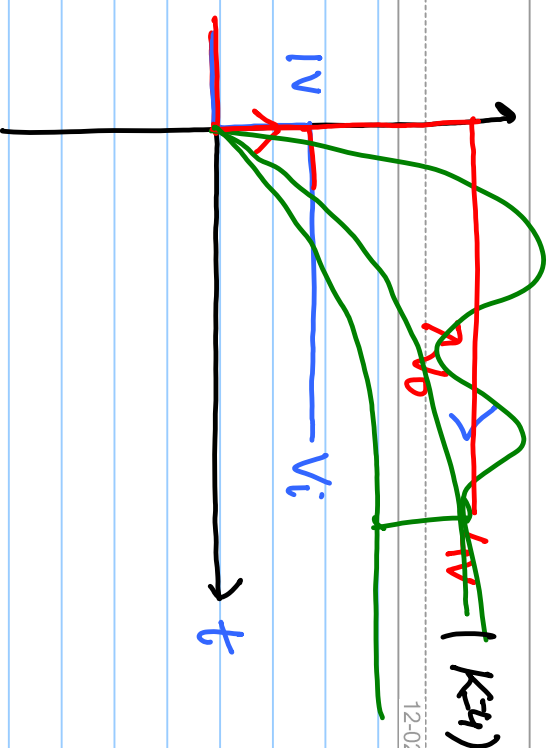
$$\frac{G_m R_o}{1 + s R_o C_1} \rightarrow A_o \rightarrow \frac{1}{p_1}$$



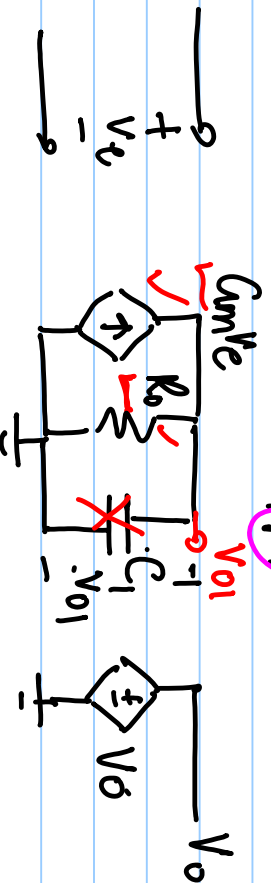Real amp: $A_o \frac{1}{1 + s/p_1} \rightarrow \frac{V_o}{V_e}$





Ideal amp: $C_1 \rightarrow 0$

Real amp: $C_1 \neq 0$

Ideal amp: $A_o = G_m R_o \rightarrow \infty$

$G_m R_o$ as large as possible
 C_1 as low as possible

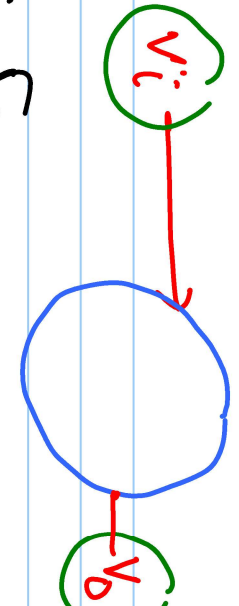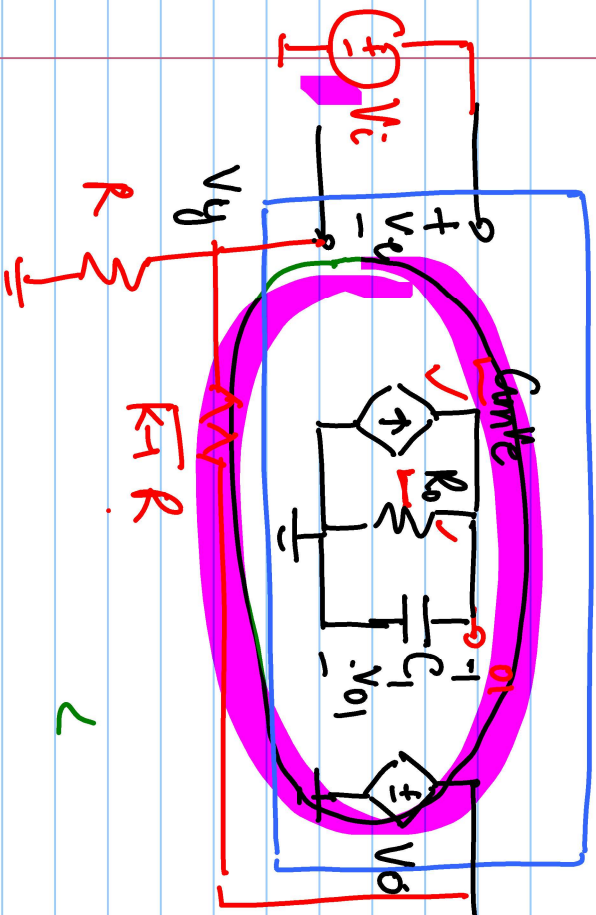\Rightarrow Finite dc gain and finite value for p_1




$$\frac{V_o}{V_i} = \frac{k}{1 + \frac{k}{A(s)}}$$

$$V_o = (V_i - V_y) A(s)$$

$$= \left(V_i - \frac{V_o}{k} \right) A(s)$$

$$V_o \left(\frac{1}{A(s)} + \frac{1}{k} \right) = V_i$$
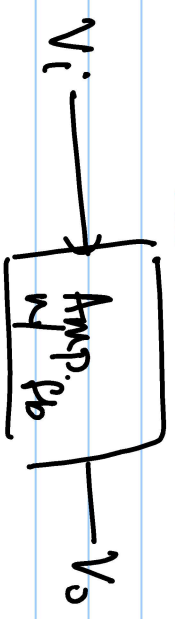
$$A(s) = \frac{V_o(s)}{V_i(s)} = k \frac{1}{1 + \frac{k}{A_0(1+s/p_1)}} = k \frac{1}{\left(1 + \frac{k}{A_0}\right) + \frac{k}{A_0 p_1} s}$$





→ poles in L.H.P

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{k}{\left(1 + \frac{k}{A_o}\right)} \frac{1}{1 + \frac{k}{A_o p_1} \left(1 + \frac{k}{A_o}\right)} = \frac{k}{\left(1 + \frac{k}{A_o}\right)} \frac{1}{1 + \frac{s}{p_1' \left(\frac{A_o+1}{k}\right)}}$$

$$= \frac{A_{DC}}{1 + \frac{s}{p_1'}}$$

$$A_{DC} = \frac{k}{1 + \frac{k}{A_o}} \approx \frac{k}{A_o}$$

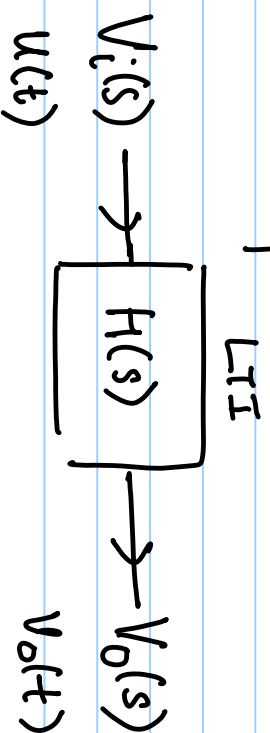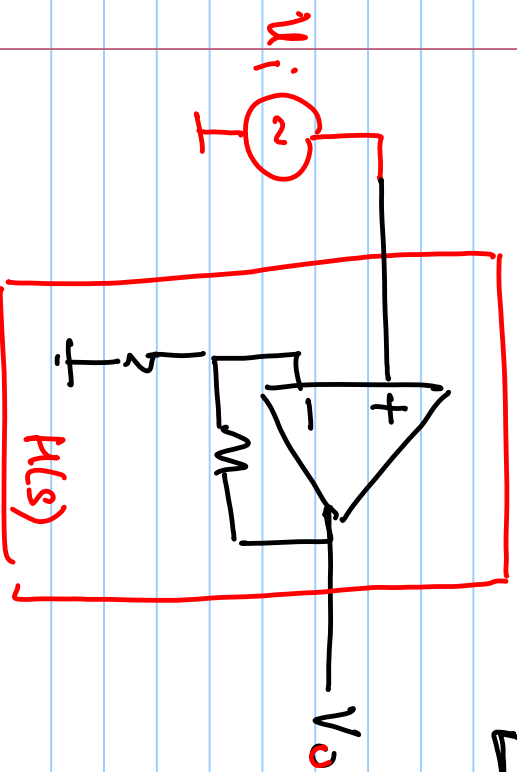1st pole $s = -p_1' = -p_1 \left(1 + \frac{A_o}{k}\right)$



$$v_o(t) = u_i(t) * h(t),$$

$$V_o(s) = V_i(s) H(s)$$

$$v_o(t) = \mathcal{L}^{-1}(V_o(s))$$

$$u_i(t) = u(t)$$

$$V_i(s) = \frac{1}{s}$$

$$V_o(s) = \frac{1}{s} \cdot \frac{A_{oc}}{1 + s/p_1'} = \frac{A_{oc} p_1'}{(s + p_1') s}$$

$$= \frac{A_{oc}}{s} + \frac{-A_{oc}}{s + p_1'}$$



$$= A_{oc} \left[\frac{1}{s} - \frac{1}{s + p_1'} \right]$$

$$v_o(t) = \mathcal{L}^{-1} [V_o(s)]$$

$$= A_{oc} [u(t) - e^{-p_1' t} u(t)]$$

$$= A_{oc} [1 - e^{-p_1' t}] u(t)$$
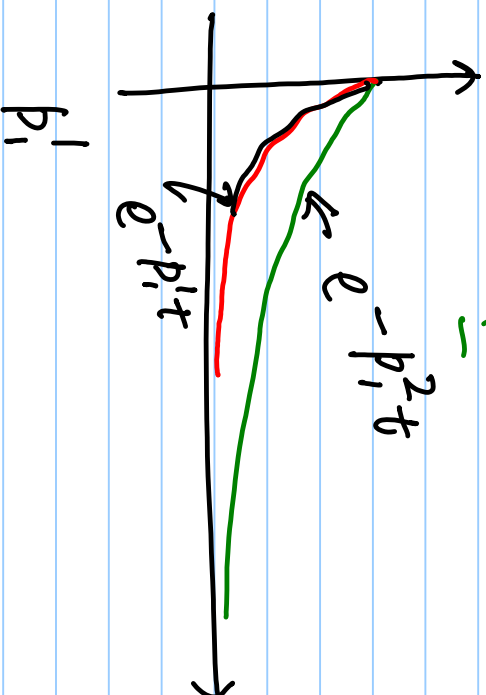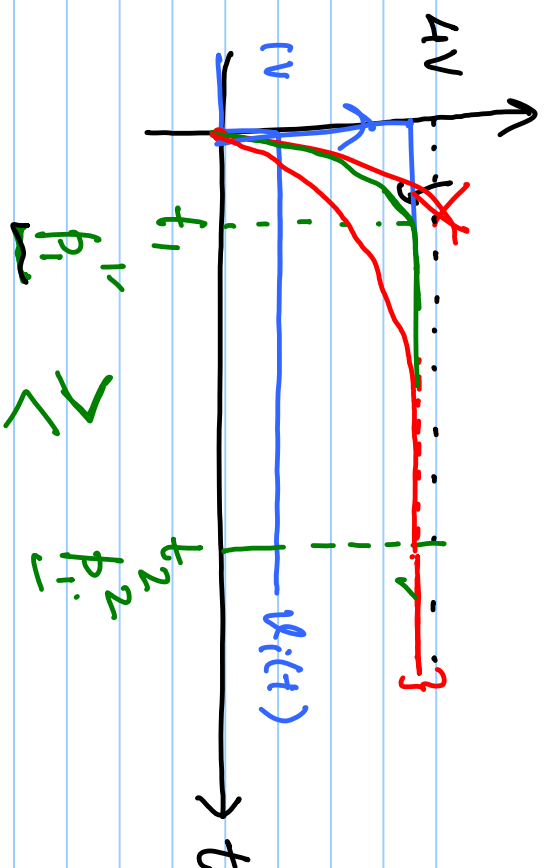
$$= \frac{A_{oc} (R)}{1 + \frac{R}{R_0}} \left[1 - e^{-p_1' (1 + \frac{R}{R_0}) t} \right] u(t)$$




$$\frac{dv_o(t)}{dt} = A_{DC} p_1' e^{-p_1' t}$$

Steady state error. $E_{static} = \lim_{t \rightarrow \infty} V_o(t) - \lim_{t \rightarrow \infty} V_o(t)$
 $t \rightarrow \infty, 1$ is ideal

$$= K U_{in} - \frac{K}{1 + \frac{K}{A_o}} U_{in}$$

$$= \frac{1}{\frac{A_o}{K} + 1} U_{in}$$

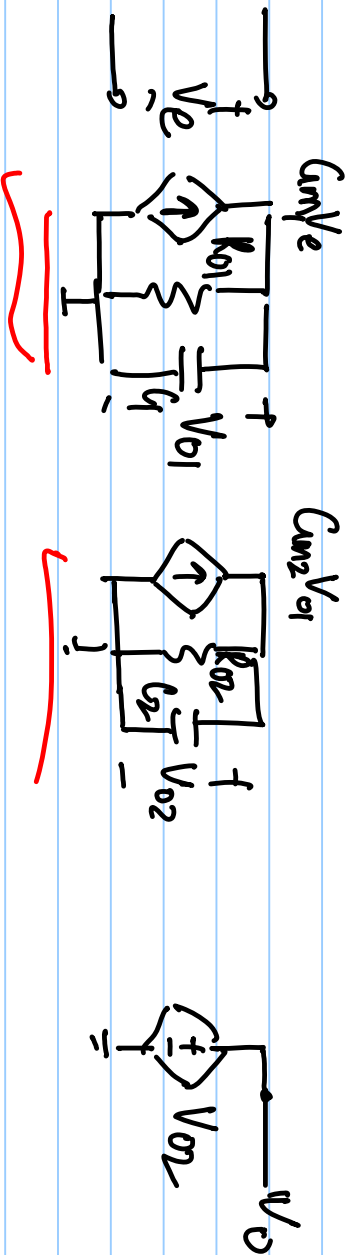


$$A(s) = \frac{V_o}{V_e} = \frac{G_{m1} R_{01}}{(1 + s R_{01} C_1)} \frac{G_{m2} R_{02}}{(1 + s R_{02} C_2)} = \frac{A_o}{(1 + s/b_1) (1 + s/b_2)}$$

$$A_0 = G_{m1} R_{o1} G_{m2} R_{o2}$$

$$s = -p_1 = -\frac{1}{R_{o1} C_1}$$

$$s = -p_2 = -\frac{1}{R_{o2} C_2}$$

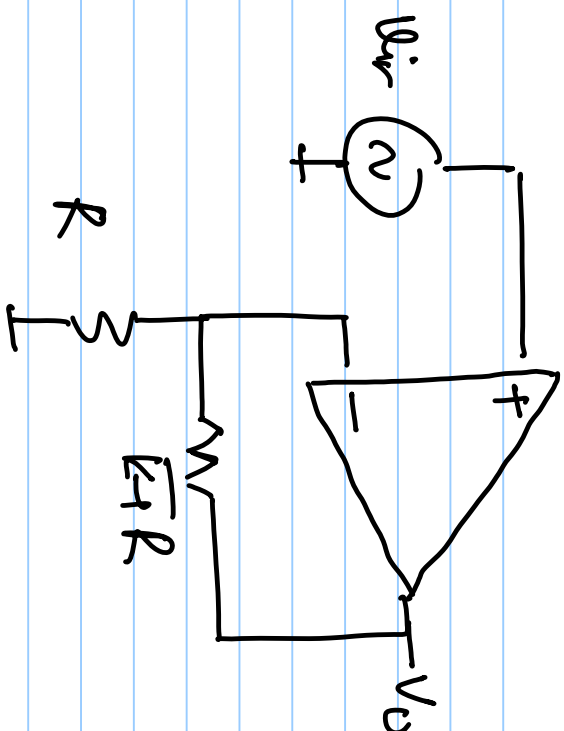

$$\frac{V_o}{V_i} = \frac{k}{1 + \frac{k}{A_0 s}} = \frac{k}{1 + \frac{k}{A_0} \left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right)}$$

$$\begin{aligned} &= \frac{k}{A_0} \frac{1}{\left[\frac{A_0}{k} + 1 \left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right) \right]} = \frac{A_0}{k} \frac{1}{A_0 + 1 + s \left(\frac{1}{p_1} + \frac{1}{p_2} \right) + \frac{s^2}{p_1 p_2}} \\ &= \frac{k}{1 + \frac{k}{A_0}} \frac{1}{\left[\frac{1 + \frac{s}{p_1} + \frac{s}{p_2} + \frac{s^2}{p_1 p_2}}{1 + \frac{s}{p_1} + \frac{s}{p_2} + \frac{s^2}{p_1 p_2} + \frac{s^2}{p_1 p_2} \left(1 + \frac{A_0}{k}\right)} \right]} \end{aligned}$$

$$\begin{aligned}
 &= \frac{A\omega_c}{(1+s)^{-1} s^2} \\
 &= \frac{A\omega_c}{s^2 + 2\zeta\omega_n s + \omega_n^2} = H(s)
 \end{aligned}$$