

Lecture #20

loop gain, $L(s) = \frac{A_0/k}{(1+\frac{s}{p_1})(1+\frac{s}{p_2})(1+\frac{s}{p_3})}$

$$H(s) = \frac{V_o}{V_i} = K \frac{L(s)}{1+L(s)}$$

$$D(s) = 1+L(s) = 0$$

if $p_1, p_2 > 0$



For second order, poles will be in L.H.P ✓

3rd order, poles in R.H.P

$$1+L(s) = 0 \Rightarrow \text{poles}$$



$$|L(s)| = 1 \Rightarrow \angle L(s) = \underline{180^\circ} \quad (2K\pi) \quad \checkmark$$

$$\underline{|L(s)| = 1}, \quad \underline{\angle L(s) < 180^\circ}$$

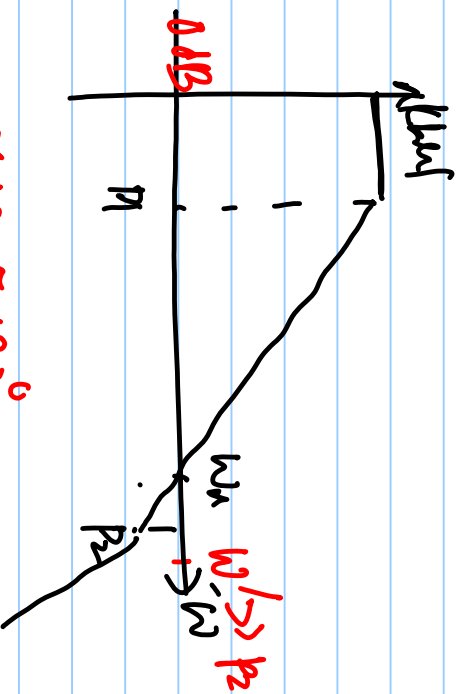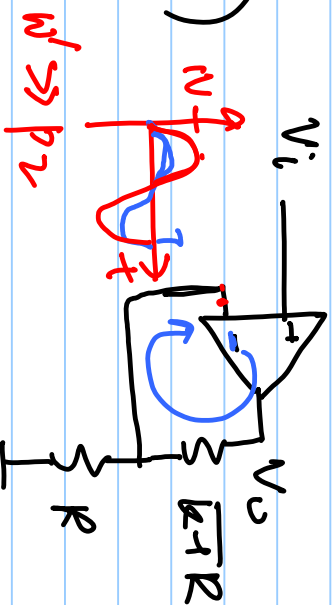


$$\angle L(s) \approx 180^\circ$$

$$|L(s)| = \frac{1}{X}$$

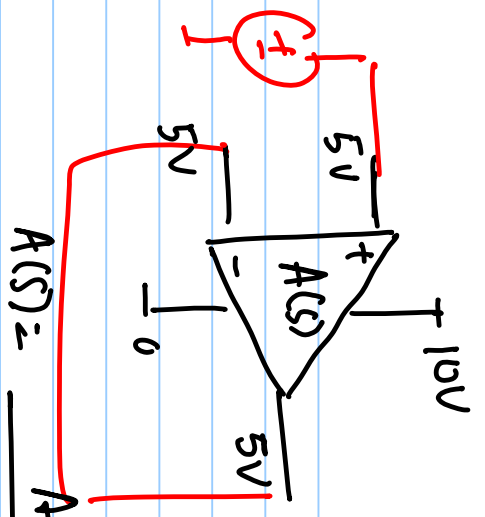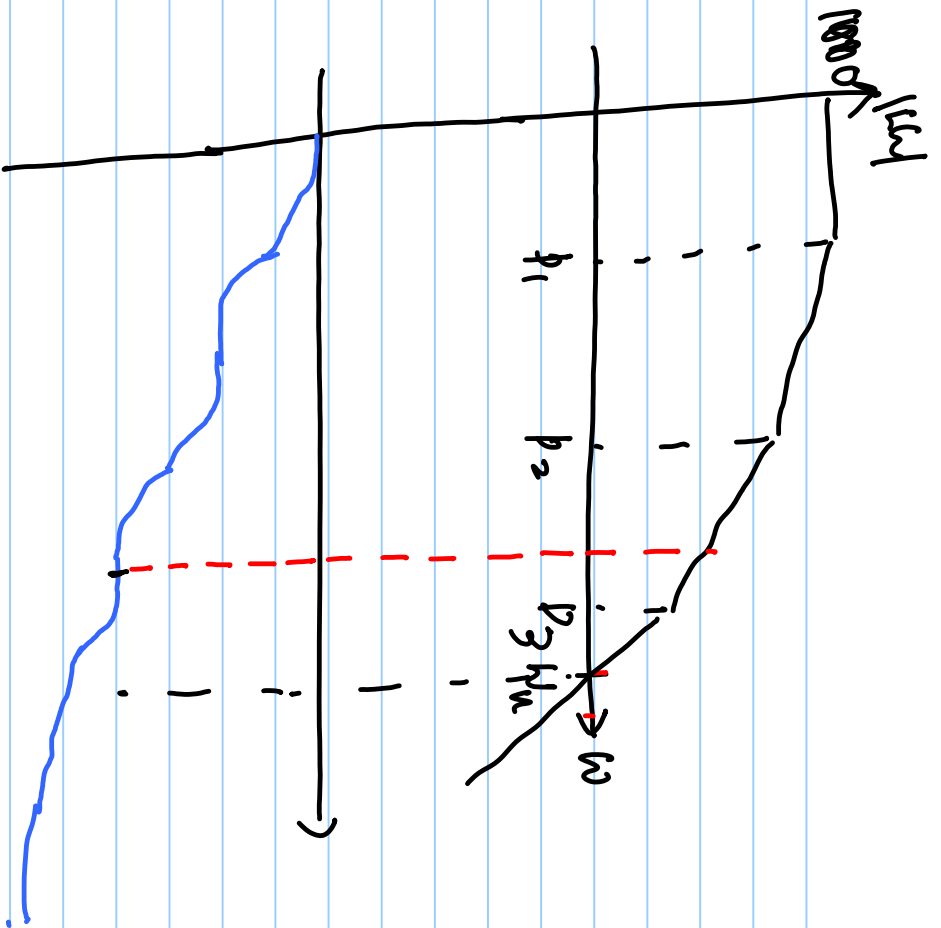
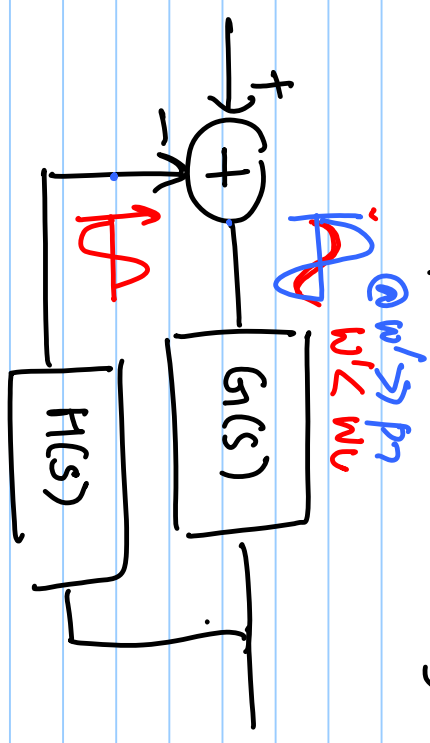
$$A(s) = \frac{A_0}{(1 + \frac{s}{p_1}) (1 + \frac{s}{p_2}) (1 + \frac{s}{p_3})}$$




$$1 + \frac{1}{x} + \frac{1}{x^2} + \frac{1}{x^3} + \dots$$

- at $\epsilon = 0$: 1
- $t = t_1$: $1/x$
- $t = t_2$: $1/x^2$

at $t=0$: 1

$t=t_1$: $(1 + \frac{1}{x})$


$t=t_2$: $(1 + \frac{1}{x}) \frac{1}{x}$

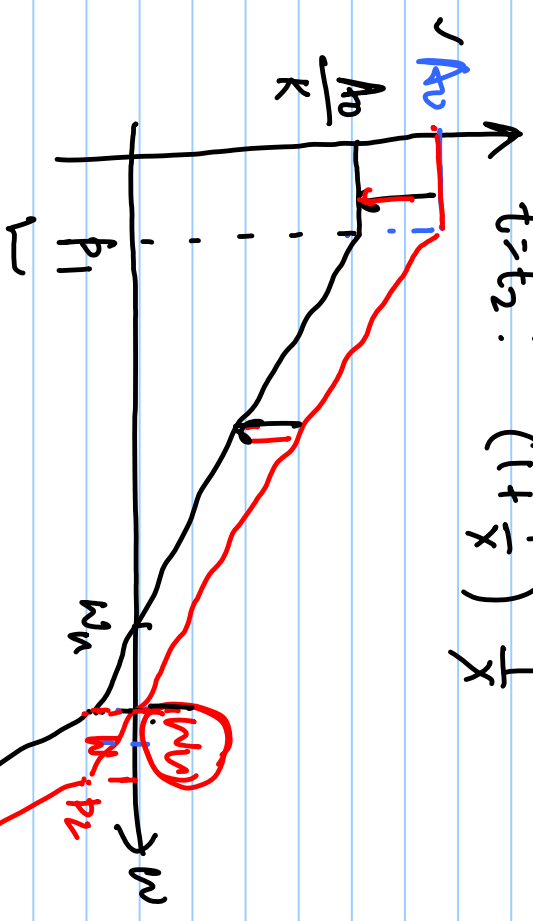


'thickly gain compensated amplifier'


$w_u = \frac{A_0 p_1}{k}$

$w_u = A_0 p_1$


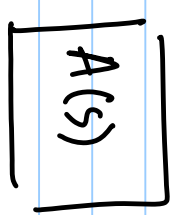


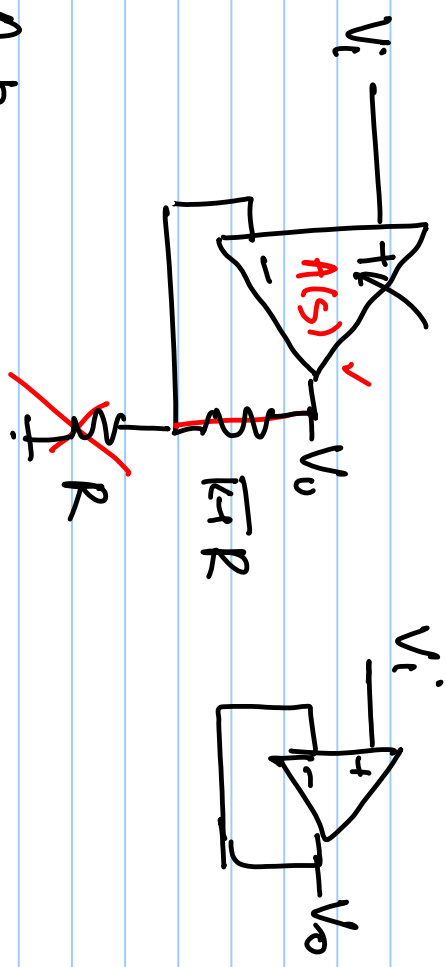$A(s) = \frac{A_0}{(1 + \frac{s}{p_1}) (1 + \frac{s}{p_2})}$




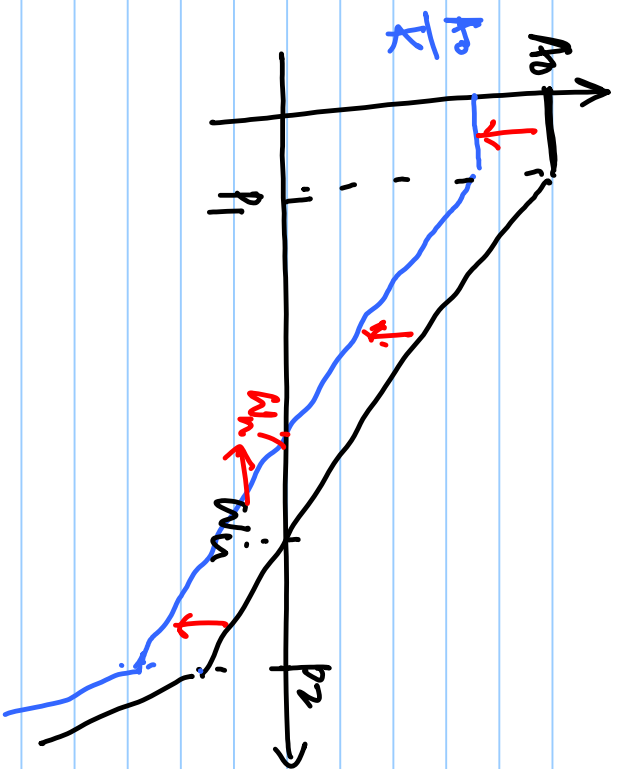

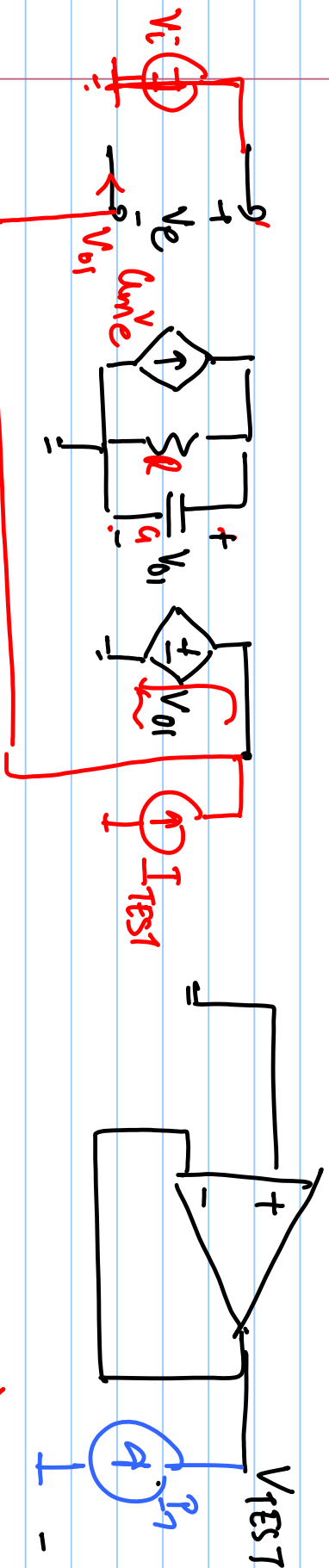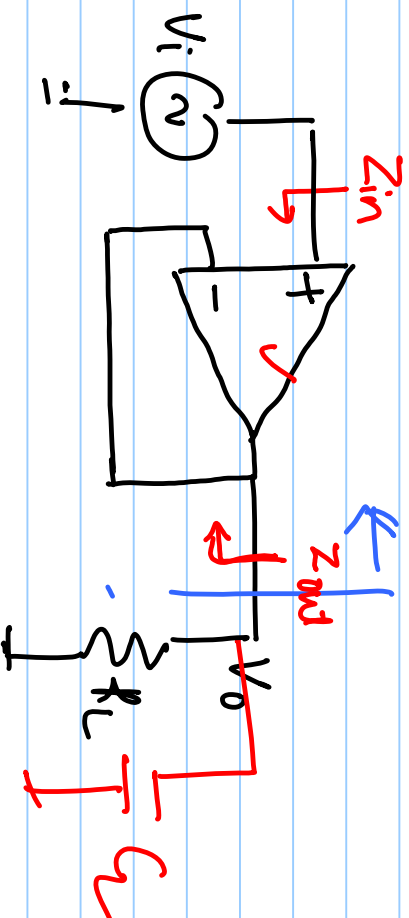
$$M_h = \frac{A_0 / K}{(1 + s/p_1)(1 + s/p_2)}$$


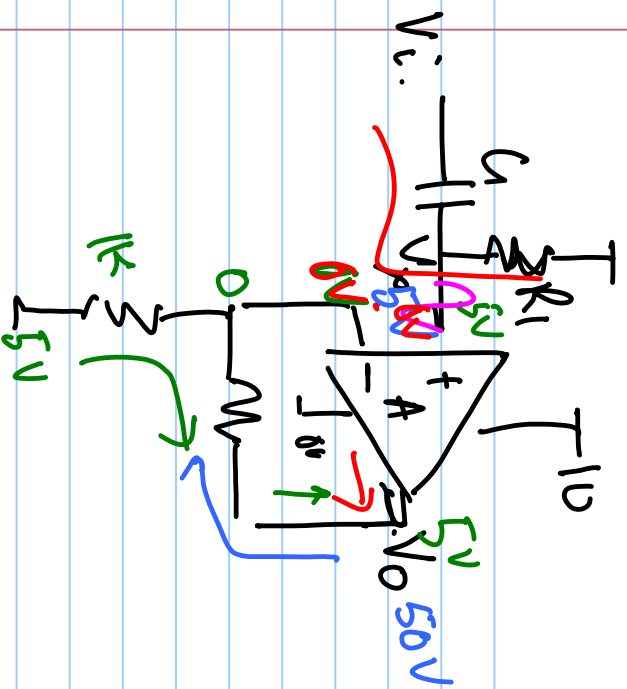
$$g_m v_e \left(R \parallel \frac{1}{sC_1} \right) = V_{o1} \Rightarrow V_{o1} \left(1 + g_m \left(R \parallel \frac{1}{sC_1} \right) \right) = 0$$


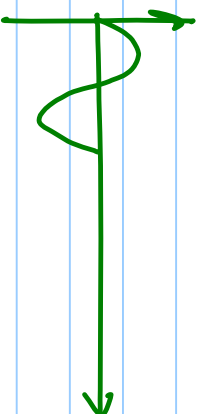
$$\frac{V_o}{V_i} = \frac{V_o}{V_n} \cdot \underbrace{\frac{V_n}{V_i}}_{\approx 1}$$



$$V_o = \frac{R_1 V_i}{R_1 + \frac{1}{sC_1}} = \frac{sC_1 R_1}{1 + sC_1 R_1} V_i$$

$$C_1 \gg 10 \text{ nF}$$