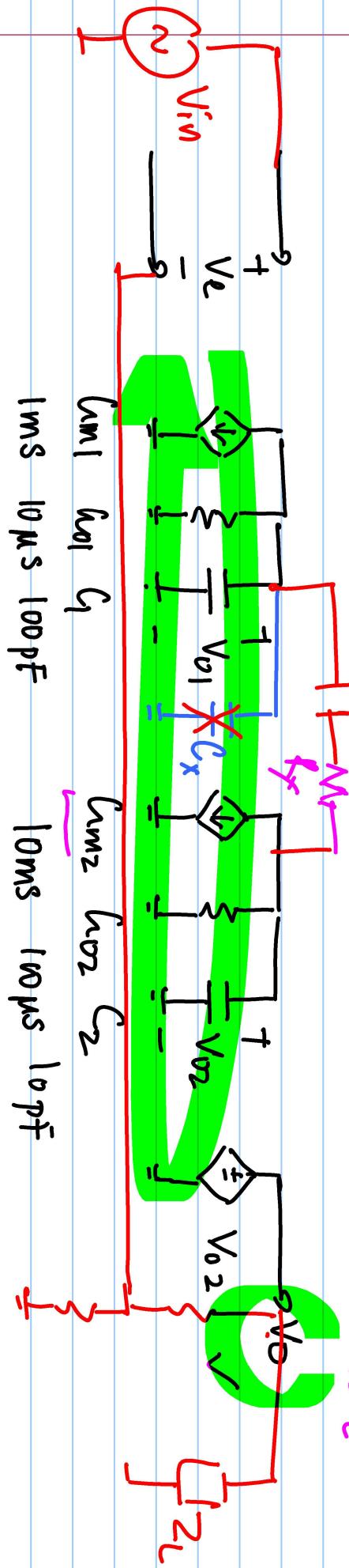


## Lecture # 25

Two-stage Amp.

$$\frac{R_x + j\omega C_x}{sC_c} = \frac{1 + sC_e R_x}{sC_e}$$



- Dominant pole compensation ( $\omega_{u1}$ )  $C_x = 9.9 \text{nF}$

- Miller compensation ( $\omega_{u2} > \omega_{u1}$ )  $C_e = 51.3 \text{ pF}$

$$- Z_1 = \frac{C_{u2}}{C_c} = 2 \times 10^8 \text{ rad/s.}$$


$$K_0 = \frac{A_0 \left(1 - \frac{s}{\omega_1}\right)}{\left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right)}$$

$$\chi_{L0} = -\tan^{-1}\left(\frac{\omega}{\omega_1}\right) - \tan^{-1}\left(\frac{\omega}{p_1}\right) - \tan^{-1}\left(\frac{\omega}{p_2}\right)$$

- ✓  $\omega_1 \gg \omega \Rightarrow \underline{\phi_m}$  roughly same -

- Any other problem?
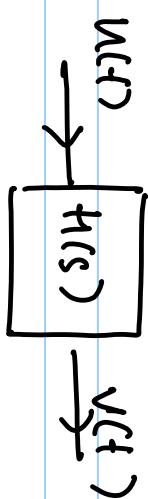
$$H(s) = \frac{(1 + s/\zeta_1)}{(1 + s/p_1)}$$



$$V(s) = H(s) U(s) \quad \left\{ \begin{array}{l} V(s) = \frac{1}{s} \frac{(1 + s/\zeta_1)}{(1 + s/p_1)} = \frac{p_1}{\zeta_1} \left[ \frac{1}{s} - \frac{(s + \zeta_1)}{s + p_1} \right] \end{array} \right.$$

$$V(t) = \mathcal{L}^{-1}(V(s)) \quad \left\{ \begin{array}{l} = \frac{p_1}{\zeta_1} \left[ \frac{\zeta_1/p_1}{s} + \frac{(\zeta_1 - p_1)/-p_1}{s + p_1} \right] \end{array} \right.$$




$$\frac{1}{V(s)} = \frac{1}{s} - \frac{\frac{1}{\lambda_1}}{\lambda_1 + p_1}$$

$$= \frac{1}{s} - \frac{\left(1 - \frac{p_1}{\lambda_1}\right)}{\lambda_1 + p_1}$$

$$v(t) = \left[ 1 - \left(1 - \frac{p_1}{\lambda_1}\right) e^{-p_1 t} \right] u(t)$$


$$\text{at } t=0, \quad 1 - \left(1 - \frac{p_1}{\lambda_1}\right) = \frac{p_1}{\lambda_1}$$

$v(t)$

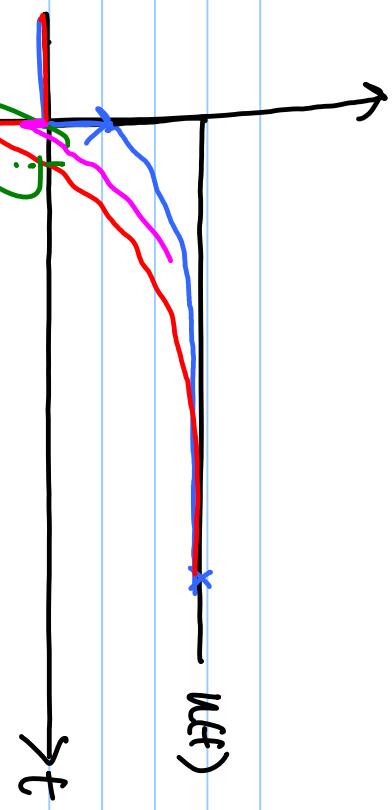

$$R_x = \frac{1}{C_{m2}}$$
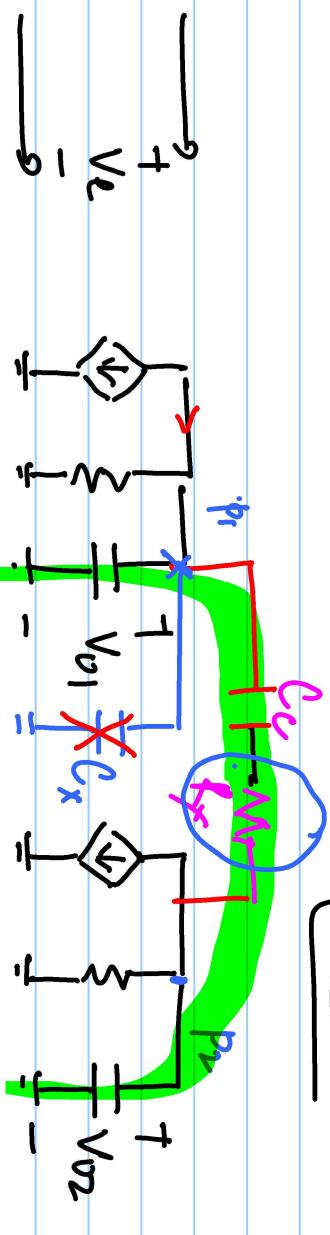
$$\beta_1 \approx \frac{\omega_1}{C_1 + C_c \left( 1 + \frac{C_{m2}}{\omega_2} \right)}$$



$$\beta_2 \approx \frac{C_{m2} + \lim \frac{C_c}{C_c + C_1}}{C_2 + \frac{C_1 C_c}{C_1 + C_2}}$$

$$\begin{bmatrix} -C_{m1}V_e \\ 0 \end{bmatrix} = \begin{bmatrix} C_{o1} + \omega_1 C_1 + \frac{\omega_1 C_c}{1 + \omega_1 C_c R_x} \\ C_{o2} - \frac{\omega_1 C_c}{1 + \omega_1 C_c R_x} \end{bmatrix} - \frac{\omega_1 C_c}{1 + \omega_1 C_c R_x} \begin{bmatrix} V_{o1} \\ V_{o2} \end{bmatrix}$$

$$I = \gamma V$$

$$\frac{1}{R_x C} = \frac{1}{R_x C_2}$$

$$\frac{V_{o2}}{V_e} = \frac{C_{m1} C_{m2} R_x C_2}{C_{m1} C_{m2} + C_{m1} C_2 + C_{m2} C_2 + \underbrace{C_{m1} C_{m2} C_c}_{\text{10ms 100μs loopf}}}$$

$$= \frac{C_{\text{mz}} - sC_c (1 - C_{\text{mz}} R_x)}{D(s)} = 0$$

$$= \frac{1}{C_c \left( \frac{1}{C_{\text{mz}}} - R_x \right)}$$

$D(s)$

$$Z_1 = \frac{C_{\text{mz}}}{C_c (1 - C_{\text{mz}} R_p)}$$

$$R_p = 0, \quad Z_1 = \frac{C_{\text{mz}}}{C}$$


$$R_p = \frac{1}{C_{\text{mz}}} \Rightarrow \text{eliminate}$$

zero

$$R_x > \frac{1}{C_{\text{mz}}}$$

$\Rightarrow$  L.H.P zero

$$Z_1 = - \frac{1}{R_x C_c}$$

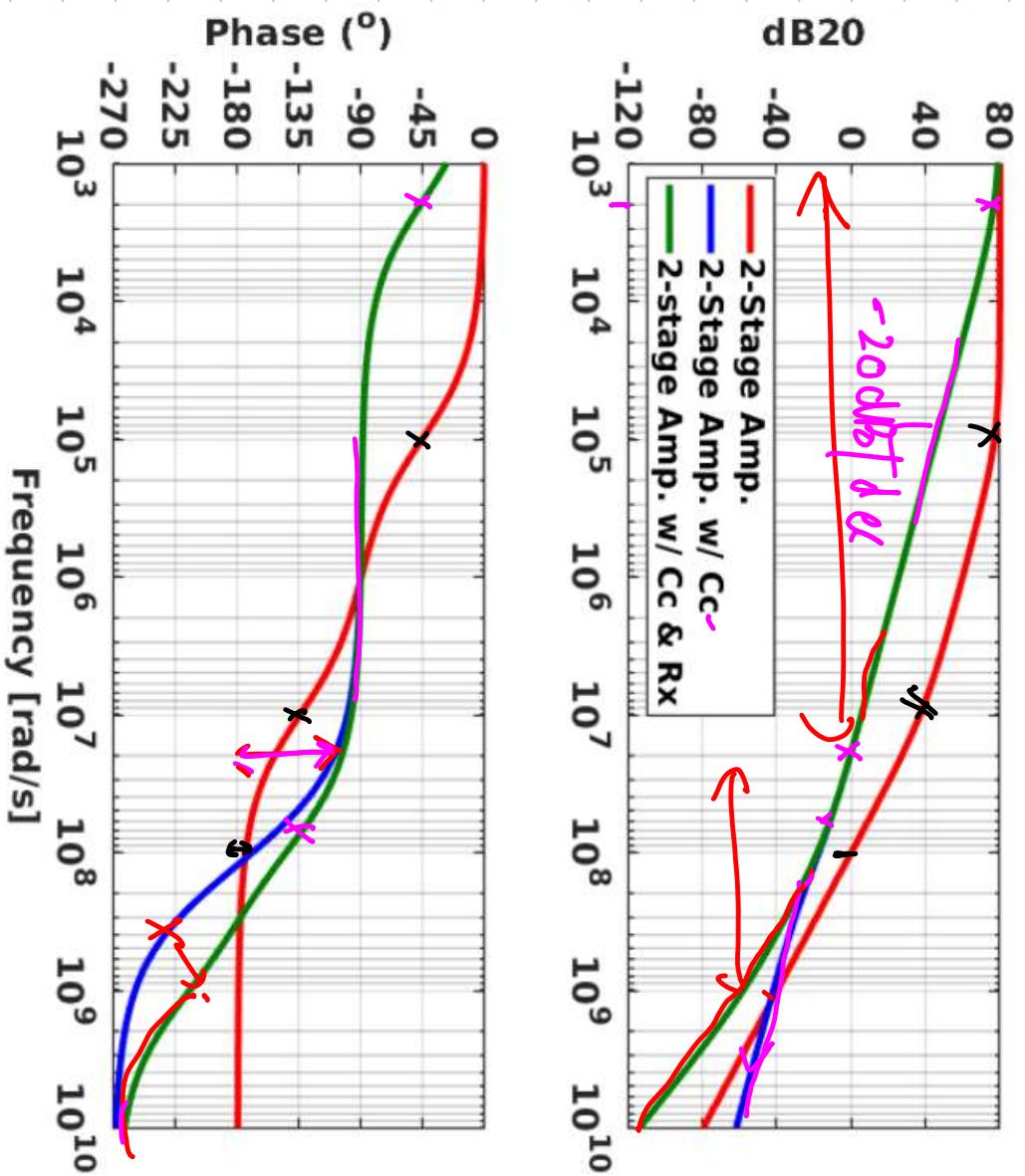

$$K(s) = \frac{A_0}{(1 + \frac{s}{\rho_1})(1 + \frac{s}{\rho_2})(1 + \frac{s}{\rho_3})}$$

$20 \log_{10} |K|$

$t_f$   
 $f_{req,s}$   
 tfdata