

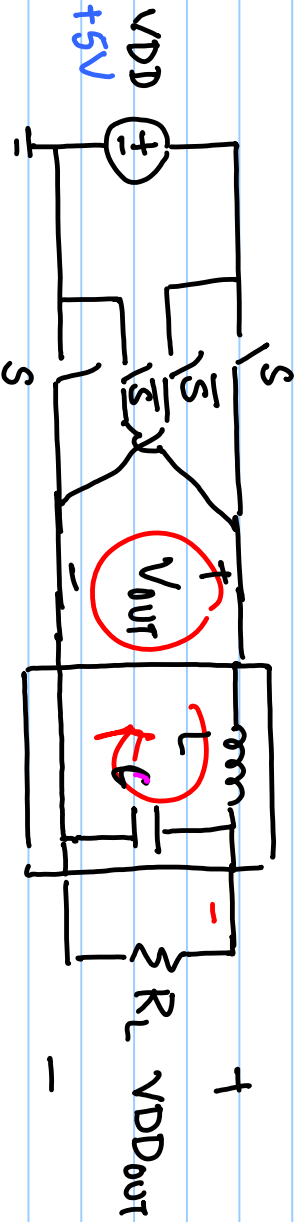


Lecture # 29

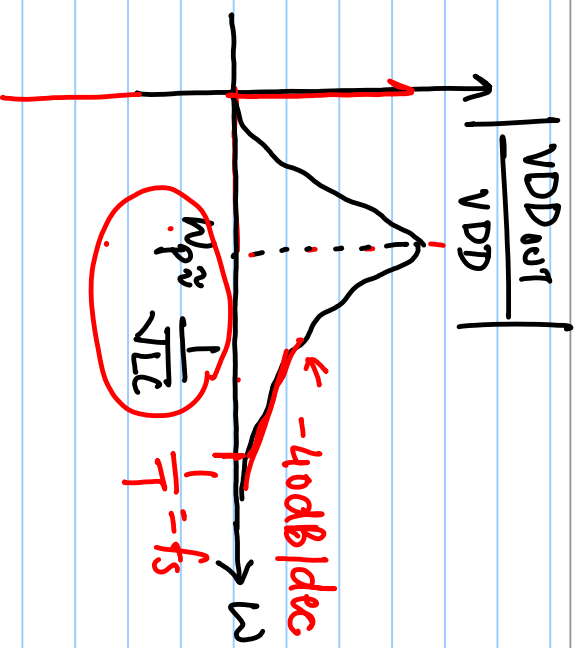

$$V_{DD_{out}} = V_{DD} (2 \cdot D - 1)$$


D = Duty Cycle

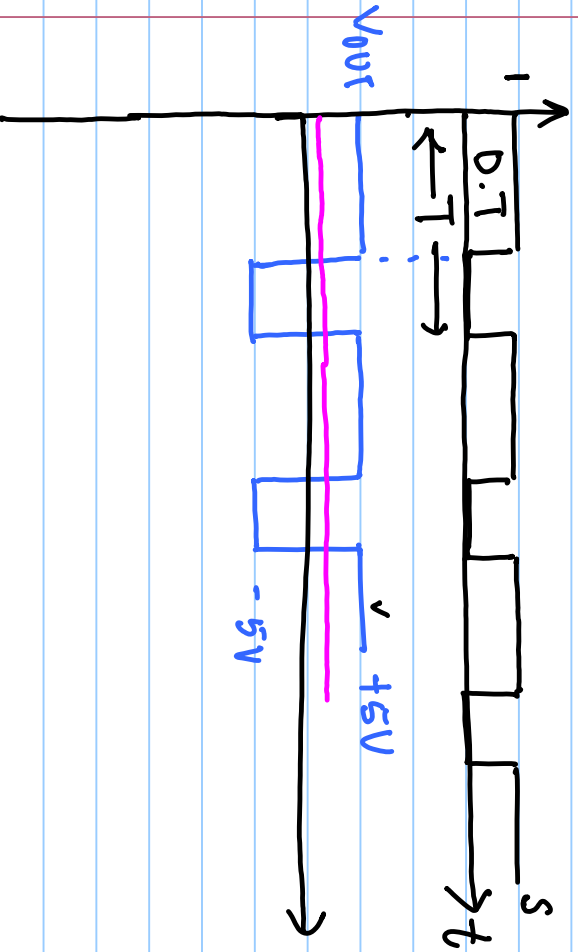

* $-V_{DD} < V_{DD_{out}} \leq +V_{DD}$

* 1.0, 1.8, 2.5, 3.0V.

*

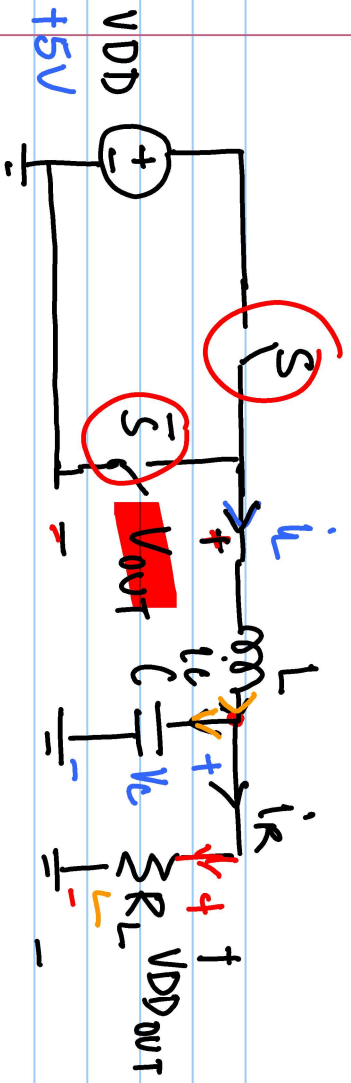


$$V_{OUT} = \frac{V_{DD} \cdot \alpha T - (T - \alpha T) \cdot 0}{T}$$


$$= \alpha \cdot V_{DD}$$

$$V_{OUT} = \alpha V_{DD} + \sum_{n=1}^{\infty} a_n \cos(n\omega_0 t) + b_n \sin(n\omega_0 t)$$

$$\omega_0 = \frac{2\pi}{T}$$

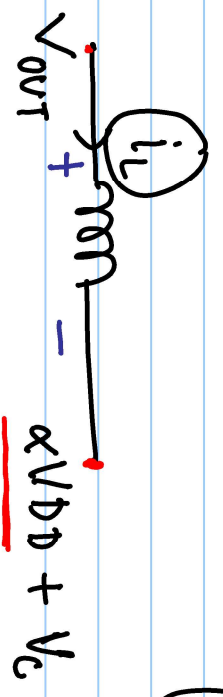

$$V_L = L \frac{di}{dt}$$

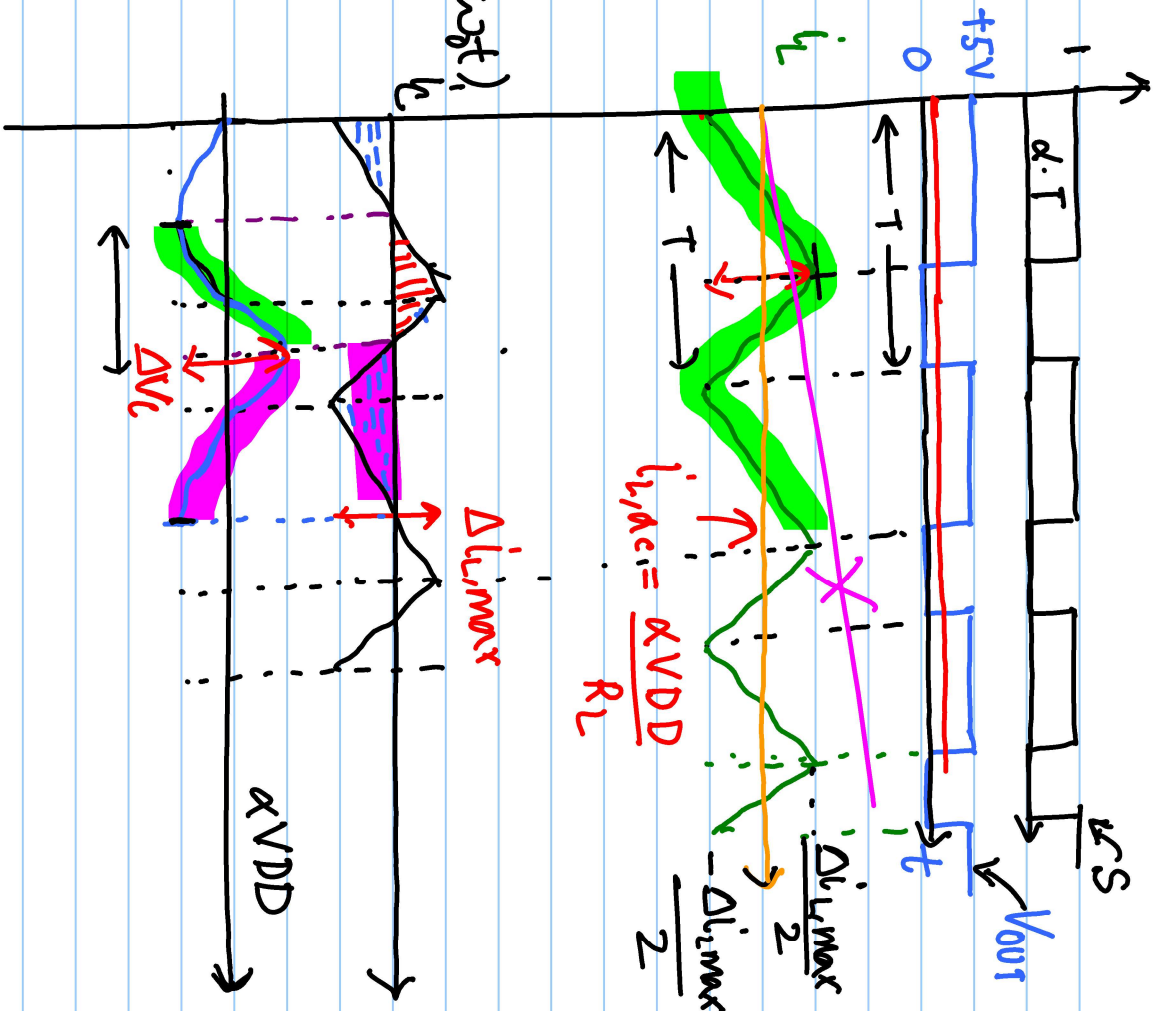


$$\underline{S=1}, \quad V_{DD} - \alpha V_{DD} = L \frac{di_i}{dt} \Rightarrow i_L = \int \frac{1}{L} V_{DD} (1-\alpha) dt$$

$$S=0, \quad 0 - \alpha V_{DD} = L \frac{di_i}{dt} \Rightarrow i_L = -\frac{1}{L} \int \alpha V_{DD} \cdot dt$$

$$\boxed{\Delta i_{L,max} = \frac{V_{DD} (1-\alpha)}{L} \cdot \alpha T}$$

$T \uparrow$: fast switching freq.

$L \uparrow$: large area.

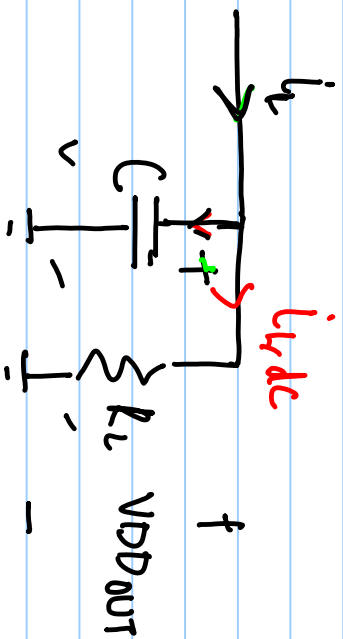

$$i_L = \frac{C d(V_{DD,out})}{dt} + \frac{V_{DD,out}}{R_L}$$

$$i_L = i_{L,dc} + \sum a_n \cos(n\omega_0 t) + b_n \sin(n\omega_0 t)$$



$$i_L = C \frac{dv_L}{dt} \Rightarrow \Delta v_L = \frac{1}{C} \int_{t_1}^{t_2} i_L \cdot dt$$

$$\frac{1}{j\omega_0 C}$$

$$\Delta V_c = \frac{1}{C} \int i_c \cdot dt$$

$$= \frac{1}{C} \int \frac{1}{2} V_{DD} (1-\alpha) t \cdot dt$$

$$\Delta V_c = f(T^2)$$

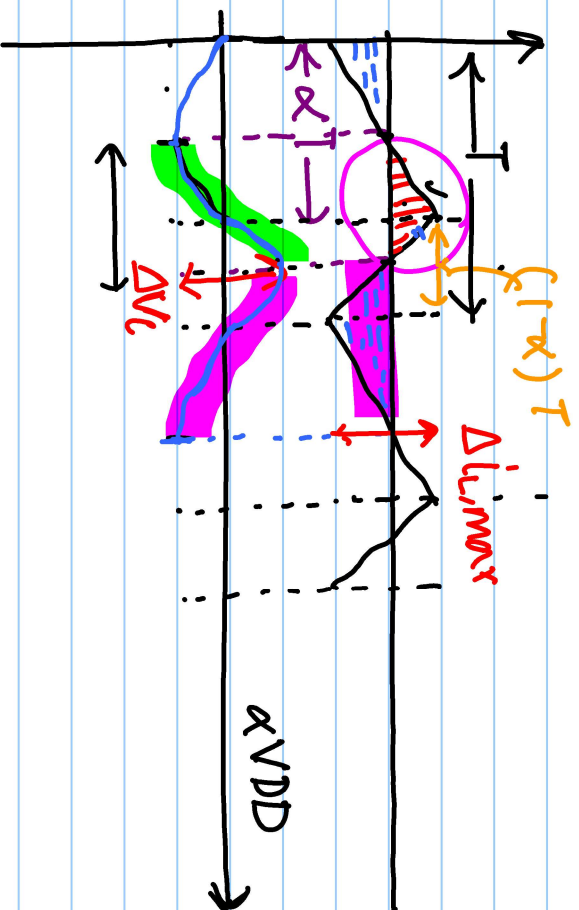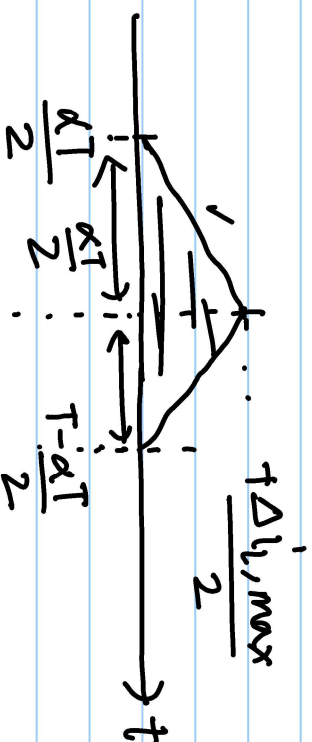

$$q = CV$$

$$\Delta V = \frac{\Delta q}{C}$$

$$= \frac{\int i_c \cdot dt}{C} = \frac{1}{C} \frac{\frac{1}{2} \left(\frac{\alpha T}{2} + \frac{(1-\alpha)T}{2} \right) \frac{\Delta i_c}{2}}{C}$$

$$\Delta V_c = \frac{V_{DD}}{82C} \cdot T^2 \alpha (1-\alpha)$$

Assume: Output voltage is fixed.

$$\Delta i_{L, \max} = \frac{V_{DD}}{L} \alpha(1-\alpha)T,$$

Assume: All ripple current goes through capacitor.

$$\Delta V_C, \max = \frac{V_{DD}}{8LC} T^2 \alpha(1-\alpha),$$

Reduce ripple voltage

- Increase switching freq. $f_s = \frac{1}{T}$
- Reduce $w_p = \frac{1}{\sqrt{LC}}$

$$\Delta V_C = \frac{V_{DD}}{8LC} \frac{1}{f_s^2} \alpha(1-\alpha)$$

$$\Delta V_C = \frac{V_{DD}}{8} \frac{w_p^2}{f_s^2} \alpha(1-\alpha) \quad \left| \quad w_p = \frac{1}{\sqrt{LC}} \right.$$


To reduce voltage ripple.

- $w_p \downarrow$

- $f_s \uparrow$

Maximum Ripple voltage } $\alpha = \frac{1}{2}$
Max. Ripple current }

"Switching Regulators"

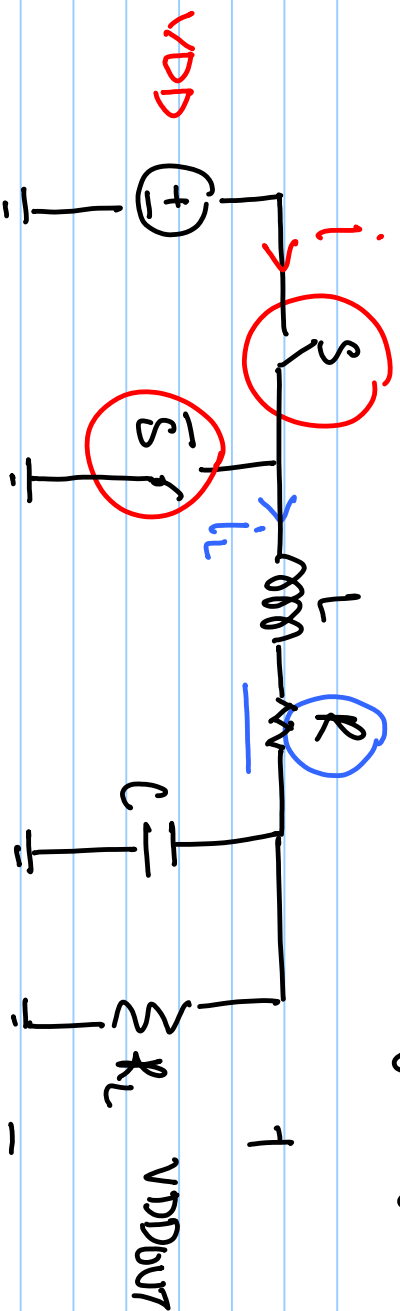

Power loss :

- Resistor associated with inductor
- Switch finite resistance loss
- Switching loss due to finite capacitance of real switches.

