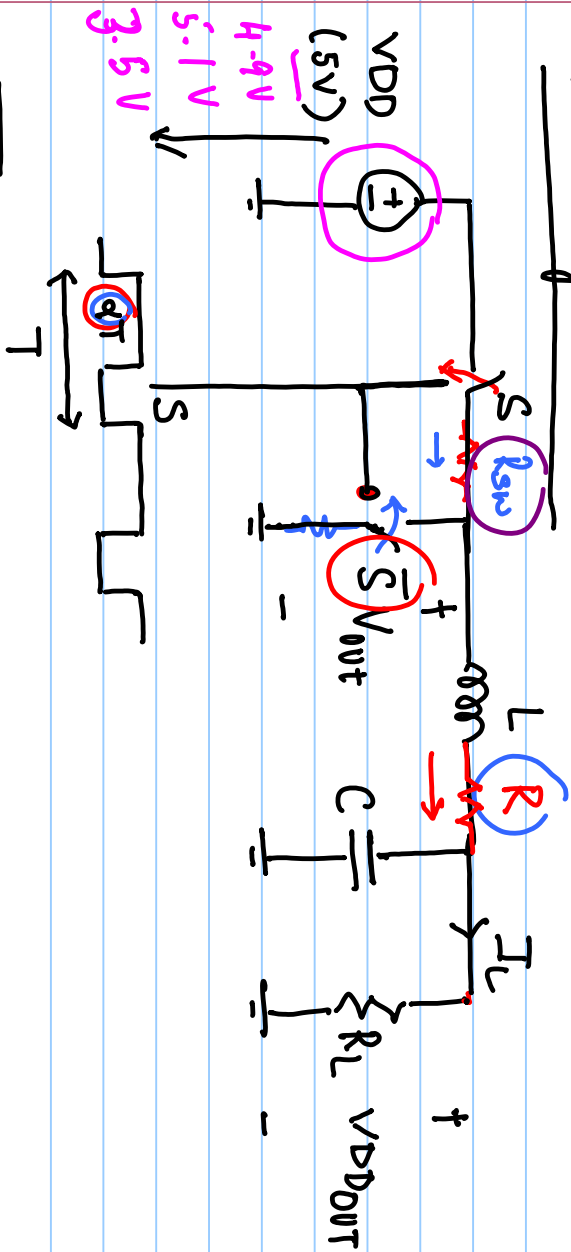


# Lecture # 3D

## Switching Converter



$$\overline{V_{out}} = \alpha V_{DD}$$

$$V_{DDout} = \alpha V_{DD} - I_L R$$

$$V_{DDout} = \alpha V_{DD}$$

$V_{DDout}$  (Desired)  $\alpha$

2.5  $\rightarrow$  0.5

1.2  $\frac{1.2}{5.0}$

0.7  $\frac{0.7}{5.0}$


1.8  $\frac{1.8}{5.0}$

$\alpha \ll 1$

$$V_{DDout} = \frac{2.5}{3.5}$$


$$0.5 \rightarrow \frac{2.5}{3.5}$$

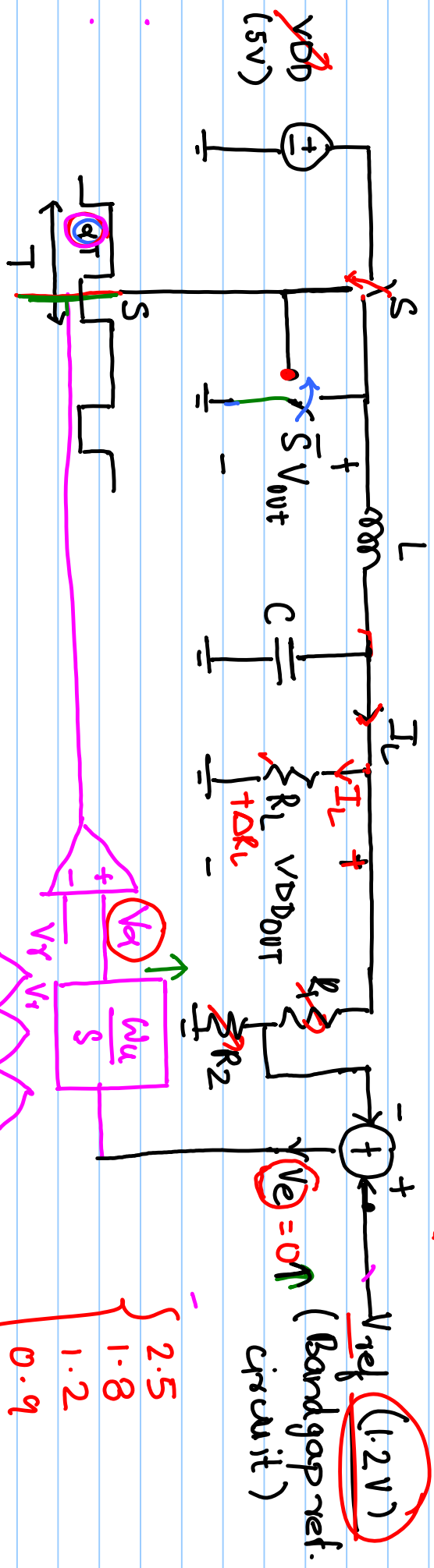RF, IC,  $I_L = 100 \mu A$ ,  $V_{DD\ out} = 1.8V$ ,  $\alpha = 1.8/5.0$   
 $I_L = 1 \mu A$ ,  $V_{DD\ out} = 1.8V$ ,  $\alpha = 1.8/5.0$



$$V_e = V_{ref} - V_{DD\ out}$$

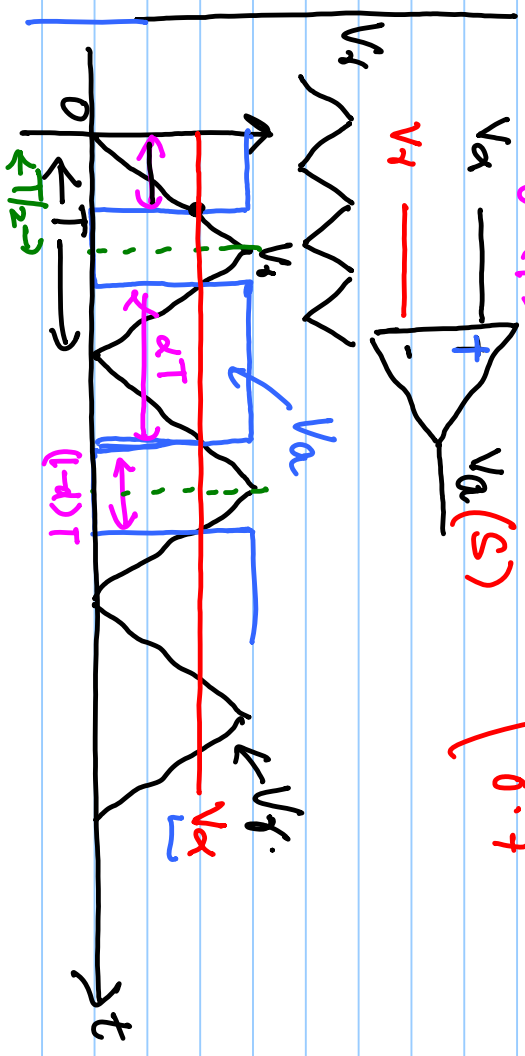$V_e > 0 \rightarrow V_{DD\ out} \rightarrow \alpha$   
 $(\alpha V_{DD})$



In steady state:

$$V_e = 0$$

$$\frac{R_2}{R_1 + R_2} V_{DD_{out}} = V_{ref.}$$

$$\alpha V_{DD} = V_{DD_{out}} = \frac{R_1 + R_2}{R_2} V_{ref.}$$

$$V_{DD_{out}} = \left(1 + \frac{R_1}{R_2}\right) V_{ref.}$$


Slope of  $V_r = \frac{V_r}{T/2}$

Duty cycle,  $\alpha$

$$\alpha T = \frac{V_{\alpha}}{V_r / (T/2)}$$

$$\frac{V_{\alpha}}{\alpha T/2} = \frac{V_r}{T/2} \Rightarrow \alpha = \frac{V_{\alpha}}{V_r}$$

- Switching converter in a closed loop

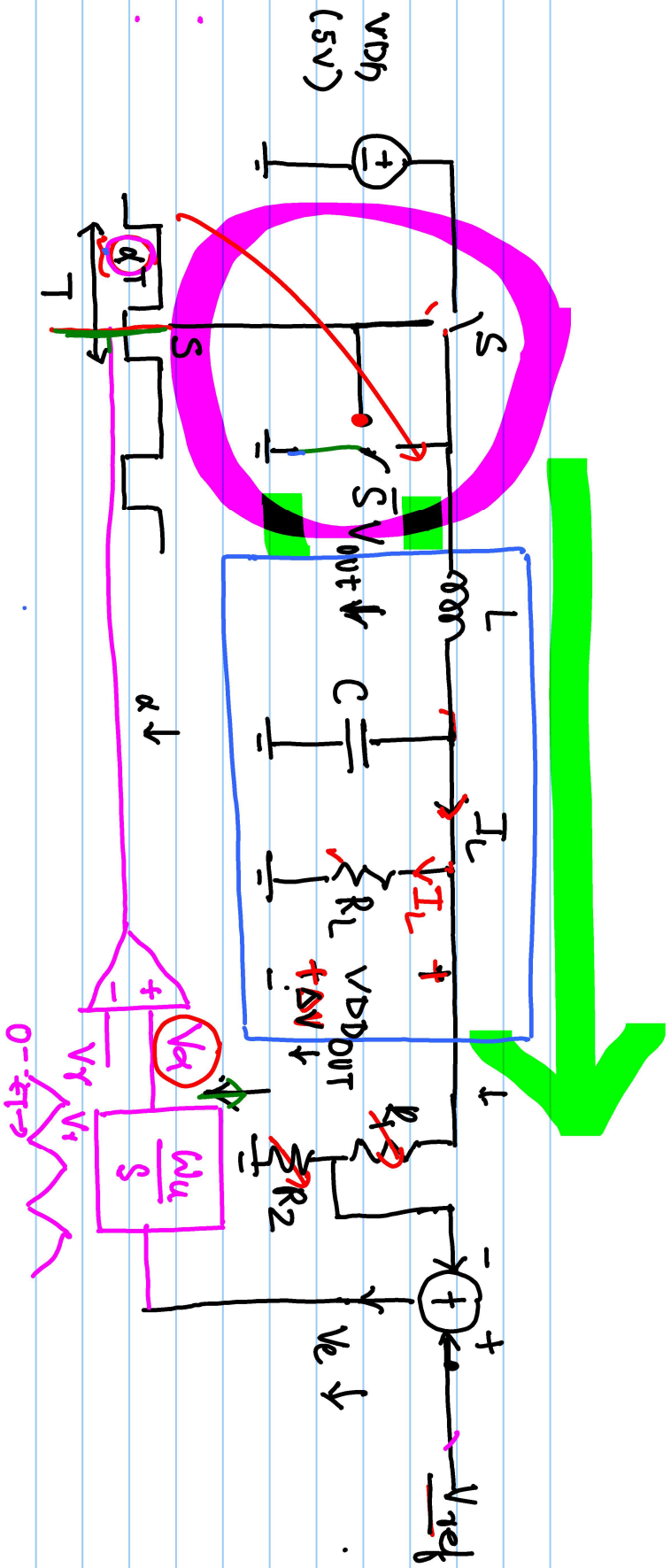

$$\frac{V_{DDOUT}}{V_{OUT}} = \frac{(R_L || \frac{1}{sC})}{sL + (R_L || \frac{1}{sC})} = \frac{R_L}{1 + sR_L C} = \frac{R_L}{sL + \frac{R_L}{1 + sR_L C}} = \frac{R_L}{sL + s^2 R_L C + R_L} = \frac{R_L}{R + sL + s^2 R_L C}$$

$$F(s) = \frac{V_{DDOUT}}{V_{OUT}} = \frac{1}{1 + s\frac{L}{R} + s^2 LC} = \frac{1}{1 + \frac{s}{\omega_{nOP}} + \frac{s^2}{\omega_n^2}}$$


$$V_e = V_{ref} - V_{DDOUT}$$

$$\frac{V_\alpha}{V_e} = \frac{M_n}{\lambda}$$

$$\alpha \approx \frac{V_\alpha}{V_T}$$

$$L_{eff} = \frac{M_n}{\lambda} \frac{V_\alpha}{V_T} \left( \downarrow \right) \times f(s)$$
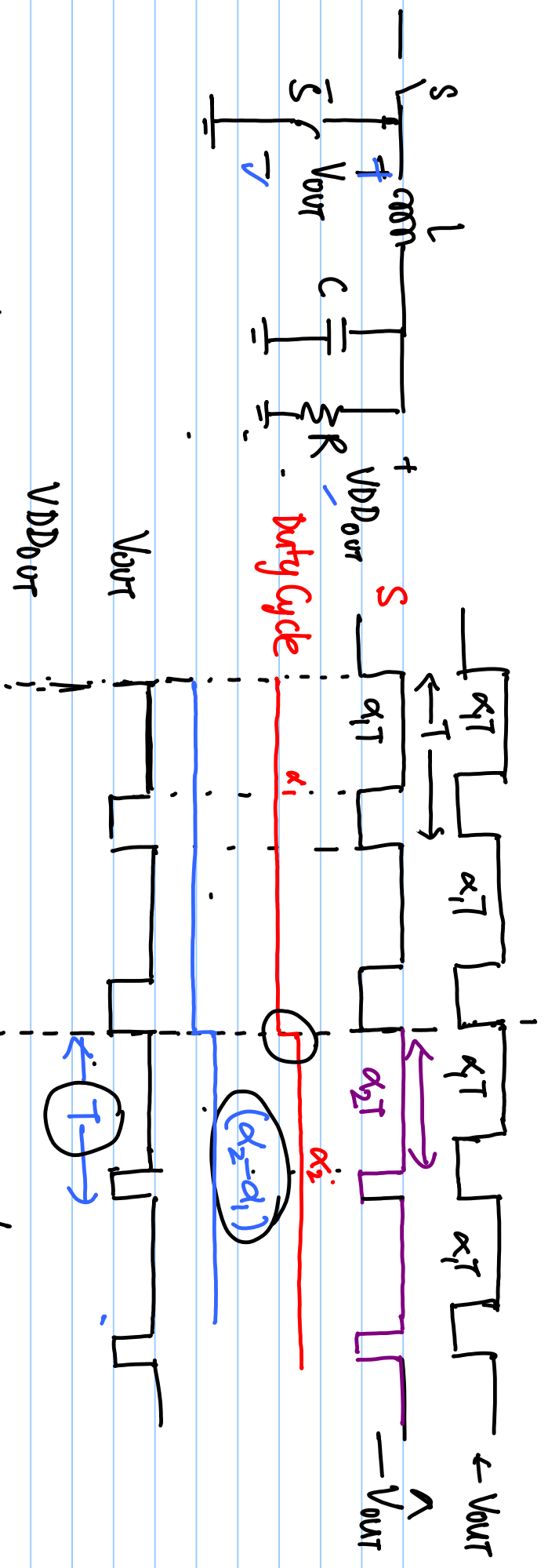
$$\underline{V_{OUT}} = \alpha V_{DD} + \sum_{n=1}^{\infty} a_n \cos(n\omega t) + b \sin(n\omega t)$$



$$F(s) = \frac{1}{1 + \frac{s}{\omega_{n0}} + \frac{s^2}{\omega_n^2}} = \frac{1}{1 + \frac{sL}{R} + s^2LC} = \frac{1}{s^2 + \frac{s}{RC} + \frac{1}{LC}}$$



$$= \frac{1}{\left(s + \frac{1}{2RC}\right)^2 + \frac{1}{LC} - \frac{1}{4R^2C^2}} = \frac{\omega_n^2}{\left(s + \frac{1}{2RC}\right)^2 + \frac{1}{LC} \left(1 - \frac{L}{4R^2C}\right)}$$

$$= \frac{\omega_n^2}{(s + \sigma)^2 + \omega_n^2 \left(1 - \frac{1}{4RQ^2}\right)} = \frac{\omega_n^2}{\omega_p^2} \cdot \frac{1}{(s + \sigma)^2 + \omega_p^2}$$

$$\frac{\omega_p}{s^2 + \omega_p^2} \xrightarrow{f(t)} \sin(\omega_p t) \quad u(t)$$

$$\frac{\omega_p}{(s + \sigma)^2 + \omega_p^2} \xrightarrow{f(t)} e^{-\sigma t} \sin(\omega_p t)$$
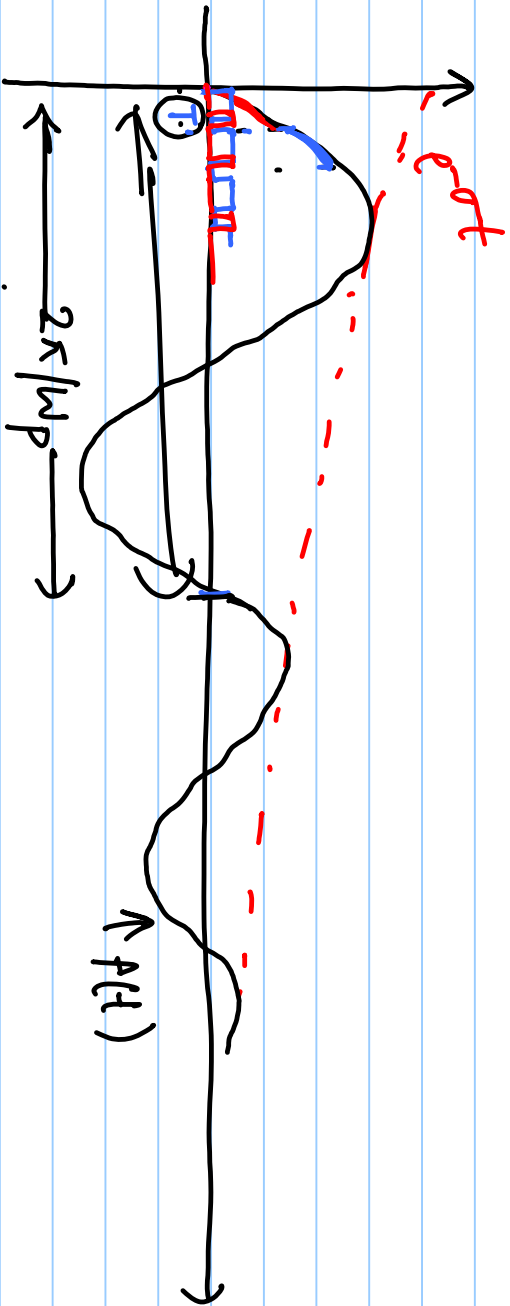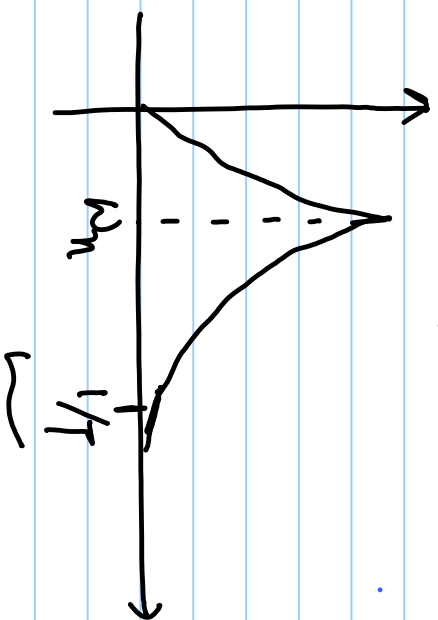
$$\omega_p = \omega_n \sqrt{1 - \left(\frac{1}{2\zeta\omega_n}\right)^2}$$




$$\Delta v_{DDOUT}(t) = f(t) * (V_{DD1} - \hat{V}_{DD1})$$

$$= \int_0^T (V_{DD1} - \hat{V}_{DD1}(\tau)) f(t-\tau) d\tau$$

$$= \int_0^T (V_{DD1} - \hat{V}_{DD1}(\tau)) f(t-\tau) d\tau$$

$$+ \int_T^{2T} (V_{DD1} - \hat{V}_{DD1}(\tau)) f(t-\tau) d\tau$$
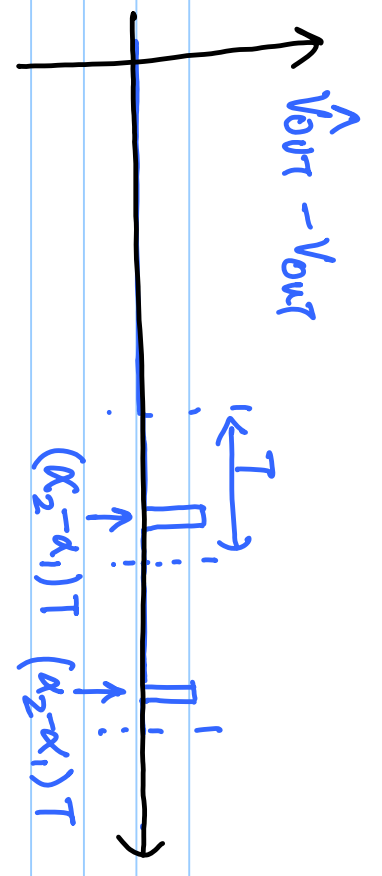
$$+ \int_{2T}^{3T} (V_{DD1} - \hat{V}_{DD1}(\tau)) f(t-\tau) d\tau$$



— During a period  $mT \rightarrow mT + T$   
 $f(t)$  remains constant



