
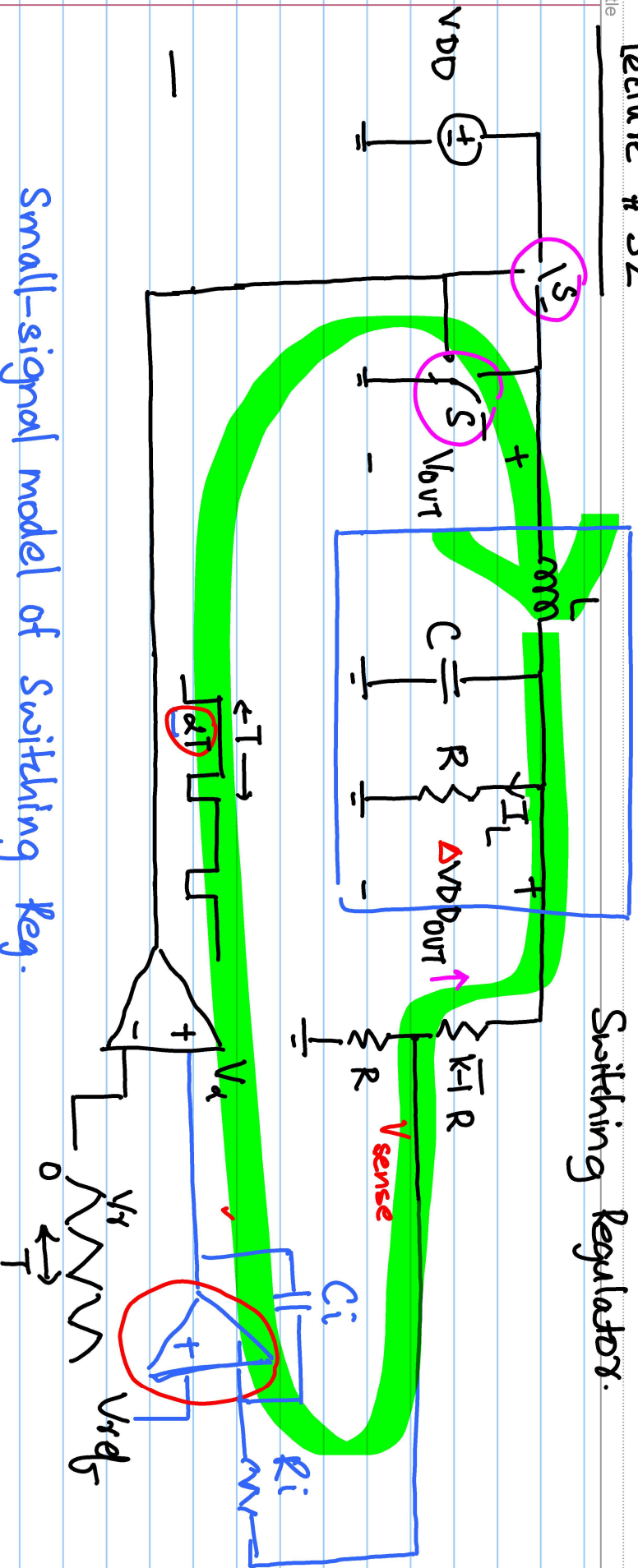


Lecture # 32

Switching Regulator.

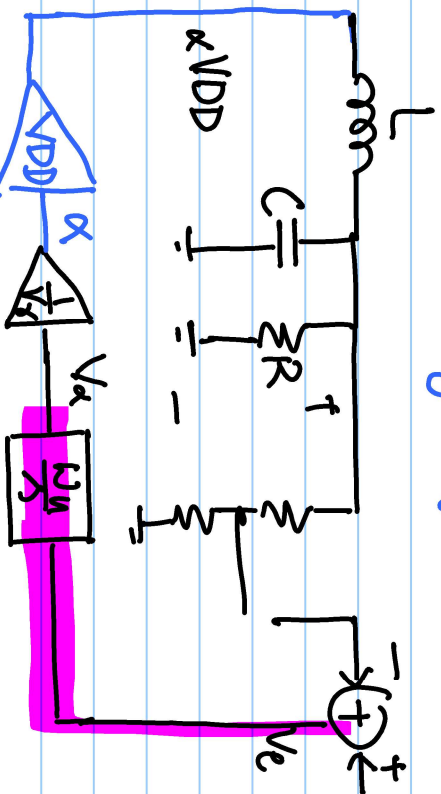


Small-signal model of switching Reg.



$$LG = \frac{1}{k} \frac{W_n}{s} \cdot \frac{1}{V_d} \cdot V_{DD} \cdot \frac{1}{1 + sL/R + s^2LC}$$

Q
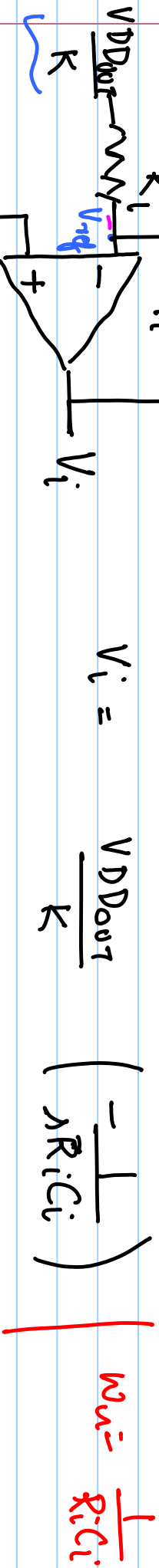
$$\text{Integrator Output} = \frac{W_n}{s} \left(V_{req} - \frac{V_{DDout}}{k} \right) = V_{req} \cdot \frac{W_n}{s} - \frac{V_{DDout}}{k} \cdot \frac{W_n}{s}$$




$$V_i = \frac{V_{DDout}}{k} \left(-\frac{1}{sR_i C_i} \right) \quad \left| \quad W_n = \frac{1}{R_i C_i} \right.$$



$$\frac{V_{req}}{R_i} = \frac{V_i - V_{req}}{1/sC_i}$$

$$V_{req} \left(\frac{1}{R_i} + sC_i \right) = V_i sC_i$$

$$V_i = \frac{V_{req}}{sR_i C_i} + V_{req}$$
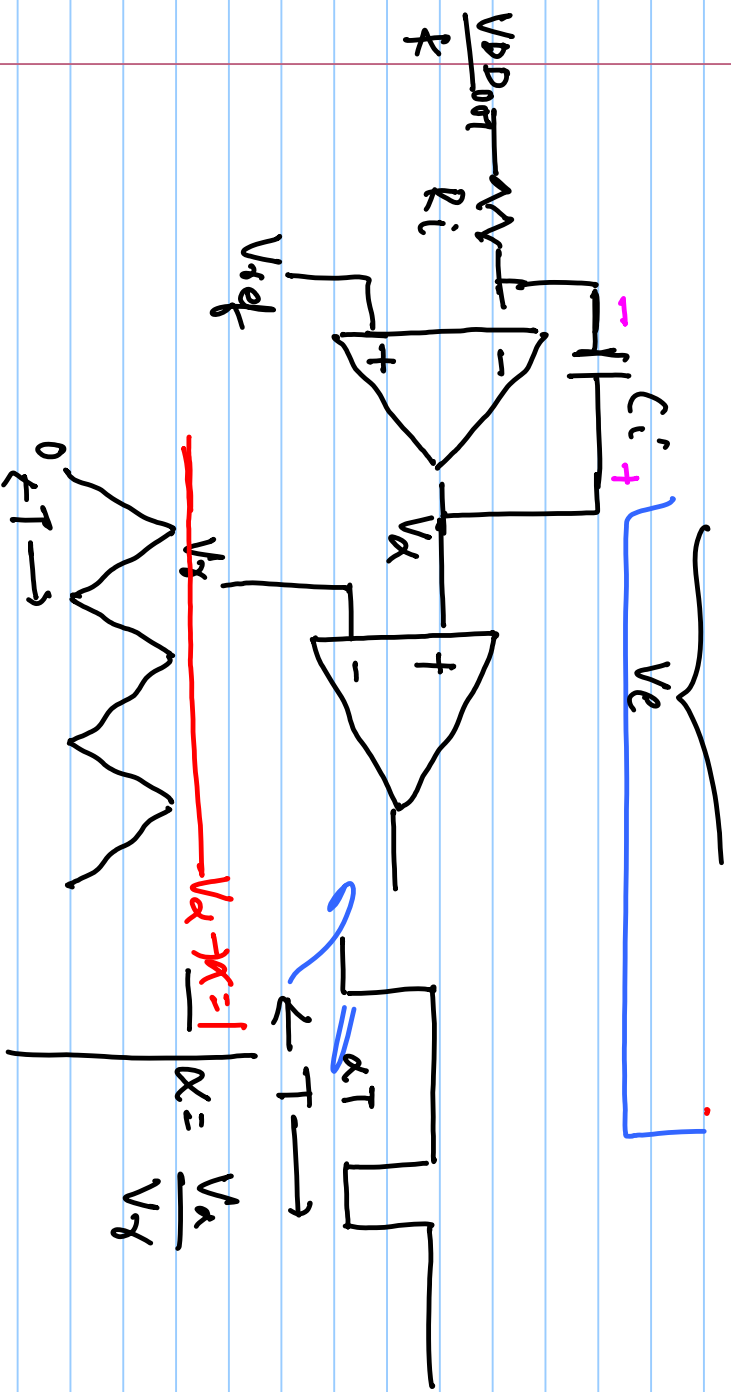
$$V_x = V_i = \left(V_{ref} - \frac{V_{DD007}}{k} \right) \frac{1}{k R_i C_i} + \textcircled{V_{ref}}$$



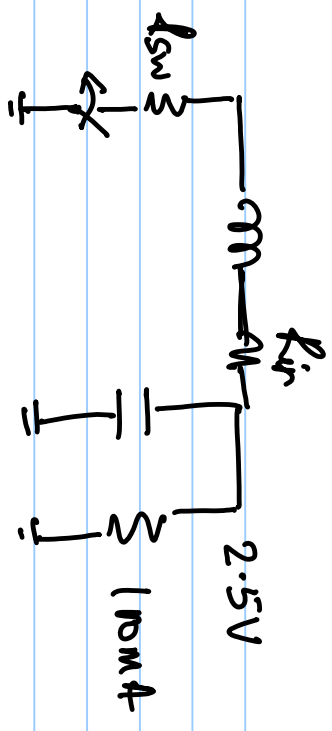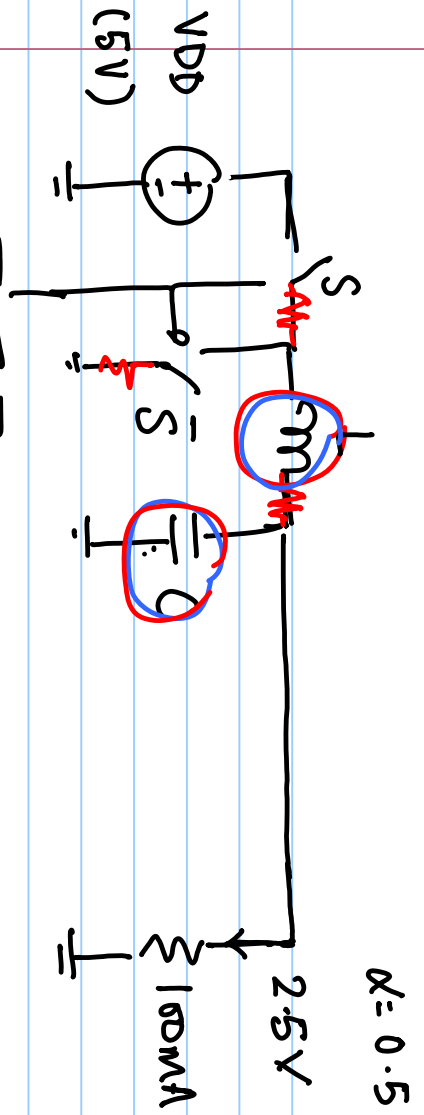


$$P_L = 2.5 \times 0.1$$

$$\text{Power dissipated} = I_L^2 (R_{sw} + R_{in})$$

$$R_{sw} = 0.25 \Omega$$

$$R_{in} = 0.1 \Omega$$

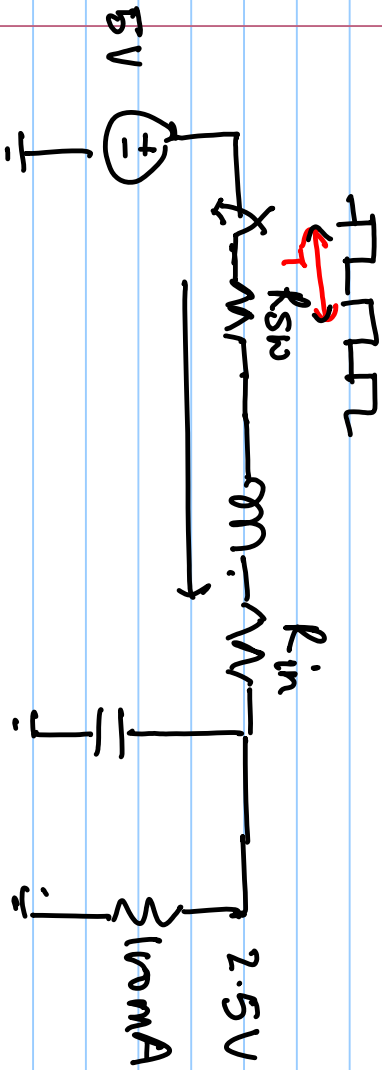



$$\text{Power delivered to load, } P_L = 2.5 \times 0.1 = 0.25 \text{ W}$$


$$\text{Power dissipated in switches, } P_{sw} = I_L^2 (R_{sw} + R_{in})$$

$$\eta = \frac{\text{Power delivered to load}}{\text{Power drawn from supply}}$$

$$= \frac{P_L}{P_L + P_{sw} + P_{clk}} = \frac{0.25}{0.25 + 0.01 (0.25 + 0.1)} = \frac{0.25}{0.25 + 0.0035} \approx 90\%$$

Clocking power:

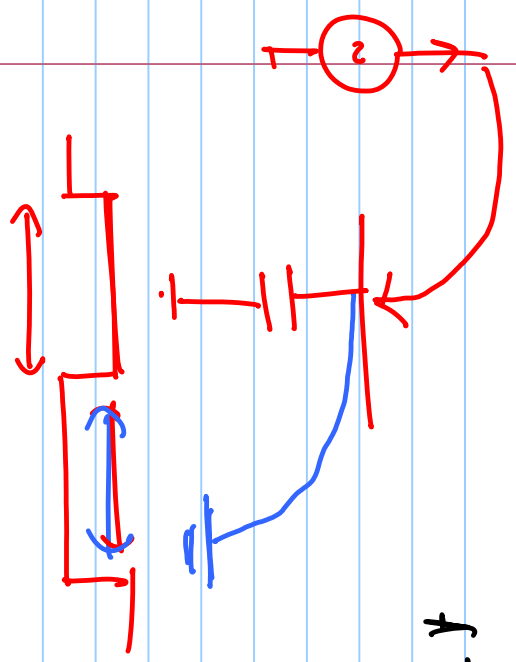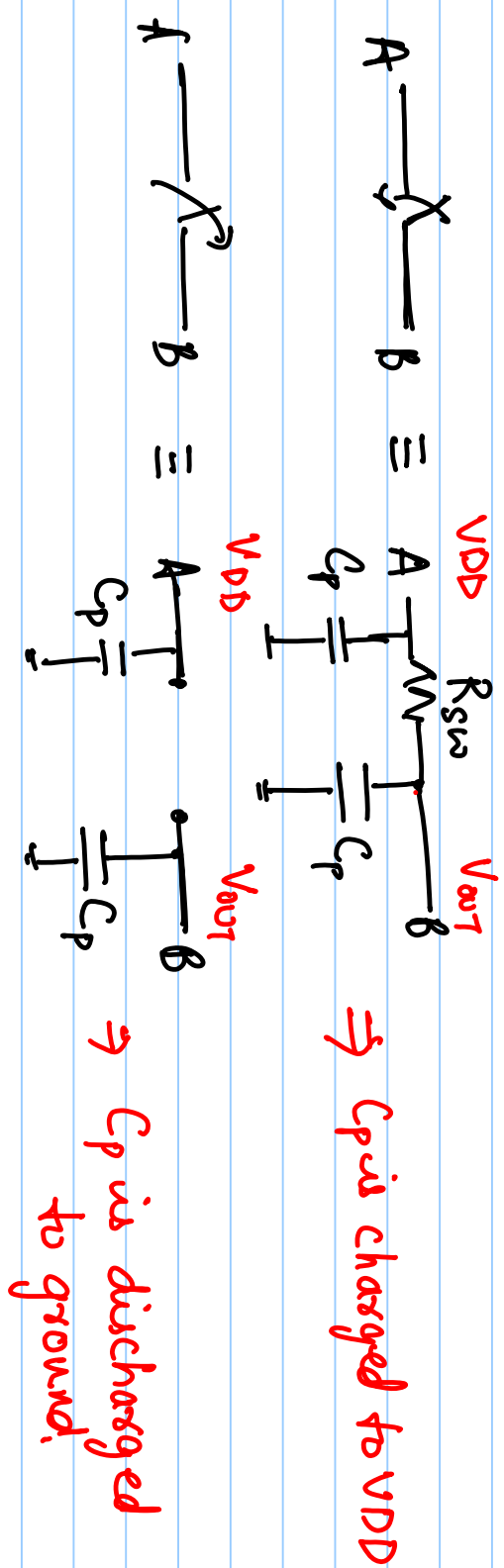

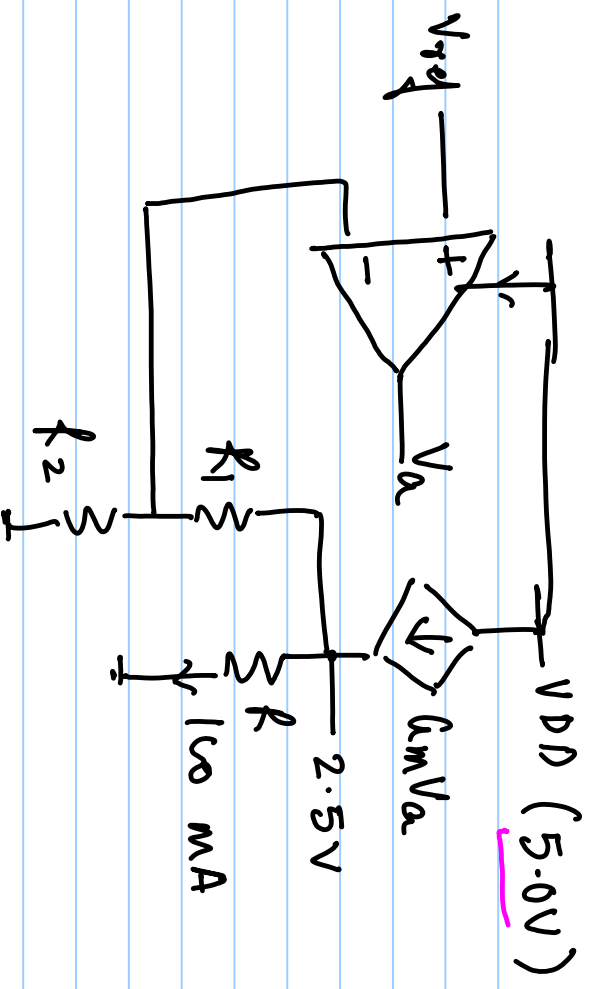


$$P_L = 2.5 \times 0.1 \text{ A} = 0.25 \text{ W}$$


$$P_S = 5.0 \text{ V} \times 0.1 \text{ A} + P_a$$

$$\eta = \frac{0.25}{0.5 + P_a} \times 100\% < 50\%$$

Does it mean LDO is not useful at all?

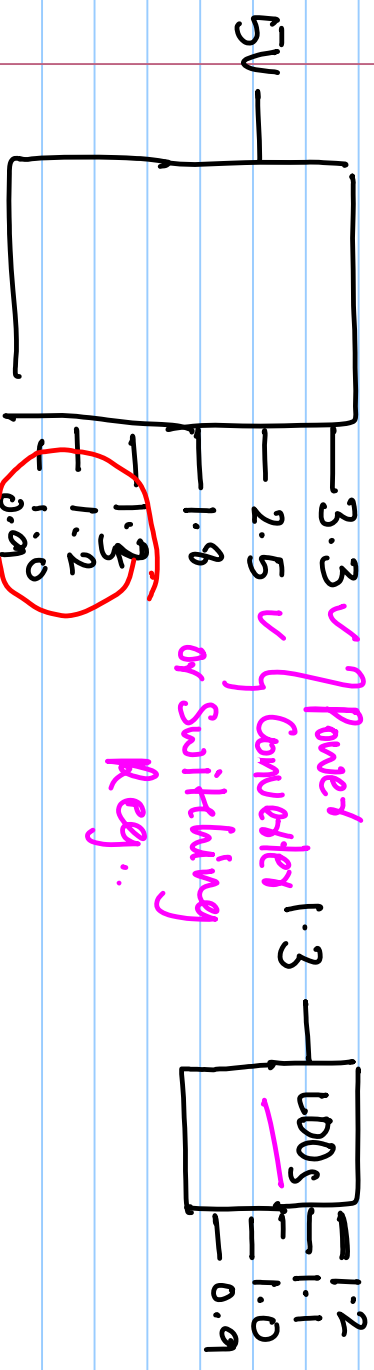LDO is quite useful when dropout voltage is lesser.



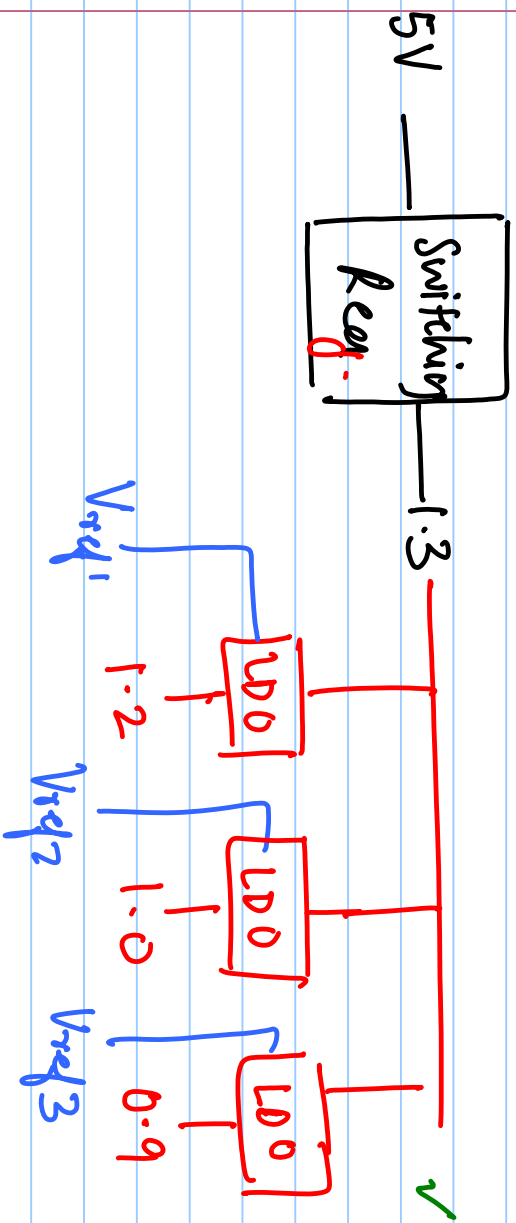

Dropout Vol. 0.1 0.3 0.1V