
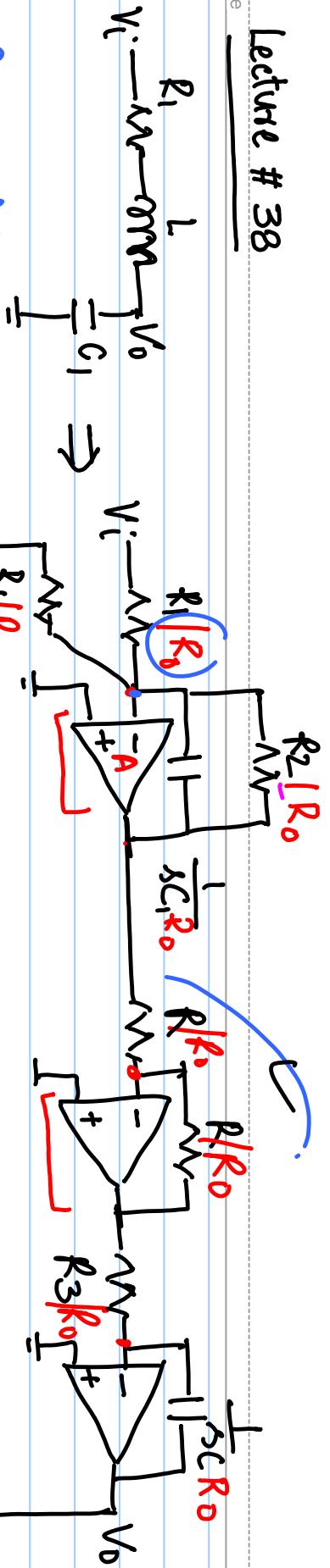


Lecture # 38

Passive filter

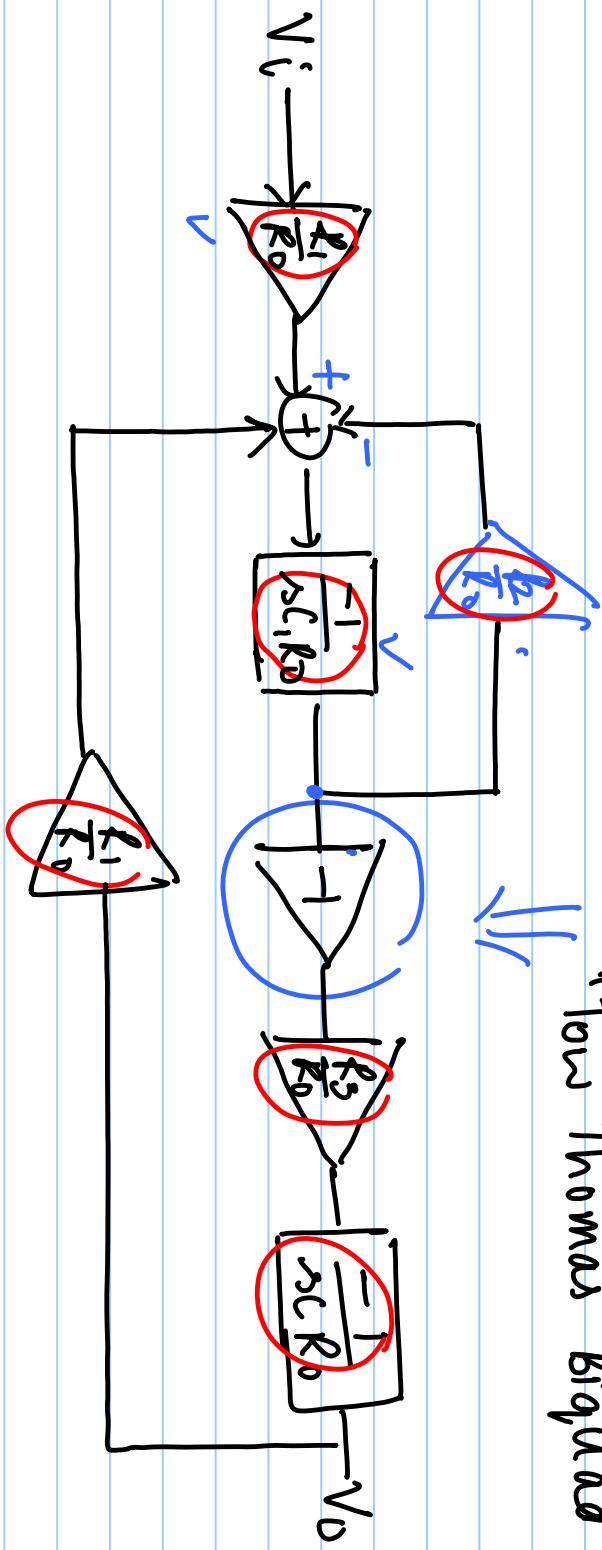

$$H(s) = \frac{1}{\frac{\lambda^2}{\omega_0^2} + \frac{s}{\omega_0 Q_P} + 1} = \frac{V_o(s)}{V_i(s)}$$

Relationship b/w V_i and V_o
in terms of gain blocks and
integrators

$$V_i(s) = V_o(s) \left(1 + \frac{s}{\omega_0 Q_P} + \frac{s^2}{\omega_0^2} \right)$$


$$\frac{\omega_0^2}{s^2} V_{in}(s) = V_o(s) \left(1 + \frac{\omega_0}{\lambda} \frac{1}{Q_P} + \frac{\omega_0^2}{\lambda^2} \right)$$

$$V_o(s) = \left\{ V_{in}(s) - V_o(s) \right\} \frac{\frac{\omega_0^2}{s^2}}{\frac{\omega_0^2}{s^2} - \frac{V_o(s)}{Q_P}}.$$

Integrator $\propto \frac{1}{s}$.

$$= \left[\left(V_{in}(s) - V_o(s) \right) \frac{\frac{\omega_0^2}{s^2}}{\frac{\omega_0^2}{s^2} - \frac{V_o(s)}{Q_P}} - \frac{1}{Q_P} V_o(s) \right] \frac{\omega_0}{\lambda}$$
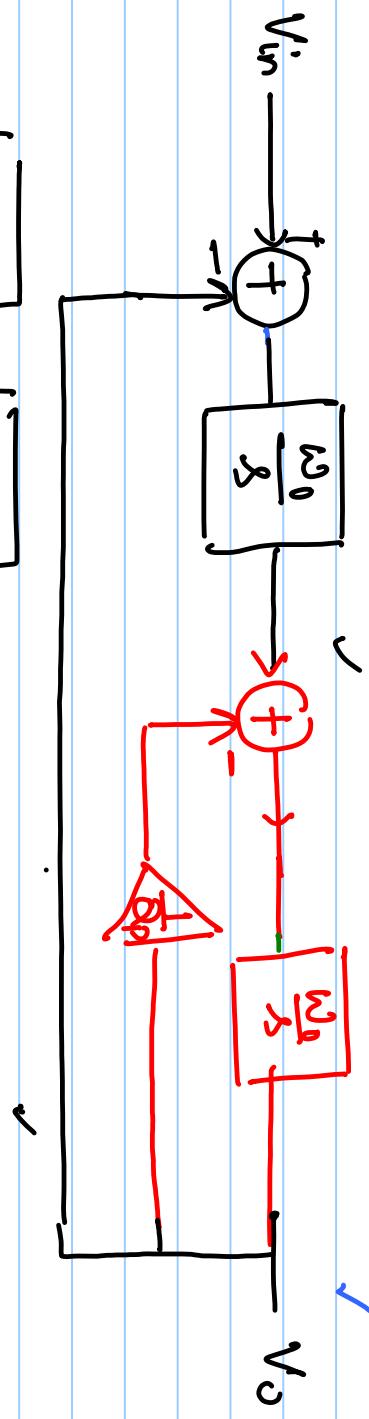
$$V_0(s) = \frac{\omega_0}{s} \left[(V_{in}(s) - V_0(s)) \frac{\omega_0}{s} - \frac{V_0(s)}{\alpha P} \right]$$



bi-quad.


$$V_i \xrightarrow{\text{Bi-quad}} \xrightarrow{\text{Bi-quad}} \xrightarrow{\text{Bi-quad}} V_o$$

4th order

$$V_i \xrightarrow{\text{First Order filte}} \xrightarrow{\text{Bi-quad}} \xrightarrow{\text{Bi-quad}} V_o$$


3rd order.

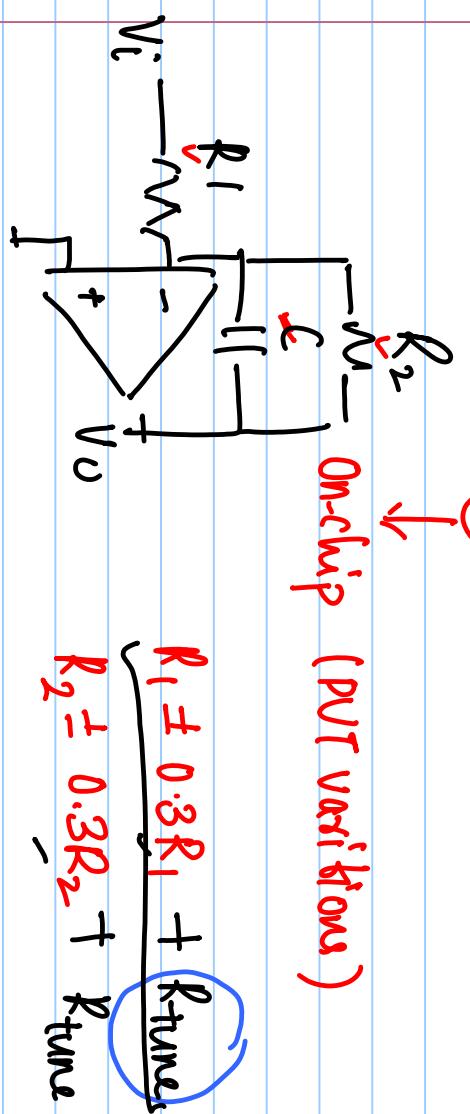Passive \rightarrow Active RC-filter
 (R, L, C)
 $(\text{Opamp}, R, C, \text{On-chip})$




$$R_1 = 0.3R_1 + R_{\text{tune}}$$

$$R_2 = 0.3R_2 + R_{\text{tune}}$$

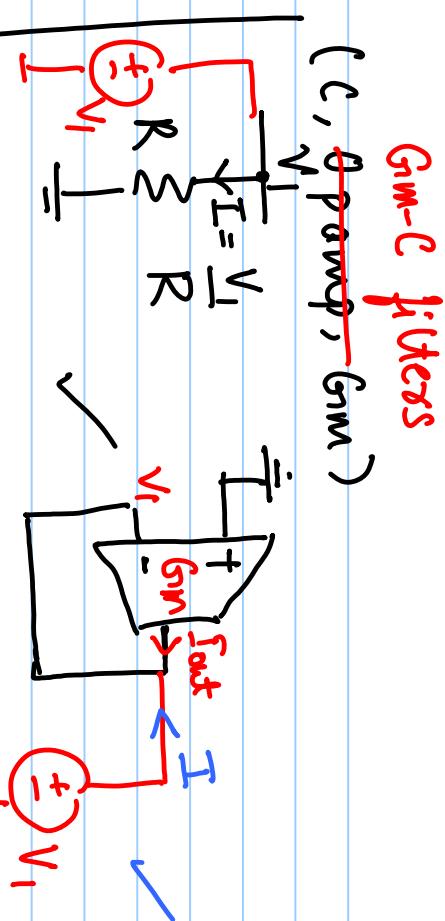

Gm-block

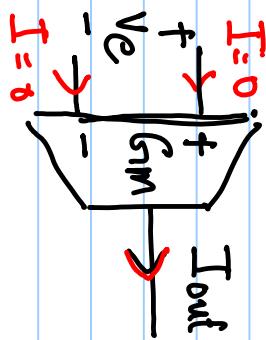


$$I_{\text{in}} = 0$$

$$V_e = G_m I_{\text{out}}$$

$$I_{\text{out}} = G_m V_e$$

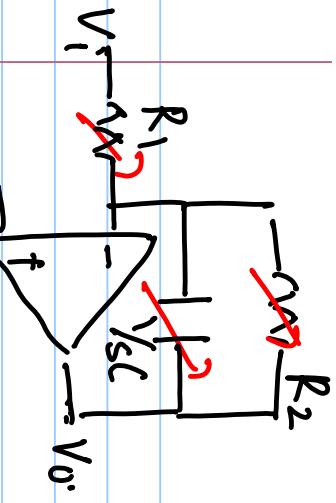function of operating point
 01 active block.



$$\frac{V_i}{R_1} = -V_o \left(\frac{1}{R_2} + sC \right)$$


$$\frac{V_o}{R_1} = -\frac{R_2}{R_1} \frac{1}{1+sCR_2}$$

$$R_1 \rightarrow R_1 + 0.3R_1$$

$$R_2 \rightarrow R_2 + 0.3R_2$$

$$C \rightarrow C$$

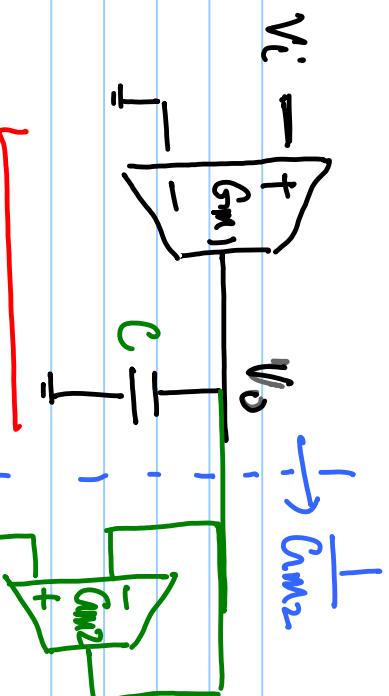
$$\omega_{-3dB} = \frac{1}{R_2 C} \rightarrow \frac{1}{1.3 R_2 C}$$



$$V_o = \left(G_m 1 \cdot V_i \right) \left(\frac{1}{sC} \parallel \frac{1}{G_m 2} \right)$$


$$\frac{V_o}{V_i} = \frac{G_m 1}{sC + G_m 2} = \frac{G_m 1 / G_m 2}{1 + sC / G_m 2}$$

$$\omega_{-3dB} = \frac{G_m 2}{C_1}$$

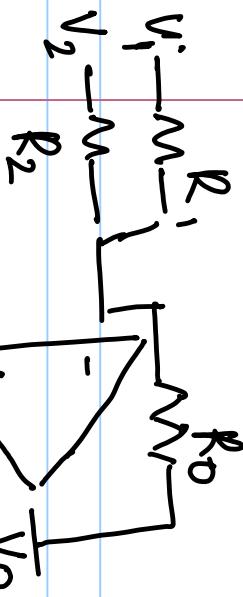



$$V_0 = - \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right) R_0$$

$\text{Am}_1 V_1$ $\text{Am}_2 V_2$

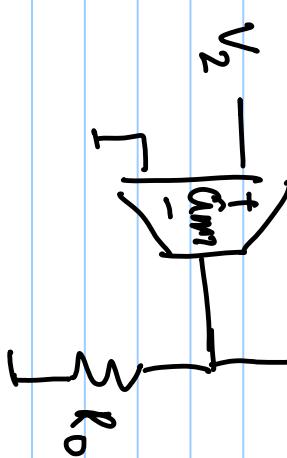
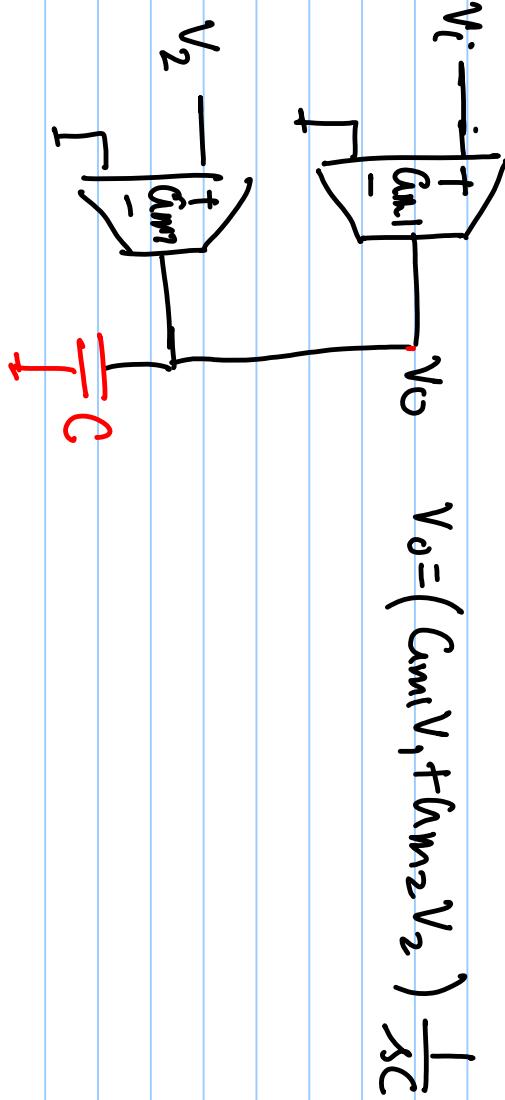
$$V_0 = + (\text{Am}_1 V_1 + \text{Am}_2 V_2) \frac{1}{sc}$$



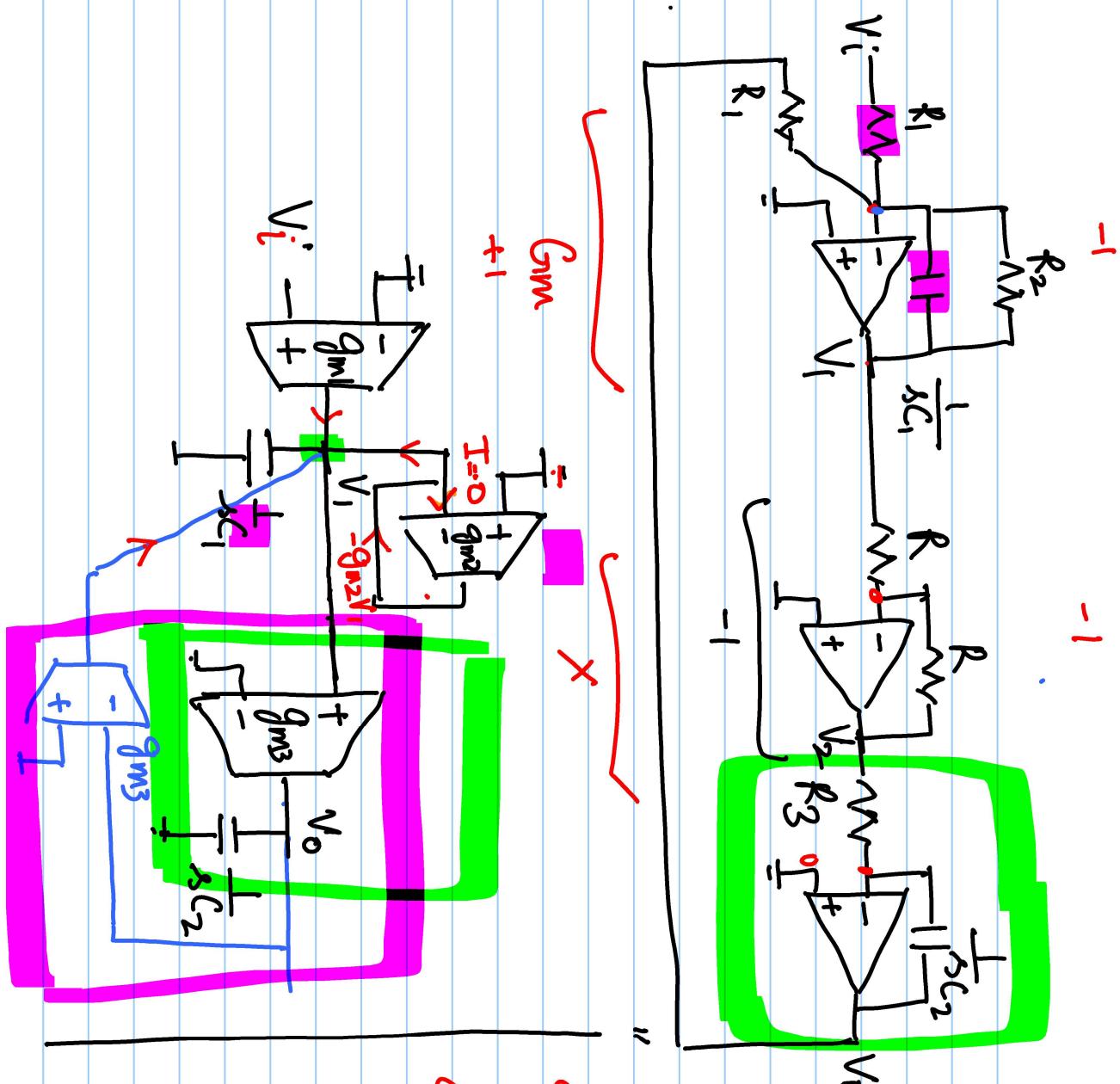

$$\begin{aligned}
 g_{m1}V_i - g_{m3}V_o - g_{m2}V_1 &= V_1sC_1 \\
 g_{m1}V_i &= g_{m2}V_1 + g_{m3}V_o + sC_1V_1 \\
 &= V_1(g_{m2} + sC_1) \\
 &\quad + g_{m3}g_{m2}\frac{V_1}{sC_2}
 \end{aligned}$$

$$g_{m1}V_i = V_1 \left(g_{m2} + \kappa C_1 + \frac{g_{m3}^2}{\kappa C_2} \right)$$

$$= \frac{V_1}{\kappa C_2} \left(g_{m2} \kappa C_2 + \kappa^2 C_1 C_2 + g_{m3}^2 \right)$$

$$\frac{V_1}{V_i} = \frac{g_{m1} \cdot \kappa C_2}{\kappa^2 C_1 C_2 + \kappa C_2 g_{m2} + g_{m3}^2}$$

$$= \kappa \frac{C_2}{g_{m3}^2} \cdot g_{m1}$$

$$\kappa^2 C_1 \frac{C_2}{g_{m3}^2} + \kappa \frac{C_2}{g_{m3}^2} \cdot g_{m2} + 1$$

$$= \kappa L / (1/g_{m2})$$

$$\times \frac{g_{m1}}{g_{m2}}$$

$\frac{g_{m1}}{g_{m2}}$, peak gain.
 $L = \frac{C_2}{g_{m3}^2}$

$$\frac{V_i}{V_o} = \frac{\alpha / \omega_{0ap}}{\frac{\kappa L}{\omega_0^2 + \frac{\Delta}{\omega_0 \alpha p} + 1}} \times \frac{g_{m1}}{g_{m2}}$$

$$\frac{V_o}{V_i} = \frac{\frac{\kappa^2}{\omega_0^2} + \frac{\kappa}{\omega_0 \alpha p} + 1}{1 - \frac{g_{m1}}{g_{m2}}} \times \frac{g_{m1}}{g_{m2}}$$


$$I_T = g_{m3} \frac{1}{\kappa C_2} \times g_{m3} \cdot V_T$$

$$\frac{V_T}{T} =$$


$$\frac{\kappa C_2}{g_{m3}}$$

$$\rightarrow \frac{1}{\kappa L g_{m2}}$$

Capacitor

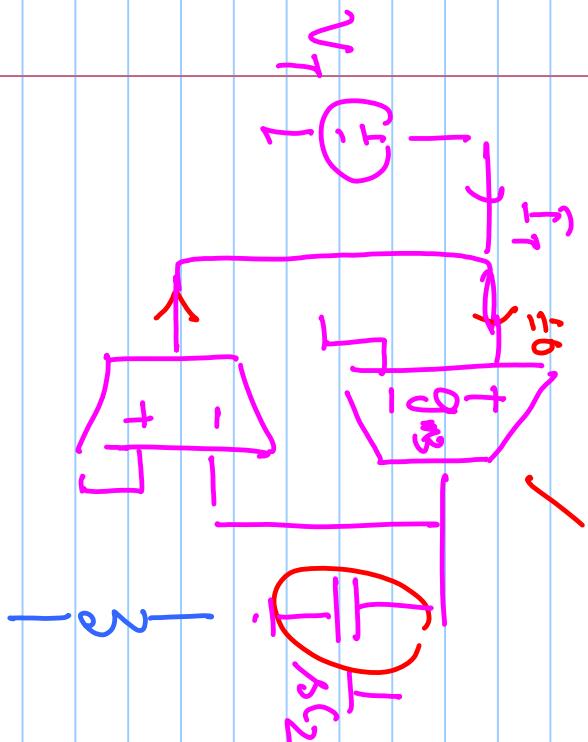

Gyrator (Impedance Inverter)

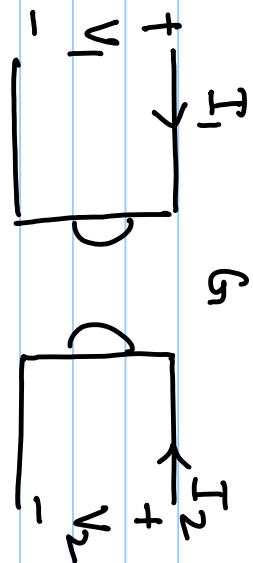

$$I_1 = G V_2$$

$$I_2 = -G V_1$$

