
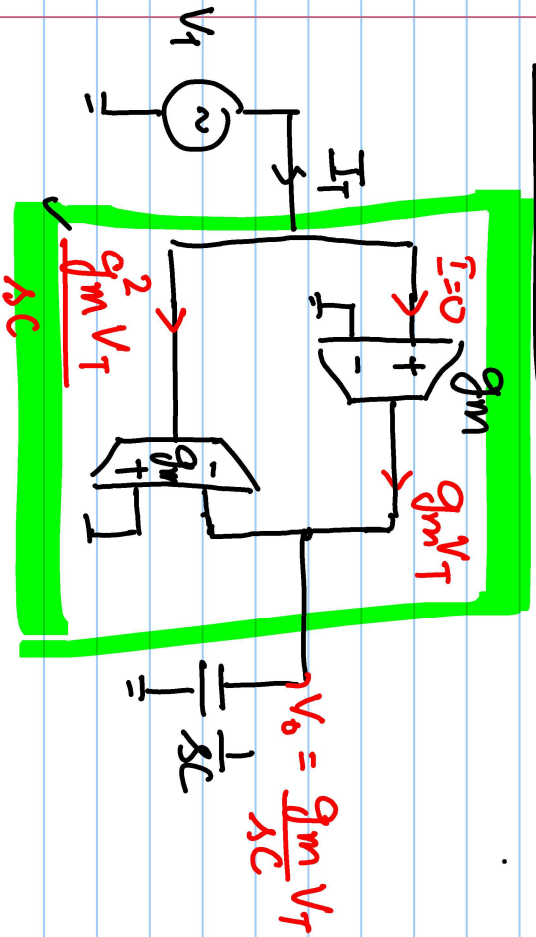



lecture # 39

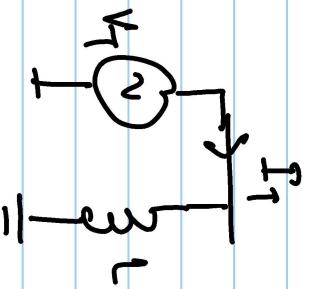

$$\frac{V_T}{I_T} = s \left(\frac{C}{g_m^2} \right) = sL$$



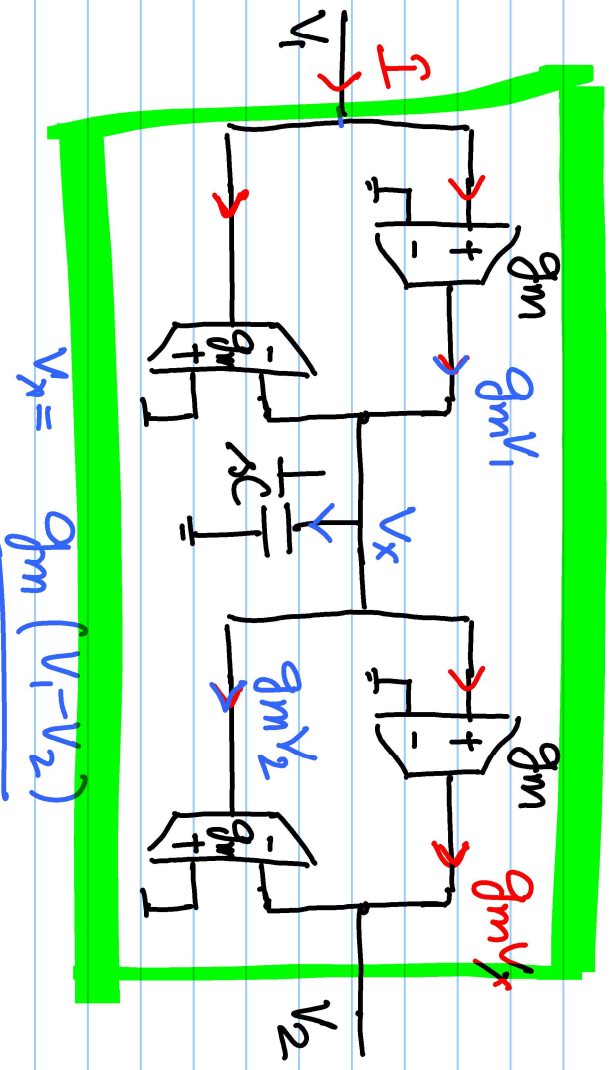
$$V_1 \xrightarrow{sL} V_2 \quad I = \frac{V_1 - V_2}{sL}$$



$$I = \frac{g_m^2 (V_1 - V_2)}{sL} = \frac{V_1 - V_2}{s \left(\frac{C}{g_m^2} \right)}$$

Band Rejected filter (BRF)

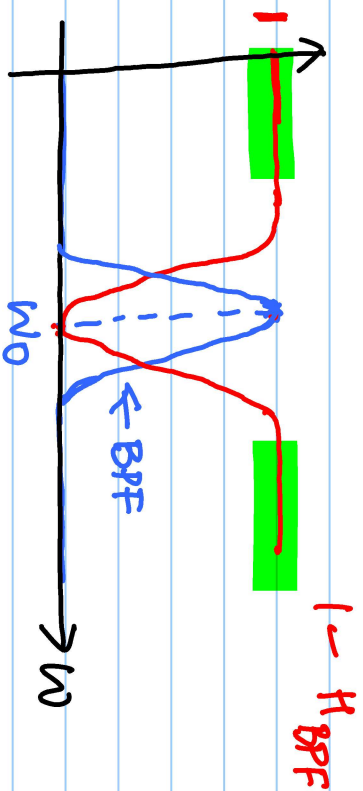


$$H_{BRF} = 1 - H_{BPF}$$

$$\frac{V_o}{V_i} = \frac{s/\omega_0 Q_p}{\frac{s^2}{\omega_0^2} + \frac{s}{\omega_0 Q_p} + 1}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

@ ω_0 : $sL \parallel \frac{1}{sC} = \frac{sL}{1+s^2LC}$

$\rightarrow \infty$

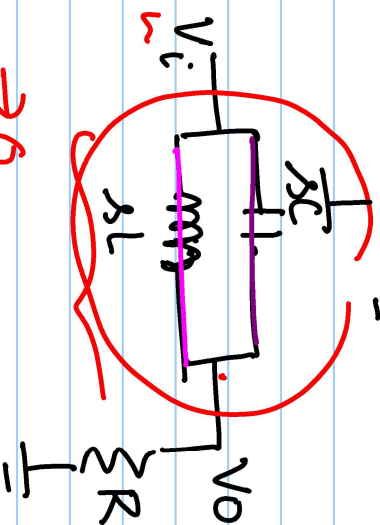

$\rightarrow 0$



$$\frac{V_o}{V_i} = \frac{R}{R + (sL \parallel \frac{1}{sC})} \rightarrow \infty$$

$$H_{BRF} = 1 - H_{BPF} = 1 - \frac{s/w_0 Q_p}{s^2/w_0^2 + \frac{s}{w_0 Q_p} + 1} = \frac{1 + s^2/w_0^2}{1 + \frac{s}{w_0 Q_p} + \frac{s^2}{w_0^2}}$$


$$\frac{V_0}{V_i} = \frac{1 + s^2/w_0^2}{1 + \frac{s^2}{w_0^2} + \frac{s}{w_0 Q_p}}$$

$$V_0 \left(1 + \frac{w_0}{s Q_p} + \frac{w_0^2}{s^2} \right) = V_i \left(\frac{w_0^2}{s^2} + 1 \right)$$
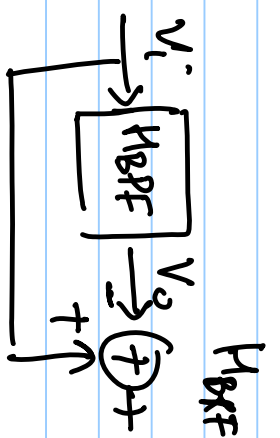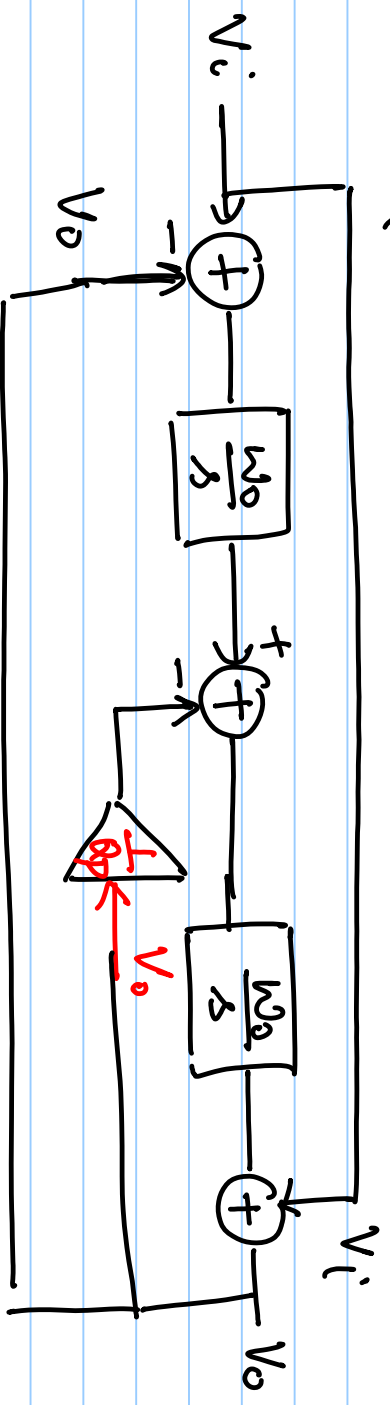
$$V_0 = \left((V_i - V_0) \frac{w_0}{s} - \frac{1}{Q_p} V_0 \right) \frac{w_0}{s} + V_i$$



Sallen Key Filter

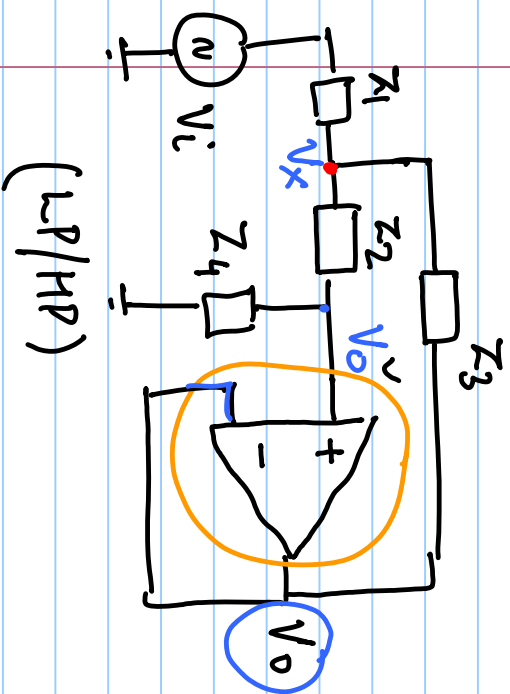

$$V_0 = \frac{Z_4}{Z_4 + Z_2} V_x \Rightarrow V_x = V_0 \left(1 + \frac{Z_2}{Z_4} \right)$$

$$V_x \left(\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} \right) = \frac{V_0}{Z_2} + \frac{V_0}{Z_3} + \frac{V_i}{Z_1}$$

$$V_0 \left(1 + \frac{Z_2}{Z_4} \right) \left(\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} \right) = V_0 \left(\frac{1}{Z_2} + \frac{1}{Z_3} \right) + \frac{V_i}{Z_1}$$

$$V_0 \left(\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \frac{Z_2}{Z_1 Z_4} + \frac{1}{Z_4} + \frac{Z_2}{Z_3 Z_4} \right) = V_0 \left(\frac{1}{Z_2} + \frac{1}{Z_3} \right) + \frac{V_i}{Z_1}$$

$$\frac{V_0}{V_i} = \frac{1}{1 + \frac{Z_1 Z_2}{Z_1 Z_4} + \frac{Z_1}{Z_4} + \frac{Z_1 Z_2}{Z_3 Z_4}} = \frac{1}{\frac{Z_3 Z_4}{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3 + Z_3 Z_4} + \frac{2 \cdot Z_2 Z_3 Z_4}{Z_1 Z_2 Z_3} + \frac{Z_1 Z_2 Z_3}{Z_4}}$$

$$= \frac{Y_1 Y_2}{Y_3 Y_4 + Y_2 Y_4 + Y_1 Y_4 + Y_1 Y_2}$$

$$Y_1 = \frac{1}{Z_1}, \quad Y_2 = \frac{1}{Z_2}, \quad Y_3 = \frac{1}{Z_3}, \quad Y_4 = \frac{1}{Z_4}$$

$$\frac{V_0}{V_i} = \frac{1}{1 + \underbrace{\frac{s}{\omega_{ppd}} + \frac{s^2}{\omega_3^2}}$$

$$Z_1 = R_1, \quad Z_2 = R_2, \quad Z_3 = \frac{1}{sC_3}, \quad Z_4 = \frac{1}{sC_4}$$

$$\frac{V_0}{V_i} = \frac{Z_3 Z_4}{(Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3 + Z_3 Z_4)} = \frac{1 / s^2 C_3 C_4}{R_1 R_2 + \frac{R_1}{sC_3} + \frac{R_2}{sC_3} + \frac{1}{s^2 C_3 C_4}}$$


$$\frac{V_0}{V_i} = \frac{1}{(1 + sC_4(R_1 + R_2) + s^2 C_3 C_4 R_1 R_2)} \quad (\text{LRF})$$

HPF

$$\begin{aligned}\frac{V_o}{V_i} &= \frac{s^2 / \omega_o^2}{\frac{s^2}{\omega_o^2} + \frac{s}{\omega_o Q_p} + 1} = \frac{Y_1 Y_2}{Y_3 Y_4 + Y_2 Y_4 + Y_1 Y_4 + Y_1 Y_2} \\ &= \frac{s^2 C_1 C_2}{\frac{1}{R_3 R_4} + \frac{s C_2}{R_4} + \frac{s C_1}{R_4} + s^2 C_1 C_2} \\ &= \frac{s^2 C_1 C_2 R_3 R_4}{(1 + s R_3 (C_1 + C_2)) + s^2 C_1 C_2 R_3 R_4}\end{aligned}$$

(HPF)
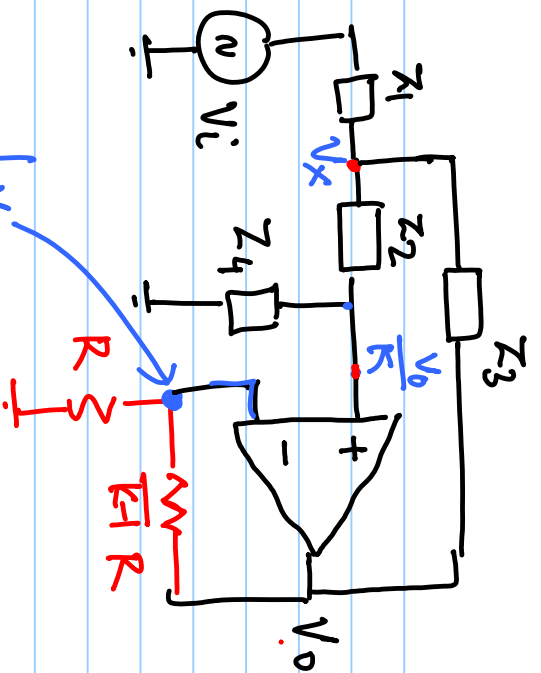
$$\left. \begin{aligned}Y_1 &= s C_1 \\ Y_2 &= s C_2 \\ Y_3 &= C_3 = 1 / R_3 \\ Y_4 &= C_4 = 1 / R_4\end{aligned} \right\}$$



$$\frac{V_0}{V_i} = \frac{k}{1 + s[R_1 C_3 (1-k) + R_1 C_4 + R_2 C_4] + s^2 C_3 C_4 R_1 R_2}$$

$$\frac{V_0}{V_i} = \frac{1}{1 + s C_4 (R_1 + R_2) + s^2 C_3 C_4 R_1 R_2} \quad \left| \begin{array}{l} \text{Previous} \\ \text{Exp.} \\ k=1 \end{array} \right.$$

$$D(s) = 1 + s \underbrace{(R_1 C_3 (1-k) + R_1 C_4 + R_2 C_4)}_b + s^2 C_3 C_4 R_1 R_2$$

$$s = - \frac{(R_1 C_3 (1-k) + R_1 C_4 + R_2 C_4) \pm \sqrt{(b^2) - 4 C_3 C_4 R_1 R_2}}{2 C_3 C_4 R_1 R_2}$$


< 0

For poles to be in R.H.P.:

$$R_1 C_3 (1-k) + R_1 C_4 + R_2 C_4 > 0$$


$$\Rightarrow K < \frac{R_1 C_3 + R_1 C_4 + R_2 C_4}{R_1 C_3}$$
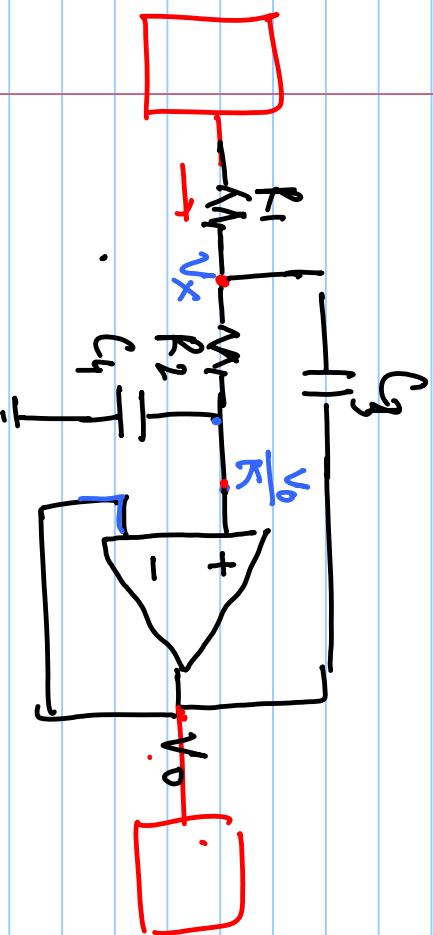
$$K < 1 + \frac{C_4}{C_3} + \frac{R_2}{R_1} \cdot \frac{C_4}{C_3}$$



Output impedance of filter is very low.
 input impedance is very high.

BPT

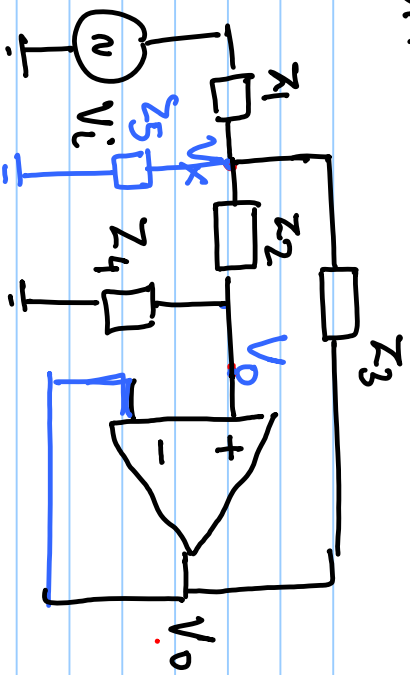

$$V_o = \frac{Z_u}{Z_u + Z_2} V_x \quad \checkmark$$

$$V_o \left(\frac{1}{z_1} + \frac{1}{z_2} + \frac{1}{z_3} + \frac{1}{z_5} \right) = \frac{V_i}{z_1} + \frac{V_o}{z_2} + \frac{V_o}{z_3} \quad \checkmark$$

$$\frac{V_o}{V_i} = \frac{z_3 z_4 z_5}{z_1 z_3 z_4 + z_1 z_2 z_5 + z_1 z_2 z_3 + z_3 z_4 z_5 + z_2 z_3 z_5}$$


$$= \frac{Y_1 Y_2}{Y_2 Y_5 + Y_2 Y_4 + Y_4 Y_5 + Y_3 Y_4 + Y_1 Y_2 + Y_1 Y_4} = \frac{R_2^2}{W_0^2} + \frac{R_3}{W_0 Q_p} + 1$$



$$Y_i = \frac{1}{z_i} \quad ; \quad i: 1, 2, 3, 4, 5$$

$$Y_1 = \frac{1}{R_1} = G_1, \quad Y_2 = sC_2, \quad Y_4 = \frac{1}{R_4} = G_4, \quad Y_3 = \frac{1}{R_3} = G_3, \quad Y_5 = sC_5$$

$$\frac{V_o}{V_i} = \frac{s C_2 C_1 (R_1 + R_3) C_3 C_4}{(1 + s (C_2 R_1 + C_2 C_3 R_4 + C_5 C_4)) \frac{C_1 C_3 R_4 + C_3 C_4 R_4}{C_1 C_3 R_4 + C_3 C_4 R_4} + \frac{s^2 C_2 C_5}{C_1 C_3 R_4 + C_3 C_4 R_4}}$$

Phase filters

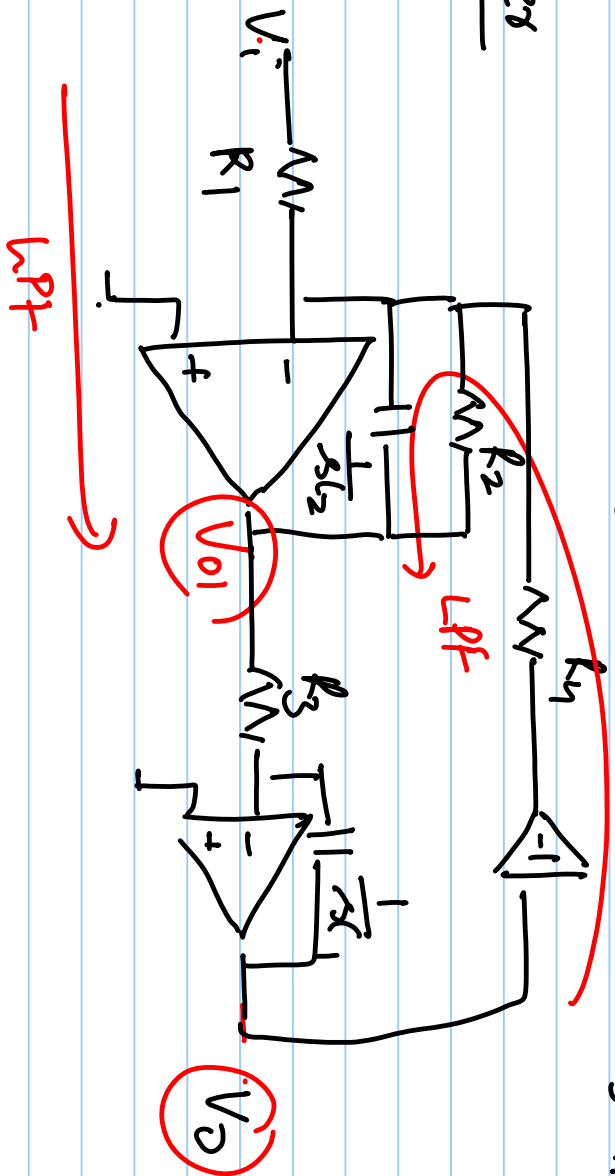

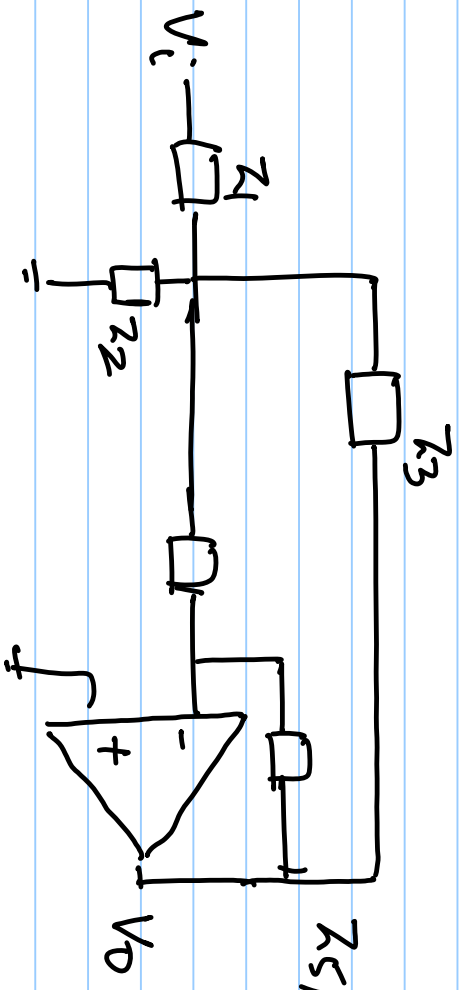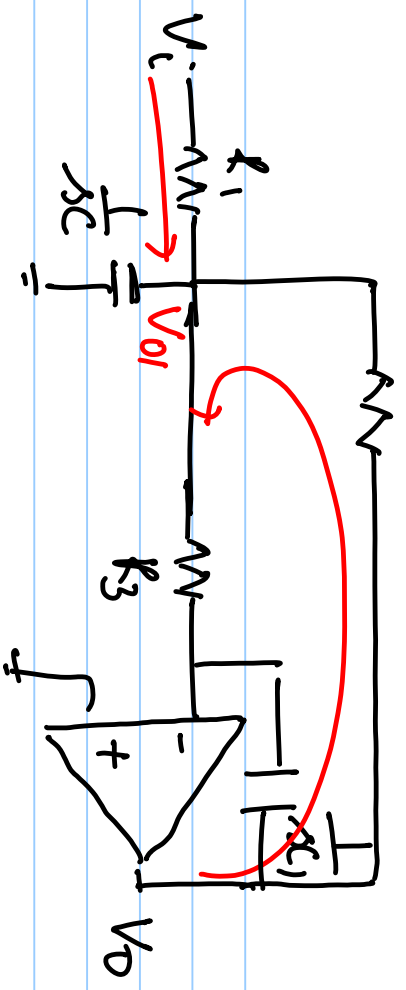

Z_1, Z_2, Z_3 can be R or C.

You can realize different filters