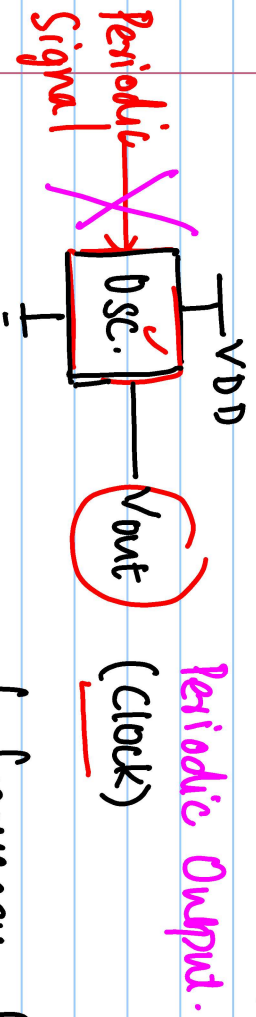


# Lecture # 41


Oscillator : Produces periodic signals



10 Mbps  $\rightarrow$  10 MHz


frequency,  $f = \frac{1}{T}$

$\omega = \frac{2\pi}{T}$

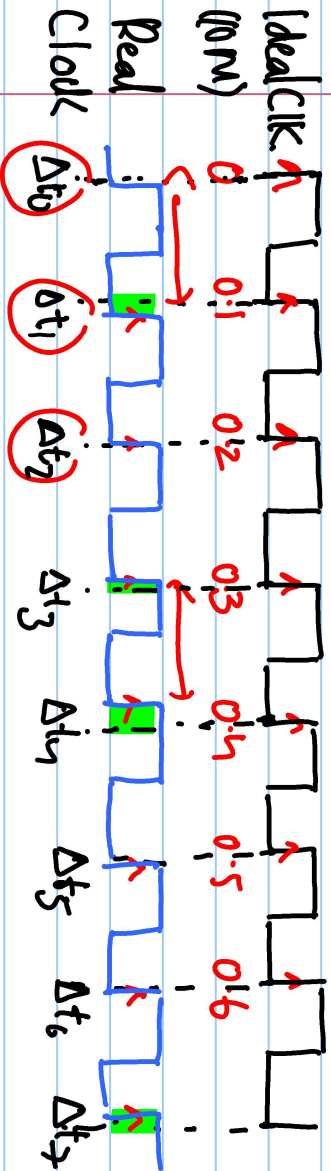

$\Delta t_i$  : Gaussian Distribution

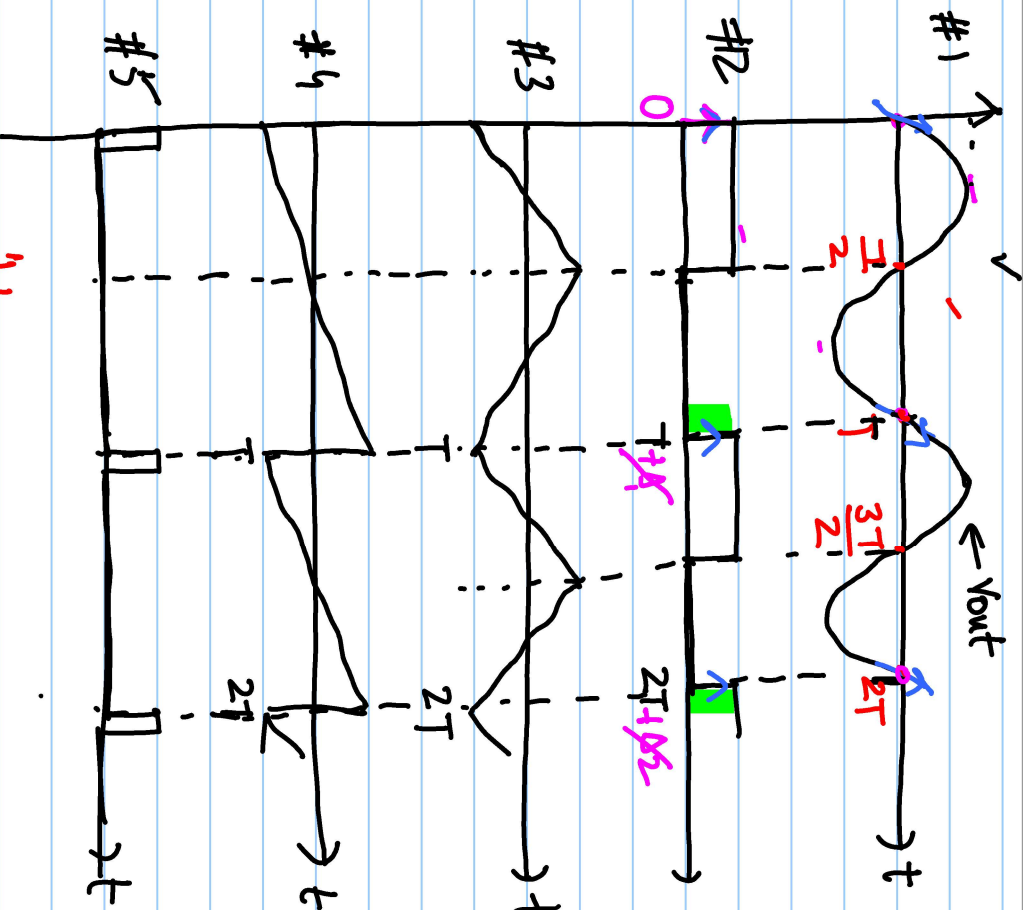Standard deviation of  $\Delta t$  as minimum as possible.




## 1. Crystal Oscillator (Piezoelectric)

- $\Delta F$  is very low. (10 ppm) Stability of the oscillator
- Very low noise
- Tunability is very low.

Q 10 MHz  $\rightarrow$  11 MHz
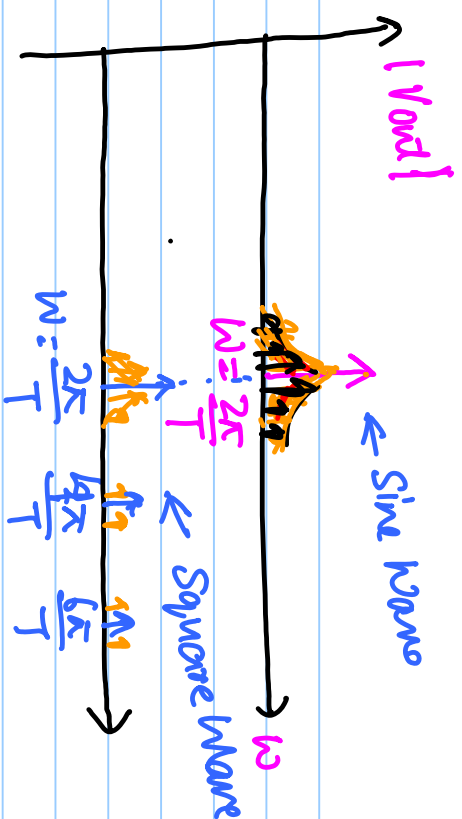
## 2. Tuned LC oscillator

- $\Delta F$  is low
- Low Noise
- Tunability is low



Clock Source,  $f_0 + \Delta F$


$$\frac{1 \text{ MHz} \times 10^6}{16 \text{ Hz}} = \frac{1}{16} \times 10^6 = 10^3$$

$\frac{\pm \Delta F}{f_0} \times 10^6 = \text{frequency error in ppm}$


$$\frac{\Delta F}{16 \text{ Hz}} \times 10^6 = 10 \text{ ppm}$$

$$\Delta F = \frac{10}{10^6} \times 10^9 = 10^4 \text{ Hz}$$

$$\Delta F \approx 10 \text{ kHz}$$

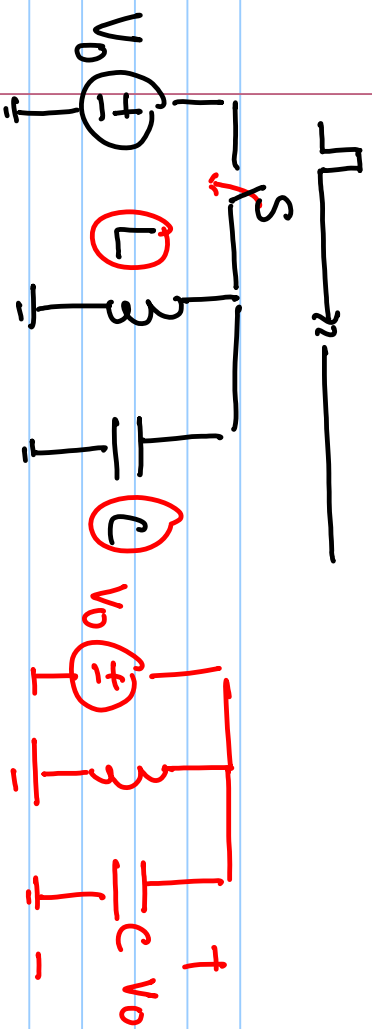


Closed Switch.

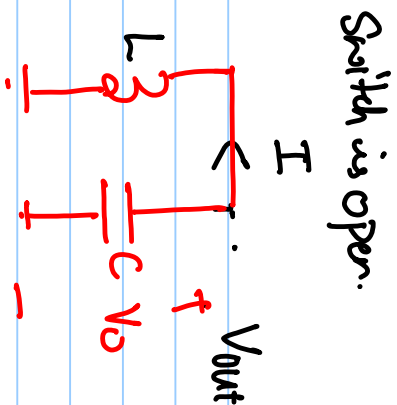

Switch is open.

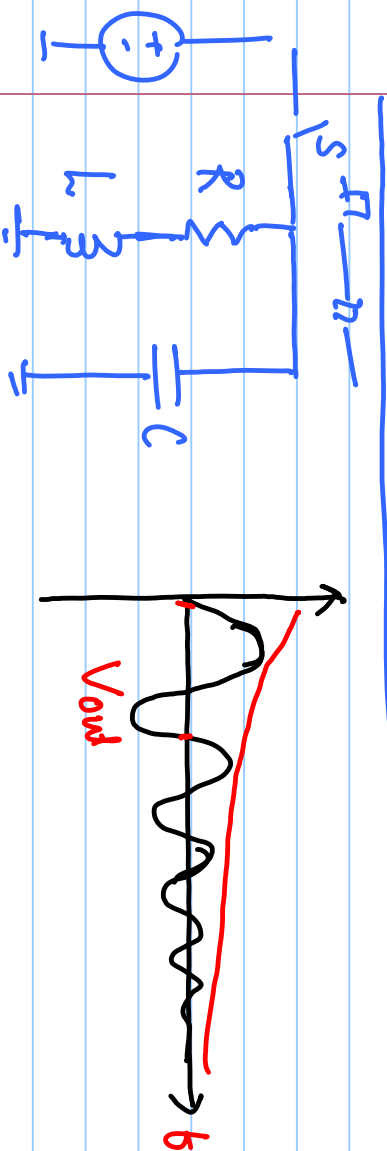
$$\omega_0 = \frac{1}{\sqrt{LC}}, \quad f_0 = \frac{1}{T} = \frac{1}{2\pi\sqrt{LC}}$$




$$C \frac{dV_{out}}{dt} = -I$$

$$V_{out} = L \frac{dI}{dt}$$
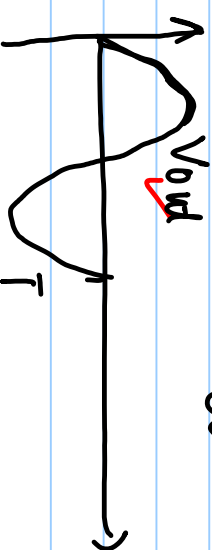
$$V_{out} = -LC \frac{d^2V_{out}}{dt^2} \Rightarrow V_{out} = A \sin(\omega t)$$


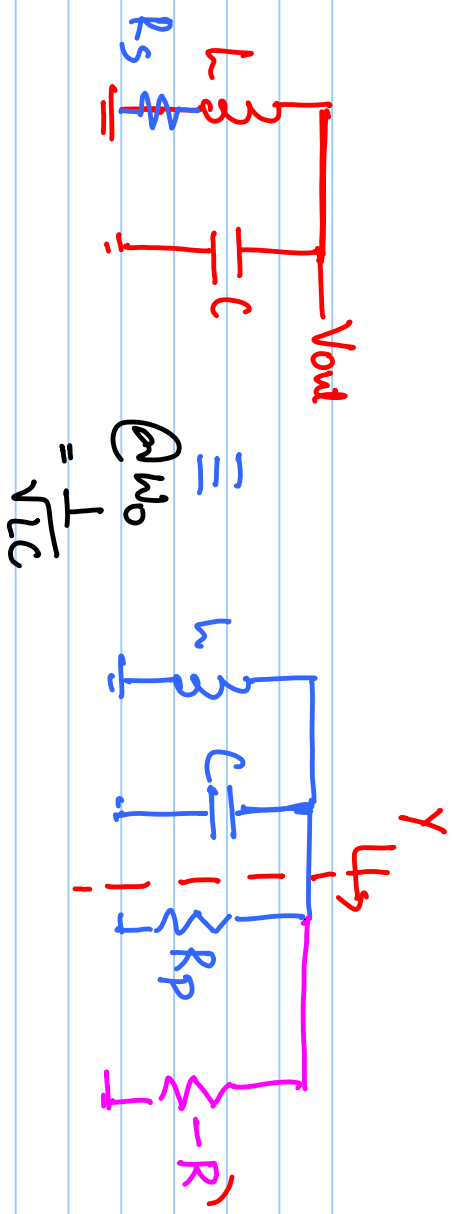
$$\omega_0 = \frac{2\pi}{T} = \frac{1}{\sqrt{LC}}$$




$$Y = \frac{1}{R_p} - \frac{1}{R}$$


$$Z = \frac{R_p (-R)}{R_p - R}$$

$$(R_s + j\omega_0 L) \parallel \frac{1}{j\omega_0 C} = (j\omega_0 L \parallel \frac{1}{j\omega_0 C} \parallel R_p)$$

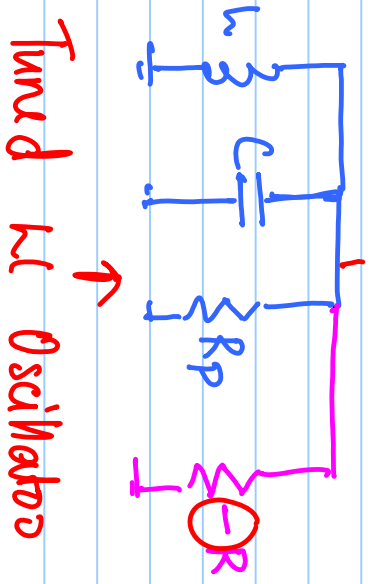
if  $R = R_p$ :  $Z \rightarrow \infty$   
 $Y \rightarrow 0$




$$R = R_p$$

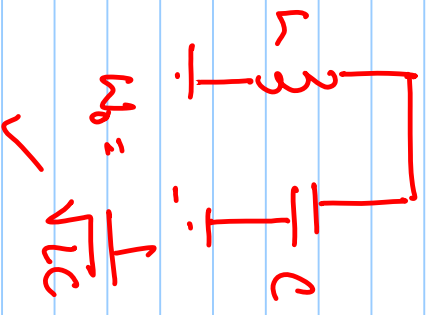


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

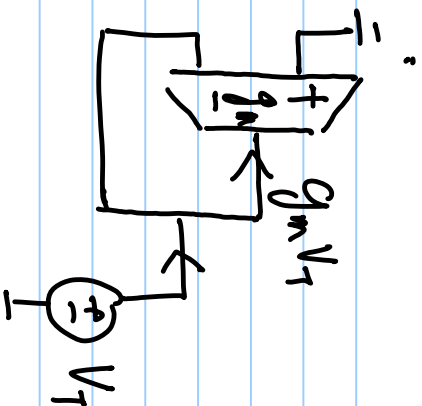


$$R = \frac{1}{g_m}$$

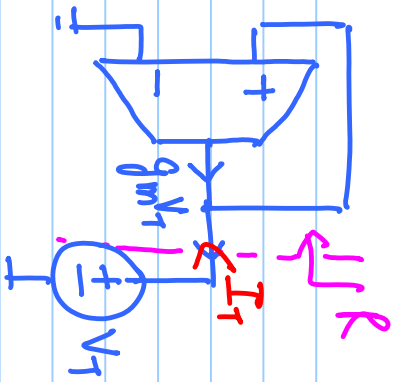

$$R = \frac{V_T}{I_T} = -\frac{1}{g_m}$$

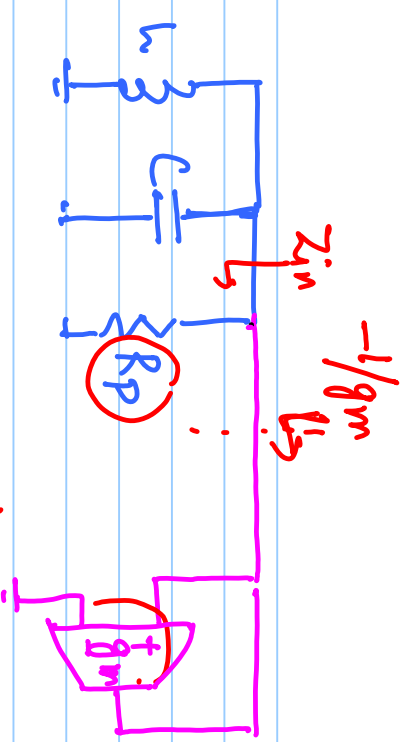


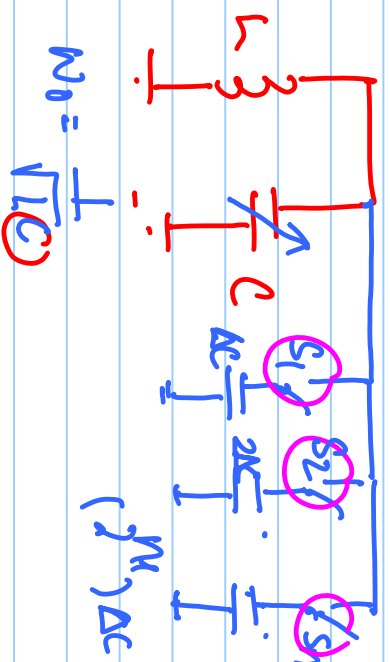
$$Z_{in} = \frac{-1}{g_m} \parallel R_P \xrightarrow{g_m \frac{1}{R_P} \rightarrow \infty}$$



$$G_{TOD} = C + S_1 \cdot \Delta C + S_2 \cdot (2\Delta C)$$
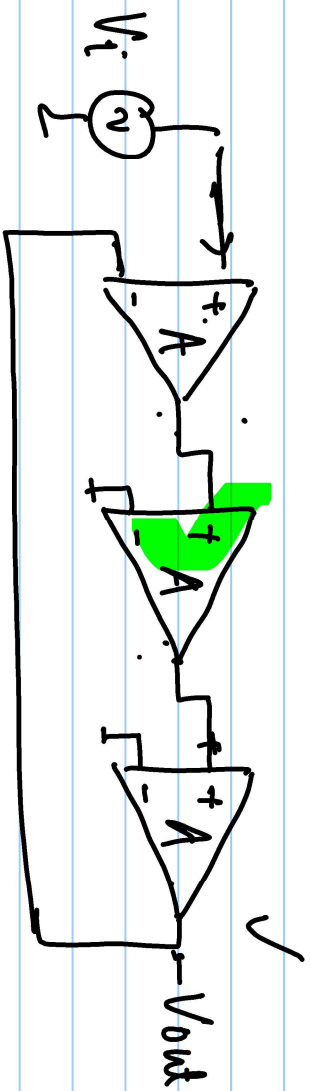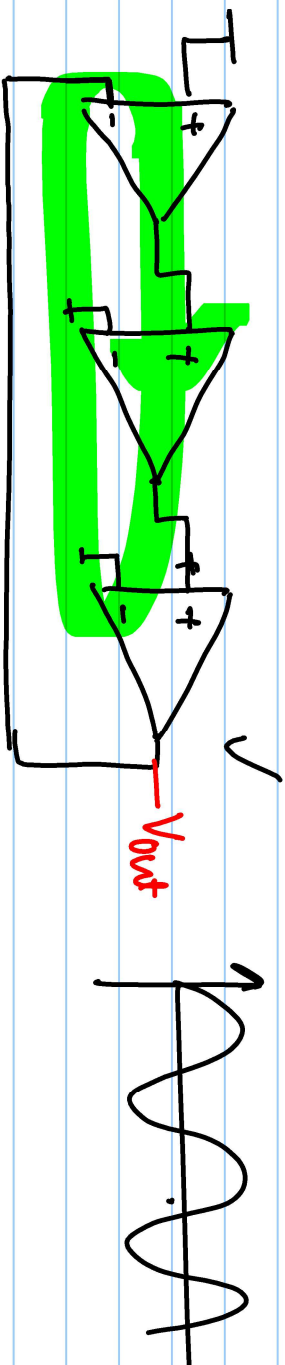
### 3. Ring Oscillator.

- Amplifiers
- Inverters (Delay Elements)



$$K_L(s) = A^3 = \left( \frac{A_D}{1 + s/\omega_D} \right)^3$$

$$\frac{V_{out}}{V_i} = 1$$



.