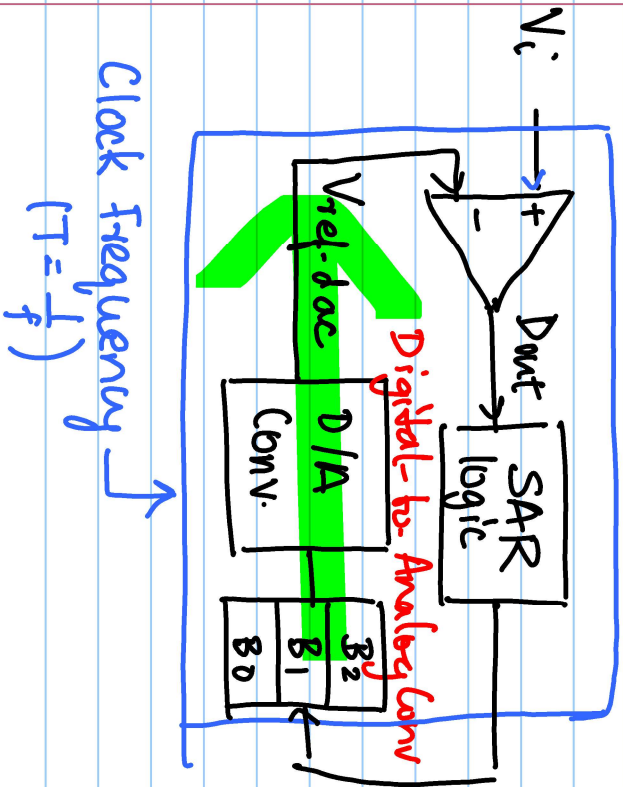



Lecture # 45



- Change $V_{ref-dac}$

- Give 'T' time for comparison

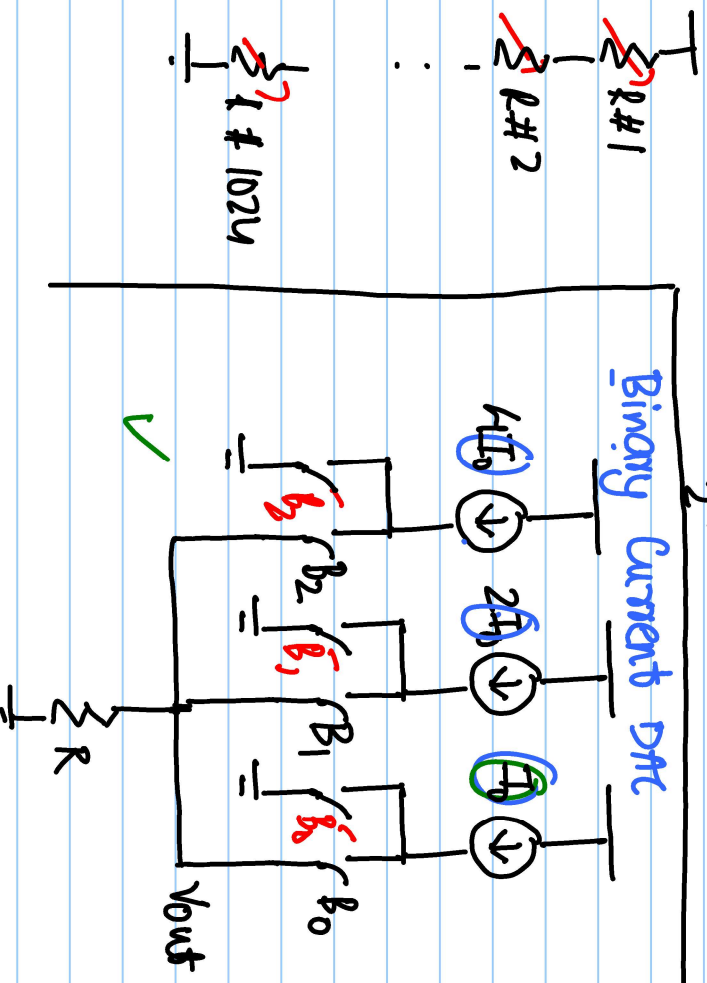
For N-bits ADC, resistor string requires 2^N resistors to generate $\frac{V_{ref} \times k}{2^N}$




$$\begin{aligned}
 V_{out} &= (4I_0 \cdot B_2 + 2I_0 \cdot B_1 + I_0 \cdot B_0) R \\
 &= I_0 R (2^2 B_2 + 2^1 B_1 + 2^0 B_0) \\
 &= \frac{V_{ref}}{8} (2^2 B_2 + 2^1 B_1 + 2^0 B_0)
 \end{aligned}$$

10-bit current DAC : 10 Current sources.

R2R DAC

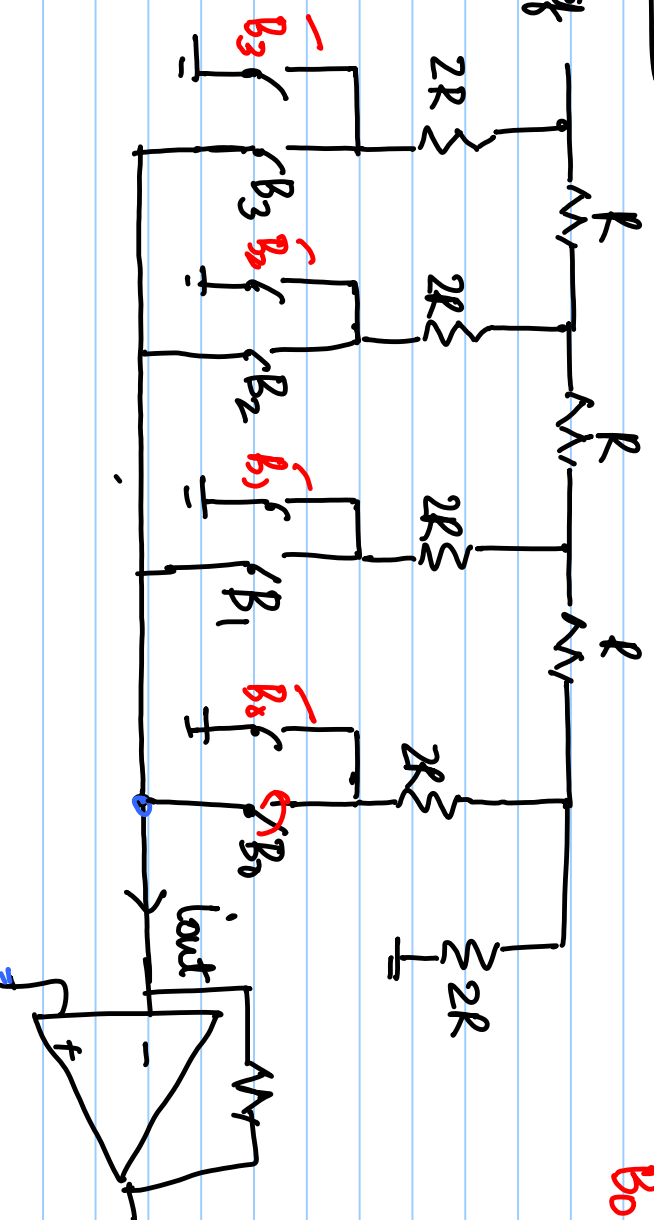

$$B_0 = 1$$

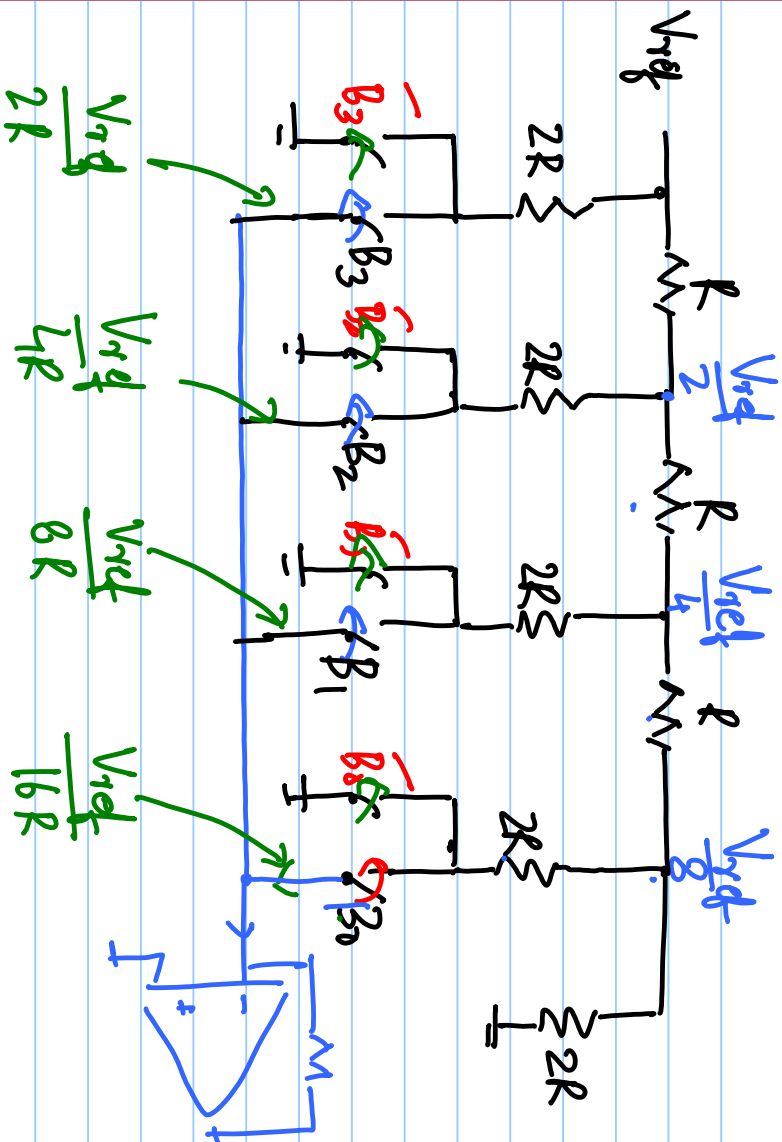

$$B_0 = B_1 = B_2 = B_3 = 1$$



$$B_0 = B_1 = B_2 = B_3 = 0$$

$$I_{out} = B_3 \cdot \frac{V_{ref}}{2R} + B_2 \cdot \frac{V_{ref}}{4R} + B_1 \cdot \frac{V_{ref}}{8R} + B_0 \cdot \frac{V_{ref}}{16R}$$

$$= \frac{V_{ref}}{16R} \left[2^3 B_3 + 2^2 B_2 + 2^1 B_1 + 2^0 B_0 \right]$$

$$0 \leq I_{out} \leq \frac{15}{16} \frac{V_{ref}}{R}$$

Capacitor DAC

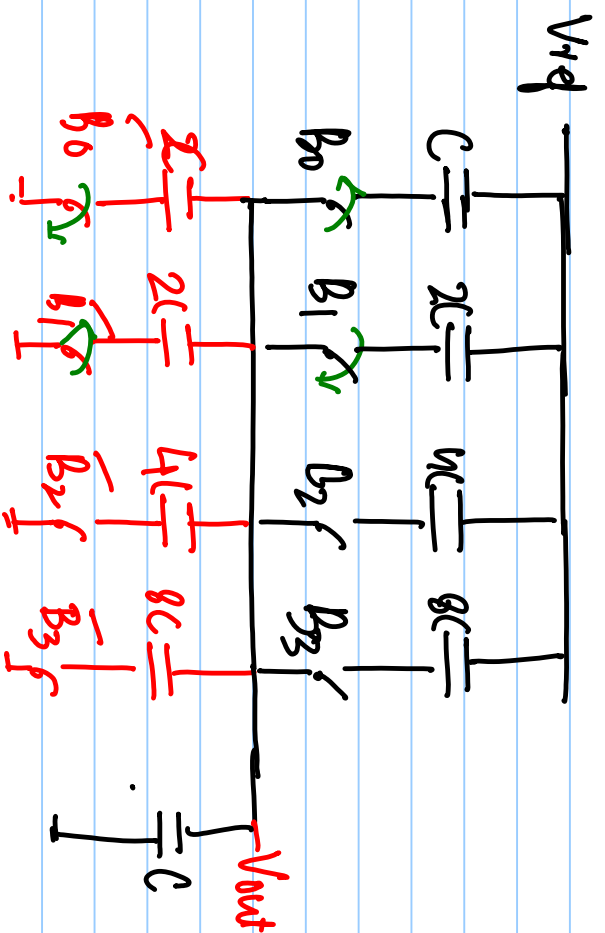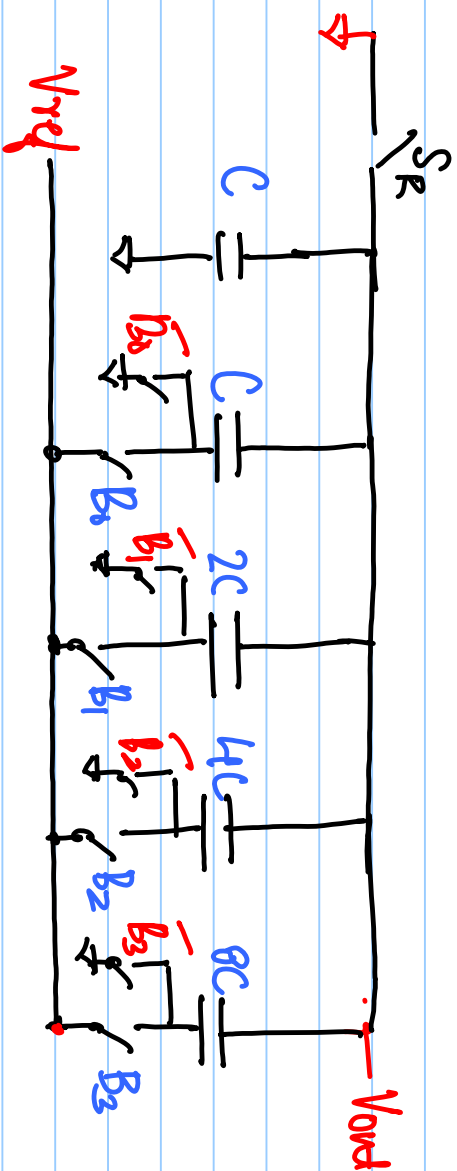

When S_R is high:

- Capacitors are reset.


When S_R is low


$$\begin{aligned}
 & \text{Circuit diagram showing } C_{top} \text{ and } C_{bot} \text{ connected to } V_{out} \\
 & = (B_0 C + B_1 2C + B_2 4C + B_3 8C) \\
 & = (C + \bar{B}_0 C + B_1 2C + \bar{B}_2 4C + \bar{B}_3 8C)
 \end{aligned}$$

$$\begin{aligned}
 V_{out} &= \frac{C_{top} V_{ref}}{C_{top} + C_{bot}} = \frac{(B_0 + 2B_1 + 4B_2 + 8B_3) C}{C + \underbrace{(1-B_0)C + (1-B_1)2C + \underbrace{(1-B_2)0C + (1-B_3)16C}_{C_{bot}})}_{V_{ref}}} \\
 &= \frac{C (8B_3 + 4B_2 + 2B_1 + B_0)}{16C} V_{ref} \\
 &= \frac{V_{ref}}{16} (8B_3 + 4B_2 + 2B_1 + B_0)
 \end{aligned}$$

Errors in A/D or D/A converters.

1. Quantization error.

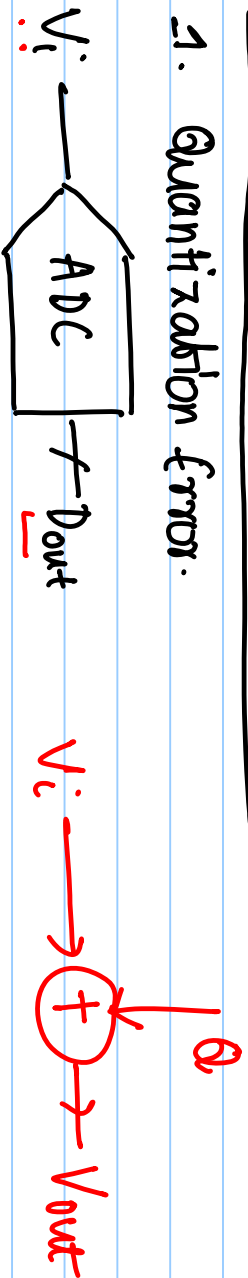

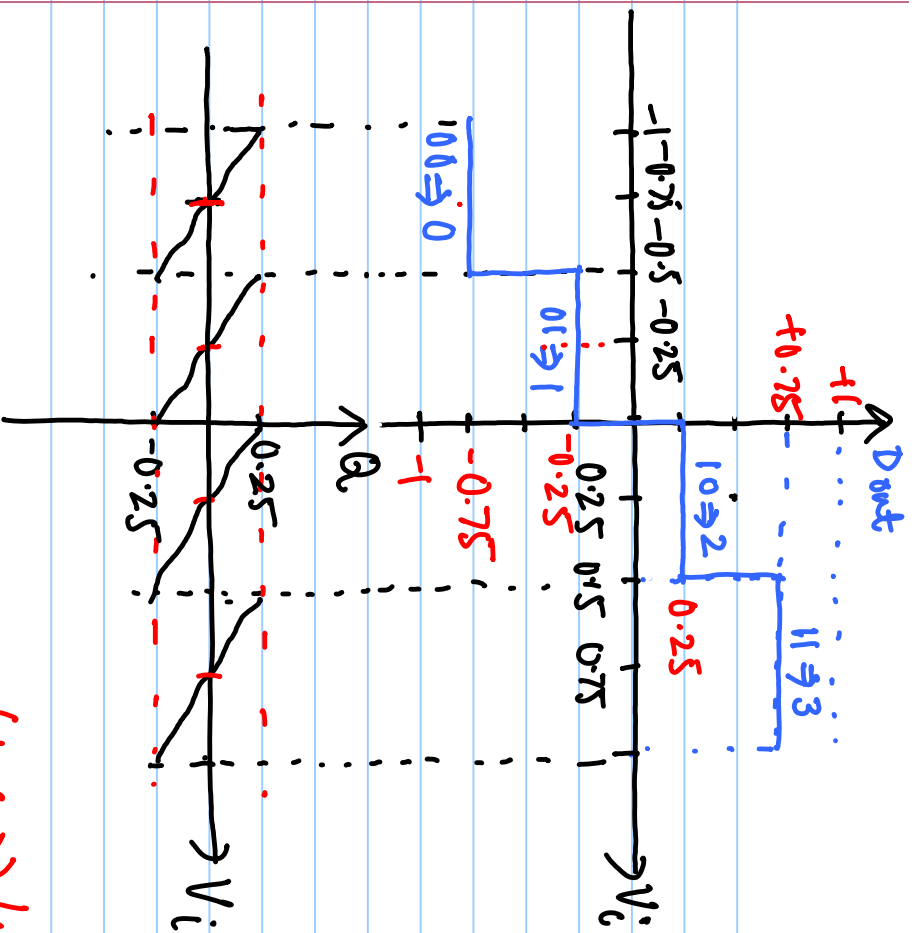

$$V_{out} = D_{out} \cdot \frac{V_{ref}}{2^2} - V_{an}$$

$$= \frac{V_{ref}}{4} (2 \cdot B_1 + 2^0 \cdot B_0) - 0.75$$

$$V_i \rightarrow D_{out} \\ (V_{out})$$

$$V_{out} = V_i + Q \Rightarrow \text{Quantization Error}$$

$$Q = V_{out} - V_i$$

$$-1 \leq V_i \leq -0.5$$

$$-1 \leq V_{out} - Q \leq -0.5$$

$$|Q| \leq \frac{LSB}{2} = \frac{(1-(-1))/4}{2} \\ = 0.25$$

$$-0.25 \leq -Q \leq 0.25$$


$$-0.25 \leq Q \leq \pm 0.25$$

Quantization error, $|Q| \leq \left(\frac{V_{ref,h} - V_{ref,l}}{2^N} \right) \frac{1}{2}$ $\Delta = \sqrt{\text{LSB size}}$

Assumption: (q_0, q_1, \dots, q_p)

- Uniform probability distribution function.
- $E[Q] = 0$
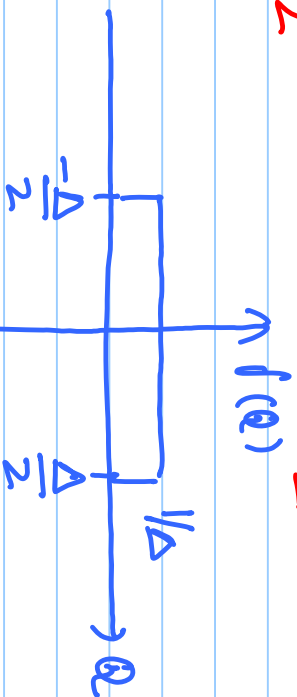
$$-\frac{\Delta}{2} \leq Q[k] \leq \frac{\Delta}{2}$$




$$\int f(Q) \cdot dQ = \int_{-\Delta/2}^{\Delta/2} \frac{1}{\Delta} \cdot dQ = 1$$

$V_i(p) \rightarrow \text{Dout}(p), Q_i(p)$

$$\text{Dout}[n] = V_i[n] + Q_i[n]$$



$V_i(0) \rightarrow \text{Dout}(0), Q_i(0)$

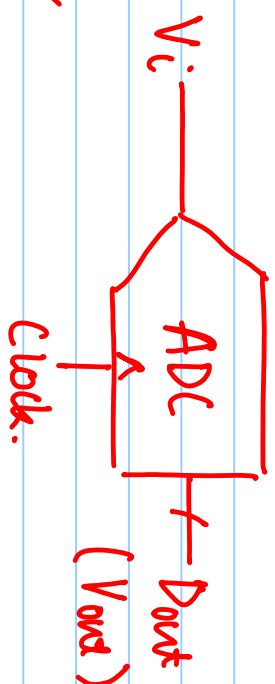$V_i(1) \rightarrow \text{Dout}(1), Q_i(1)$



$$E[Q^2] = \int_{-\Delta/2}^{\Delta/2} Q^2 \cdot \frac{1}{\Delta} \cdot dQ = \frac{1}{\Delta} \left. \frac{Q^3}{3} \right|_{-\Delta/2}^{\Delta/2} = \frac{1}{3 \cdot \Delta} \frac{2\Delta^3}{8} = \frac{\Delta^2}{12}$$

$$E[Q^2] = \Delta^2/12 \checkmark$$

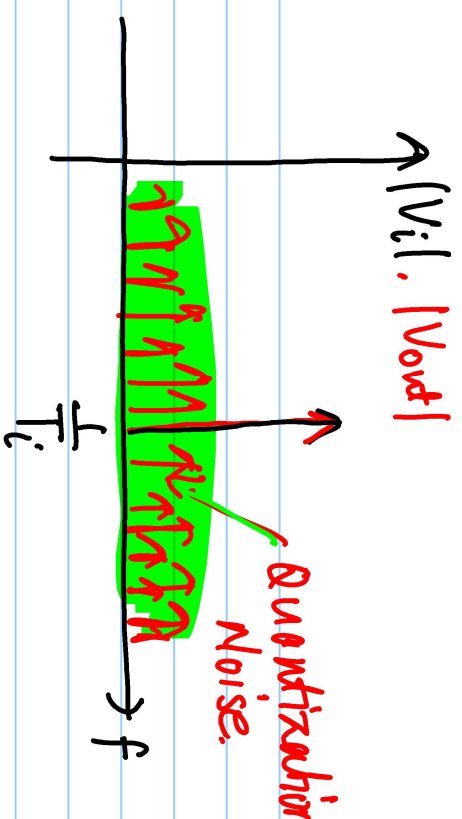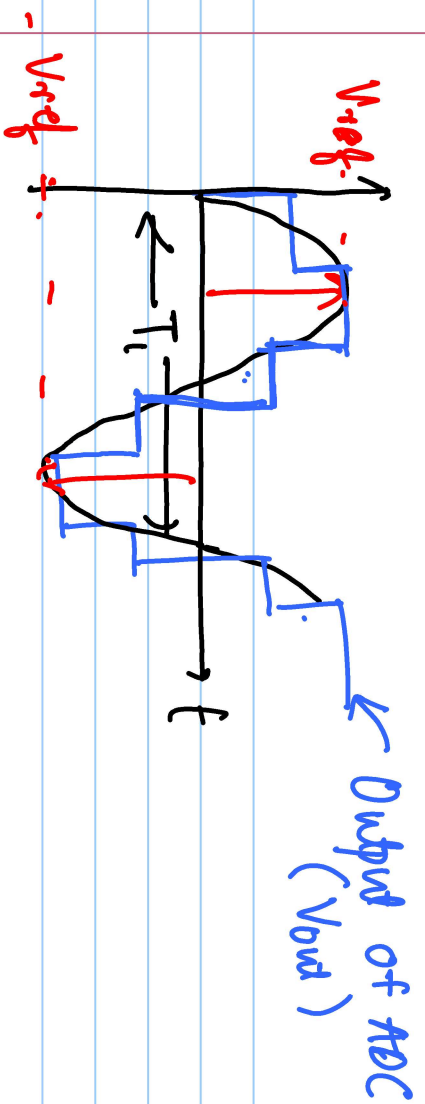

Signal to Noise Ratio (SNR) = $10 \log_{10} \left(\frac{\text{Signal Power}}{\text{Quantization Noise Power}} \right)$

(Signal-to-Quantization Ratio)

$$E[Q^2] = \frac{\Delta^2}{12} = \frac{\left[(V_{ref} - (-V_{ref})) / 2^N \right]^2}{12}$$

$$= \frac{1}{2^{2(N+1)}} \cdot \frac{1}{12} \cdot V_{ref}^2$$

Signal power = $\frac{V_{ref}^2}{2}$

SNR [dB] = $6.02N + 1.76$ ✓

$$\text{SNR} = 10 \log_{10} \left(\frac{V_{ref}^2 / 2}{\frac{V_{ref}^2}{12 \times 2^{2(N+1)}}} \right)$$

$$= 10 \log_{10} \left(\frac{3}{4 \times 2^{2N}} \right)$$

$$= 10 \log_{10} (2^{2N}) + 10 [\log_{10}(3) - \log_{10}(2)]$$

$$= 2N \times 0.301 + 10 (0.477 - 0.301)$$

$$= 6.02N + 1.76$$