
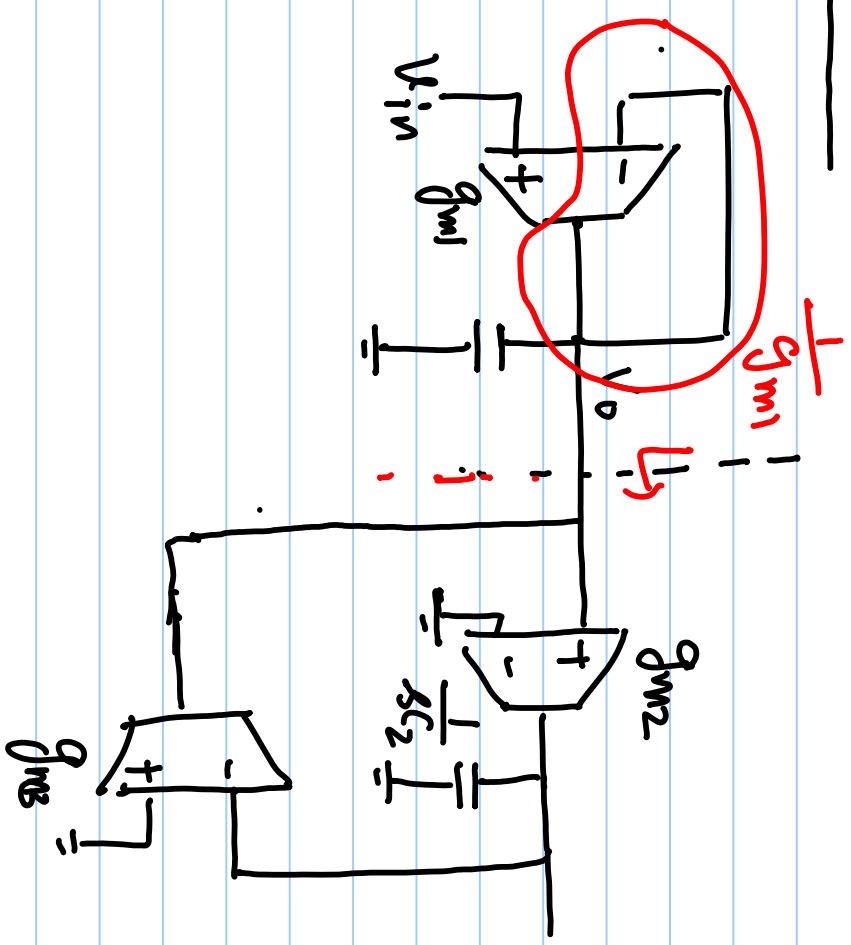



Gm-C filter

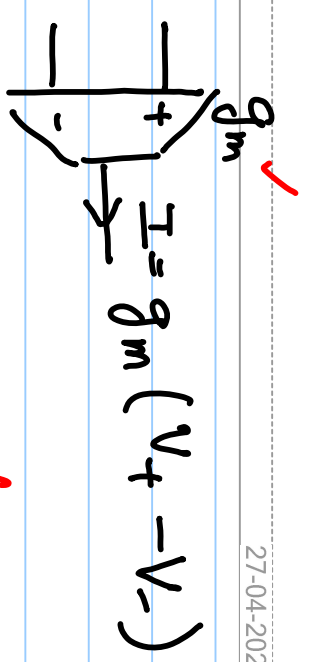

$$\frac{V_0(s)}{V_i(s)} = \frac{s (g_{m2} C_2)}{s^2 C_1 C_2 + \frac{s g_{m1} C_2}{g_{m2} g_{m3}} + 1}$$




$-g_m \quad I = -g_m (V_+ - V_-)$

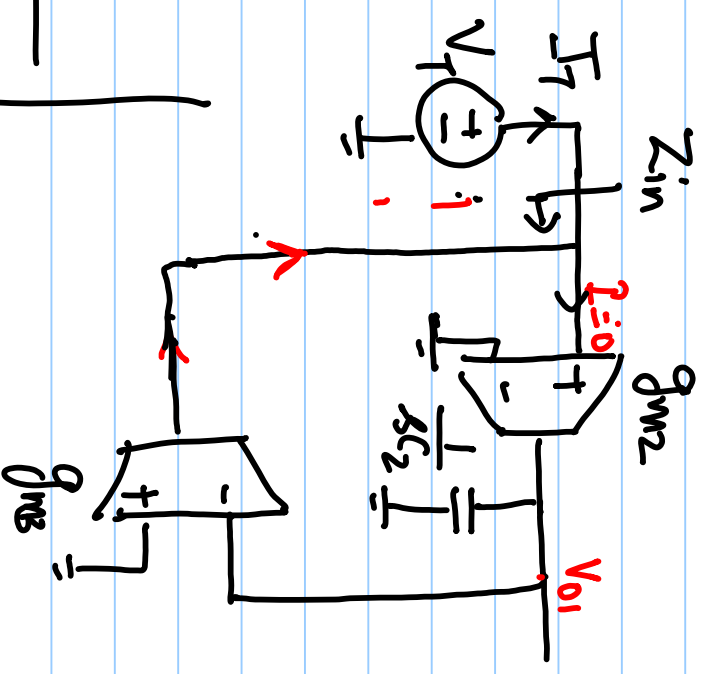

$I_T = -g_{m3} (0 - g_{m2} \frac{V_1}{s C_2})$

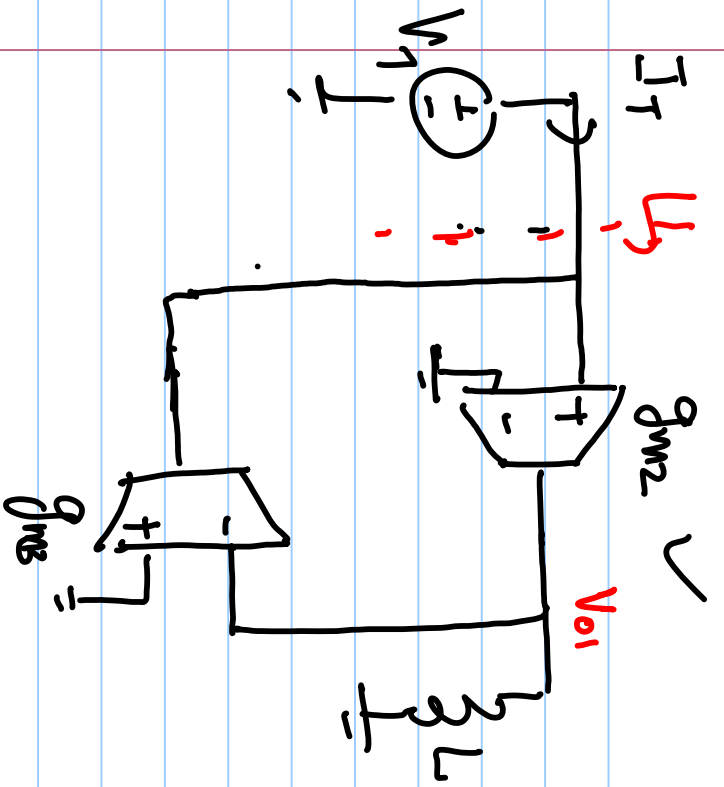$\frac{V_1}{I_T} = A = s \frac{C_2}{g_{m2} g_{m3}}$





$$\frac{V_0}{V_i} = \frac{s(R/L) \times g_{m2}/g_{m1}}{s^2 LC_1 + s \frac{L}{R} + 1}$$


$$I_T = -g_{m3} (0 - g_{m2} V_T \cdot sL)$$

$$\frac{V_T}{I_T} = \frac{1}{s (g_{m2} g_{m3} L)} = \frac{1}{sC}$$

Gyrator or Impedance inverter

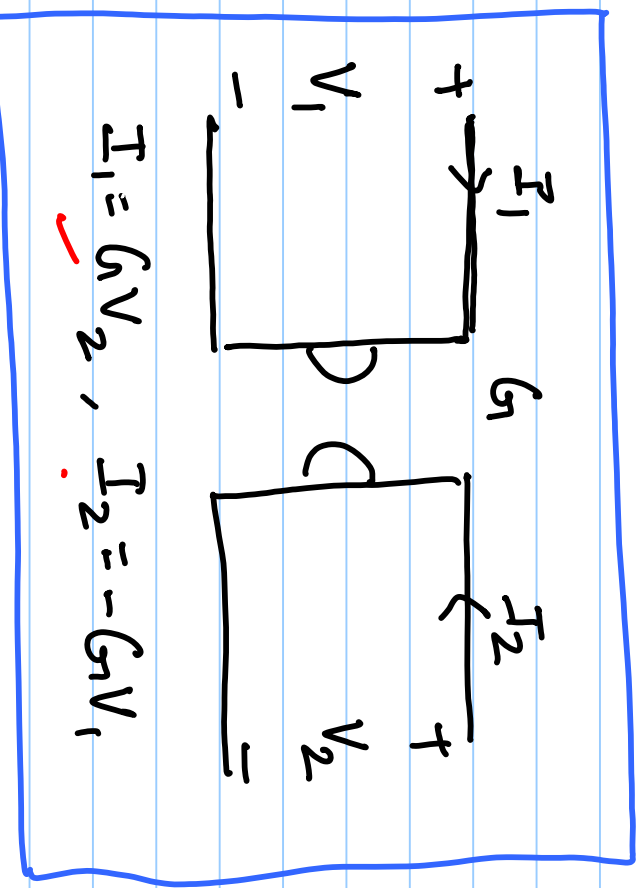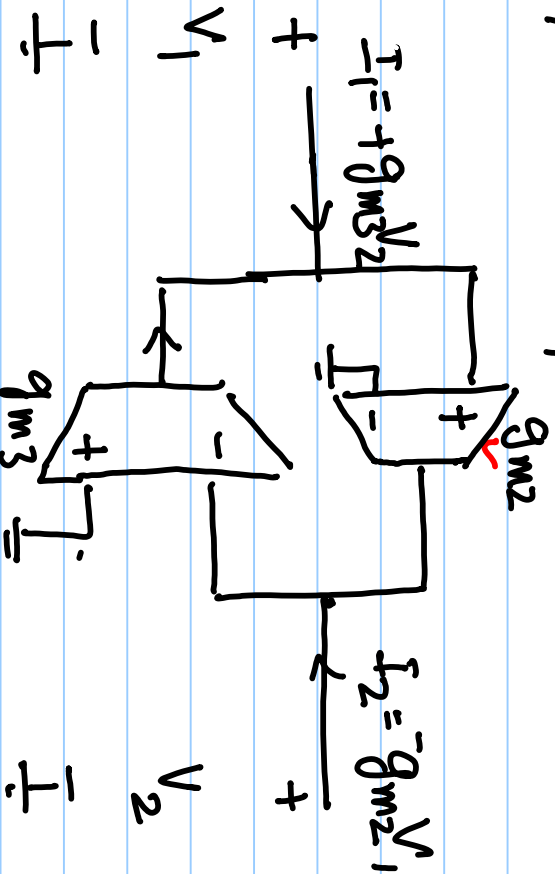


$$I_1 = G_1 V_2, \quad I_2 = -G_1 V_1$$


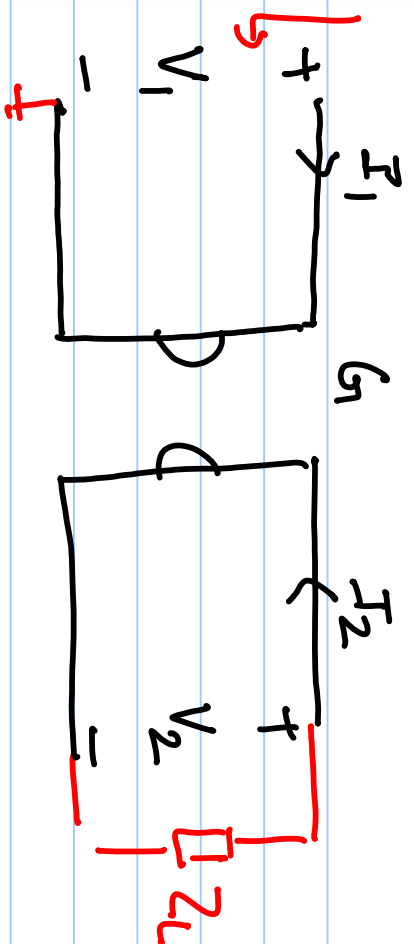


if \$Z_L = 1/sC\$

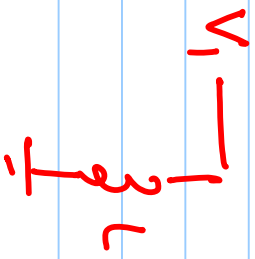
$$Z_{in} = \frac{\Delta C}{\omega^2} = sL$$


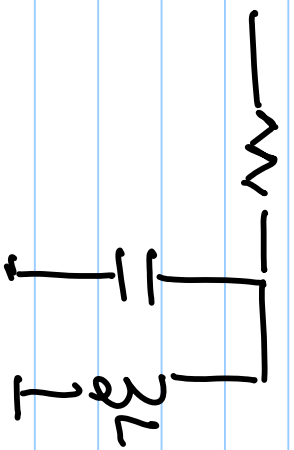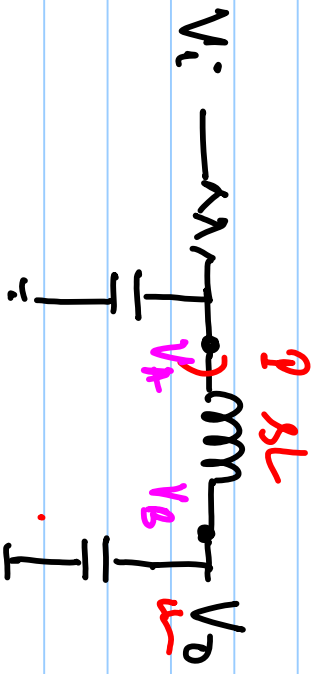
$$\frac{V_1}{I_1} = \frac{V_1}{gV_2} = \frac{V_1}{\omega(-I_2 Z_L)} = \frac{V_1}{\omega Z_L (gV_1)} = \frac{1}{\omega^2 Z_L}$$



$$I_2 = \frac{V_o - V_B}{sL}$$

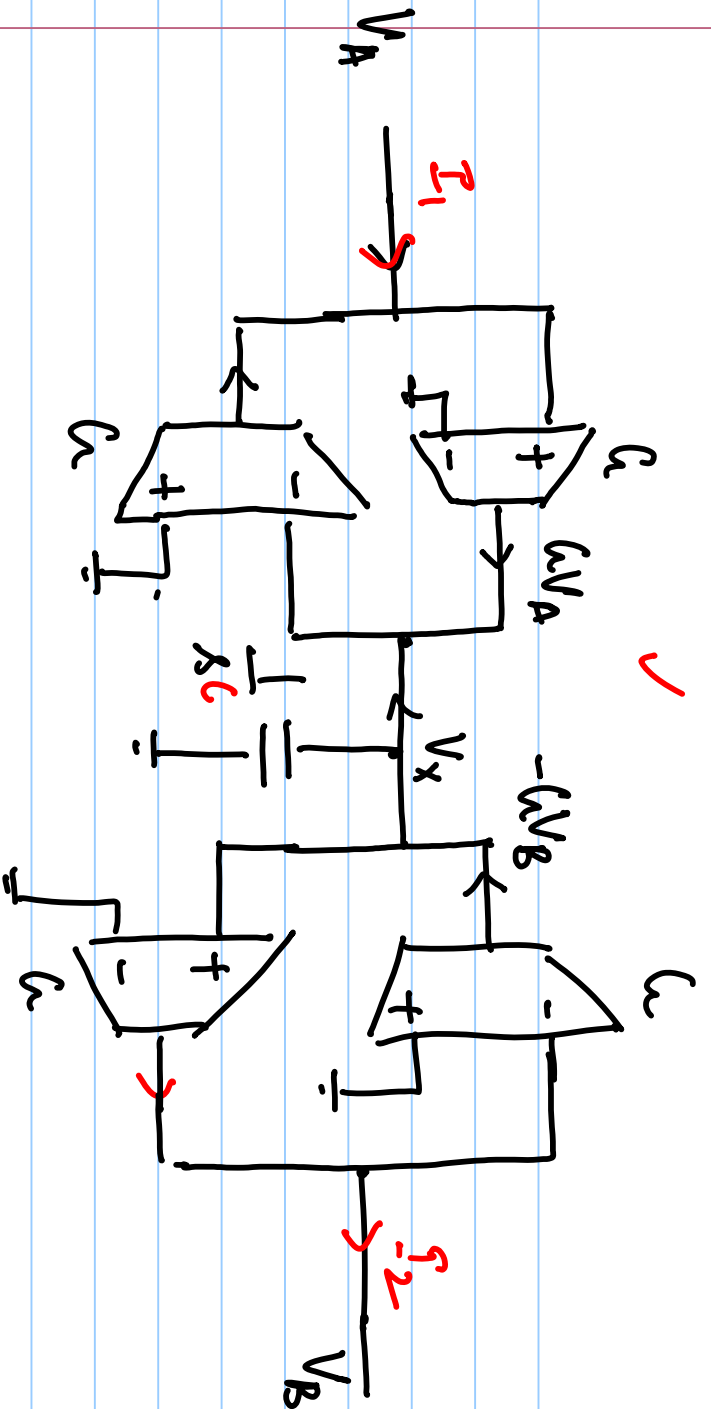


$$V_x = g_m (V_A - V_B) \frac{1}{g_m C}$$

$$I_1 = -g_m (0 - V_x) = \frac{g_m^2}{g_m C} (V_A - V_B) =$$

$$I_2 = \frac{g_m^2}{g_m C} (V_A - V_B)$$

$$\frac{V_A - V_B}{I} = \frac{1}{g_m^2 (1/g_m C)} = R \left(\frac{1}{g_m^2} \right) = R L \checkmark$$



Band Reject Filters

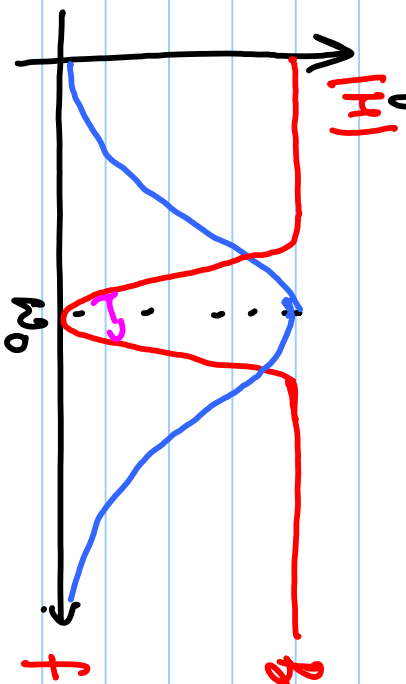

Band Reject filters

$$\frac{V_o}{V_i} = \frac{s/\omega_0 Q_p}{1 + \frac{s}{\omega_0 Q_p} + \frac{s^2}{\omega_0^2}}$$

$$H_{BRF} = 1 - H_{BPF}$$

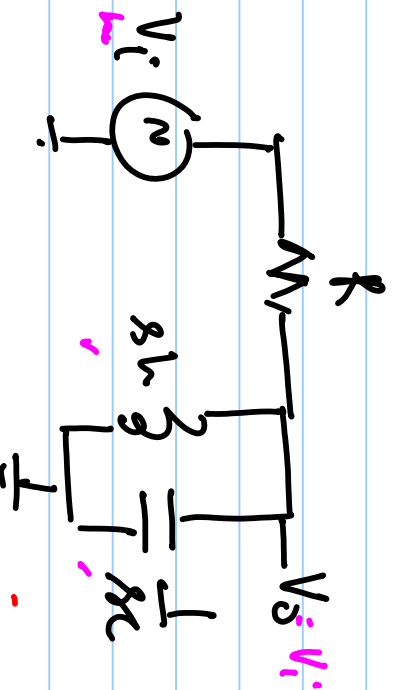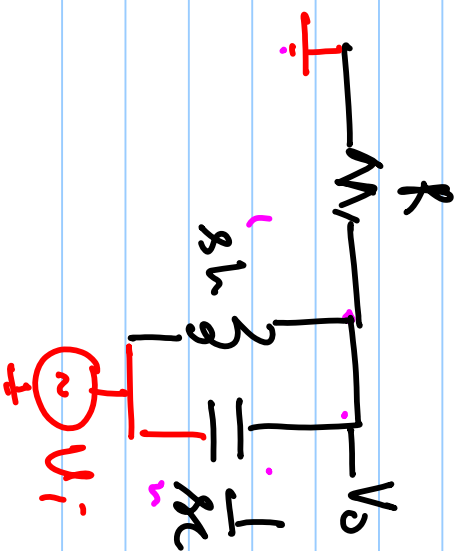

$$\frac{V_o}{V_i} = \frac{s/\omega_o Q_p}{1 + \frac{s}{\omega_o Q_p} + \frac{s^2}{\omega_o^2}}$$

$$H_{BKF} = 1 - \frac{s/\omega_o Q_p}{(1 + s/\omega_o Q_p + s/\omega_o^2)} = \frac{1 + s^2/\omega_o^2}{1 + \frac{s}{\omega_o Q_p} + \frac{s^2}{\omega_o^2}} = \frac{V_o}{V_i}$$

$$\frac{V_o}{V_i} = \frac{1 + s^2/\omega_o^2}{1 + \frac{s}{\omega_o Q_p} + \frac{s^2}{\omega_o^2}} = \frac{1 + \omega_o^2/s^2}{1 + \frac{\omega_o}{s} \cdot \frac{1}{Q_p} + \frac{\omega_o^2}{s^2}}$$

$$V_o \left(1 + \frac{\omega_o}{s} \frac{1}{Q_p} + \frac{\omega_o^2}{s^2} \right) = V_i \left(1 + \frac{\omega_o^2}{s^2} \right)$$

$$(V_o - V_i) \frac{\omega_o^2}{s^2} + V_o \frac{\omega_o}{s} \frac{1}{Q_p} + (V_o - V_i) = 0$$

$$+ \int \left(\underbrace{-V_0 + V_i}_{\omega_0} \right) \frac{\omega_0}{s} - V_0 \frac{1}{s} \left. \right\} \frac{\omega_0}{s} + V_i = +V_0$$

