
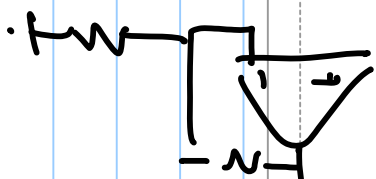


Lecture # 40

Sallen Key filter

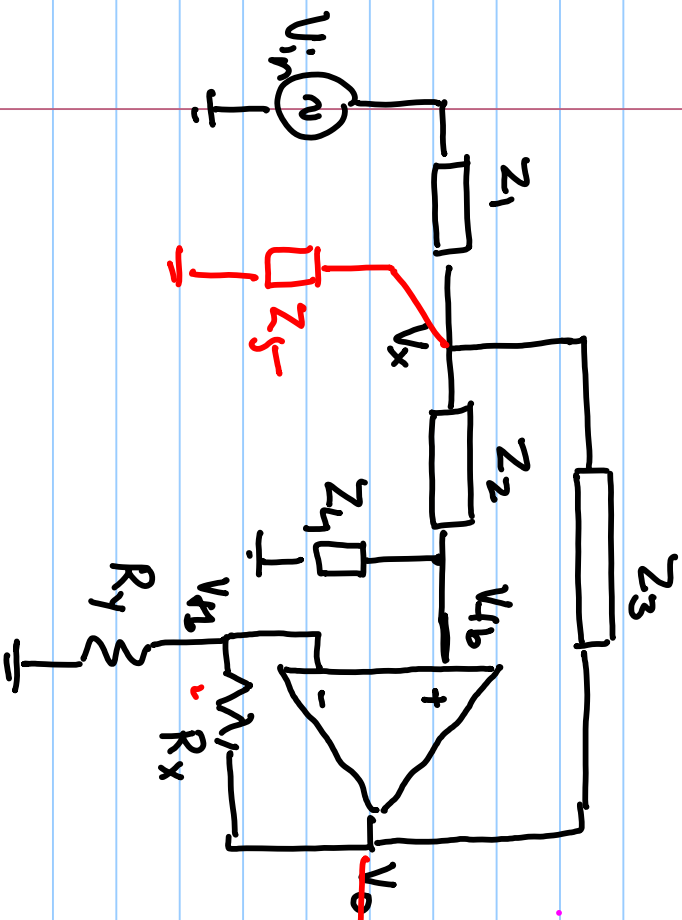

$$V_{b0} = \frac{R_y}{R_y + R_x} V_o = \alpha V_o = \frac{1}{K} V_o$$

$$\frac{V_o}{V_i} = \frac{\frac{1}{\alpha} Z_3 Z_4}{Z_3 Z_4 + Z_1 Z_4 \left(1 - \frac{1}{\alpha}\right) + Z_1 Z_3 + Z_1 Z_2 + Z_2 Z_3}$$

For unity feedback.

$$H(s) = \frac{1}{1 + \frac{s}{\omega_0 Q_p} + \frac{s^2}{\omega_0^2}}$$

$$\frac{V_o}{V_i} = \frac{Z_3 Z_4}{Z_3 Z_4 + Z_1 Z_3 + Z_1 Z_2 + Z_2 Z_3}$$

$$\frac{V_o}{V_i} = \frac{Y_1 Y_2}{Y_1 Y_2 + Y_2 Y_4 + Y_3 Y_4 + Y_1 Y_4}$$

Num: $Y_1 Y_2$ no frequency term

Den: $Y_1 Y_2 + Y_2 Y_4 + Y_1 Y_4 + Y_3 Y_4$ (s^2 term, s , s^0)

$$Y_1 = a_1, \quad Y_2 = a_2$$

$$\text{Den: } a_1 a_2 + a_1 Y_4 + a_2 Y_4 + Y_3 Y_4$$

$$Y_3 = sC_3, \quad Y_4 = sC_4$$

$$H(s) = \frac{a_1 a_2}{a_1 a_2 + s a_1 C_4 + s a_2 C_4 + s^2 C_3 C_4}$$

$$\frac{V_0}{V_i} = \frac{1}{1 + sC_4 \left(\frac{1}{a_2} + \frac{1}{a_1} \right) + \frac{s^2 C_3 C_4}{a_1 a_2}}$$

$$\frac{V_0}{V_i} = \frac{1}{1 + sC_4 (R_1 + R_2) + \frac{s^2 C_3 C_4 R_1 R_2}{a_1 a_2}}$$


$$\frac{V_o}{V_i} = \frac{\frac{1}{\alpha} Z_3 Z_4}{Z_3 Z_4 + Z_1 Z_4 \left(1 - \frac{1}{\alpha}\right) + Z_1 Z_3 + Z_1 Z_2 + Z_2 Z_3}$$

$$= \frac{K}{Z_3 Z_4} \frac{1}{Z_1 Z_2 + Z_1 Z_3 + Z_1 Z_4 (1-K) + Z_2 Z_3 + Z_3 Z_4}$$

$$= \frac{K \times 1}{s C_3 s C_4} \frac{1}{R_1 R_2 + \frac{R_1}{s C_3} + \frac{R_1}{s C_4} (1-K) + \frac{R_2}{s C_3} + \frac{1}{s^2 C_3 C_4}}$$

$$= \frac{K}{1 + s C_4 R_1 + s C_3 R_1 (1-K) + s C_4 R_2 + s^2 C_3 C_4 R_1 R_2}$$
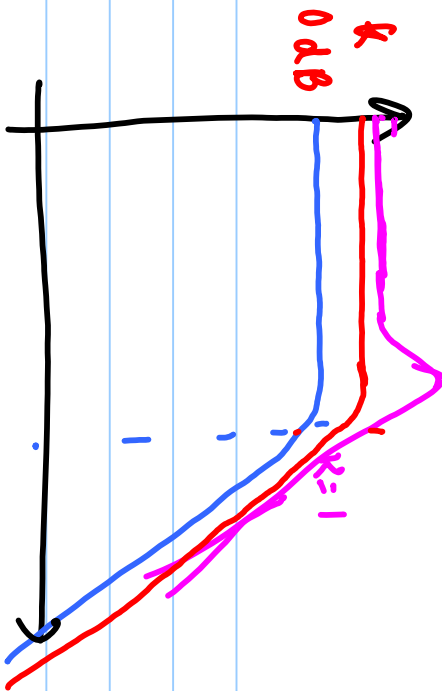
$$\frac{V_o}{V_i} = \frac{K}{1 + s [R_1 C_3 (1-K) + R_1 C_4 + R_2 C_4] + s^2 C_3 C_4 R_1 R_2}$$



$$x_1 + x_2 \leq 0$$

$$R_1 C_3 (1-k) + R_1 C_1 + R_2 C_1 > 0$$

$$1-k + \frac{C_1}{C_3} + \frac{R_2}{R_1} \frac{C_1}{C_3} > 0$$

$$k \leq 1 + \left(\frac{R_2}{R_1} + 1 \right) \frac{C_1}{C_3}$$

$$k \leq 3$$

$$x_1 = a + jb$$

$$x_2 = a - jb$$


$$x_1 + x_2 \leq 0$$

$$-\frac{b}{a} \leq 0$$

$$b > 0$$

$$C_1 = C_3$$

$$R_1 = R_2$$

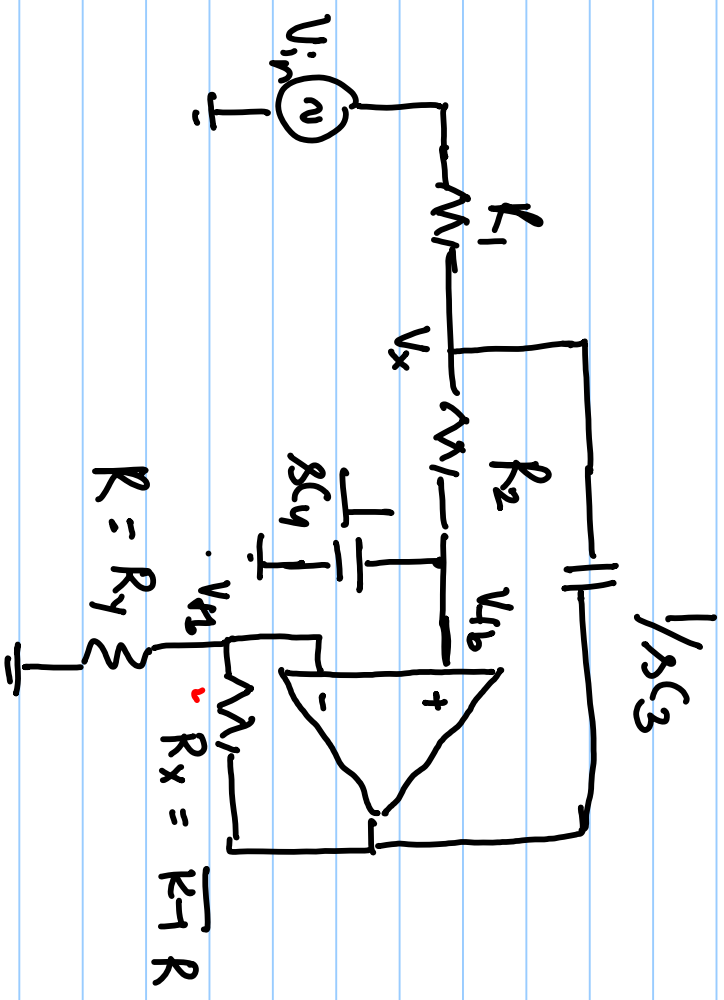


$$\frac{1}{1 + \frac{s}{\omega_0 Q_p} + \frac{s^2}{\omega_0^2}}$$

$$\omega_0 = \frac{1}{RC}$$

$$\omega_0 Q_p = \frac{1}{RC(3-k)} = \frac{Q_p}{RC}$$

$$Q_p = \frac{1}{3-k}$$
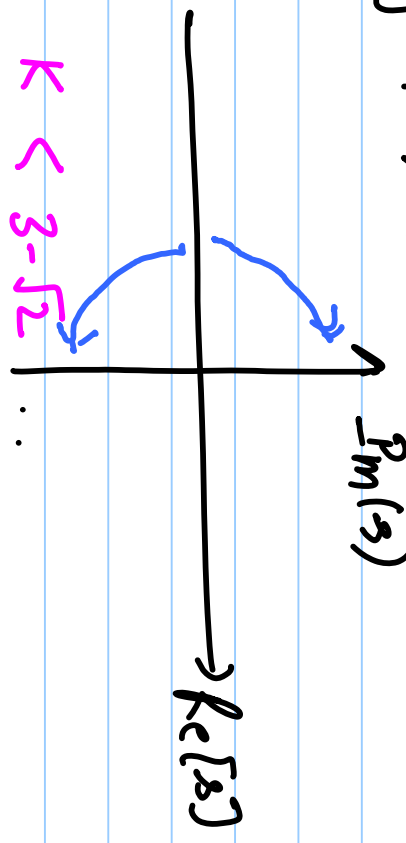
$$\frac{V_o}{V_i} = \frac{k}{1 + s[RC(1-k) + RC + kC] + s^2 R^2 C^2}$$




$$Q_p < \frac{1}{\sqrt{2}} \Rightarrow \frac{1}{3-k} < \frac{1}{\sqrt{2}} \Rightarrow k < 3 - \sqrt{2}$$

$k=1$

$$\frac{V_0}{V_i} = \frac{z_3 z_4 z_5}{z_1 z_3 z_4 + z_1 z_3 z_5 + z_1 z_2 z_3 + z_1 z_2 z_5 + z_3 z_4 z_5 + z_2 z_3 z_5}$$


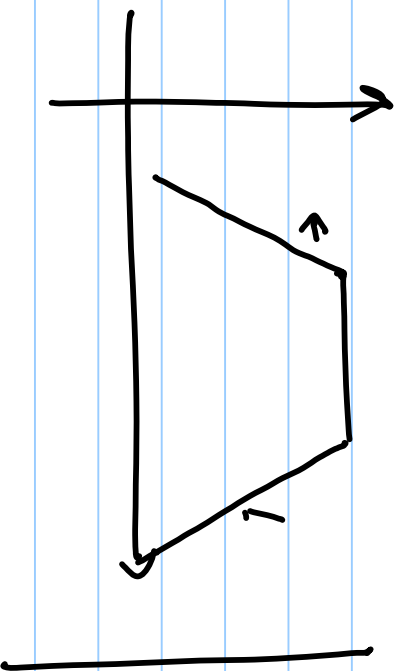
$$= \frac{Y_1 Y_2}{Y_2 Y_5 + Y_2 Y_4 + Y_4 Y_5 + Y_3 Y_4 + Y_1 Y_2 + Y_1 Y_4} \quad = \quad \frac{(A)P}{(B)P}$$



$$Y_1 = G_1, \quad Y_2 = S C_2$$

$$Y_3 = S C_3, \quad Y_4 = G_4, \quad Y_5 = S C_5$$

Butterworth filters

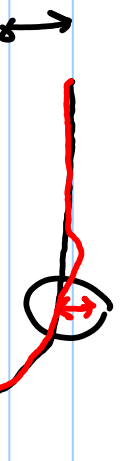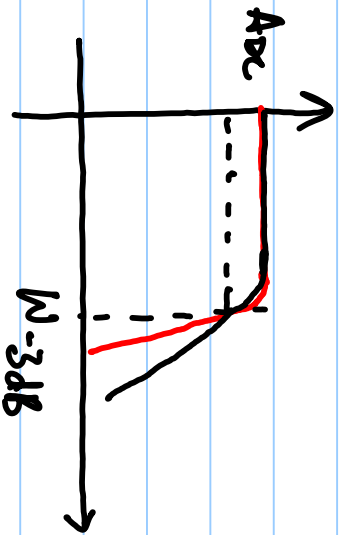

$$H(s) = \frac{1}{D(s)}$$

$$|H(j\omega)|^2 = H(j\omega) H(j\omega)^*$$

$$= H(j\omega) H(-j\omega)$$

= Even fn. of ω .

$$H(s) = \frac{1}{\alpha_0 + \alpha_1 s + \alpha_2 s^2 + \dots}$$

$$= \frac{1}{\sum_{k=0}^{\infty} \alpha_{2k} (s^2)^k + \sum_{p=0}^{\infty} \alpha_{2p+1} s^{2p+1}}$$

$$|H(j\omega)|^2 = \frac{1}{\underbrace{\sum_{k=0}^{\infty} \alpha_{2k} (-\omega^2)^k + \sum_{p=0}^{\infty} \alpha_{2p+1} (j)^{2p+1} \omega^{2p+1}}^2}$$

$$= \frac{1}{\left[\sum_{k=0}^{\infty} \alpha_{2k} (-1)^k \omega^{2k} + j \sum_{p=0}^{\infty} \alpha_{2p+1} (-1)^p \omega^{2p+1} \right]^2}$$

$$= \frac{1}{\left[\sum_{k=0}^{\infty} \alpha_{2k} (-1)^k \omega^{2k} \right]^2 + \left[\sum_{p=0}^{\infty} \alpha_{2p+1} (-1)^p \omega^{2p+1} \right]^2}$$

$$(\omega^{2p+1})^2 = \omega^{2(p+q)+2}$$

$$|H(j\omega)|^2 = \frac{1}{1 + K_1 \omega^2 + K_2 (\omega^2)^2 + \dots + K_{n-1} (\omega^2)^{n-1} + K_n (\omega^2)^n}$$

"maximally flat"

$$|D(j\omega)|^2$$

