
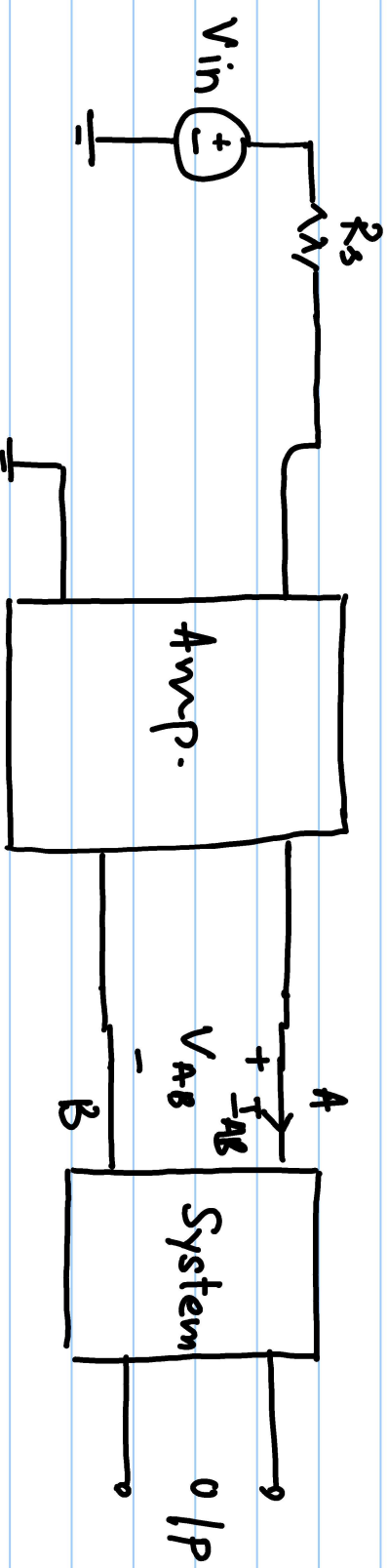



Lecture # 2

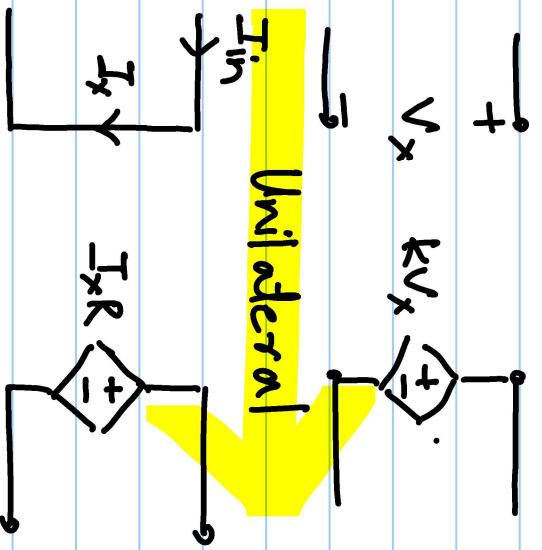


VCVS:




CCVS

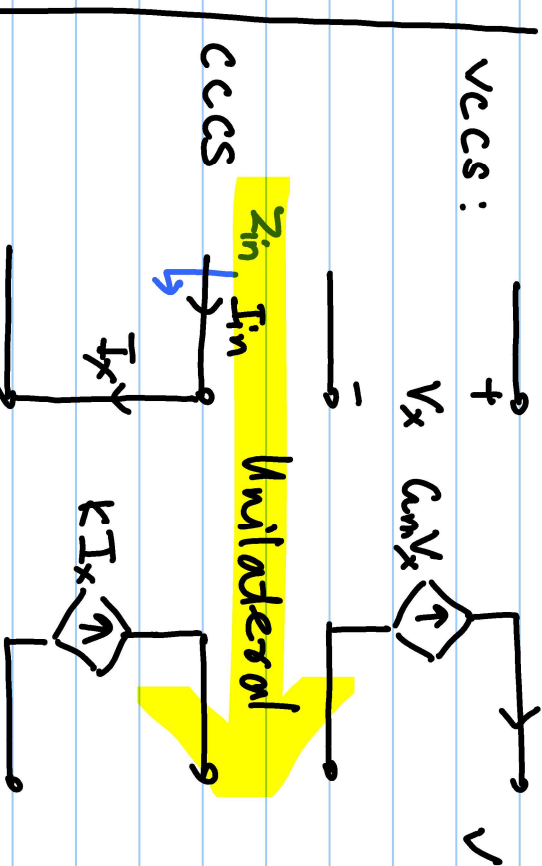

VCCS:

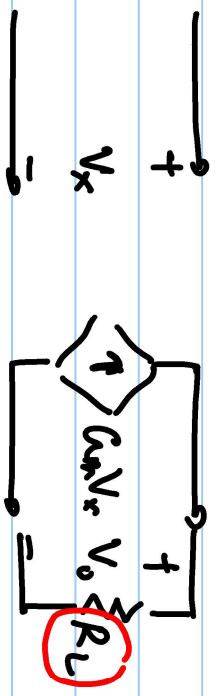

VCCS:

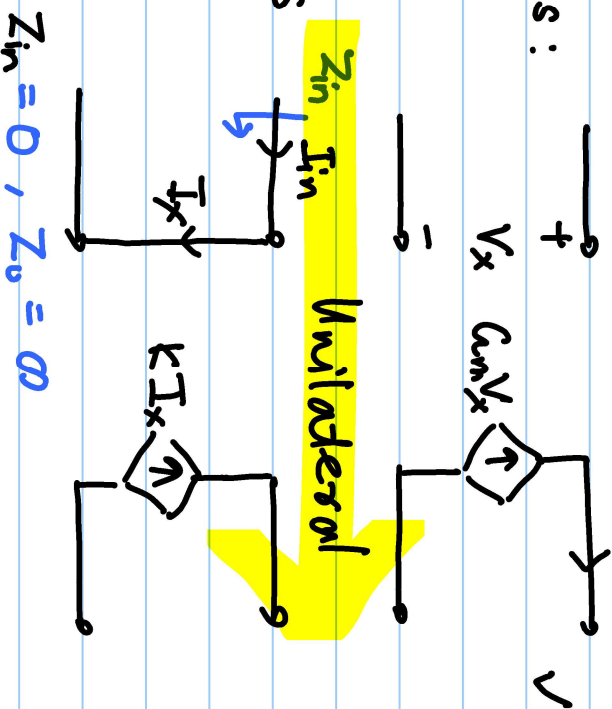

CCCS


$$V_0 = (G_m V_x) R_L = (G_m R_L) V_x$$

$$I_0 = G_m V_x = \frac{V_x}{(1/G_m)} = \frac{V_x}{R_x}$$

$Z_{in} = 0, Z_o = \infty$


$$V = f(I)$$
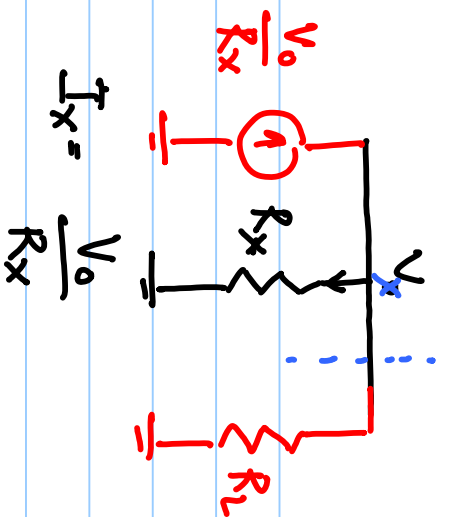
$$V_x = \frac{V_o}{R_x} (R_x \parallel R_L)$$




$$I_x = \frac{V_o}{R_x}$$

$$V_x = \frac{V_o}{R_x} R_x = V_o$$

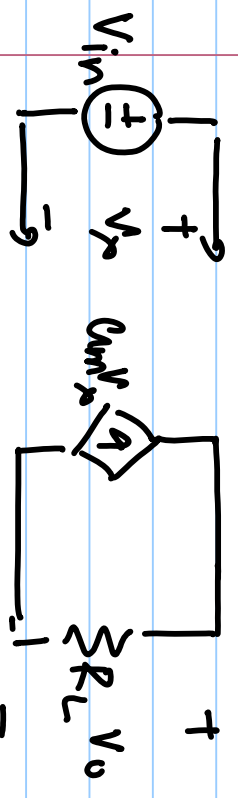


$$V_o = (g_m V_{in}) R_L$$

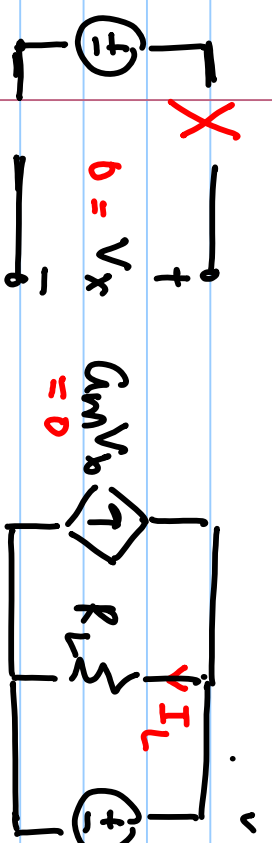


$$V_o = (g_m V_x) R_L \longrightarrow V_x = V_i$$

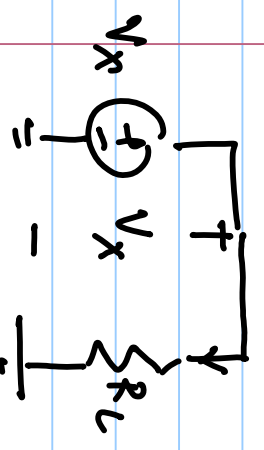
$$I_L = \frac{(g_m V_x) R_L}{R_L} = g_m V_x$$




$$I_L = \frac{V_x}{R_L}$$

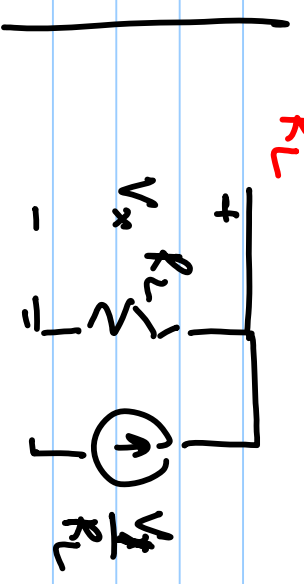

$$V_x = V_i$$

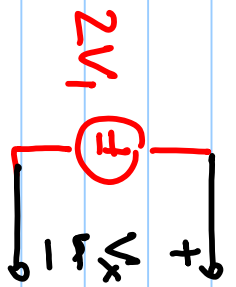

$$gmV_x = 2gmV_1$$

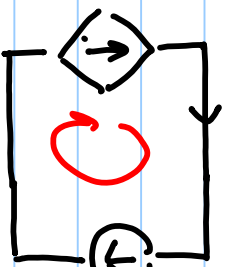


$$I_1 = gmV_1 \neq 0$$


$$gmV_x = I_1 = gmV_1 \quad \text{---(1)}$$

$$V_x = V_1$$

$$V_x = 0 \quad \text{---(2)}$$

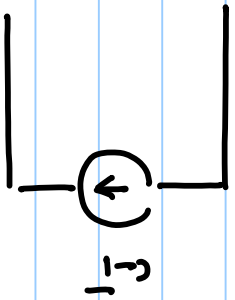

VCVS

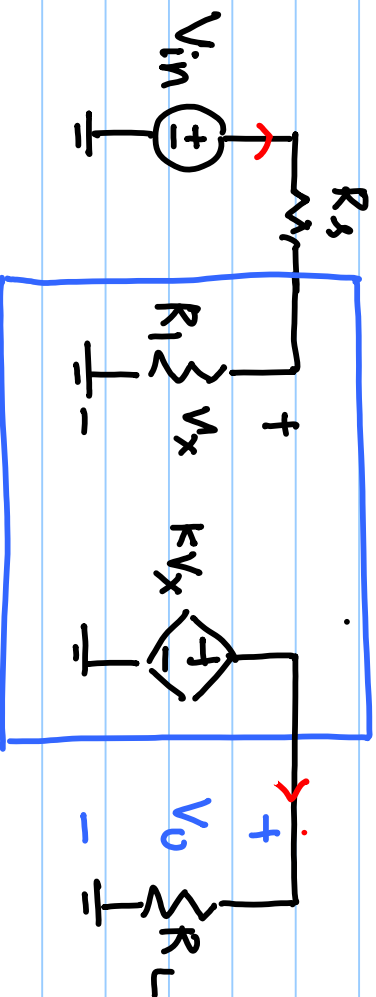

$$V_x = \frac{R_1}{R_1 + R_s} V_{in}$$

$$V_o = \frac{k R_1}{R_1 + R_s} V_{in}$$


$$P_{in} = \frac{V_{in}^2}{R_s + R_1}, \quad P_o = k^2 \frac{R_1^2}{(R_1 + R_s)^2} V_{in}^2 \times \frac{1}{R_L}$$

$$\frac{P_o}{P_{in}} = \frac{k^2 R_1^2 / R_L (R_1 + R_s)^2}{1 / (R_s + R_1)} = \frac{k^2 R_1^2}{R_L (R_1 + R_s)}$$

$$\frac{P_o}{P_{in}} = k^2 \frac{R_1^2}{R_L(R_1 + R_s)}$$



When $R_1 \rightarrow \infty$, $P_{in} = 0$, $P_o = \frac{k^2 V_{in}^2}{R_L}$ #1

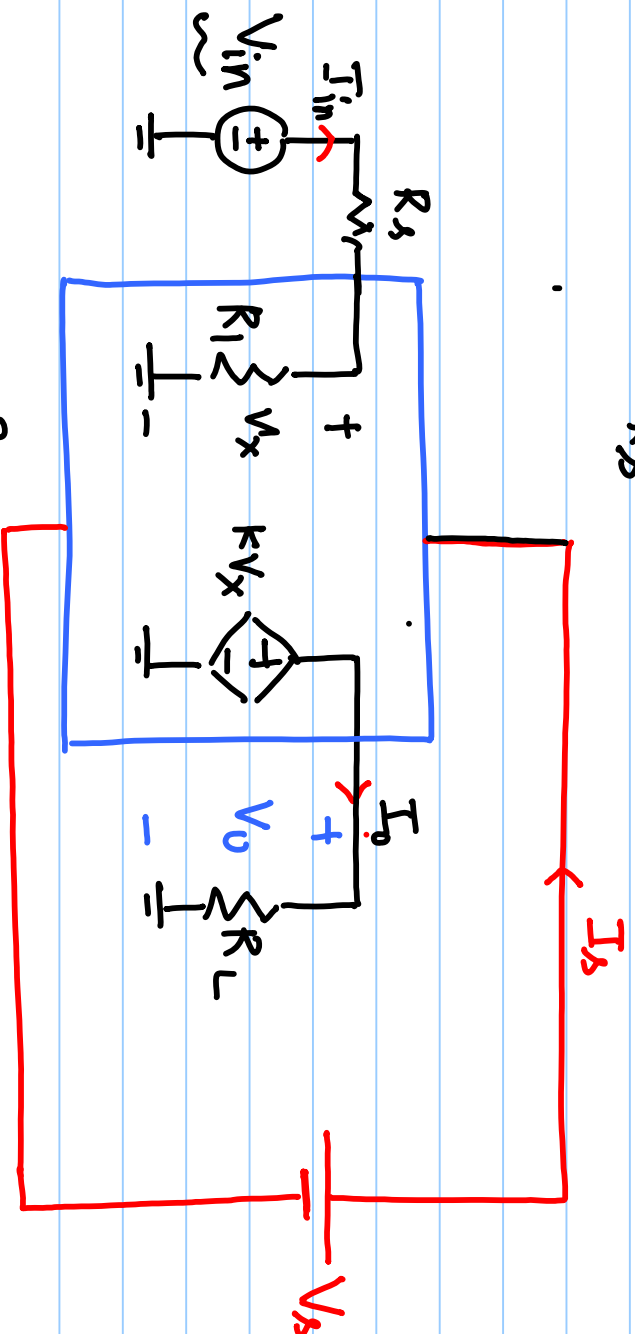$R_1 \rightarrow 0$, $P_{in} = \frac{V_{in}^2}{R_s}$, $P_o = 0$ #2



— $V_{in} I_{in} + V_s I_s = I_o^2 R_L$

— $V_{in} I_{in} < I_o^2 R_L$

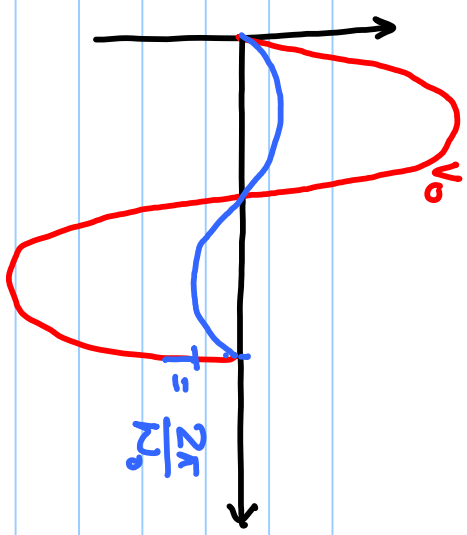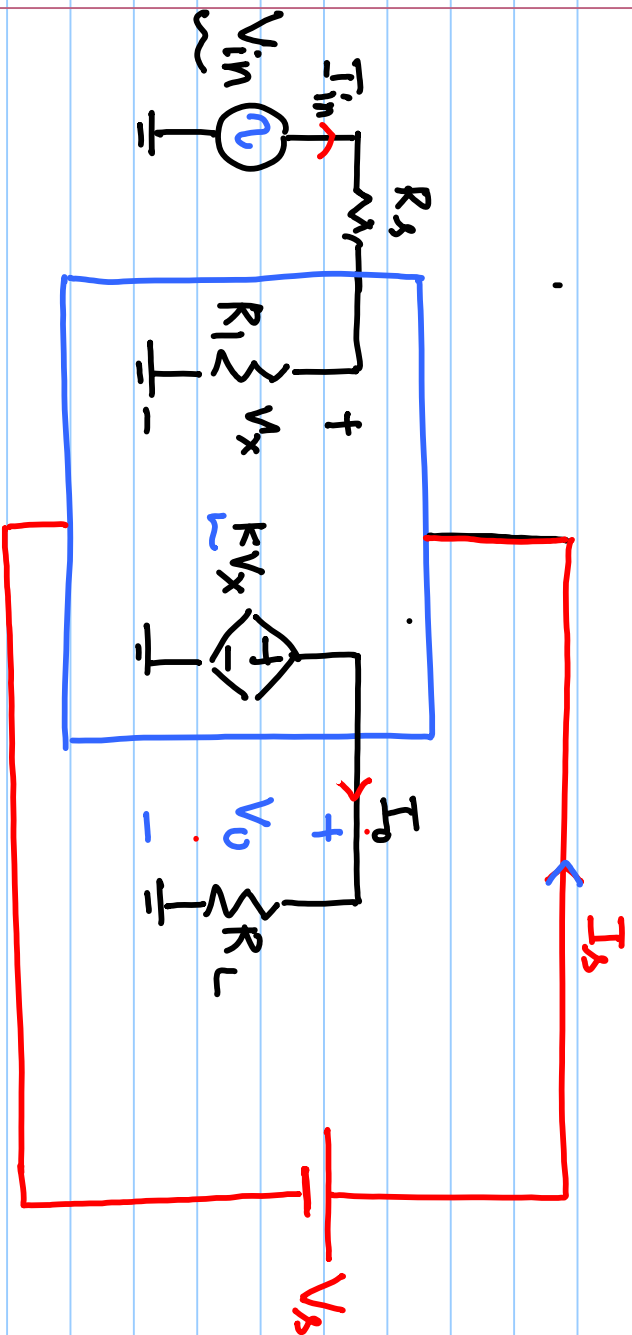

- Power drawn from i/p supply at ω_0

$$V_{in} = A \sin(\omega_0 t)$$

$$P_{in} = \frac{A^2}{2(K_1 + R_3)}$$

- Power supplied to the load R_L at ω_0

$$V_o = \frac{R_1}{R_1 + R_3} \cdot K \cdot A \sin(\omega_0 t)$$

$$P_o =$$



$$V_o = f(V_{in}, V_s)$$