
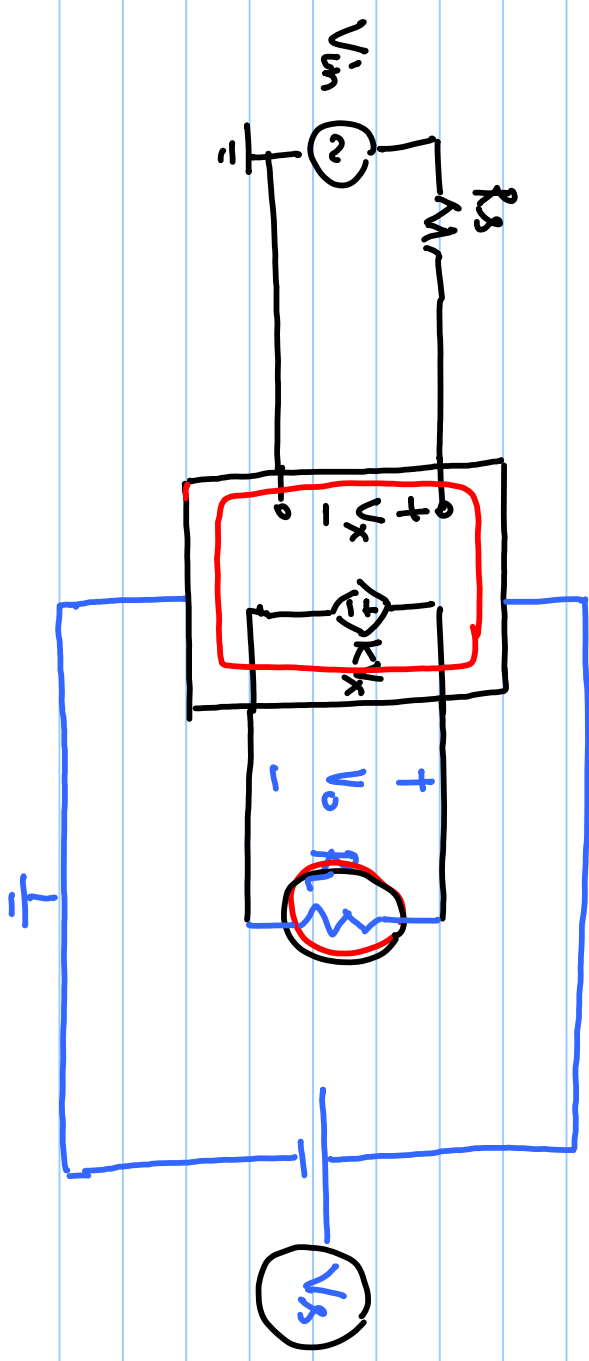


# lecture # 3

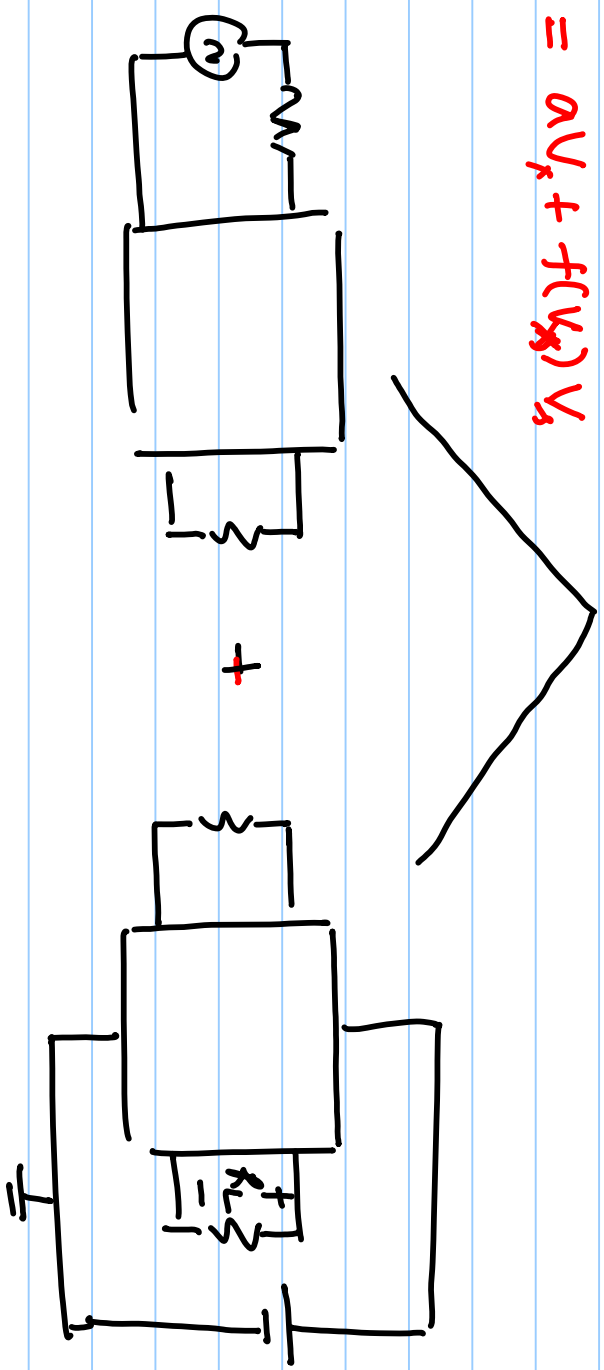

$$V_o = aV_x + bV_s = aV_x + f(V_x)V_s$$

$$V_{in} = A \sin(\omega t)$$




$$V_o = \alpha V_x + f(V_x) V_s = \alpha V_x + \underbrace{R V_x \cdot V_s}_{\text{MO}} = \frac{1}{2} V_x + 4 V_x \cdot (10V)$$

$$f(V_x) = R_1 V_x$$


$$V_o = f(V_x, V_s)$$



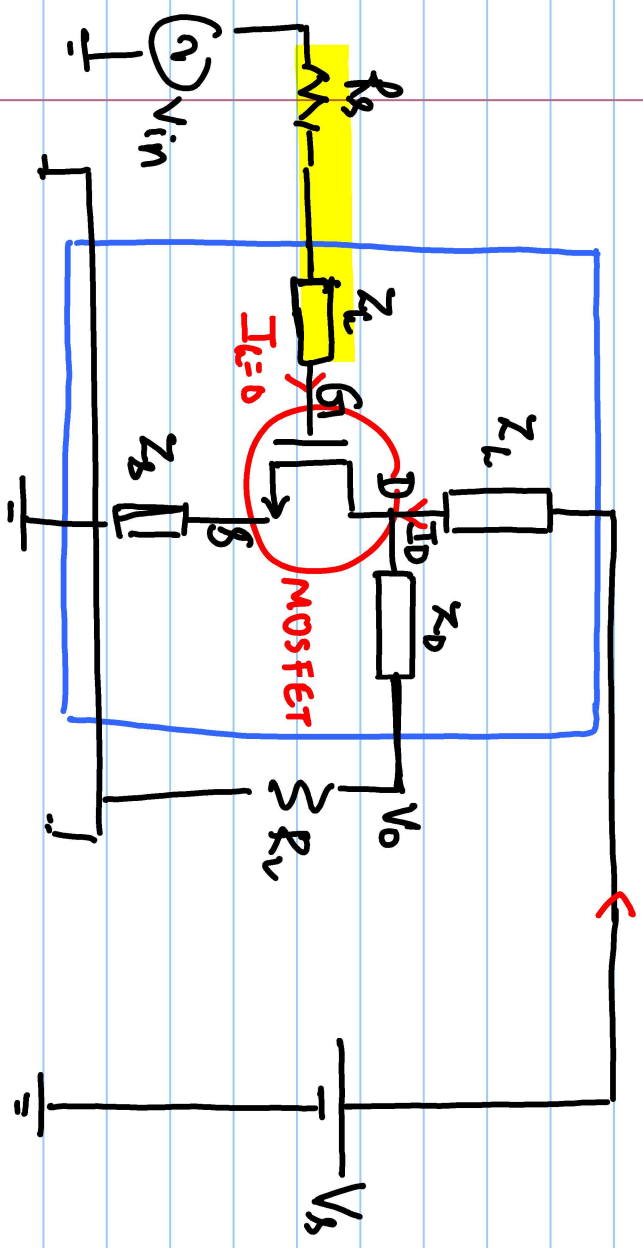
$$= \underbrace{\alpha_0 (\alpha V_x + \beta V_s)} + \alpha_1 (\alpha V_x + \beta V_s)^2 + \dots$$




$$V_o = f(V_{in}, V_s)$$

$$I_{DS} = f(V_{in}, V_s)$$

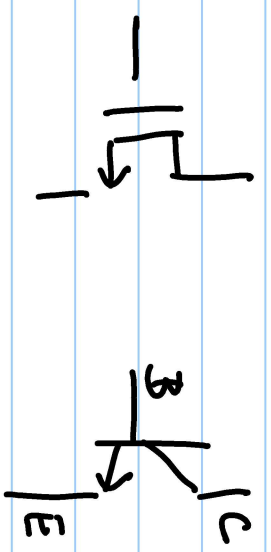


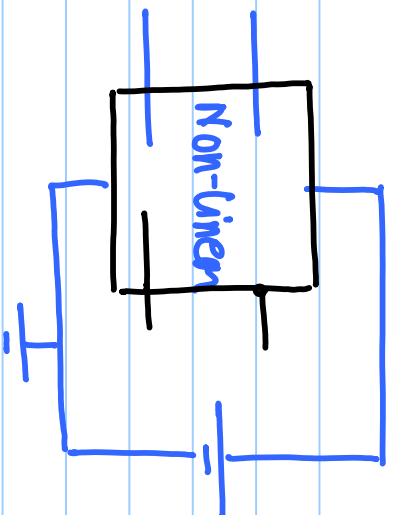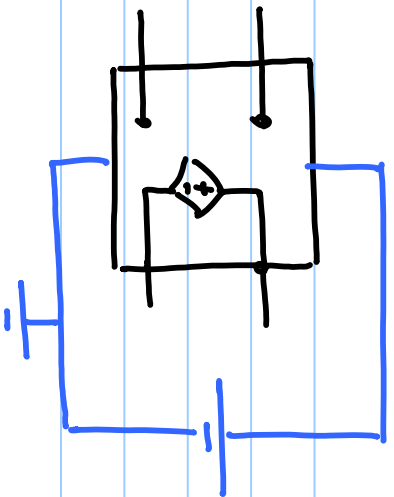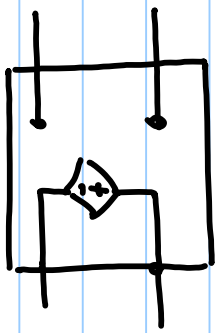





$$V_o = f(V_{in}, V_s)$$

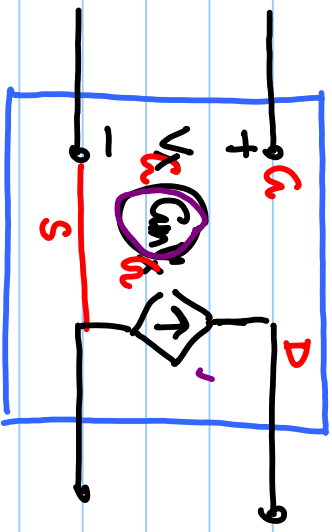

MOSFETs

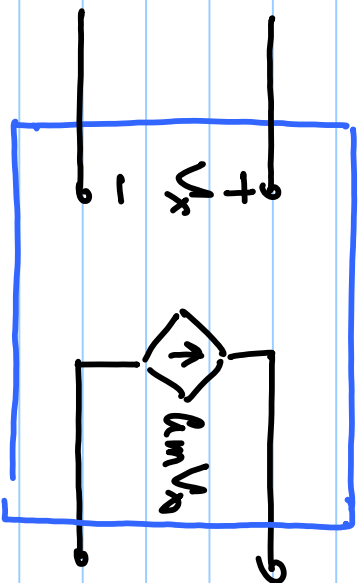

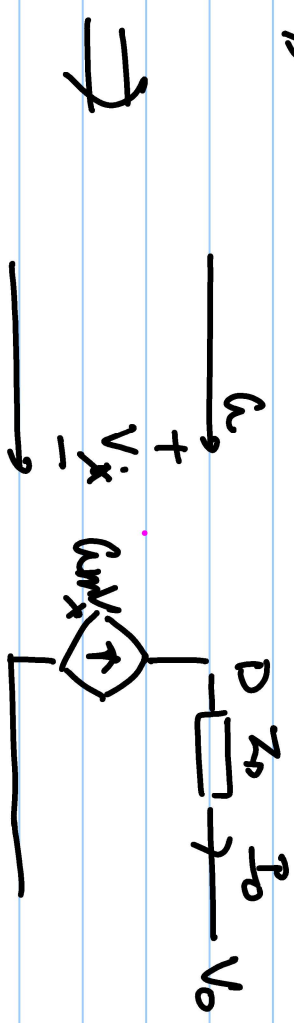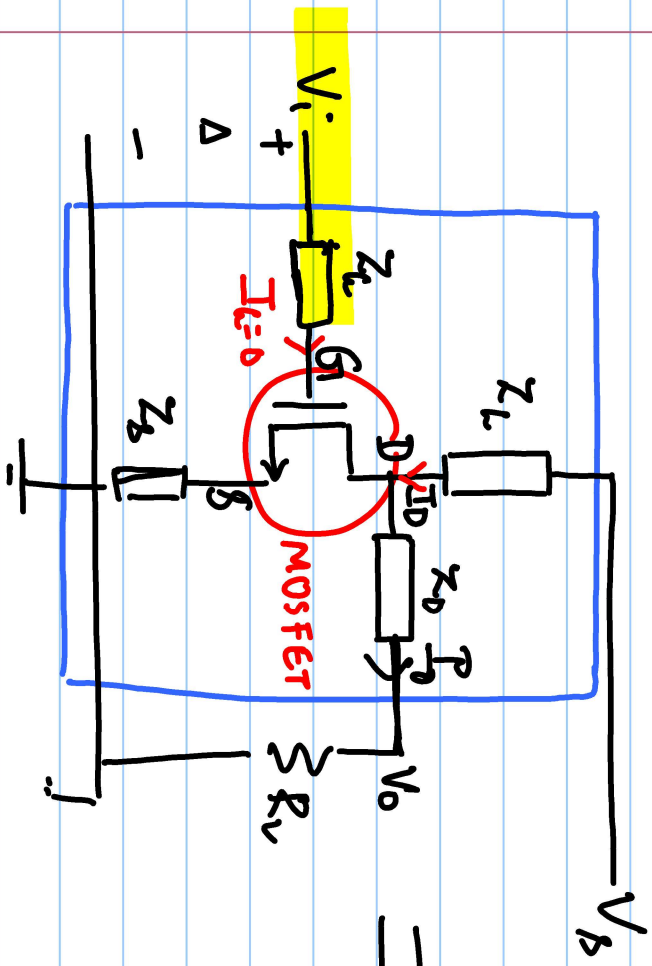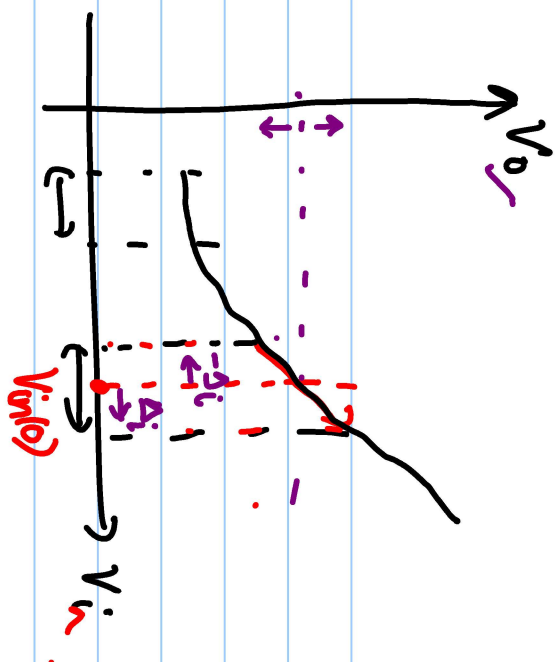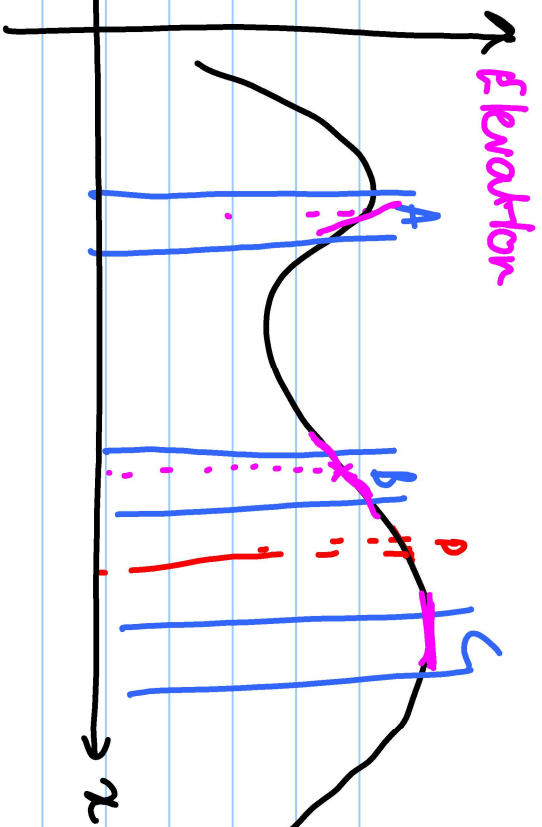- Non-linear elements are required to implement voltage/power gain
- for analysis, non-linear circuit can be simplified as VCCS.
- Power is supplied by supply voltage.
- $g_m$  depends on  $i_{fp}$  &  $o_{fp}$  voltages.





$$I_0 = g_m V_x = g_m \Delta$$

$$I_0 = f(V_x, V_B) \quad \checkmark$$


$$\begin{aligned}
 V_{I_0} &= a_0 (\alpha V_i + \beta V_s) + a_1 (\alpha V_i + \beta V_s)^2 + \dots \\
 &= a_0 (\alpha \Delta + \beta V_s) + a_1 (\alpha \Delta + \beta V_s)^2 + \dots \\
 &= a_0 (\alpha \Delta + \beta V_s) + a_1 (\alpha^2 \Delta^2 + 2\alpha \beta \Delta V_s + \beta^2 V_s^2) + \dots
 \end{aligned}$$
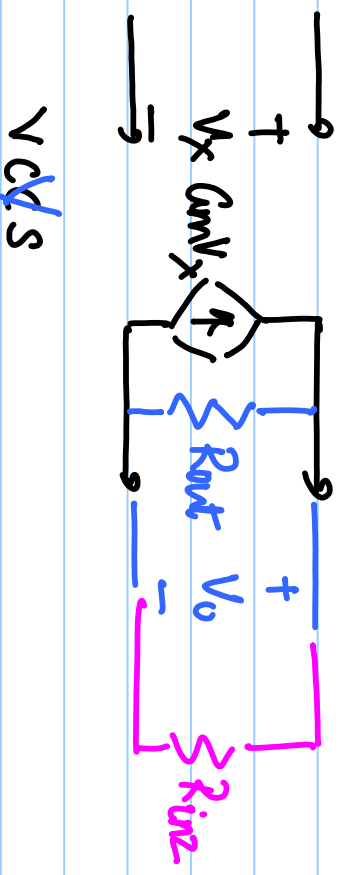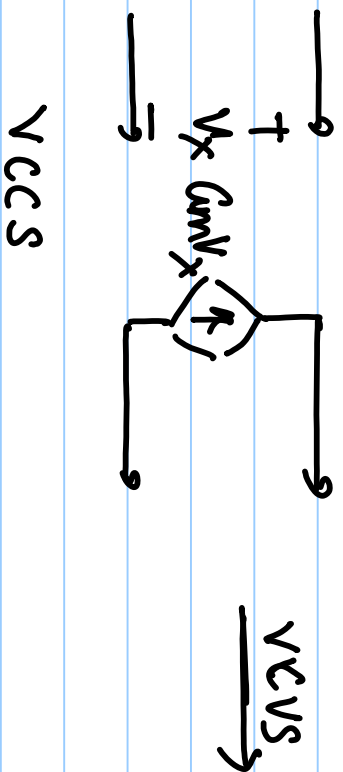
$$I_0 = \underbrace{(a_0 \alpha + a_1 2\alpha \beta V_s)}_{G_m} \Delta + \dots$$



$$\begin{aligned}
 V_o &= (G_m R_{out}) V_x \\
 &= K \cdot V_x
 \end{aligned}$$
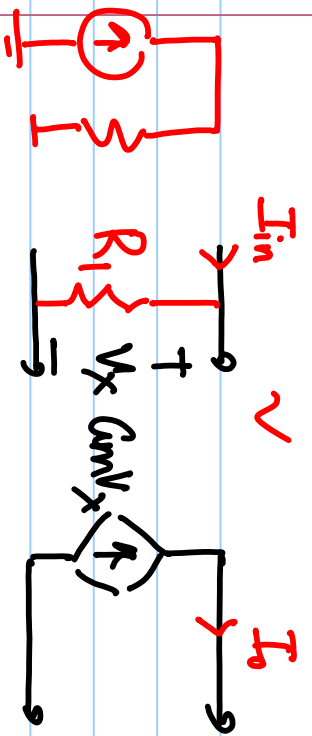
$$\begin{aligned}
 &= G_m (R_{out} \parallel R_{in2}) V_x \\
 &\approx G_m R_{out} V_x
 \end{aligned}$$




VCCS


$$I_o = g_m (I_{in} \cdot R_1)$$

$$= (g_m R_1) I_{in}$$

$$= k I_{in}$$

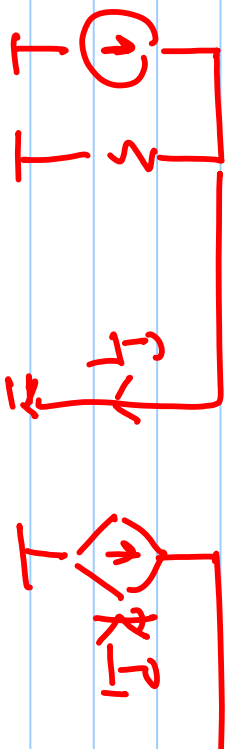

V

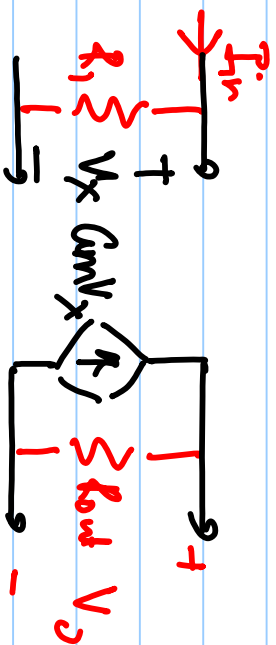

VCCS

$$V_o = g_m (I_{in} \cdot R_1) R_{out}$$

$$= (g_m R_1 R_{out}) I_{in}$$

$$= k I_{in}$$