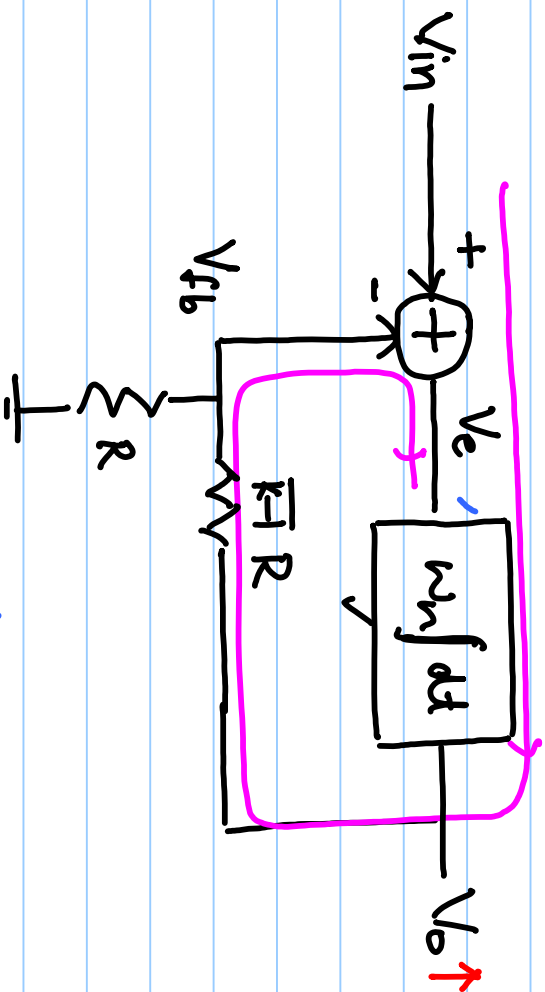


Lecture # 5



"Negative feedback"

$$V_{fb} = \frac{R}{R + K \int R} V_o = \frac{V_o}{K}$$

$$V_e = V_{in} - V_{fb}$$

$$V_e = V_{in} - \frac{V_o}{K}$$

$$V_o = k_n \int V_e dt$$


$$V_o = k_n \int \left(V_{in} - \frac{V_o}{K} \right) dt \quad \checkmark$$

$$\frac{dV_o}{dt} = k_n \left(V_{in} - \frac{V_o}{K} \right)$$

$$\frac{dV_o}{dt} + \frac{k_n}{K} V_o = k_n \cdot V_{in} \quad \checkmark$$

$$\frac{d}{dt} \left(V_o e^{k_n t / K} \right) = k_n V_{in} \cdot e^{k_n t / K} \left| \begin{array}{l} V_o = e^{-k_n t / K} \int k_n \cdot V_{in} e^{+k_n t / K} dt + B \cdot e^{-k_n t / K} \end{array} \right.$$

for $t < 0$, $V_{in} = 0$, $V_o = 0$

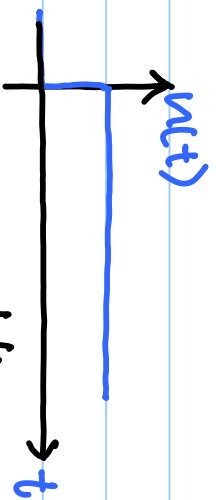


$t = 0$, $V_{in} = v(t) \times V_{in}(0)$

$$V_o = e^{-\omega_n t/k} \int \omega_n \cdot e^{+\omega_n t/k} dt + Q e^{-\omega_n t/k}$$

$$= e^{-\omega_n t/k} \frac{\omega_n \cdot e^{+\omega_n t/k}}{\omega_n/k} + Q e^{-\omega_n t/k}$$

$$V_o = k + Q e^{-\omega_n t/k}$$

$$\left| \frac{dV_o}{dt} = k \cdot e^{-\omega_n t/k} \times \frac{+\omega_n}{k} = \omega_n e^{-\omega_n t/k} \right.$$

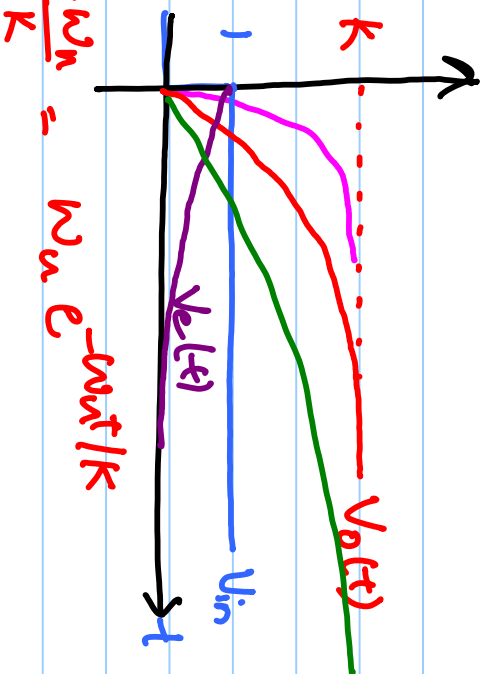

at $t=0$, $V_o = 0$

$$\Rightarrow 0 = k + Q \Rightarrow Q = -k$$

$$V_o = k - k e^{-\omega_n t/k}$$


$$V_o = k V_{in}(0) (1 - e^{-\omega_n t/k})$$

at $t \rightarrow \infty$, $V_o = k$

$$V_o(t) = V_{in} - \frac{V_o - V_{in}}{\omega_n} e^{-\omega_n t/k}$$

- Does final value of V_o depend on integrator coefficient ω_n ?

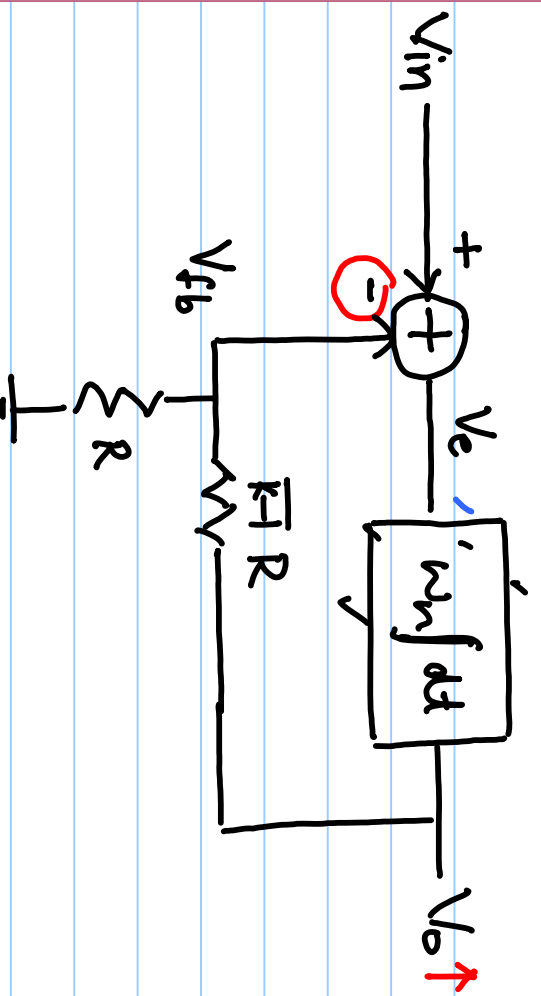- Does V_o depend on ω_n in steady state?




$$V_c = \frac{1}{C} \int i_c \cdot dt$$

$$i_c = C \frac{dV_c}{dt}$$

$$V_c = L \frac{di_L}{dt}$$

$$i_L = \frac{1}{L} \int V_c \cdot dt$$

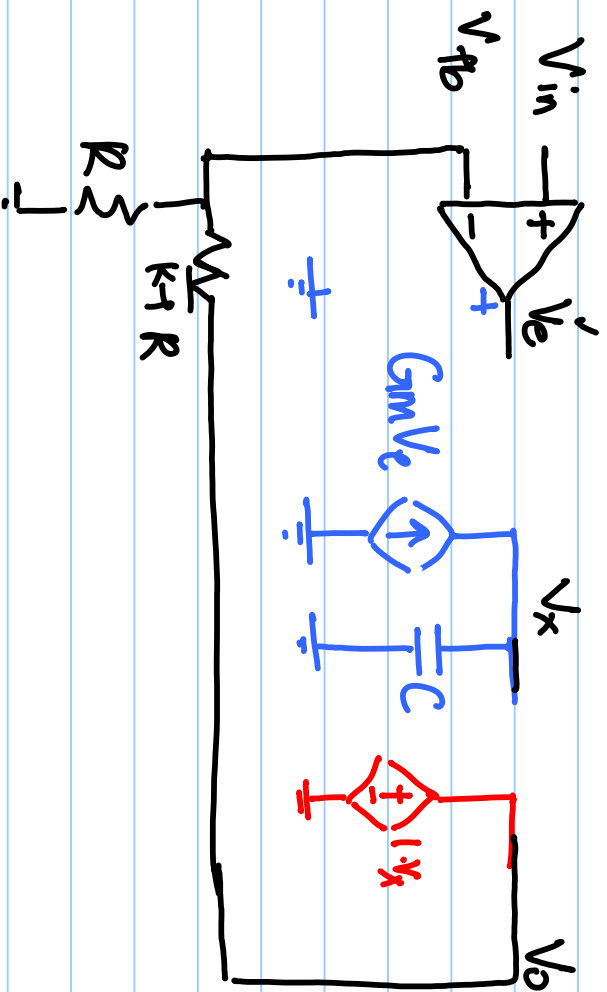


$$-V_o = \alpha \int V_c \cdot dt$$




$$-V_c = \frac{1}{C} \int i_c \cdot dt$$

$$= \frac{1}{C} \int (G_m \cdot V_c) \cdot dt$$

$$= \frac{G_m}{C} \int V_c \cdot dt$$

$t \rightarrow \infty$

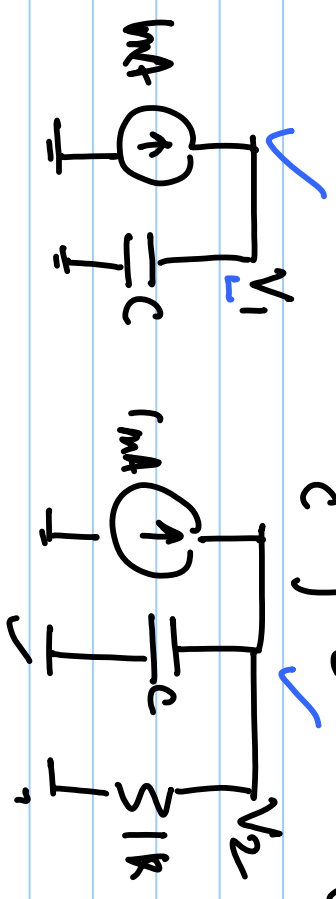

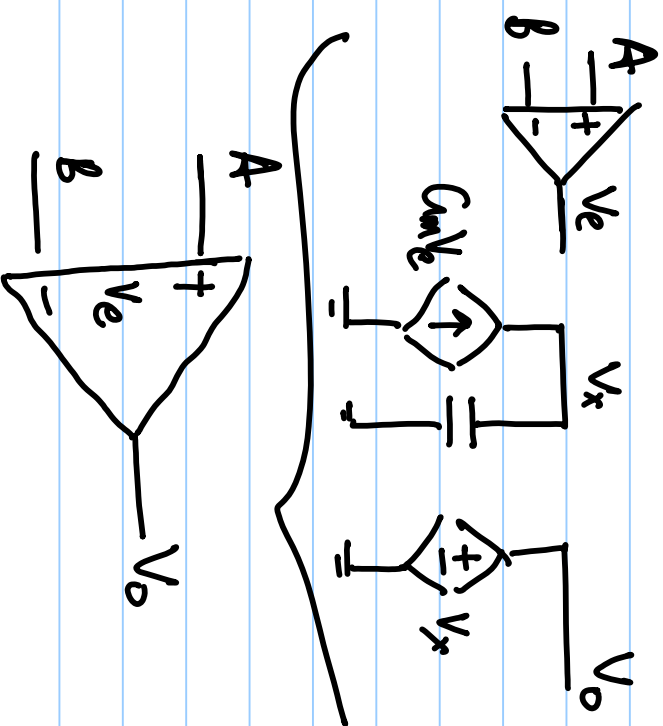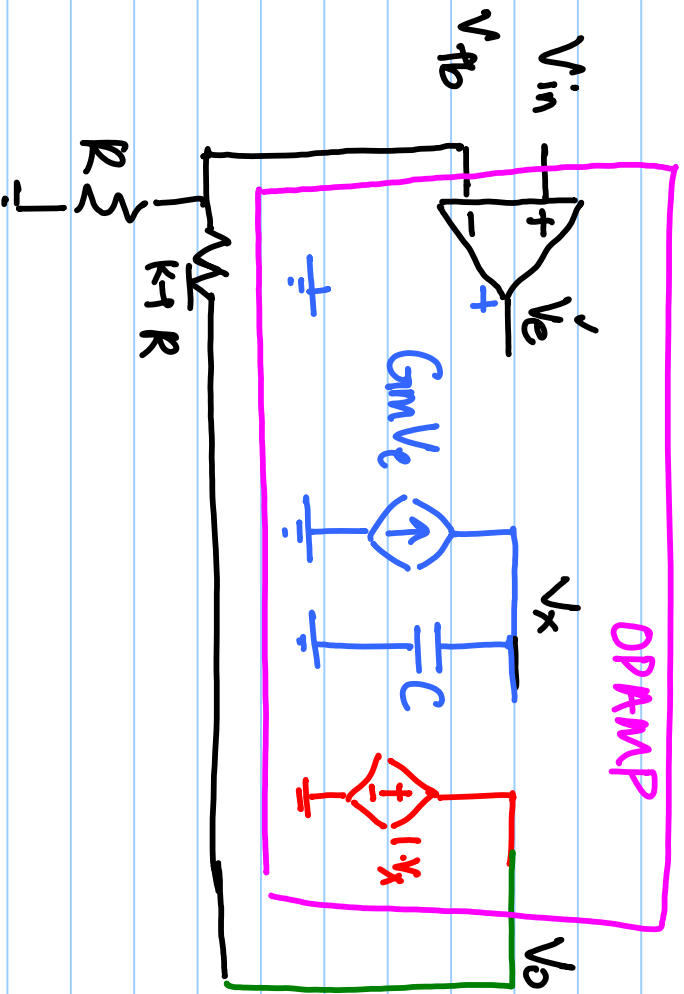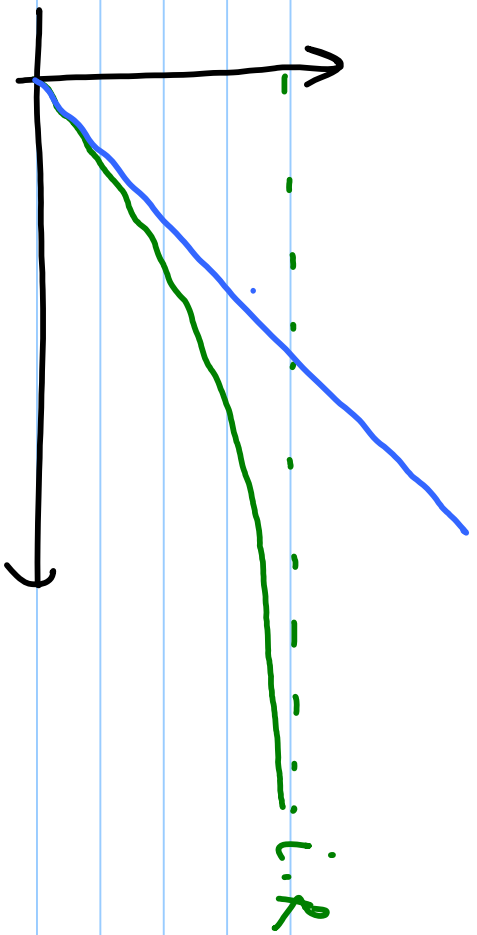

$$\frac{V_o(s)}{V_c(s)}$$