
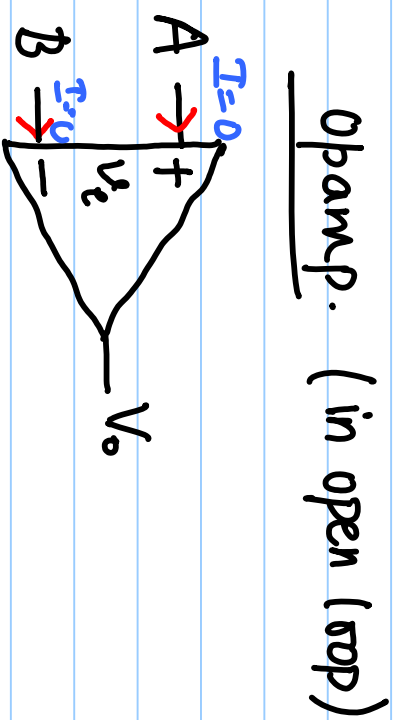


Lecture # 6

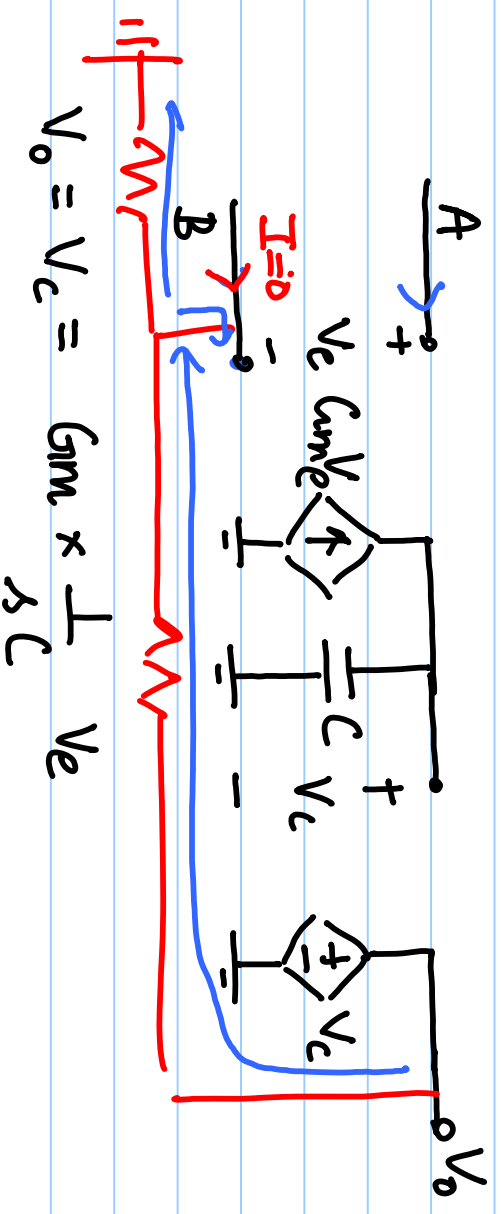


Opamp. (in open loop)

$$H(s) = \frac{V_o}{V_e} = \frac{G_m}{C} \frac{1}{s} = \frac{\omega_u}{s} \quad \text{where } \omega_u = \frac{G_m}{C}$$

pole at $s=0$,

unity gain freq. $= \omega_u = \frac{G_m}{C}$
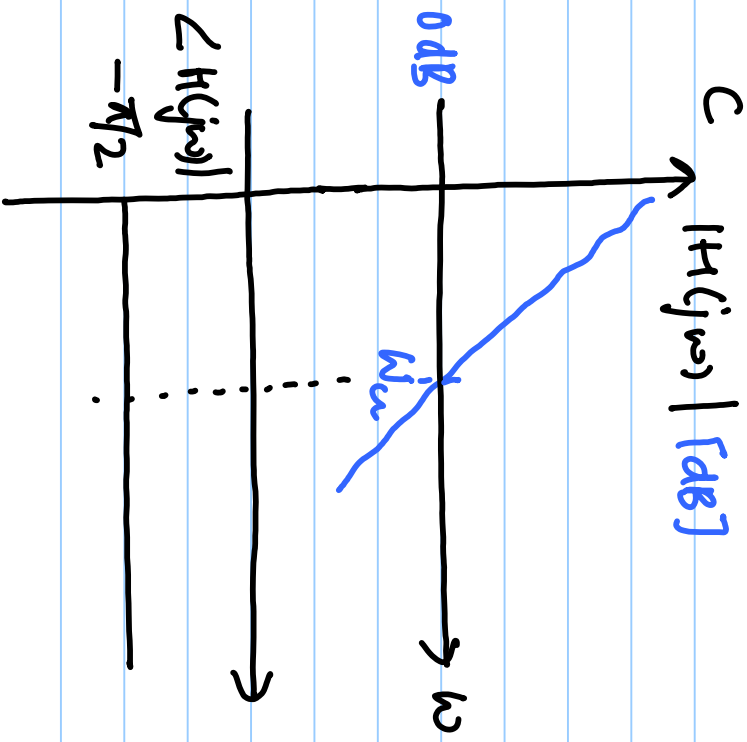
$$\angle H(j\omega) = \angle \left(\frac{\omega_u}{j\omega} \right)$$



In open loop

$$\frac{V_{out}}{V_e} = \frac{\omega_n}{s}$$


$$V_e = V_{in} - V_{fb}$$

$$V_e = V_{in} - \frac{V_{out}}{k}$$

$$V_{out} = \frac{\omega_n}{s} V_e = \frac{\omega_n}{s} \left[V_{in} - \frac{V_{out}}{k} \right]$$

$$V_{out} \left[1 + \frac{\omega_n}{s} \cdot \frac{1}{k} \right] = \frac{\omega_n}{s} V_{in}$$
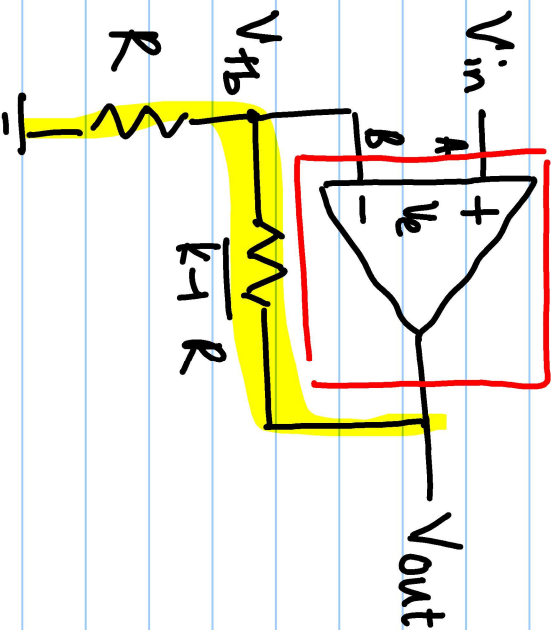
$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + \frac{s}{k \omega_n}}$$



$$\checkmark V_{out}(t) = k V_{in}(t) (1 - e^{-\omega_n t / k})$$

$$\text{for } V_{in}(t) = V_{in}(0) \cdot u(t)$$

$$H_G(s) = \frac{V_{out}}{V_{in}} = \frac{1}{1 + \frac{s}{\omega_n}} \quad \checkmark$$

$$|H_G(j\omega)| = k$$

$$s = -\omega_n \quad \text{pole}$$


$$H_G(s) = \left(\frac{k}{1 + \frac{s}{\omega_n k}} \right)$$

$$|H_G(j\omega_n')| = 1 \Rightarrow | = \frac{k}{\sqrt{1 + \left(\frac{\omega_n'}{k}\right)^2}}$$

$$| = \frac{k}{\sqrt{1 + \left(\frac{\omega_n'}{k}\right)^2}}$$

$$| = \frac{k}{\omega_n' / (\omega_n k)}$$

$$\omega_n' = \omega_n$$

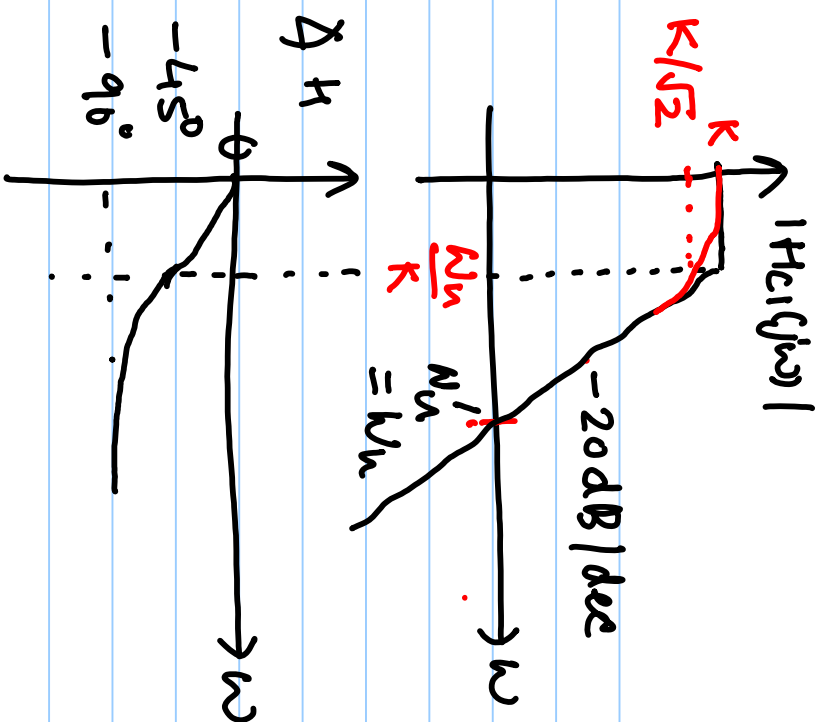

$$\phi_H(j\omega) = -\tan^{-1} \left(\frac{\omega}{\omega_n k} \right)$$

$$x = a + jb \quad \cdot \quad y = \frac{1}{a + jb}$$

$$\phi_x = \tan^{-1} \left(\frac{b}{a} \right) \quad \left| \quad \phi_y = \frac{a + jb}{a^2 + b^2} \right.$$



$$H(s) = \frac{1}{1 + s/\omega_p}$$


pole: $s = -\omega_p$

$$|H(j\omega)| = \left| \frac{1}{1 + \frac{j\omega}{\omega_p}} \right|$$

$$= \frac{1}{\sqrt{1 + \omega^2/\omega_p^2}}$$
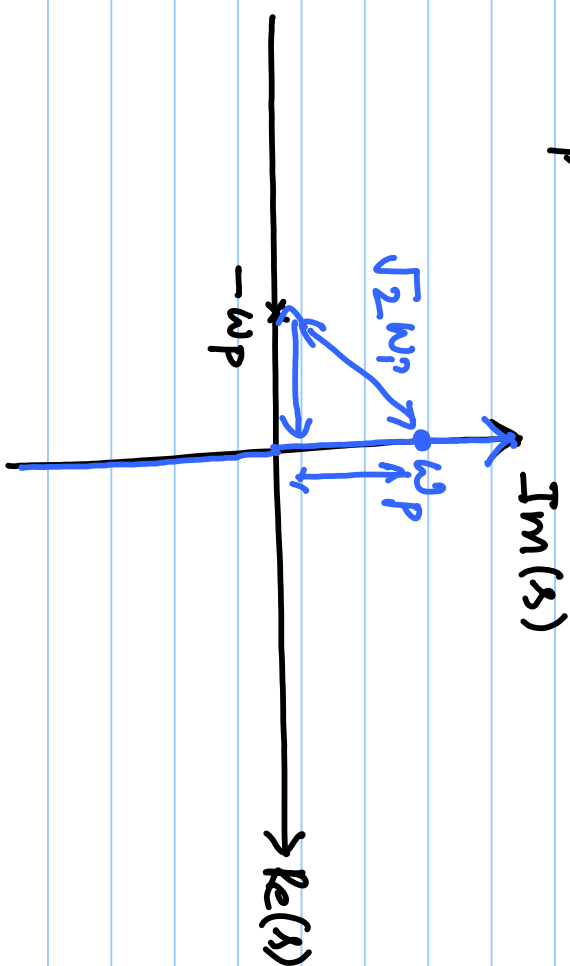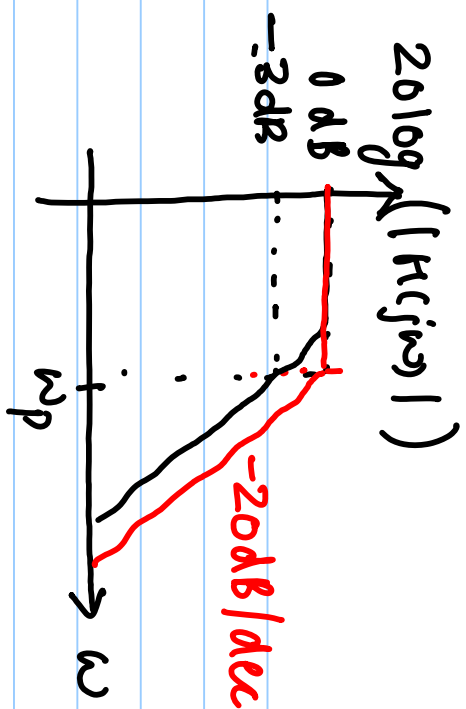
$$20 \log_{10} \left(\frac{1}{\sqrt{1 + \omega^2/\omega_p^2}} \right)$$



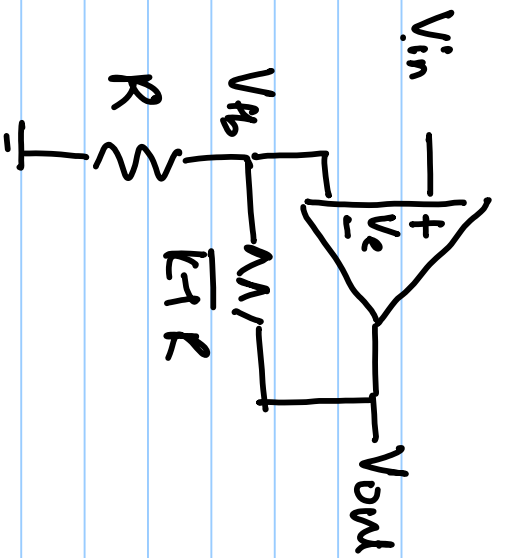

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + \frac{s}{\omega_u}}$$

at $t=0$, $V_{in}(t) = \underline{V_{in}(0)} u(t)$

$$\int_{t \rightarrow \infty} \int_{s \rightarrow 0} V_{out}(t) = \int_{s \rightarrow 0} s \cdot V_{out}(s) \checkmark$$

"Final Value Theorem"

$$V_{out}(t) = \mathcal{L}^{-1} [V_{out}(s)]$$

$$\int_{t \rightarrow \infty} V_{out}(t) = \int_{s \rightarrow 0} s \cdot V_{in}(s) \frac{1}{1 + \frac{s}{\omega_u}}$$

$$= \int_{s \rightarrow 0} \beta \cdot \frac{V_{in}(0)}{\beta} \frac{1}{1 + \frac{s}{\omega_u}}$$


$$= K \cdot V_{in}(0)$$

$$V_e(t) = V_{in}(t) - \frac{V_{out}(t)}{K}$$

$$V_e(s) = V_{in}(s) - \frac{V_{out}(s)}{K}$$

$$= V_{in}(s) \left[\frac{s \left(\frac{\omega_u}{\omega_u} \right)}{1 + \frac{s}{\omega_u}} \right] \checkmark$$
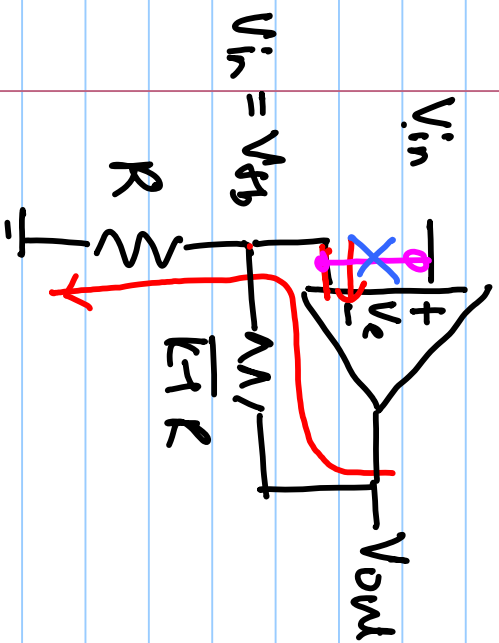
$$\int_{t \rightarrow \infty} V_e(t) = \int_{s \rightarrow 0} s \cdot V_e(s)$$



$$V_e = 0 \Rightarrow V_{in} - V_{fb} = 0$$

$$V_{fb} = V_{in}$$

$$\frac{V_{out} - V_{in}}{k-1} = \frac{V_{in}}{R}$$

$$V_{out} = k \cdot V_{in}$$

$$V_e(s) = V_{in}(s) - \frac{V_{in}(s)}{k} \frac{1}{1 + \frac{s}{\omega_n}}$$

$$= V_{in}(s) \left[1 - \frac{1}{k \left(1 + \frac{s}{\omega_n} \right)} \right]$$

$$= V_{in}(s) \frac{s / (\omega_n k)}{1 + s / (\omega_n k)}$$

$$\lim_{t \rightarrow \infty} V_e(t) = \lim_{s \rightarrow 0} \frac{s \cdot V_{in}(s)}{s} \frac{s / (\omega_n k)}{1 + s / (\omega_n k)}$$


$$= 0$$

$$- V_A = V_B \Rightarrow V_e = 0$$



- I/P terminals of OPAMP are virtually short.

- Non-inverting amplifier

$$\frac{V_{out}}{V_e} = -\frac{w_1}{s}$$

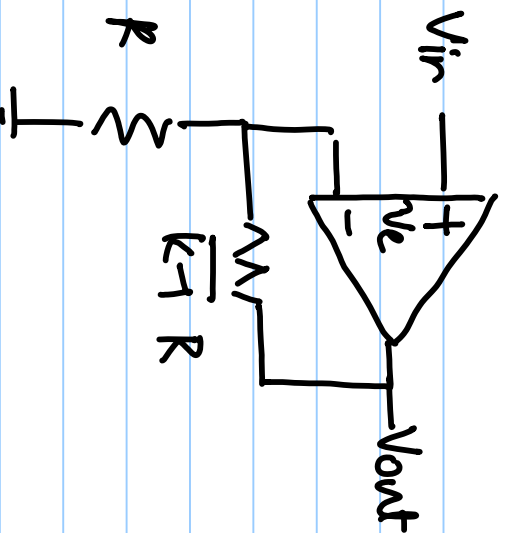

$$\frac{V_{out}}{V_{in}} = -k$$

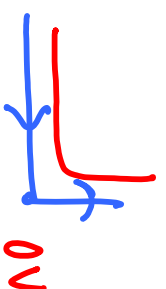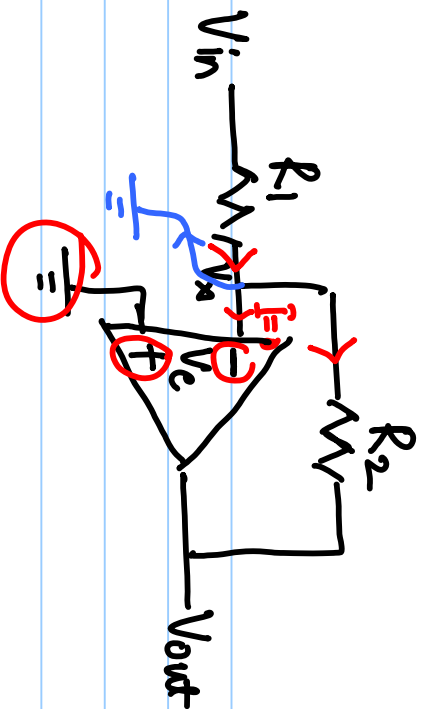

- Assume $V_e = 0$ in steady state


$$- V_x = 0$$

$$\Rightarrow \frac{V_{in} - 0}{R_1} = \frac{0 - V_{out}}{R_2}$$

$$\frac{V_{out}}{V_{in}} = -\left(\frac{R_2}{R_1}\right)$$

= -ve.

Inverting Amplifier

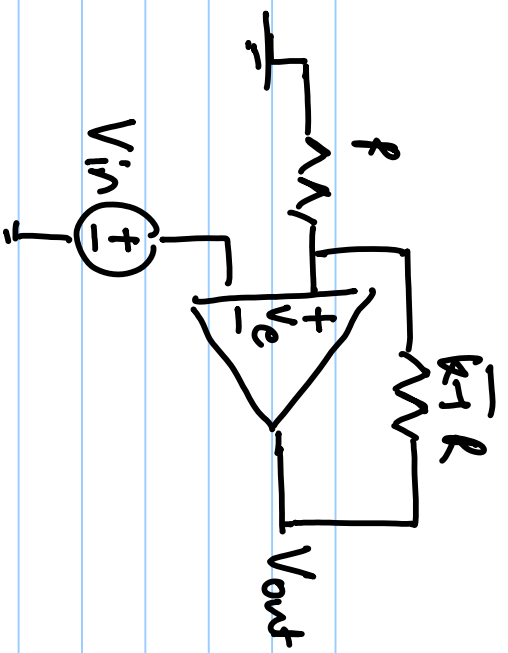

$$V_e = \frac{V_{out}}{k} - V_{in}$$

$$V_{out} = \frac{\mu_{Au}}{\beta} V_e = \frac{\mu_{Au}}{\beta} \left(\frac{V_{out}}{k} - V_{in} \right)$$

$$V_{out} \left(\frac{\beta}{\mu_{Au}} - \frac{1}{k} \right) = -V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{-1}{\left(\frac{\beta}{\mu_{Au}} - \frac{1}{k} \right)}$$