
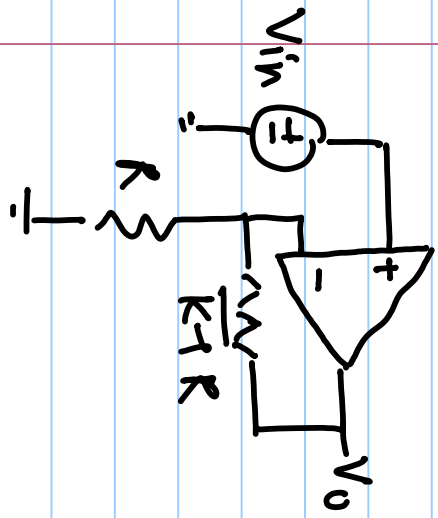



Lecture #7

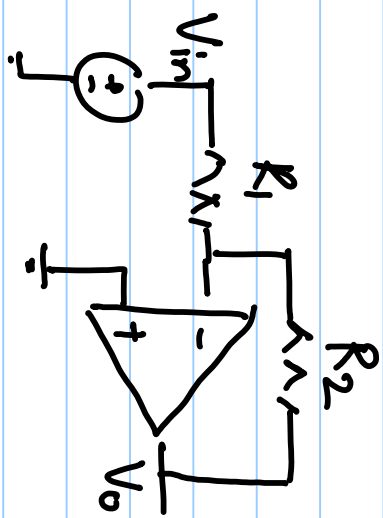

$$\frac{V_0}{V_{in}} = K$$


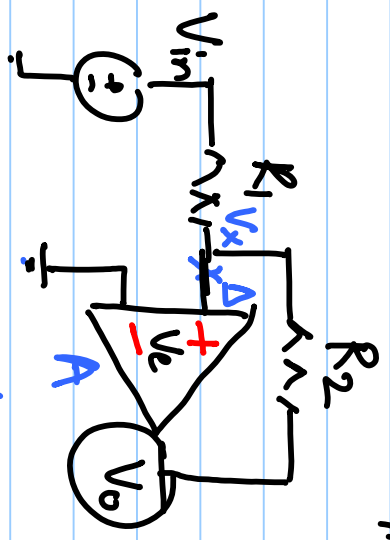
$$\frac{V_0}{V_{in}} = -\frac{R_2}{R_1}$$




$$\frac{V_0}{V_{in}} =$$

$$\frac{V_0}{V_e} = \frac{G_{um}}{A \Delta}$$

"Positive feedback"

$$V_e = \Delta \rightarrow A \Delta$$
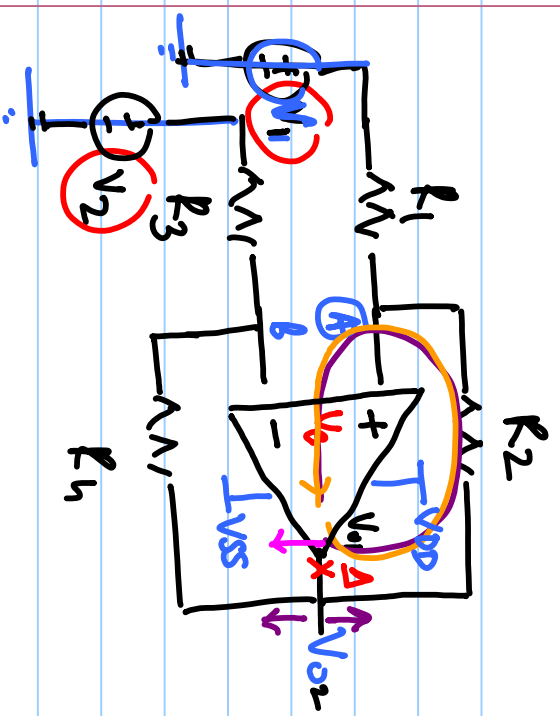
$$V_x = \frac{R_1}{R_1 + R_2} \cdot A \Delta$$



$$V_o = f(V_1, V_2)$$

Whether it is in negative or positive feedback?

$$V_e = V_A - V_B$$

$$V_e = \left(\frac{R_1}{R_1 + R_2} - \frac{R_3}{R_3 + R_4} \right) \Delta$$


Apply Δ at V_{o2}




if $V_e > 0 \rightarrow V_{o1}$ *trv* feedback

if $V_e < 0 \rightarrow V_{o1}$ *-trv* feedback

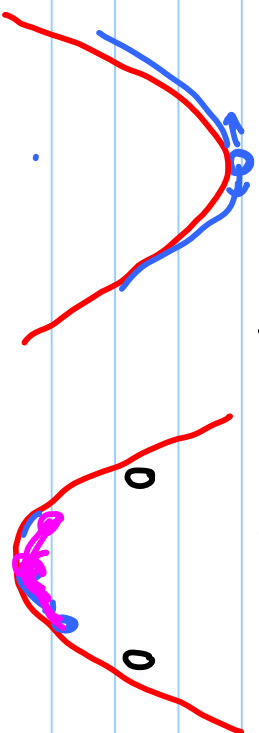if it is negative feedback. then $V_A = V_B$ ✓









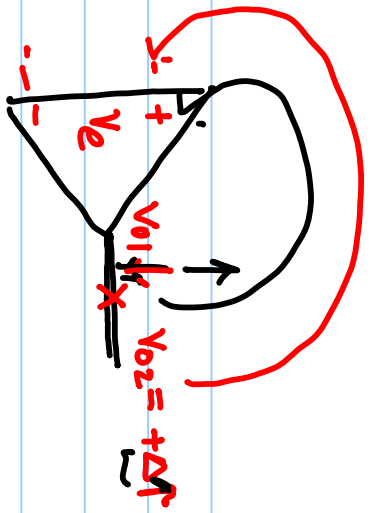


$$\frac{V_{o1}}{V_e} = +2$$


$$V_{o1} = +2(A) \times V_e$$

$$= +2(A) \times (-V_e) \cdot A$$

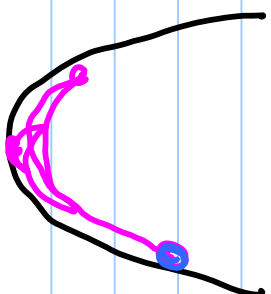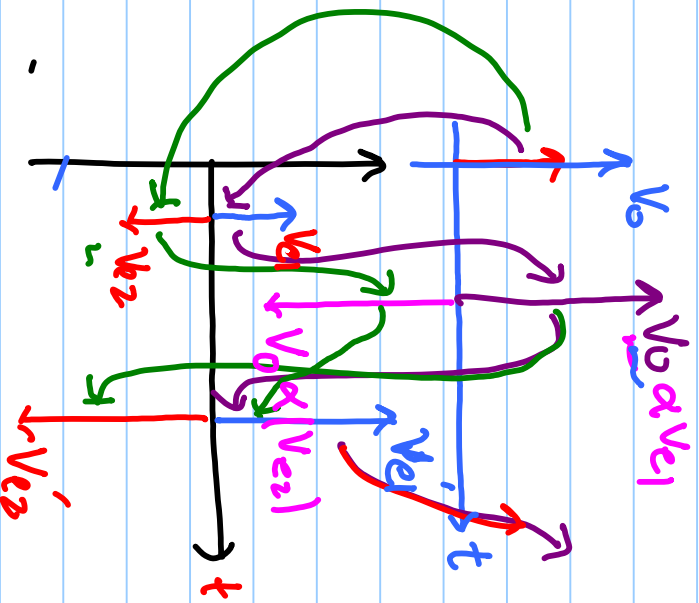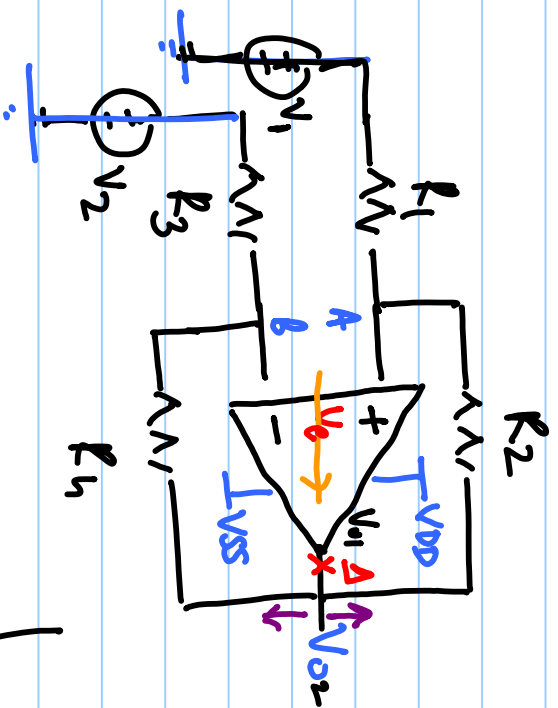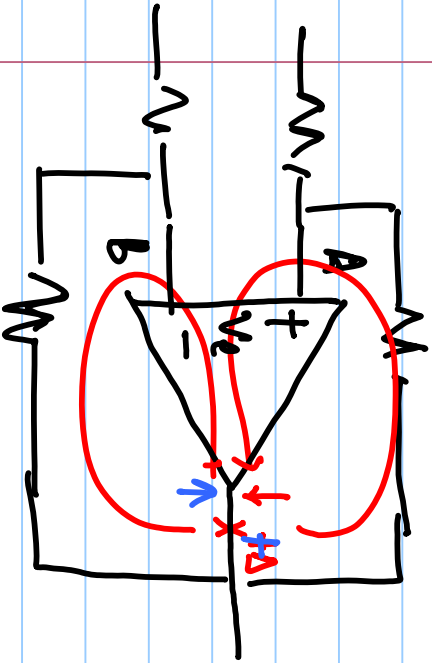

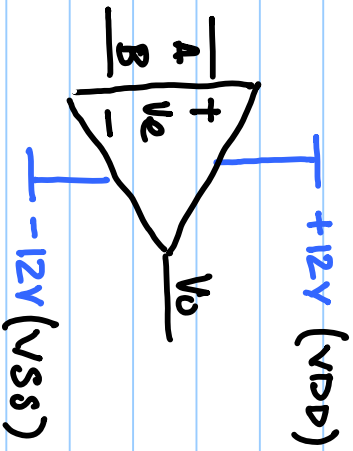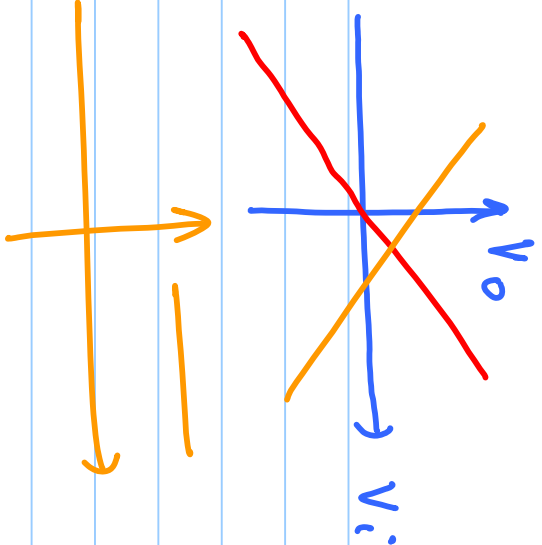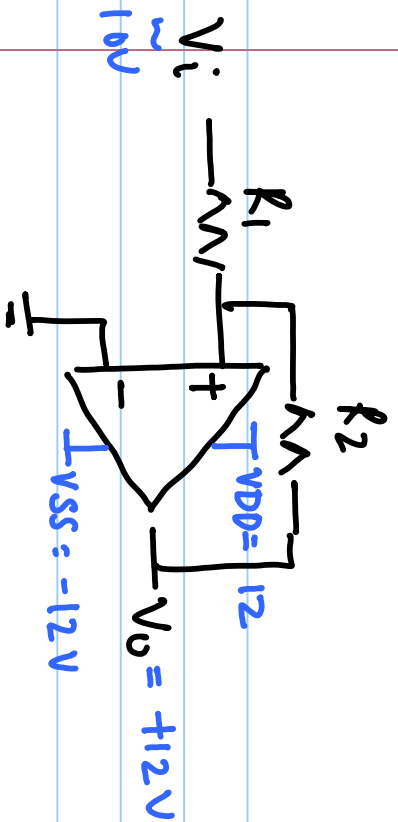

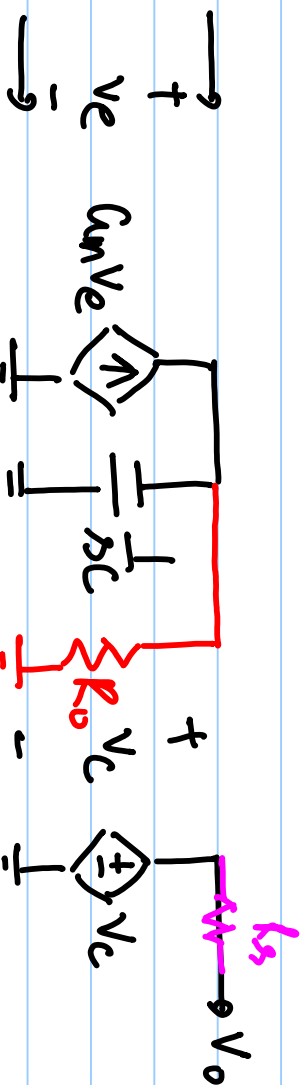
$$\frac{V_o(s)}{V_e(s)} = \frac{g_m}{sC}$$



$$V_{SS} \leq V_o \leq V_{DD}$$

$$|H(s)| = \frac{V_o(s)}{V_e(s)} = \frac{g_m R_o}{1 + sC R_o} \quad \left| \begin{array}{l} \text{DC gain of } H(s) \\ = |H(s=j\cdot 0)| \end{array} \right.$$

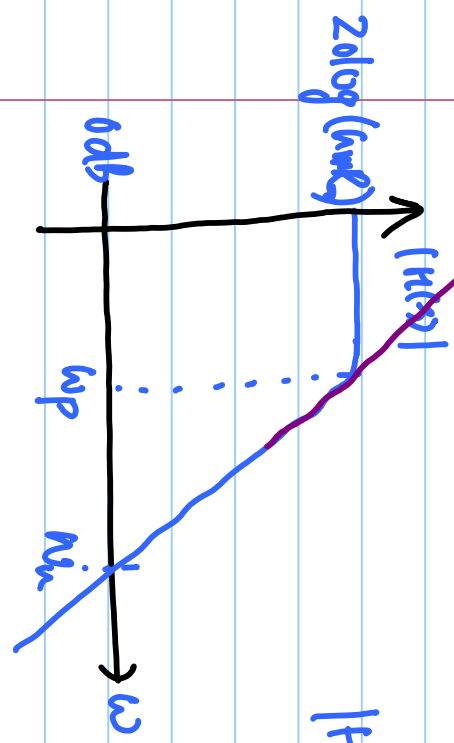
$$\text{pole} = -\omega_p = \frac{-1}{C R_o}$$



$$A_o = g_m R_o \quad (\text{DC gain})$$

$$|H(j\omega_n)|_{dB} = \frac{A_{m0}}{\sqrt{1 + \frac{\omega_n^2}{\omega_p^2}}} \approx \frac{A_{m0}}{\omega_n/\omega_p}$$


$$\omega_n = \frac{C_m}{C}$$

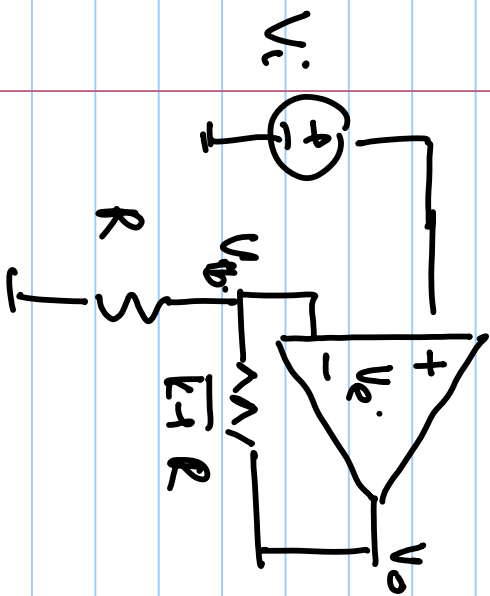


$$\left(V_i - \frac{V_o}{k} \right) \cdot A_0 = V_o$$

$$V_o = \frac{V_i}{\frac{1}{k} + \frac{1}{A_0}}$$

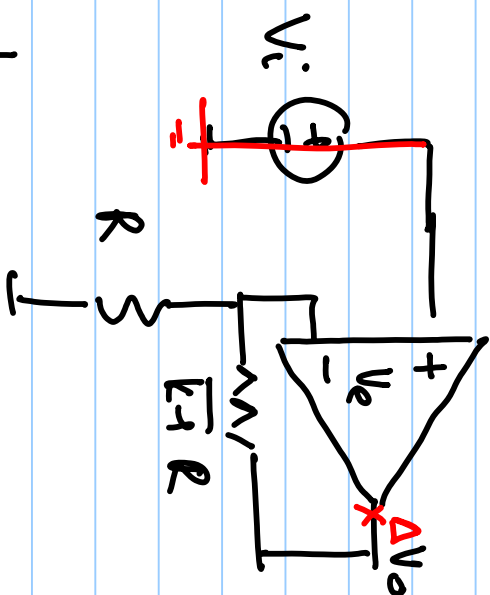
$$V_o = \frac{k V_i}{(1 + k/A_0)} \xrightarrow{A_0 \rightarrow \infty} V_o = k V_i$$


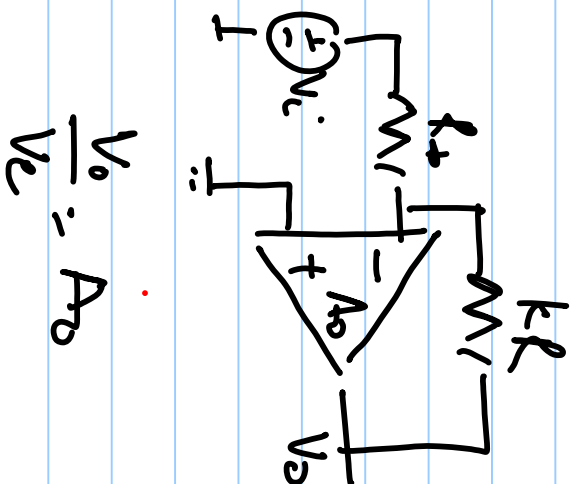
$$V_e = 0 - \frac{R}{k \cdot k} \cdot \Delta = -\frac{\Delta}{k}$$



$$\frac{V_o}{V_e} = A_0$$

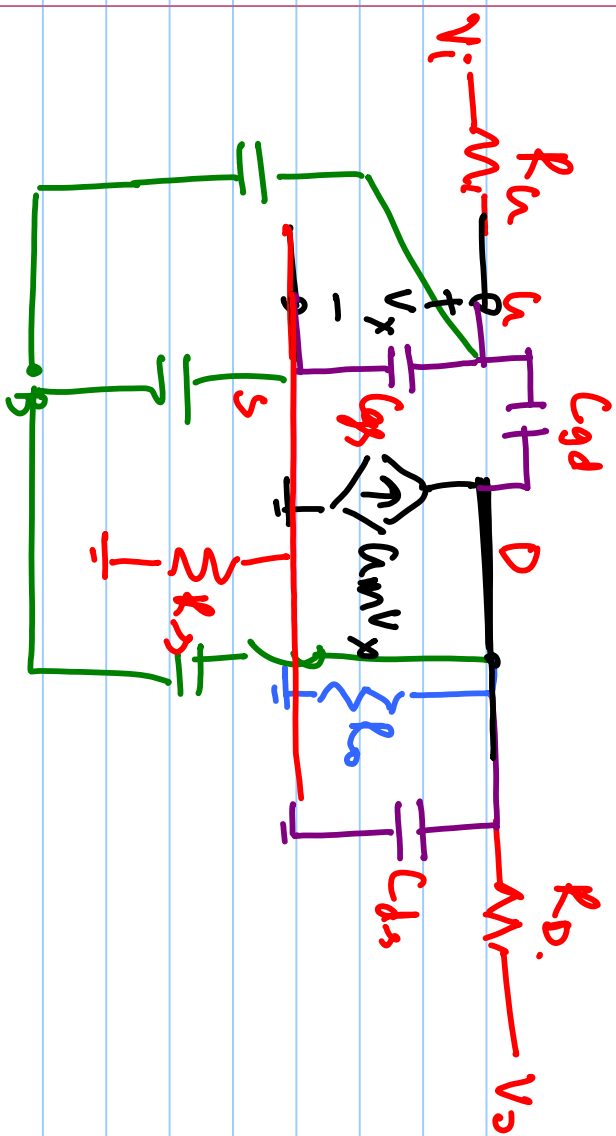

1