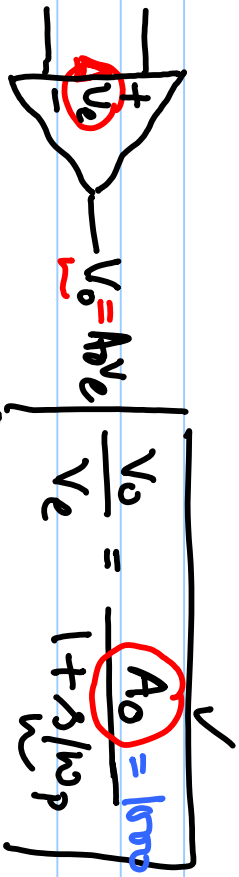


Lecture # 8



$$\frac{V_o}{V_e} = \frac{A_o}{1 + s/w_p}$$



Ideal Amp.

$$\frac{V_o}{V_e} = \frac{G_m}{sC}$$





$$V_o = G_m(R) = G_m(R_{o1} || R_1)$$

$$= \frac{G_m R_o}{1 + sC R_o}$$

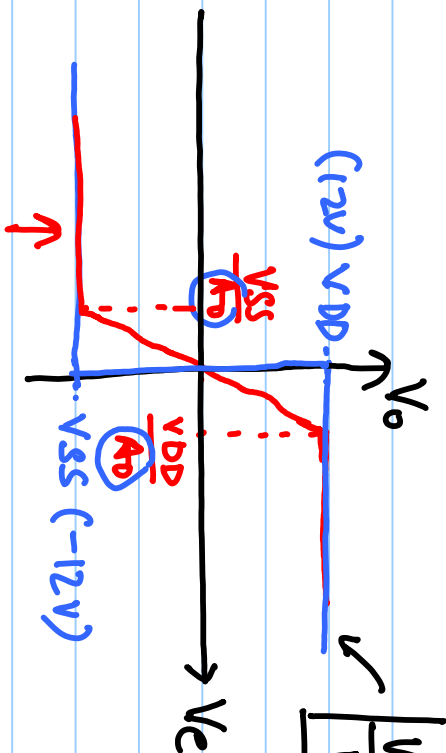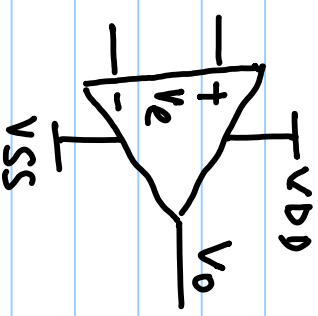

$$\frac{V_o}{V_e} = \frac{A_o}{1 + s/w_p}$$

.

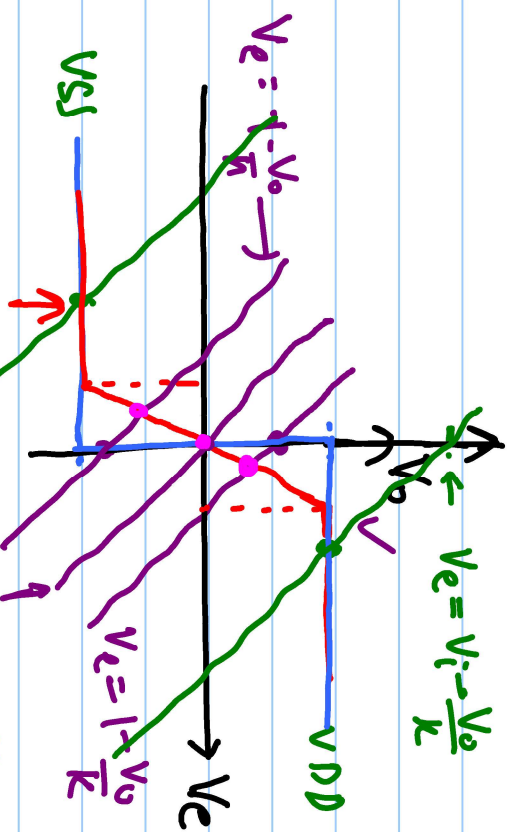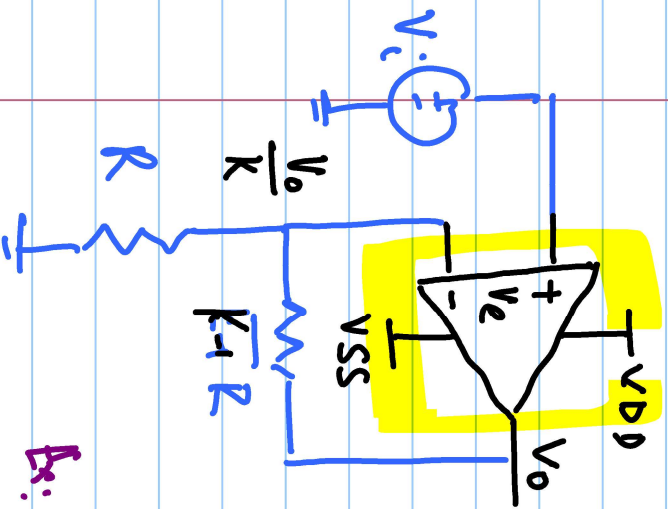


$$V_e = V_i - \frac{V_o}{k}$$

Ex: $V_i = 1V \Rightarrow V_e = 1 - \frac{V_o}{k}$

$V_i = -1V \Rightarrow V_e = -1 - \frac{V_o}{k}$


$V_i = 0 \Rightarrow V_e = -\frac{V_o}{k}$
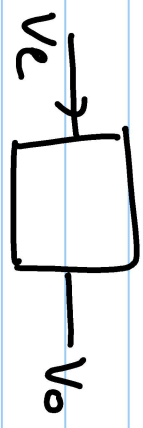
$$\frac{V_o}{V_e} = \frac{A_o}{1 + s/\omega_p}$$



$$\mathcal{L}\{V_o(t)\} = \mathcal{L}\{s \cdot V_o(s)\}$$


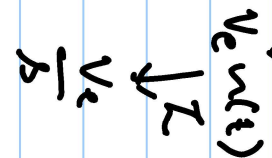
$$= \mathcal{L}\{s \cdot \frac{A_o}{1 + s/\omega_p} \cdot V_e(s)\}$$



$$= \mathcal{L}\{s \cdot \frac{A_o}{1 + s/\omega_p} \cdot \frac{V_e}{s}\}$$

$$= A_o V_e$$


Inverting "Schmitt" Trigger

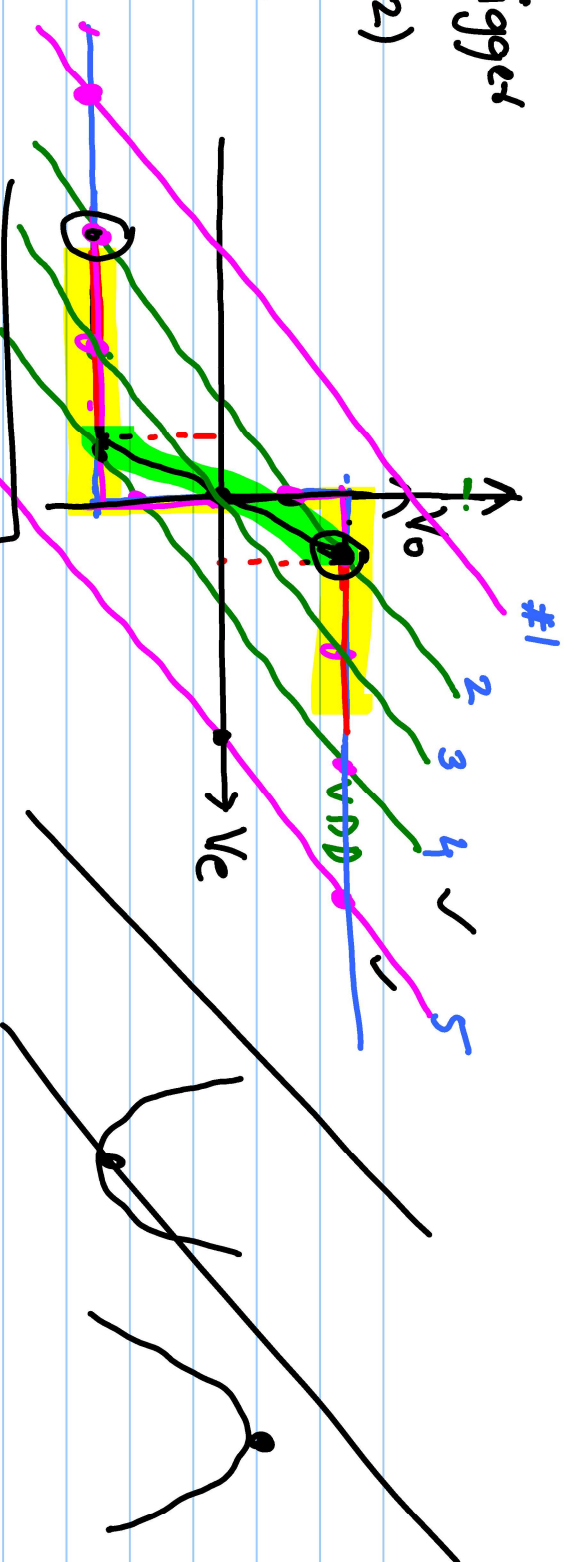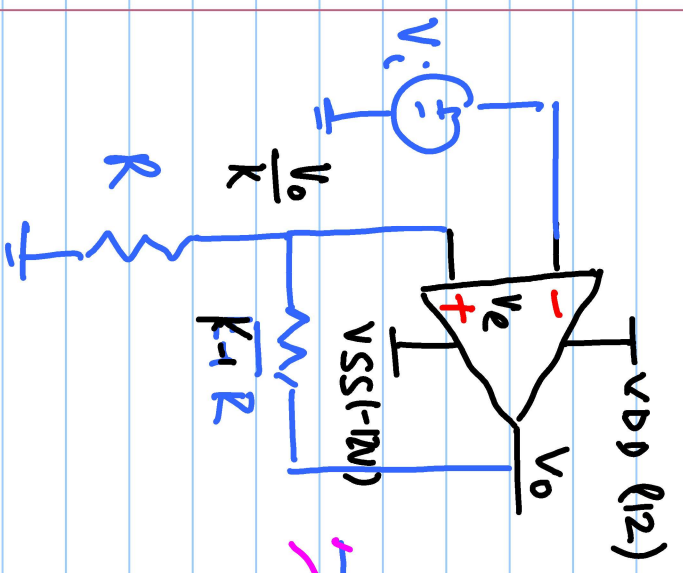

$$V_e = \frac{V_o - V_i}{k}$$

$$V_i = 0, \quad V_e = \frac{V_o}{k}$$

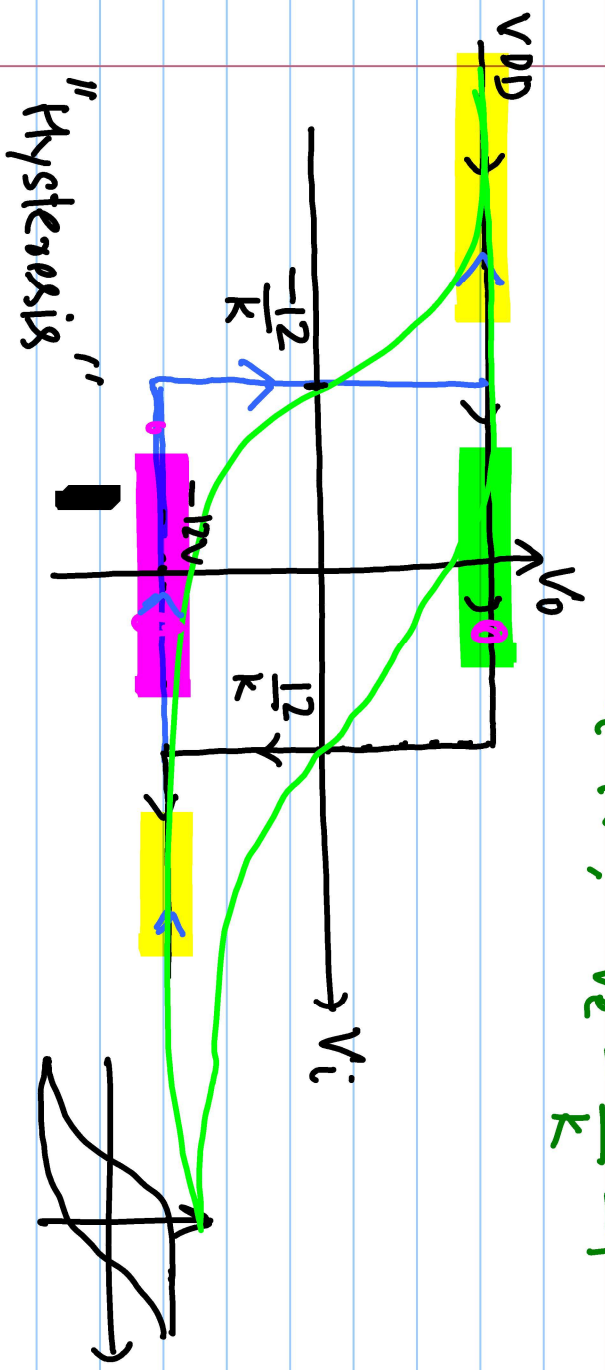
$$V_i = 1V, \quad V_e = \frac{V_o}{k} - 1$$



"Hysteresis"

- large -ve i/p V_i , $V_o = V_{DD}$
- $V_e = \frac{12}{k} - V_i$
- $V_i = 0, \quad V_e > 0$
- $V_e = \frac{12}{k} - V_i < 0$
- $V_i > \frac{12}{k}$
- large +ve i/p V_i :
- $V_e = \frac{-12}{k} - V_i < 0$
- $V_e = \frac{-12}{k} - V_i > 0 \Rightarrow V_i < \frac{-12}{k}$

"Non-inverting" Schmitt Trigger.

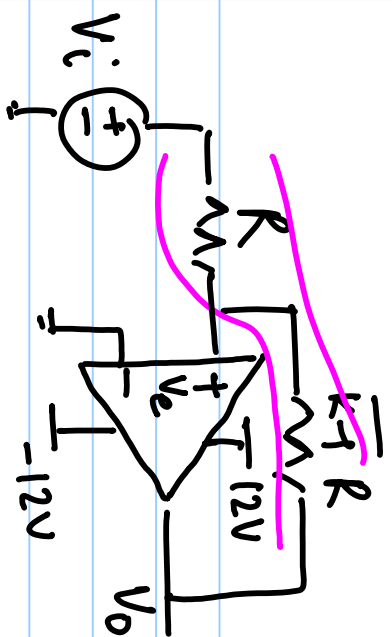

$$V_e = \frac{1}{k} \cdot V_0 + \frac{k-1}{k} V_i$$

$$V_e = \frac{12}{k} + \frac{k-1}{k} \cdot V_i < 0$$

$$V_i < -\frac{12}{k-1}$$

