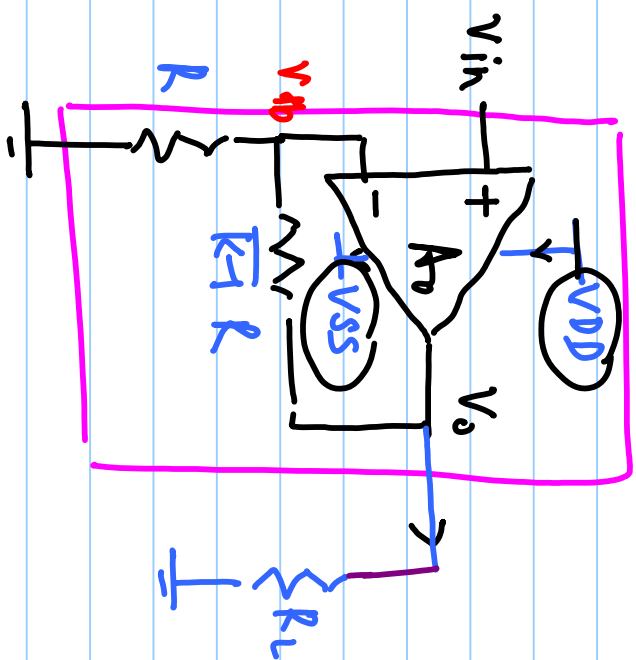


# Lecture # 9



#1: OPAMP is ideal with infinite gain and infinite bandwidth.

#2: OPAMP has finite DC gain but infinite bandwidth

#3: OPAMP has finite DC gain and bandwidth

#1:  $V_{in} = A \sin(\omega t)$


$V_{fb} = V_{in}$

$V_o = V_{in} \Rightarrow V_o = k V_{in}$

#2:  $(V_{in} - \frac{V_o}{k}) A_o = V_o$

$V_o = \frac{V_{in}}{\frac{1}{k} + \frac{1}{A_o}} = \frac{k V_{in}}{1 + k/A_o}$

#3.

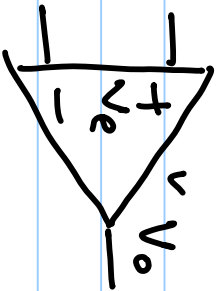

$$\frac{V_o}{V_e} = \frac{A_o}{1 + s/\omega_p} \quad \checkmark$$

$$\left( V_{in} - \frac{V_o}{k} \right) \frac{A_o}{1 + s/\omega_p} = V_o$$

$$V_{in} = V_o \frac{(1 + s/\omega_p)}{A_o} + \frac{V_o}{k}$$


$$\frac{V_o}{V_{in}} = \frac{1}{\frac{1}{k} + \frac{1}{A_o} + \frac{s}{A_o \omega_p}}$$



$$H(s) = \frac{V_o}{V_{in}} = \frac{k}{1 + \frac{k}{A_o} + \frac{s}{(A_o \omega_p / k)}}$$

$$V_i(s) \rightarrow [H(s)] \rightarrow V_o(s)$$


$$V_o(s) = H(s) V_i(s)$$
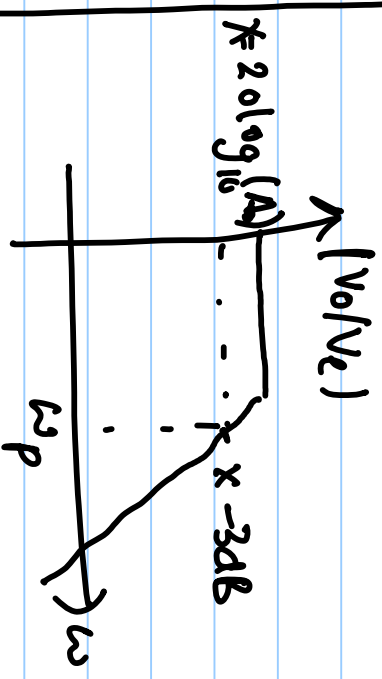
$$V_o(t) = \mathcal{L}^{-1} \{ V_o(s) \}$$





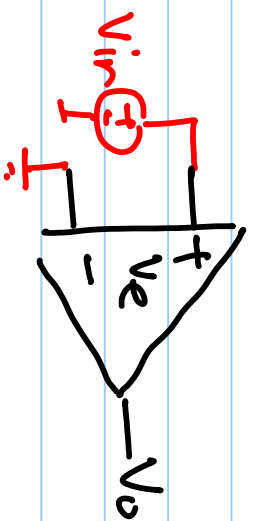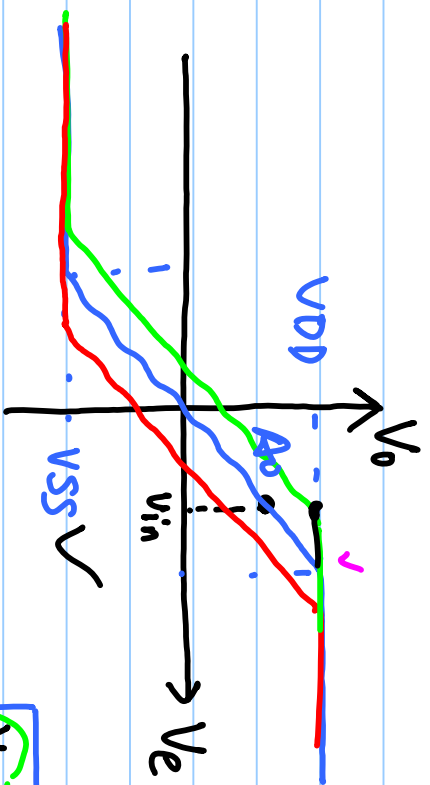

$$A_0 = 1000$$

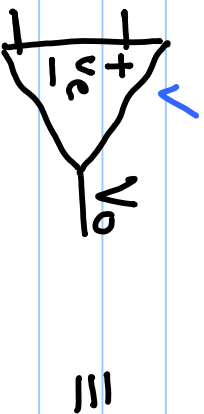


Opamp w/ offset

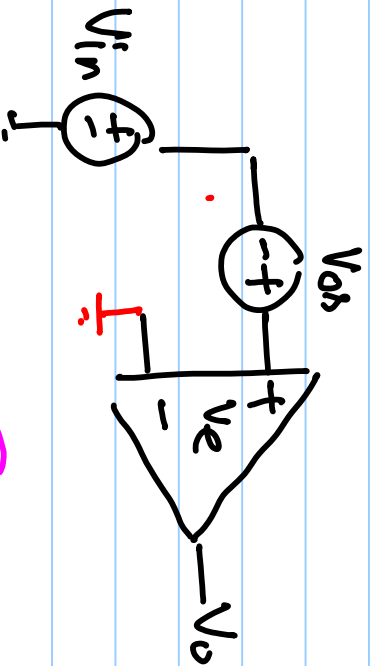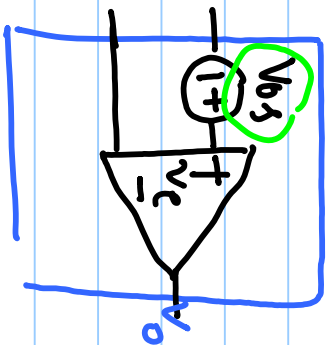


$$V_o = A_0 (V_{in} + V_{os}) = K (V_{in} + V_{os})$$

$$= K V_{in} + K V_{os}$$

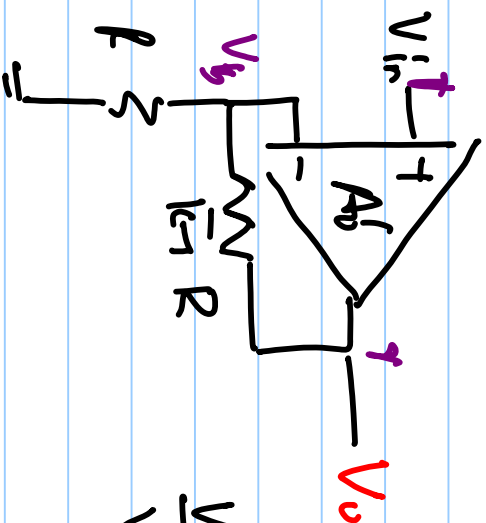

$$\frac{V_o}{V_{in}} = 1000$$


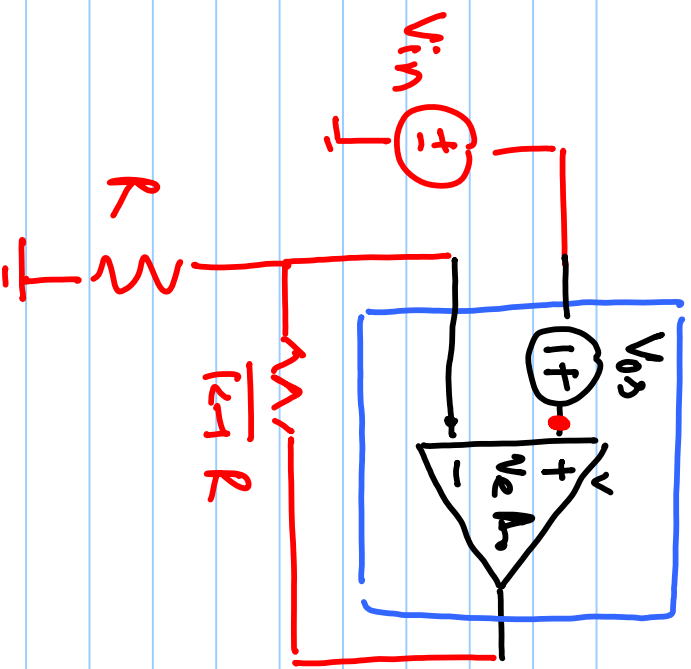


$$(V_{in} + V_{os} - \frac{V_o}{k}) A_o = V_o$$

$$V_{in} + V_{os} = V_o \left( \frac{1}{k} + \frac{1}{A_o} \right)$$



$$V_o = \frac{k V_{in}}{1 + \frac{k}{A_o}} + \frac{k V_{os}}{1 + \frac{k}{A_o}}$$

Opamp w/ offset

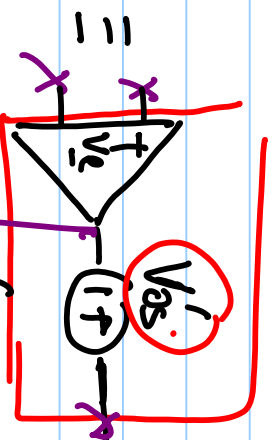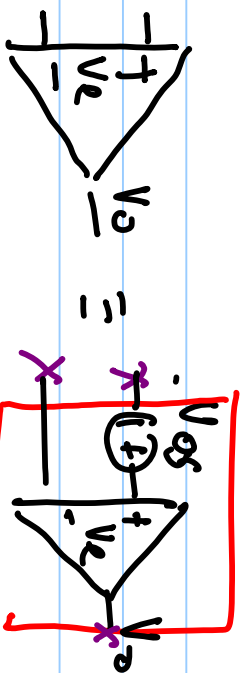

$$V_{os}' = A_o V_{os}$$


~~$A_o V_{os}$~~

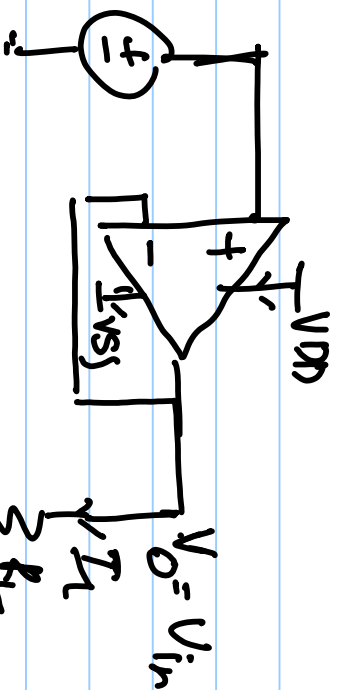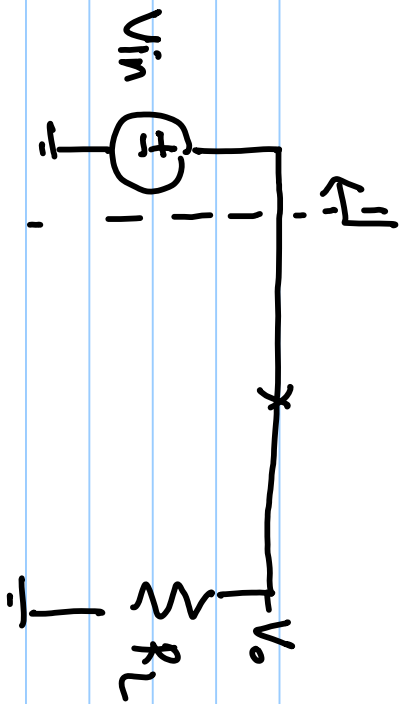

"Voltage Buffer"

- Gain blocks with the /-ve sign

- Buffers
- Schmitt Trigger.

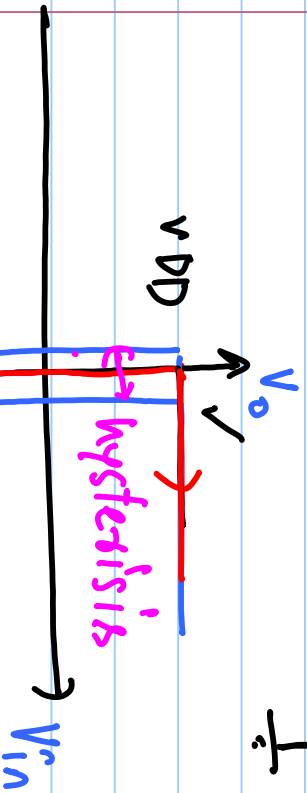

"Comparator"

