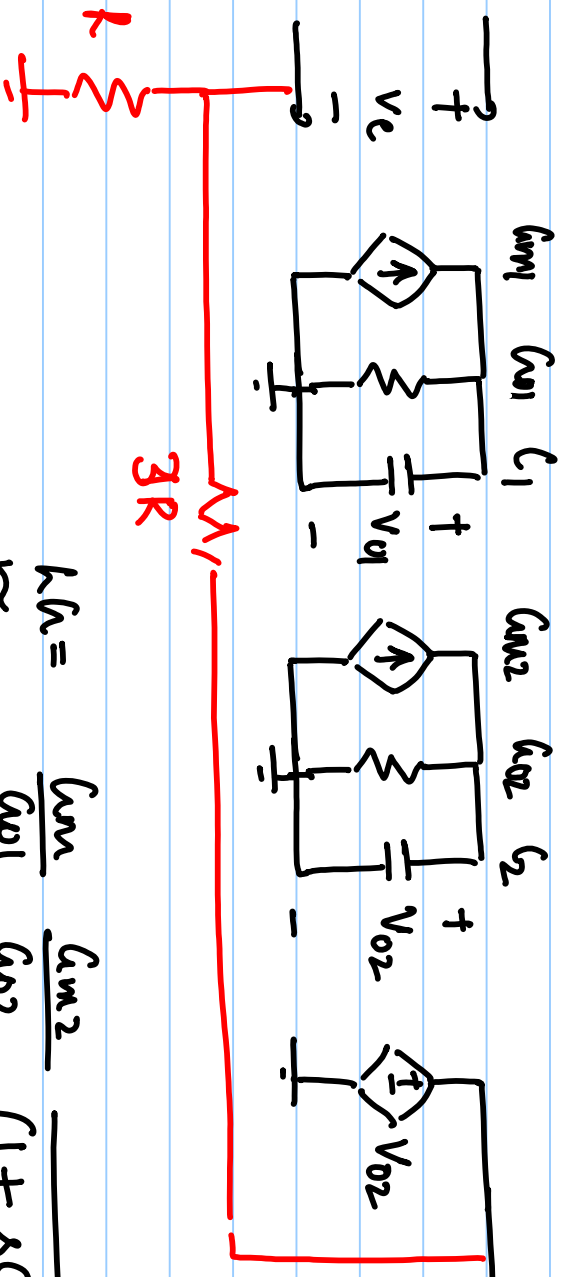


Lecture # 17

- Nyquist Stability Criterion.
- Loop Gain & Phase Margin.

Ex:




$$k_{fb} = \frac{g_{m1}}{g_{o1}} \frac{g_{m2}}{g_{o2}} \frac{1}{\left(1 + sC_1/g_{m1}\right) \left(1 + \frac{sC_2}{g_{o2}}\right)} \times \frac{1}{4}$$

$$A_{dc} = \frac{1}{4} \times 100 \times 100$$

$$p_1 = \frac{g_{o1}}{C_1} = \frac{0.1 \times 10^{-3}}{1 \times 10^{-9}} = 10^5 \text{ rad/s}$$

$$p_2 = \frac{g_{o2}}{C_2} = \frac{0.01 \times 10^{-3}}{20 \times 10^{-12}} = \frac{10^7}{20} = 5 \times 10^5 \text{ rad/s}$$
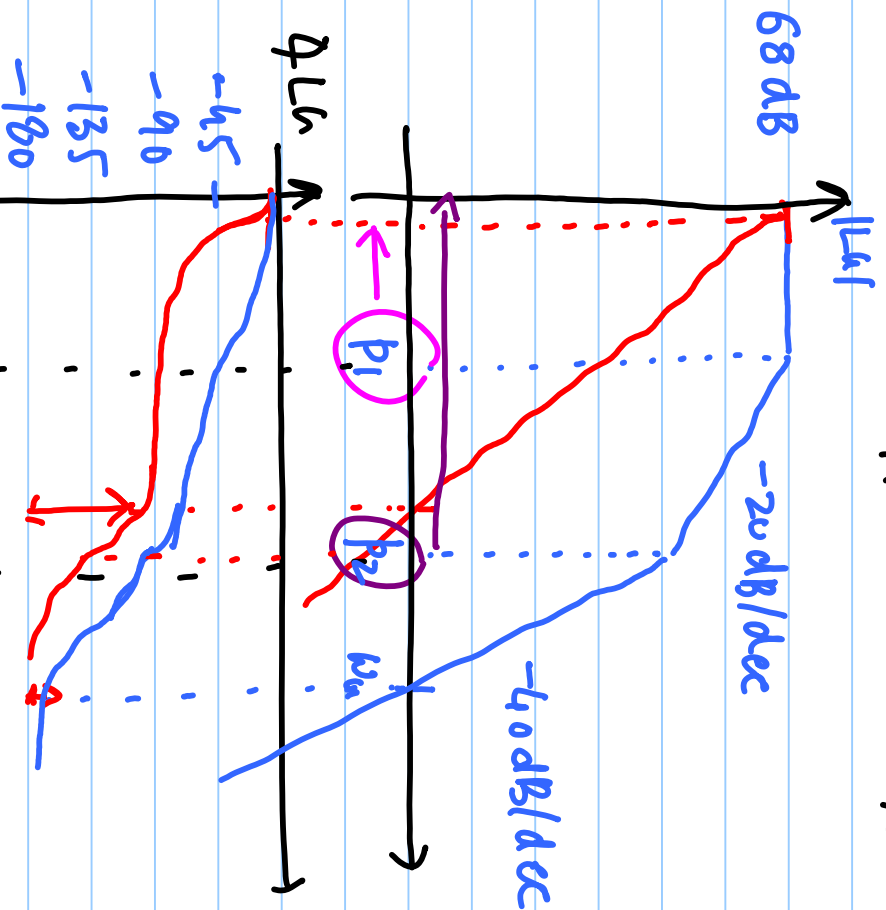
$$\angle L_u = -\tan^{-1}\left(\frac{\omega}{p_1}\right) - \tan^{-1}\left(\frac{\omega}{p_2}\right)$$



$$\begin{aligned} \phi_m &= 180^\circ - \tan^{-1}\left(\frac{\omega_n}{p_1}\right) - \tan^{-1}\left(\frac{\omega_n}{p_2}\right) \\ &= 180^\circ - \tan^{-1}\left(\frac{1111}{1}\right) - \tan^{-1}\left(\frac{111}{5}\right) \end{aligned}$$

$$20 \log\left(\frac{10^4}{n}\right) = 80 - 12 = \underline{\underline{68 \text{ dB}}}$$

$\omega_n > p_2, p_1$



$$|L_u(j\omega_n)| = 1$$

$$\frac{A_{DC}}{\sqrt{\left(1 + \frac{\omega_n^2}{p_1^2}\right) \left(1 + \frac{\omega_n^2}{p_2^2}\right)}} = 1$$

$$\frac{A_{DC}}{\omega_n^2} \approx 1 \Rightarrow \omega_n = \sqrt{A_{DC} \cdot p_1 p_2}$$

$$\begin{aligned} \omega_n &= \sqrt{2500 \times 10^5 \times 5 \times 10^5} \\ &= \sqrt{125 \times 10^6} \\ &= 11.1 \times 10^3 = 111 \times 10^5 \text{ rad/s} \end{aligned}$$
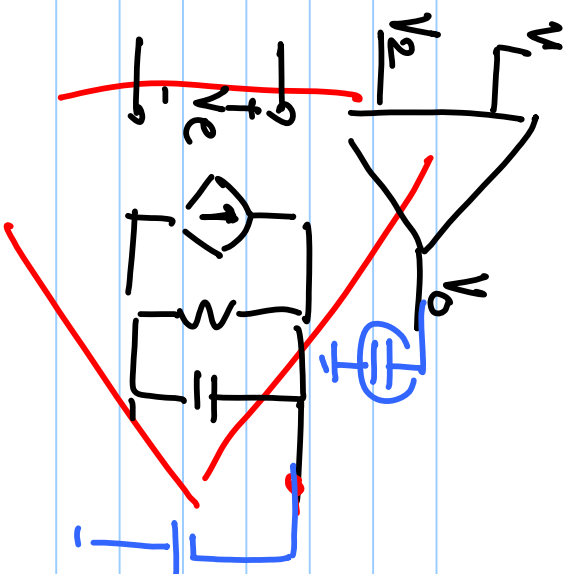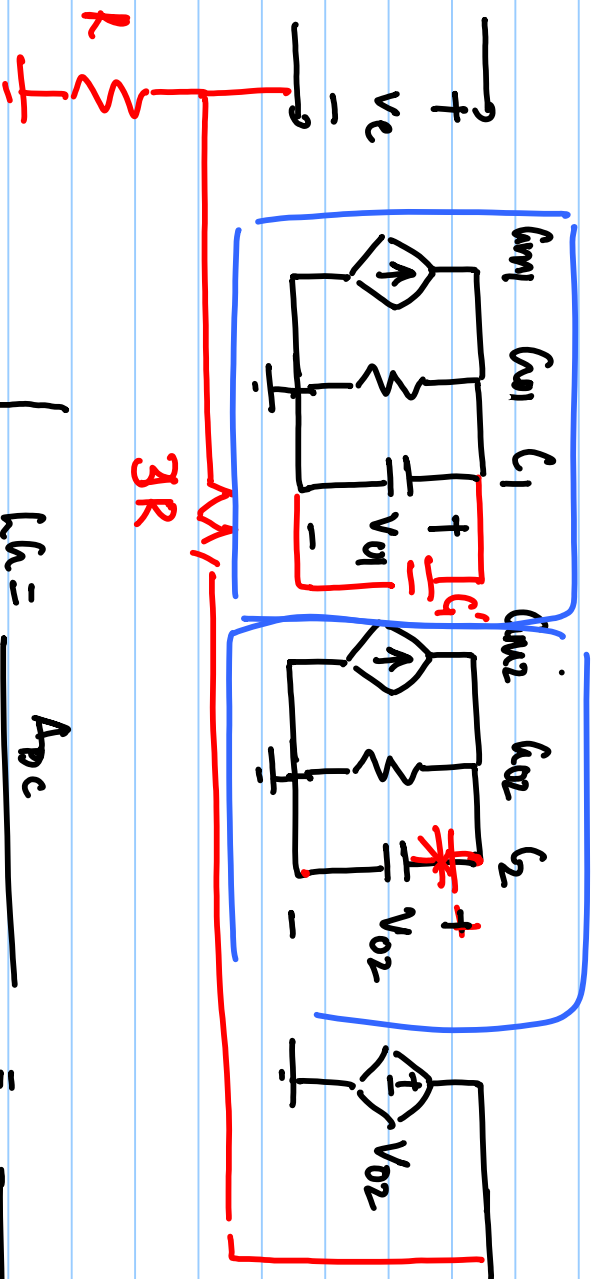
$$\phi_m = 180^\circ - 89.5^\circ - 87.4^\circ = 3.1^\circ$$



$$p_1 = \frac{A_{01}}{C_1}$$

$$p_2 = \frac{\omega_{02}}{C_2}$$

$$k_A = \frac{A_{0c}}{(1 + \frac{s}{p_1})(1 + \frac{s}{p_2})} = \frac{k \cdot \omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

$$\zeta = \frac{1}{2} \left(\sqrt{\frac{p_1}{p_2}} + \sqrt{\frac{p_2}{p_1}} \right) \frac{1}{\sqrt{1 + A_0/k}} = 1 \Rightarrow \phi_m = 76^\circ$$

$$\zeta = 1 \Rightarrow \frac{p_1'}{p_2} + \frac{p_2}{p_1'} + 2 = 4 \left(1 + \frac{A_0}{k} \right)$$

$$p_2 \gg p_1' \Rightarrow \frac{p_2}{p_1'} \approx 4 \left(1 + \frac{A_0}{k} \right) - 2 = 2 + 4 \frac{A_0}{k}$$

$$p_2 = \frac{4A_0 p_1'}{4\omega_u K} = 4\omega_u K$$

$$\phi_m = 76^\circ \Rightarrow p_2 = \frac{4A_0 p_1'}{K} \Rightarrow p_1' = \frac{p_2}{4A_0/K} = \frac{5 \times 10^5}{4 \times 10^4} = 50 \text{ rad/s}$$

$$p_1 = 10^5 \text{ rad/s} \longrightarrow p_1' = 50 \text{ rad/s}$$

" Dominant Pole "
Compensation


$$p_1' = \frac{\omega_{01}}{C_1'} = \frac{0.1 \times 10^{-3}}{C_1'} = 50$$

$$C_1' = \frac{1}{5} 10^{-5} = 2 \times 10^{-6} = 2 \mu\text{F}$$

$$C_1 = 1 \text{ nF}$$

$$\Delta C = C_1' - C_1 = 2 \mu\text{F} - 1 \text{ nF} = 1.999 \mu\text{F}$$

$$p_1 = 4. A_0$$

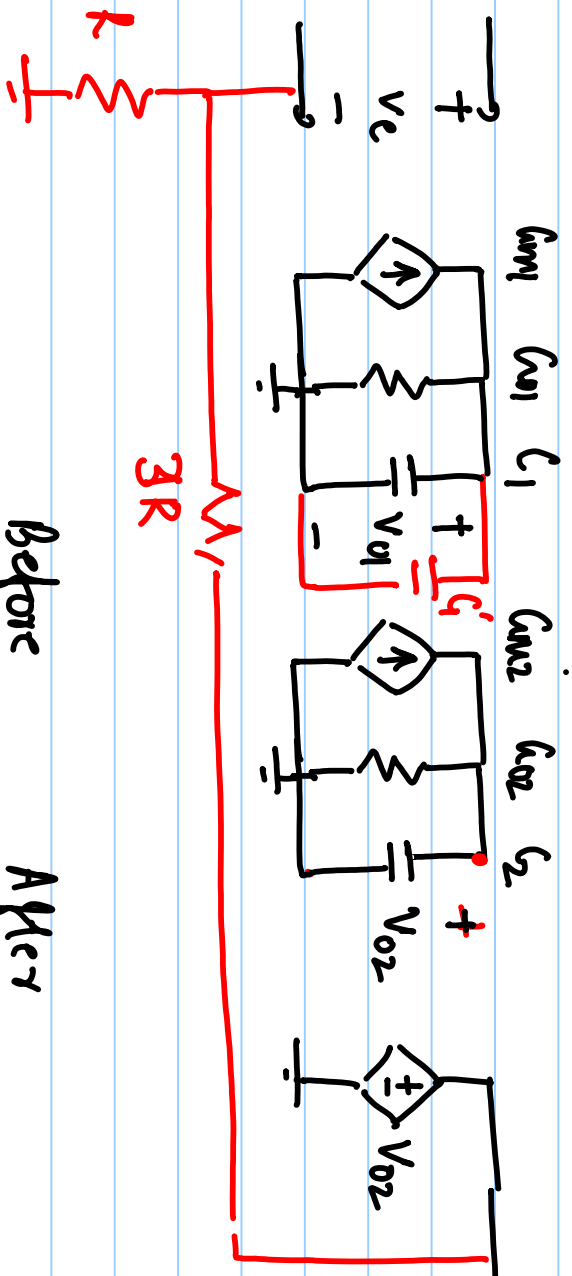

	Before	After
DC gain	2500	2500


p_1	10^5	50
-------	--------	----

p_2	5×10^5	5×10^5
-------	-----------------	-----------------


ω_n	117×10^5	1.25×10^5
------------	-------------------	--------------------

ϕ_m	3.4°	76°
----------	-------------	------------


C_1	1nF	$2\mu F$
-------	-----	----------

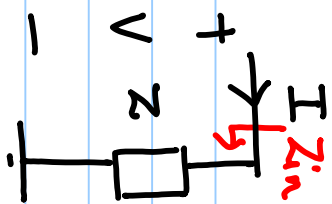

$$Z_{in} = \frac{V}{I} = Z$$

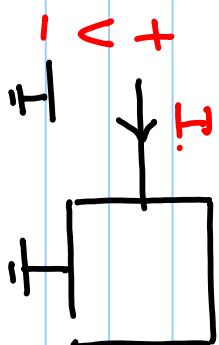

$$\frac{V}{I} = Z$$

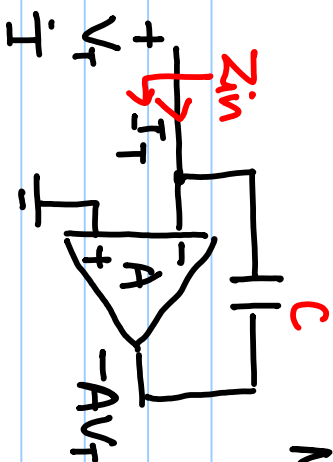

"Miller Multiplication"

$$I_T = \frac{V_T - (-AV_T)}{1/sC}$$

$$I_T = (1+A) V_T \times sC$$

$$Z_{in} = \frac{V_T}{I_T} = \frac{1}{s(1+A)C} = \frac{1}{sC \times}$$

$$C_x = (1+A)C$$