
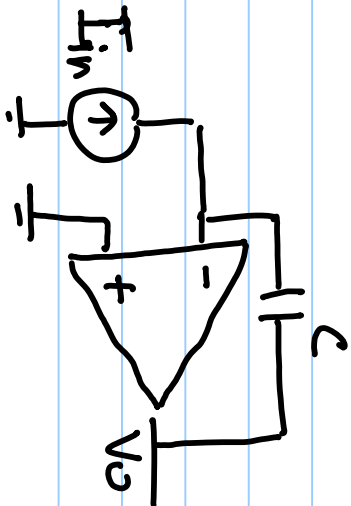


Lecture # 21

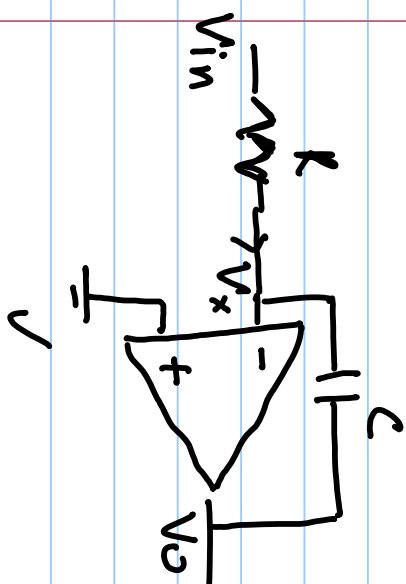

$$V_o = - \frac{I_{in} \cdot t}{C}$$



$$V_x = 0$$

$$\frac{V_{in}}{R} = - C \frac{dV_o}{dt}$$



$$\frac{dV_o}{dt} = - \frac{V_{in}}{RC}$$

$$V_o(t) = - \frac{1}{RC} \int V_{in} \cdot dt$$


$$\frac{V_{in}}{R} = \frac{-V_o}{1/sC}$$

$$\frac{V_o}{V_{in}} = \frac{-1}{sRC} = -\frac{k_i}{s}$$


Ex:

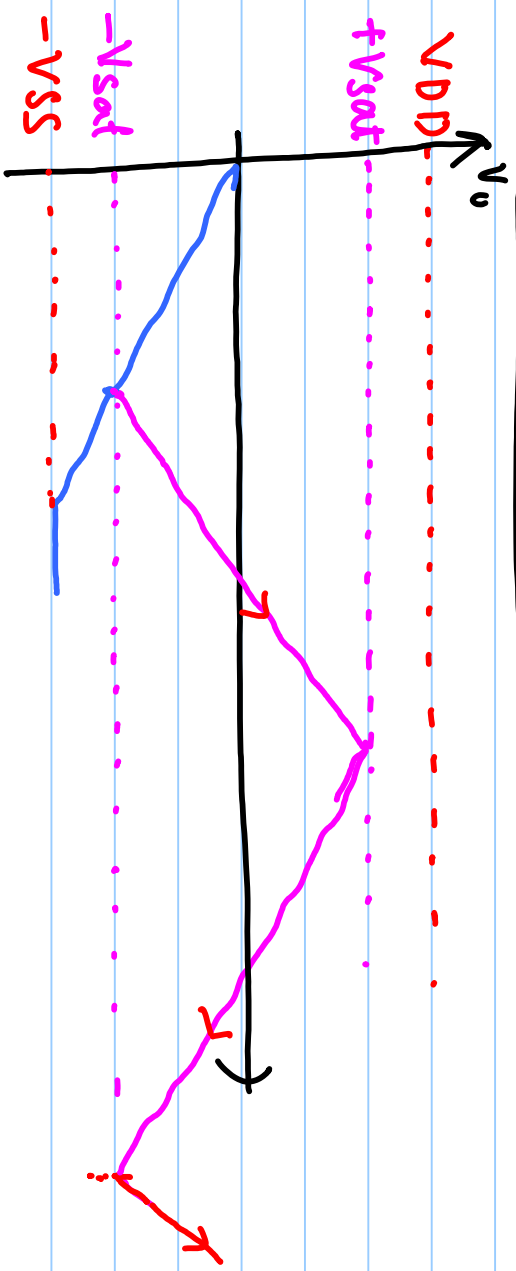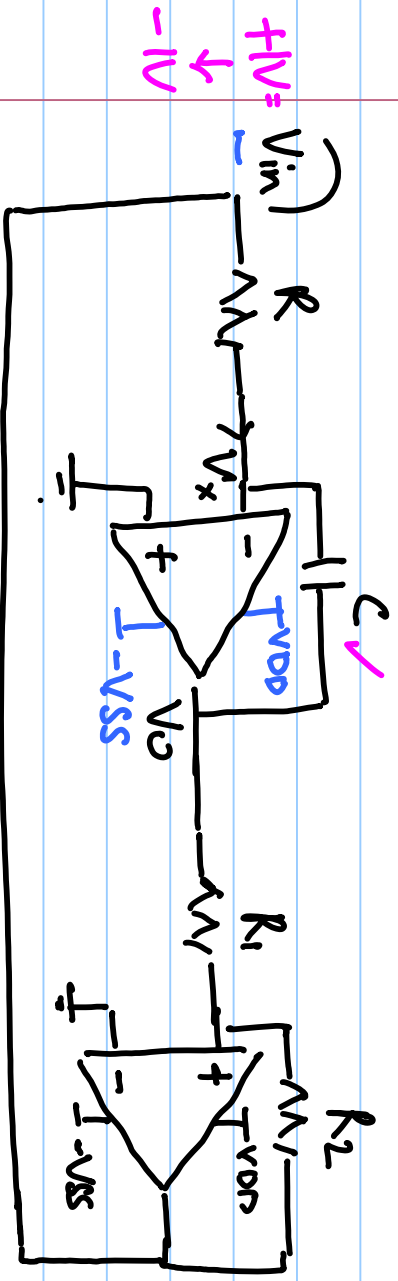

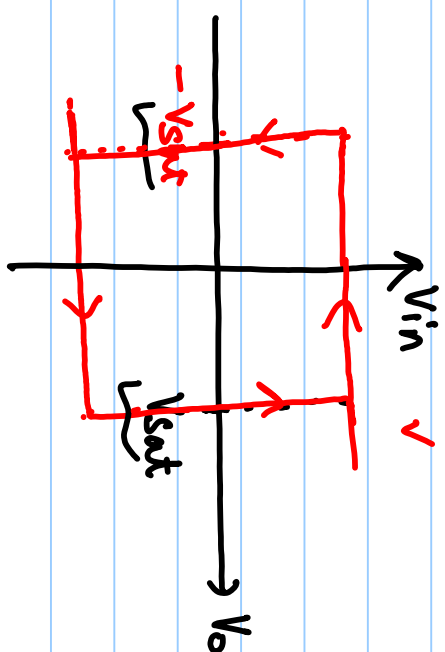$V_0 > V_{sat} \Rightarrow V_{in} = +1V$
 $V_0 < -V_{sat} \Rightarrow V_{in} = -1V$



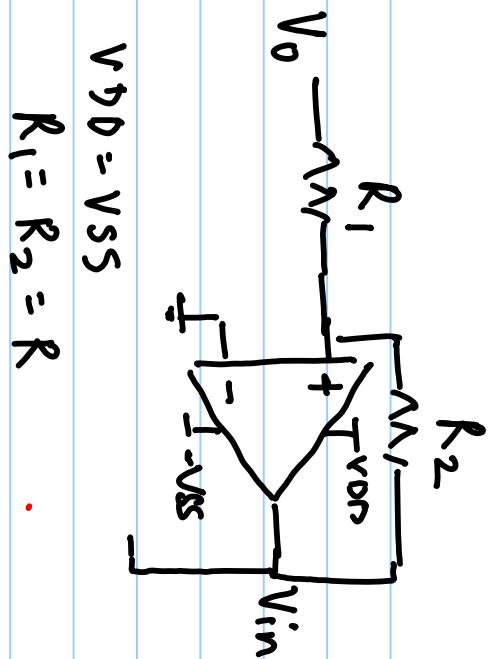
$$V_{sat} = \frac{k_1}{k_2} V_{DD} = \frac{k_1}{k_2} V_{SS}$$



$$V_{DD} = V_{SS}$$

$$R_1 = R_2 = R$$
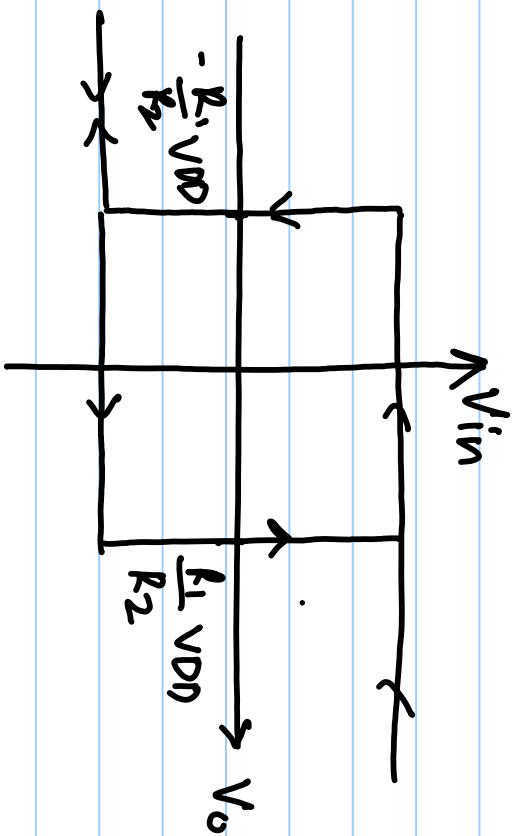
$$V_e = \frac{R_1}{R_1 + R_2} V_{in} + \frac{R_2}{R_1 + R_2} V_0 - 0$$





if $V_e > 0 \Rightarrow V_{in} = V_{DD}$

$V_e < 0 \Rightarrow V_{in} = -V_{SS}$

$$V_e = \frac{R_2}{R_1 + R_2} V_0 + \frac{R_1}{R_1 + R_2} \cdot V_{DD} < 0$$

$$V_0 = -\frac{R_1}{R_2} V_{DD}$$

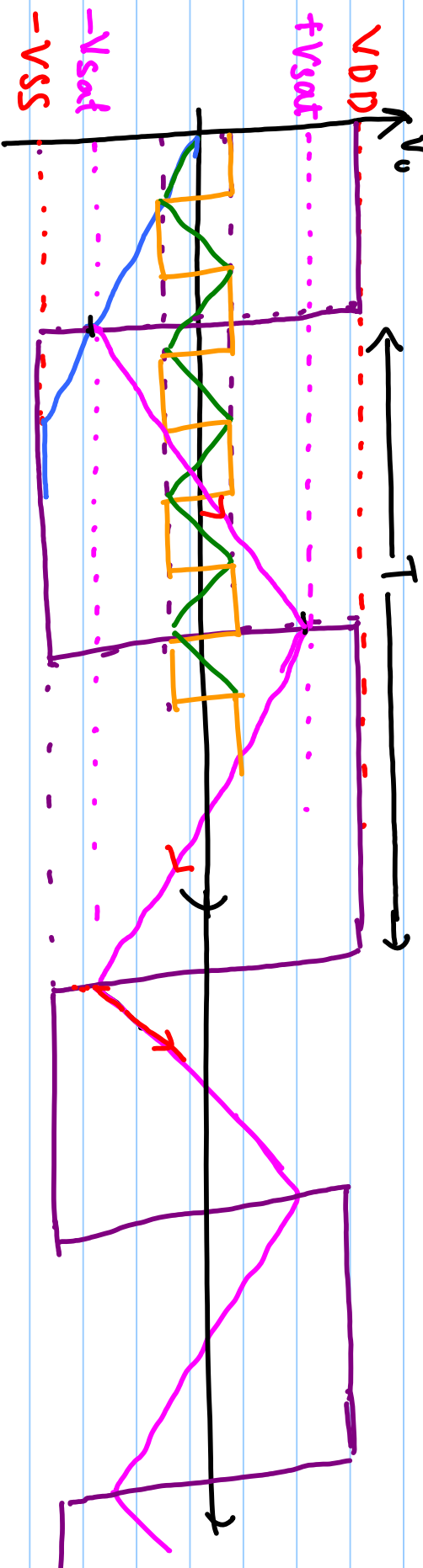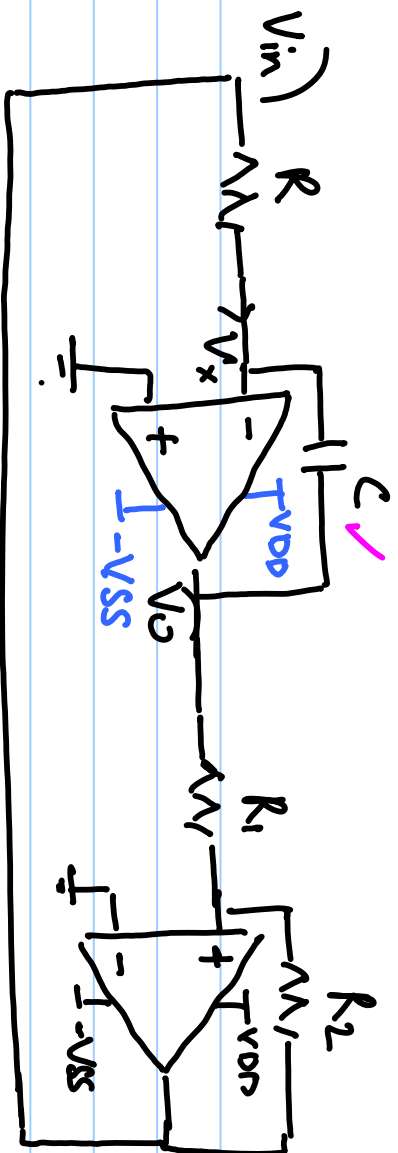

$$\frac{V_{DD}}{R} = -C \frac{dV_o}{dt}$$

$$\int dV_o = \int -\frac{V_{DD}}{RC} dt$$


$$\Delta 2V_{sat} = \frac{f V_{DD}}{RC} \cdot \frac{T}{2}$$

$$T = 4V_{sat} \cdot RC / V_{DD}$$

$$f = \frac{1}{T} = \frac{V_{DD}}{4RC \cdot V_{sat}}$$

$$= \frac{V_{DD}}{4RC \cdot \frac{R_1}{R_2} V_{DD}}$$

$$= \frac{R_2}{4RR_1C}$$

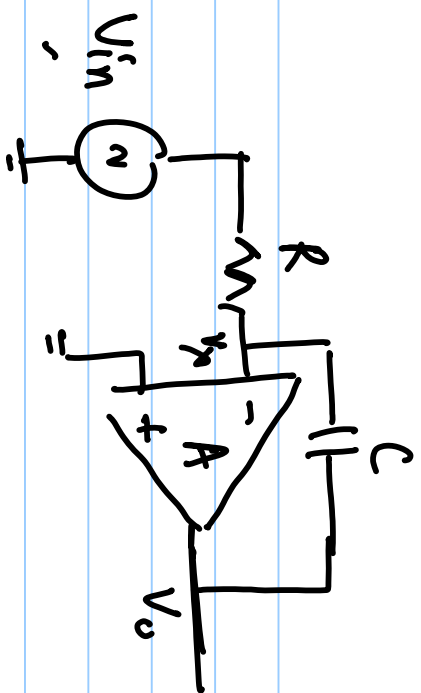

$$V_{in} = a \cdot \sin(\omega_0 t)$$

$$\frac{V_{in} - V_x}{R} = -C \frac{d(V_x - V_o)}{dt}$$

$$+ \frac{V_{in}}{RC} = - \frac{d(-\frac{V_o}{A} - V_o)}{dt} + \frac{-V_o/A}{RC}$$

$$= + \left(1 + \frac{1}{A}\right) \frac{dV_o}{dt} - \frac{V_o}{RC}$$

$$V_o(t) = a \left| H(j\omega_0) \right| \sin(\omega_0 t + \varphi)$$

$$V_o(t) = - \frac{aRC \left(1 + \frac{1}{A}\right)}{\frac{1}{A} + \omega_0 RC \sqrt{\left(1 + \frac{1}{A}\right)^2}} \sin(\omega_0 t) + \left\{ \cos(\omega_0 t) - e^{-\frac{t}{RC(1+1/A)}} \right\}$$