

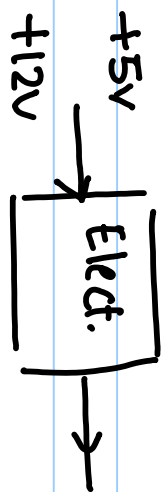


Lecture # 22

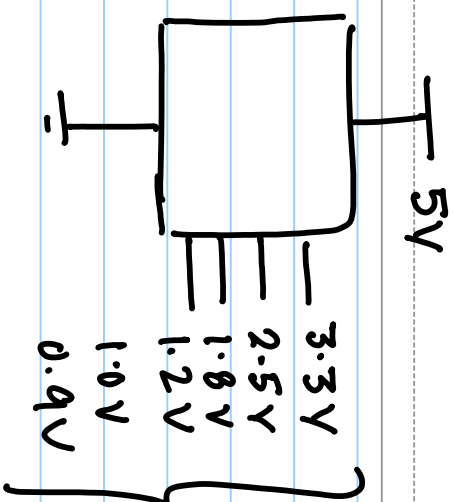

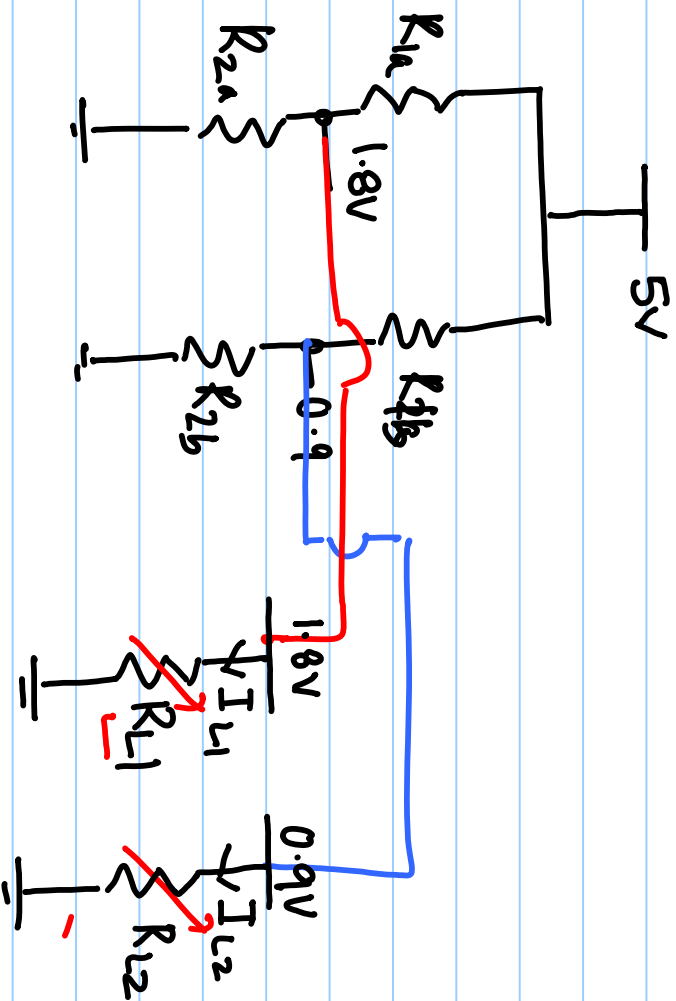Cell Phone:
 — Wireless Tx/Rx ✓
 — Audio ✓
 — Display ✓
 — Processor ✓




$$- \frac{R_{2a} || R_{L1}}{R_{1a} + (R_{2a} || R_{L1})} \times 5V = 1.8V$$

- Power dissipation (loss) in

$R_{1a}, R_{2a}.$

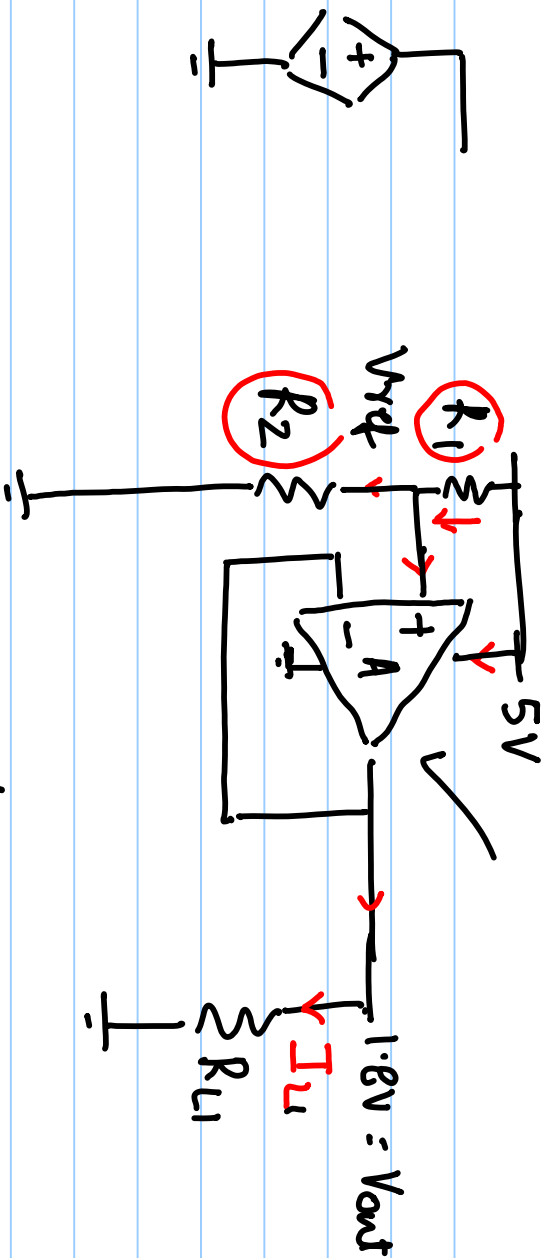- I_{L1}, I_{L2} vary. But, I don't want V_{L1}, V_{L2} to vary.



$$V_{rd} = \frac{R_2}{R_1 + R_2} \cdot 5V = 1.8V$$

$$V_{out} = V_{rd} = 1.8V$$

Power delivered to load = $V_{out} \cdot I_L$


Power dissipated in the circuit

$$= 5V \cdot (I_{L1} + I_{OPA}) + \text{Power in } L_1 \text{ and } R_2$$

$$\text{Efficiency, } \eta = \frac{V_{out} \cdot I_L}{V_{DD} \cdot (I_{L1} + I_{OPA})} \times 100$$

Best case, $\eta = 100 \times \frac{V_{out} \cdot I_L}{V_{DD} \cdot I_L} = \frac{V_{out}}{V_{DD}} \times 100$


$$\eta = \frac{1.8}{5.0} \times 100$$

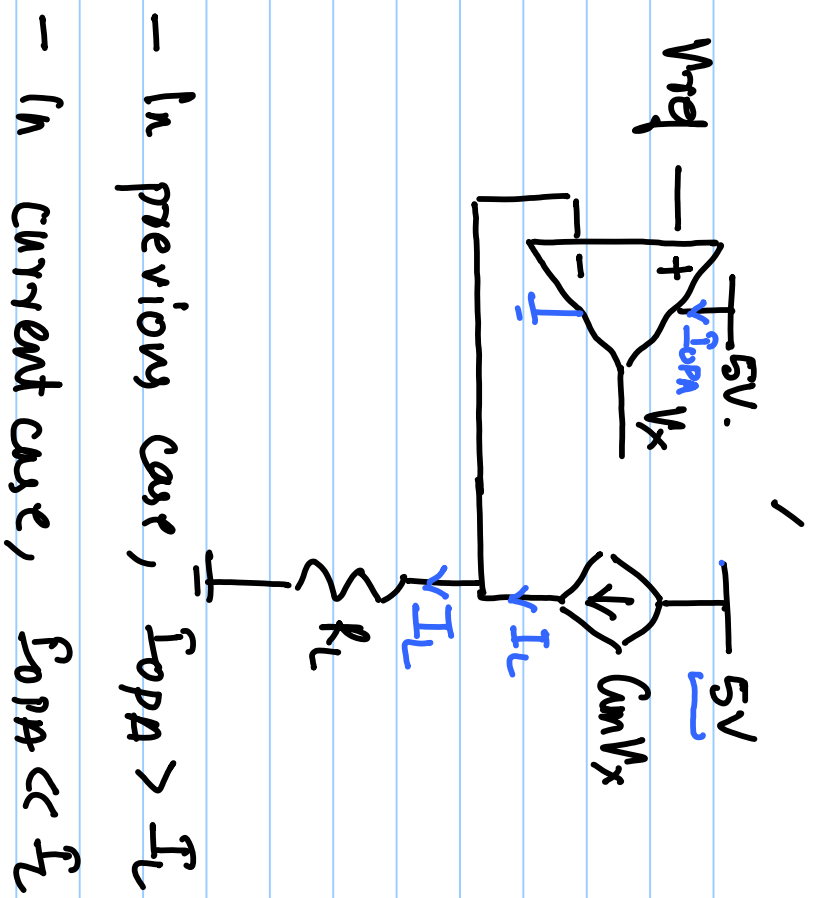

VECS: Using MOSFETs or BJTs


- In previous case, $I_{DPA} > I_L$

- In current case, $I_{DPA} \ll I_L$

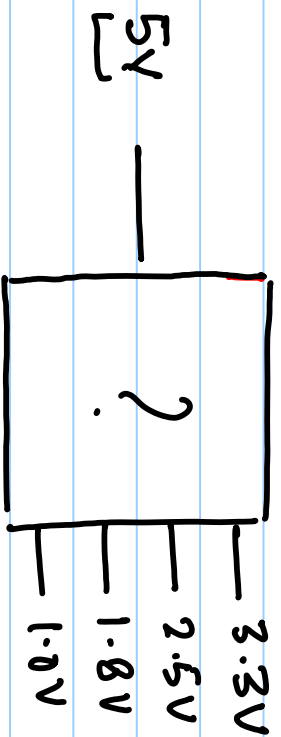


lossless




- Inductor
- Capacitor
- Transformer

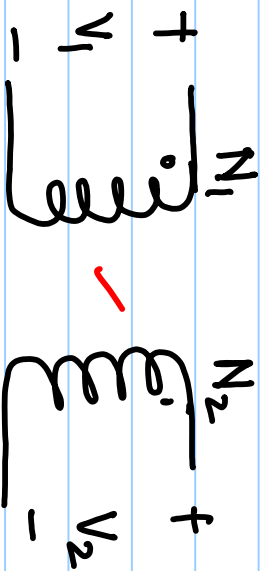

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

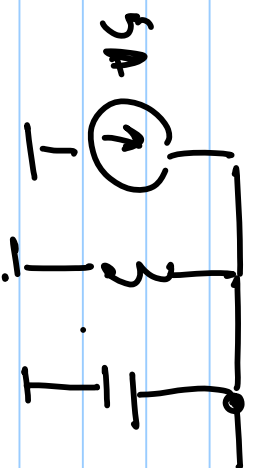

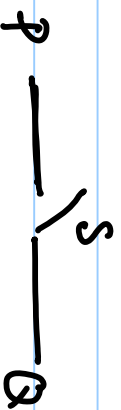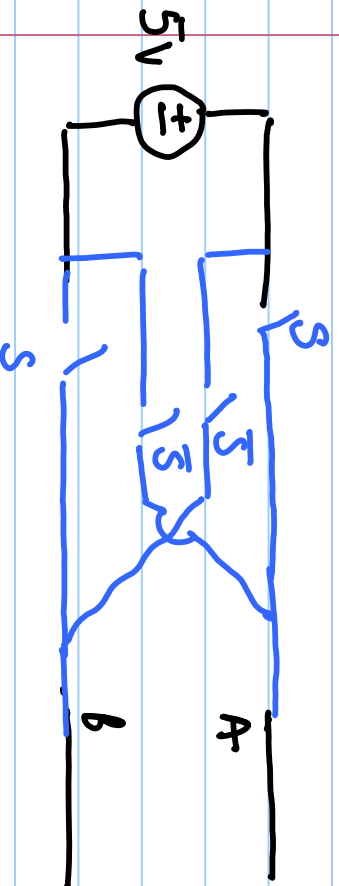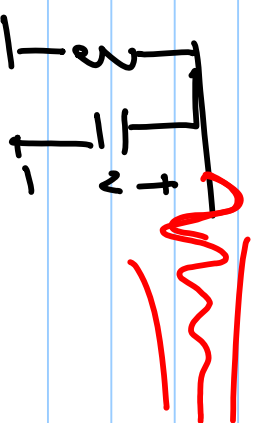DC \rightarrow AC \rightarrow AC \rightarrow DC




S is high: P \rightarrow X \rightarrow Q

P and Q are shorted

S is low: P \rightarrow \swarrow \searrow Q



P and Q are not connected.

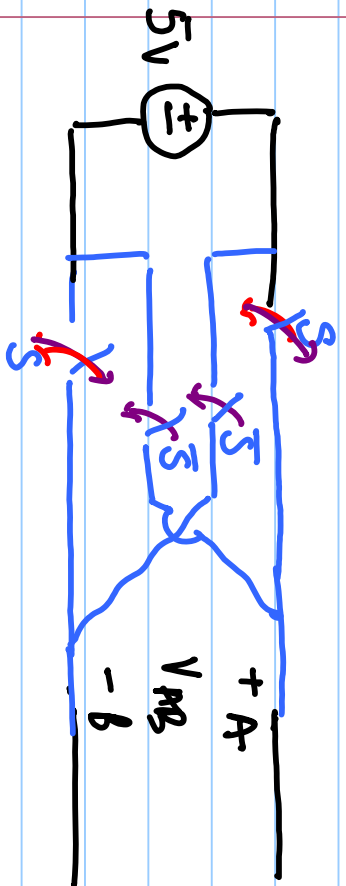

$$s \text{ is } 0, \bar{s} \text{ is } 1$$

$$V_{AB} = a_0 + \sum a_n \cos(n\omega_0 t) + b_n \sin(n\omega_0 t)$$

$$\omega_0 = \frac{2\pi}{T}$$

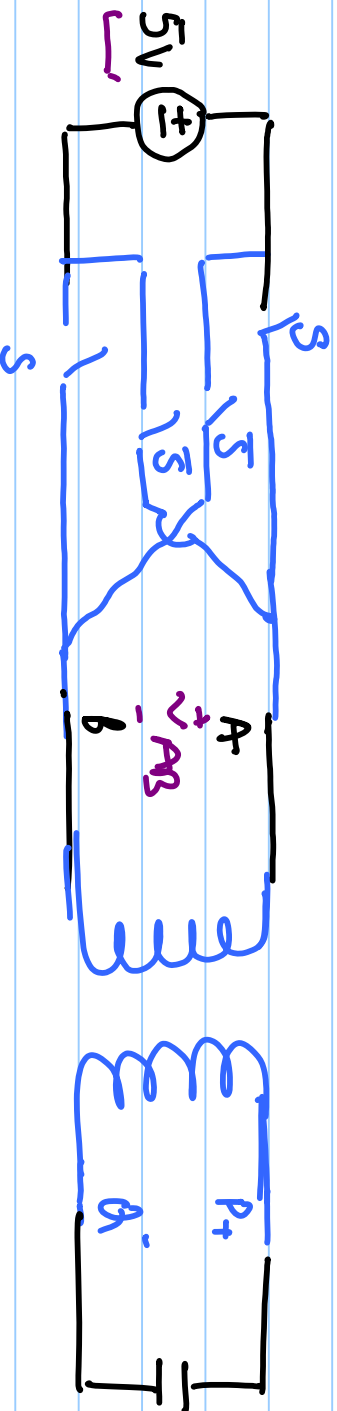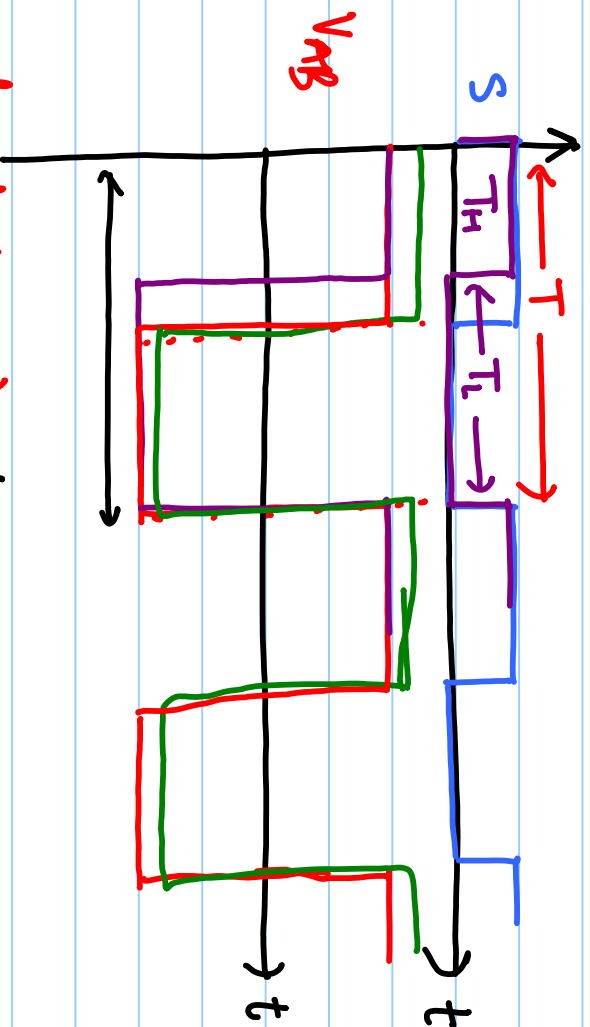

DC component of

$$V_{AB} = \frac{5V \cdot (T_H) - 5V T_L}{T_H + T_L}$$

$$= 5V \left(\frac{T_H - T_L}{T} \right)$$

$$= 5V \left(\frac{T_H - (T - T_H)}{T} \right)$$

$$= 5V \left(2 \cdot \frac{T_H}{T} - 1 \right)$$

$$= 5V (2 \cdot D - 1)$$

D is duty-cycle.

