

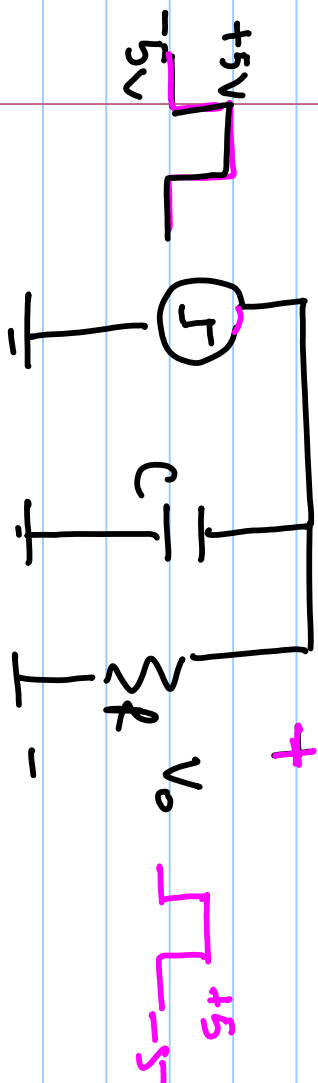
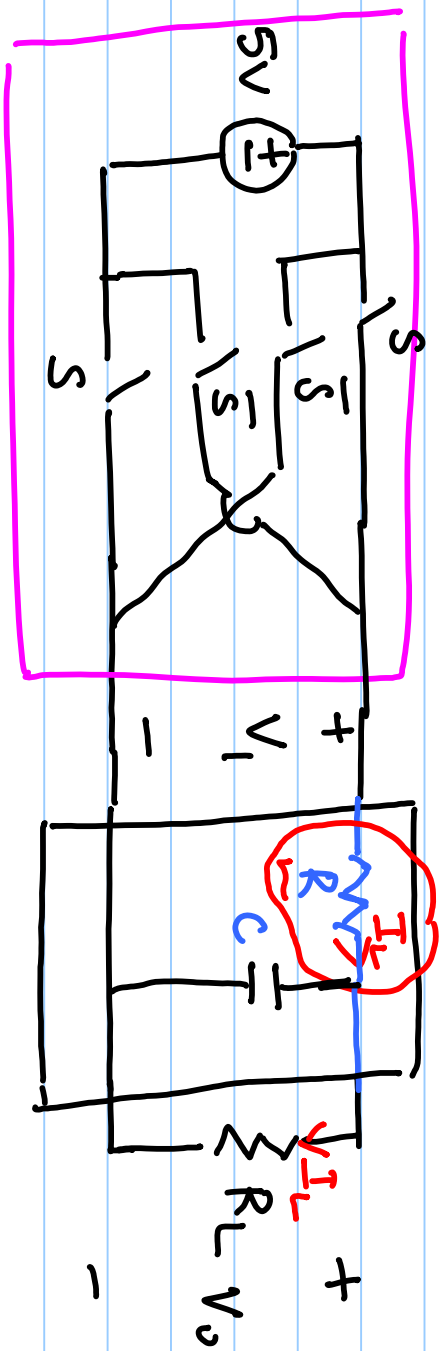


Lecture # 23

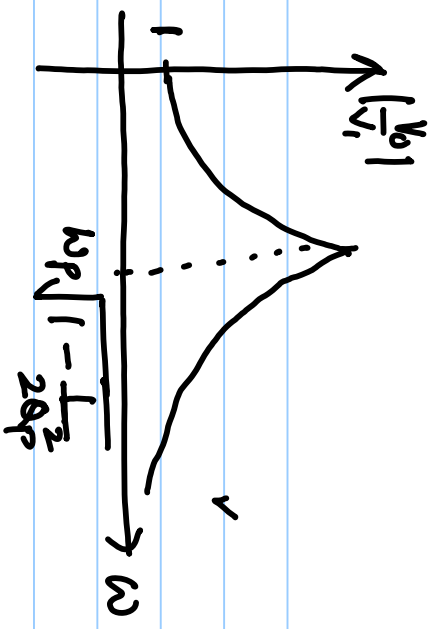

$$\frac{V_0}{V_1} = \frac{(R_L || \frac{1}{g_c})}{(R_L || \frac{1}{g_c}) + R_1}$$

$$= \frac{R_L}{R_L + R_1}$$

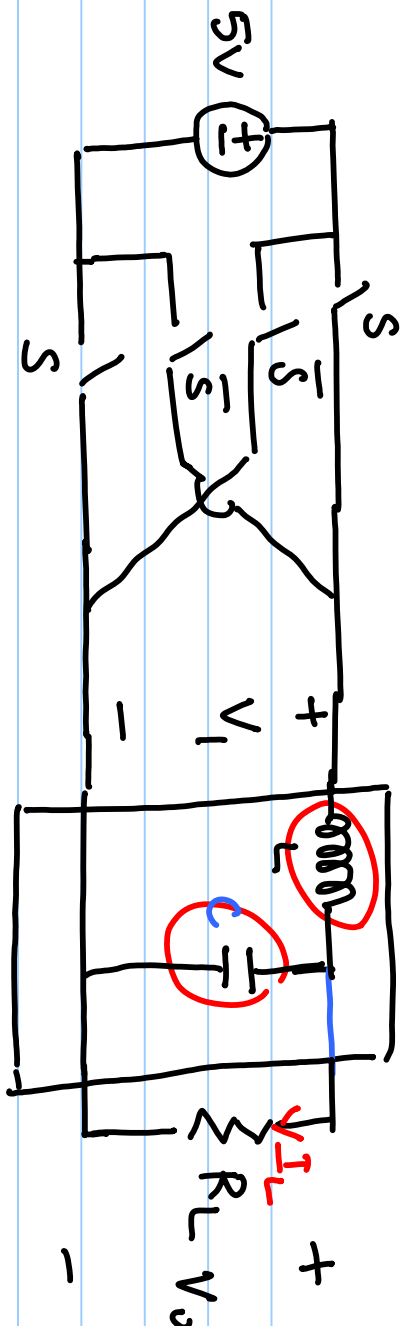


$$\frac{V_0}{V_1} = \frac{(R_L \parallel \frac{1}{sC})}{(R_L \parallel \frac{1}{sC}) + sL} = \frac{R_L / (1 + sCR_L)}{\frac{R_L}{1 + sCR_L} + sL} = \frac{R_L}{R_L + sL + s^2LC \cdot R_L}$$

$$= \frac{1}{s^2LC + s\frac{L}{R_L} + 1} = \frac{1}{(\frac{s}{\omega_p})^2 + \frac{s}{\omega_p Q_p} + 1}$$

$$\omega_p = \frac{1}{\sqrt{LC}}$$


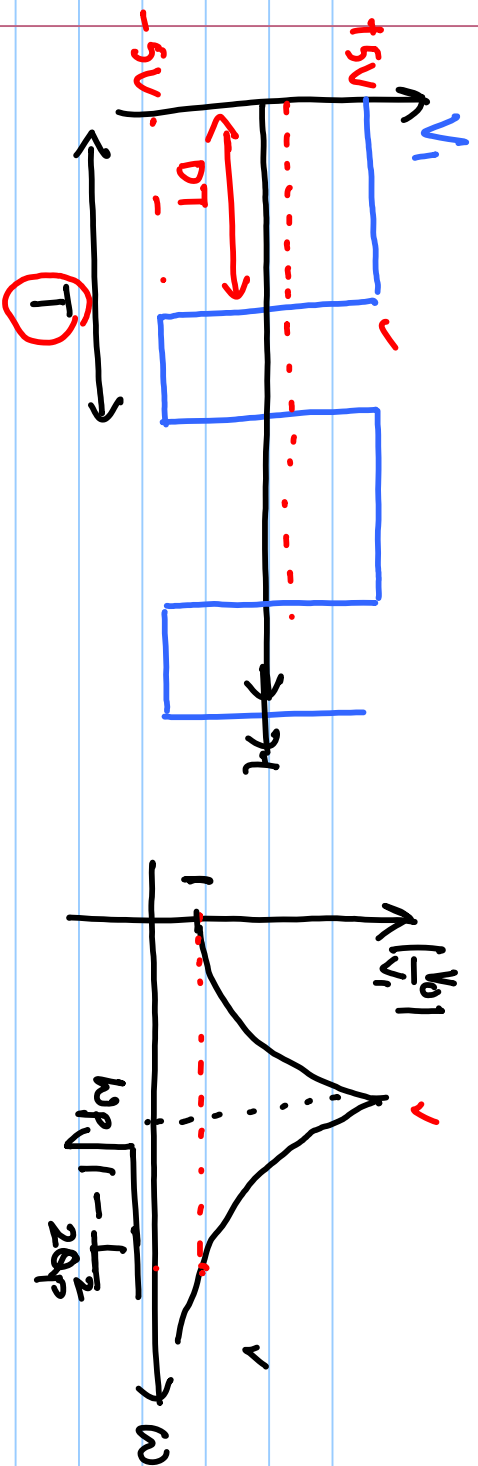
$$\omega_{pQ_p} = \frac{R_L}{L} \Rightarrow Q_p = \sqrt{LC} \frac{R_L}{L} = R_L \sqrt{\frac{C}{L}}$$



Sampling frequency, $f_s = \frac{1}{T}$, $\omega_s = 2\pi f_s = \frac{2\pi}{T}$

V_1 has dc component and frequency dependent components at $n f_s$.
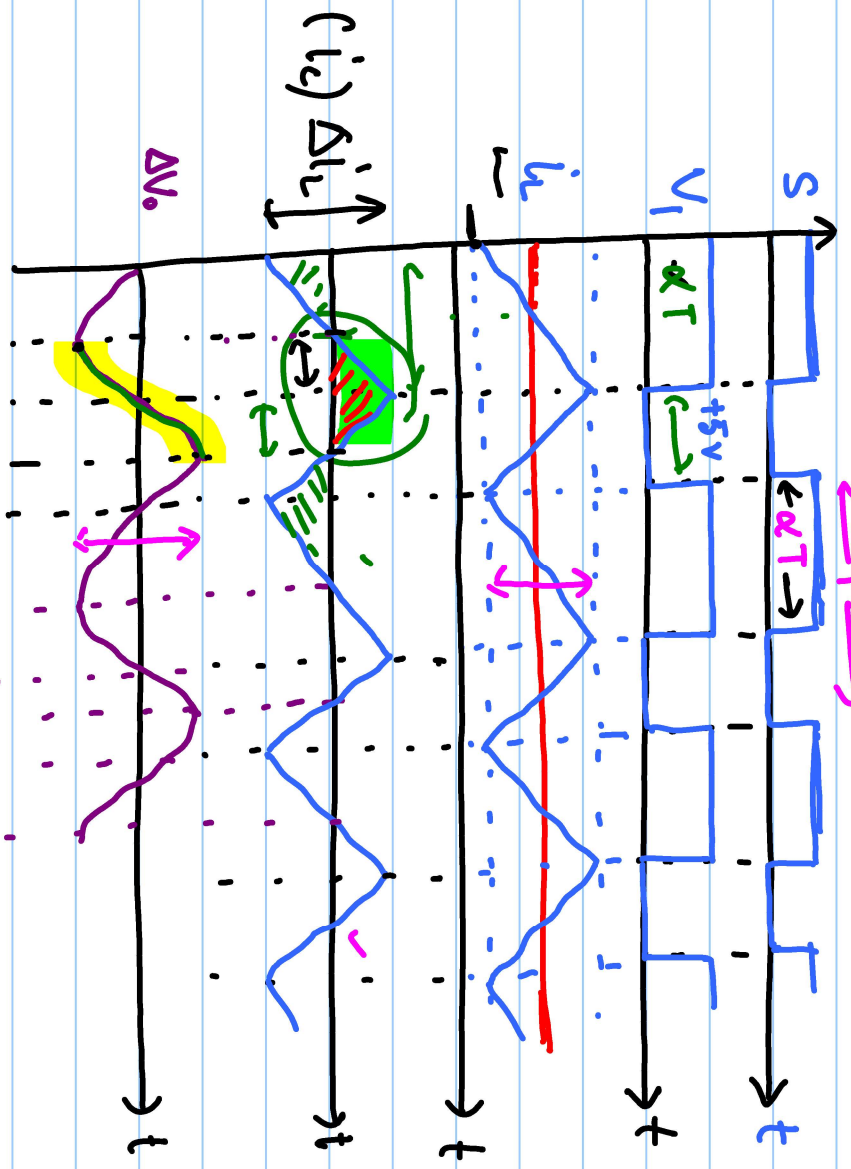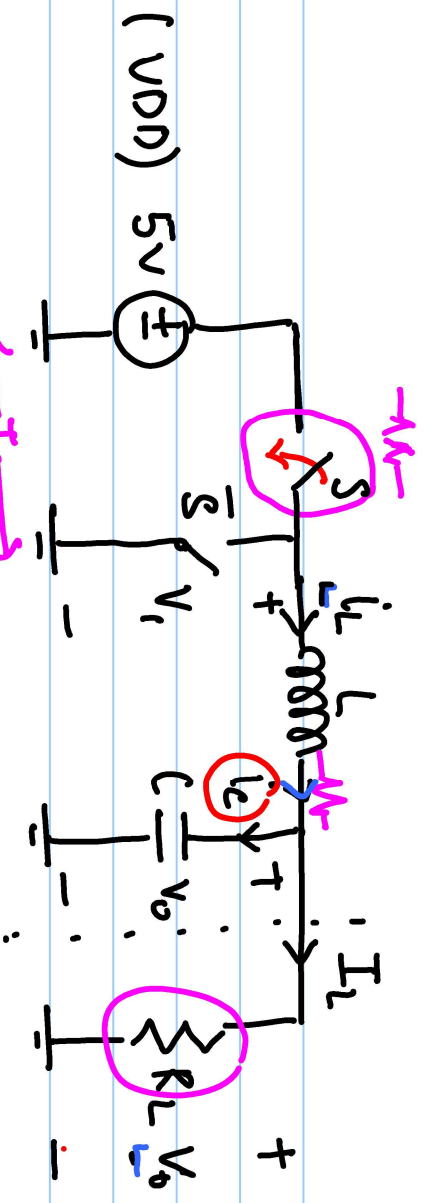
$$\omega_s \gg \omega_p \sqrt{1 - \frac{1}{2Q_p^2}}$$



$$i_L = C \frac{dV_0}{dt} \Rightarrow \int dV_0 = \frac{1}{C} \int i_L dt$$

- To find i_L , we assume V_0 is constant.

- When s is high,

$$V_{DD} - V_0 = L \frac{di_L}{dt} \quad (1)$$

$$0 - V_0 = L \frac{di_L}{dt} \quad (2)$$

$$i_L = \frac{V_{DD} - V_0}{L} \cdot t$$

$$i_L = -\frac{V_0}{L} \cdot t$$

$$V_0 = \frac{\alpha T \cdot V_{DD} + (1-\alpha) \cdot 0}{T} = \alpha V_{DD}$$

$$\Delta i_L = \frac{V_{DD} - \alpha V_{DD}}{L} \cdot \alpha T$$

$$\Delta i_L = \frac{\alpha(1-\alpha)V_{DD} \cdot T}{L}$$

$$\Delta V_o = \frac{1}{2} \left[\frac{\alpha T}{2} \cdot \frac{\Delta i_L}{2} + \frac{(1-\alpha)T}{2} \cdot \frac{\Delta i_L}{2} \right]$$

$$+ \text{norm} \checkmark$$

$$= \frac{1}{8C} T \cdot \Delta i_L \cdot (\alpha + (1-\alpha))$$

$$= \frac{1}{8C} T \alpha (1-\alpha) V_{DD} \frac{T}{L}$$

$$= \frac{T^2}{8LC} \alpha (1-\alpha) V_{DD}$$

$$\Delta V_o = \frac{1}{8LC f_s^2} \alpha (1-\alpha) V_{DD} \checkmark$$

- Power efficiency of "Buck" converter is 95%.

- To minimize ΔV_o , increase f_s, LC
 - Increasing L or C cost area
 - Increasing f_s , losses in switches will increase.
- Δi_L results in power loss in resistance in series w/ inductor

$$V = L \frac{di}{dt}$$

$$V = \frac{1}{C} \int i \cdot dt$$