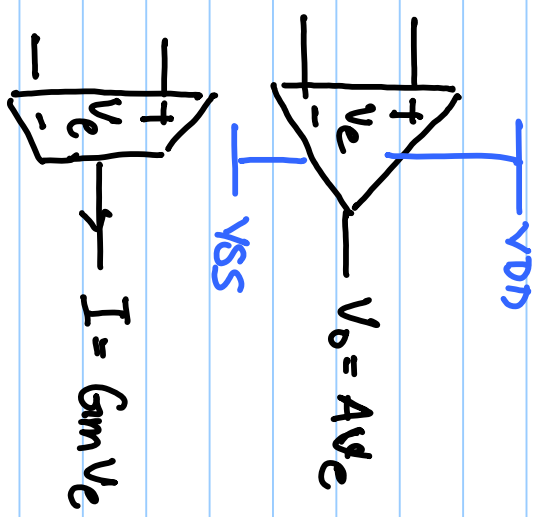


EE2019 : Analog Systems.


1. Opamp : voltage gain + power gain

Voltage buffers, filters, oscillators,

2. Transconductance  $G_m$  :



3. Linear elements  $R, L, C, v$

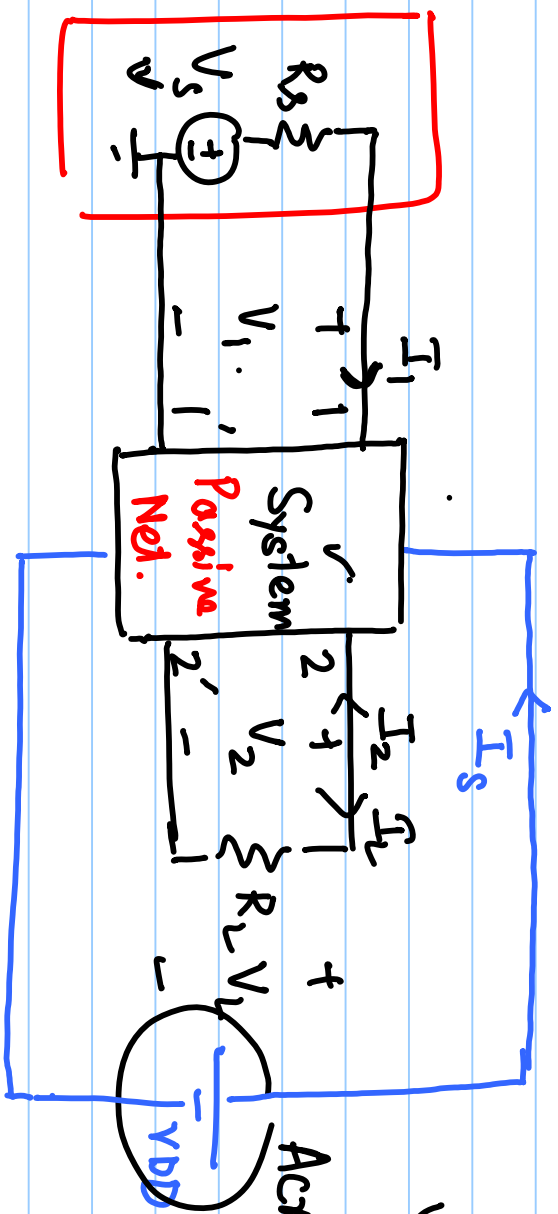

$$V_1 I_1 + V_2 I_2 > 0$$


Across load  $R_L$ ,

$$P_L = -I_2 V_2 = -I_2 V_L$$


$$V_1 I_1 + \underbrace{V_{DD} I_s}_{> 0} + V_2 I_2 > 0$$

$$-V_2 I_2 > V_1 I_1 \quad \checkmark$$

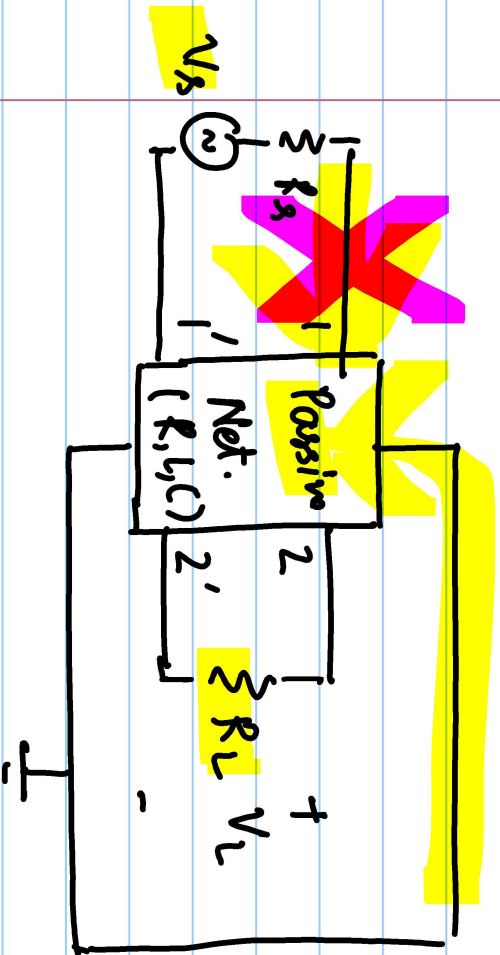If  $V_s = a \sin(\omega t) \quad \checkmark \rightarrow P_L = \frac{V_L^2}{R_L}$



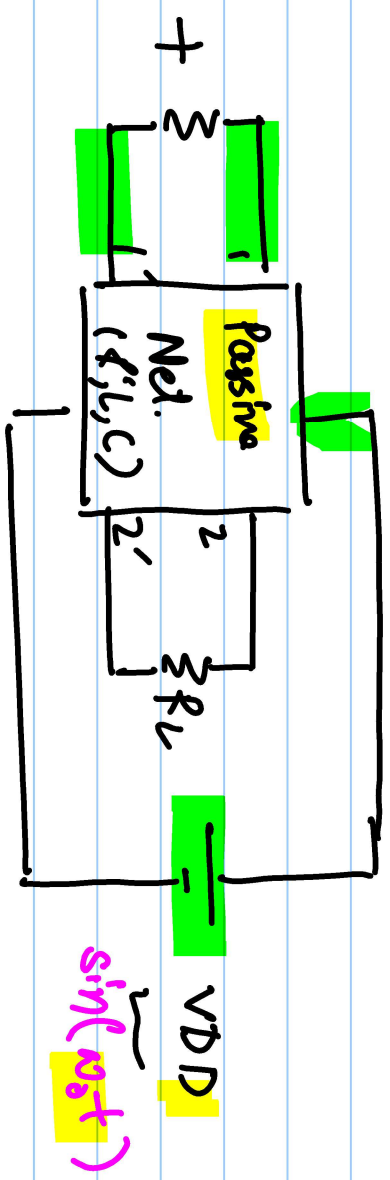
Passive and non-linear  
Passive and linear




#1: Non-linear elements to deliver power  
to the load  $R_L$ .
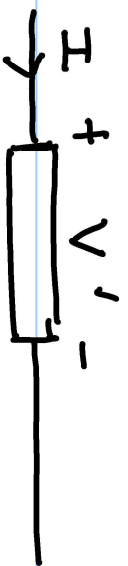
#2: Active elements


$V_L I_L$ : Power delivered to the load  $\checkmark$



$$I = f(V) \quad \text{Non-linear}$$

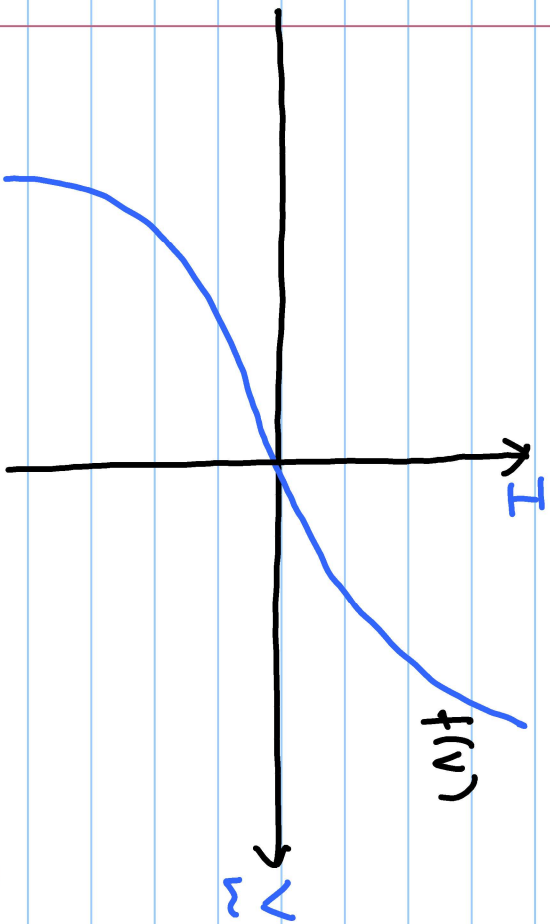

$$V \cdot I \geq 0$$


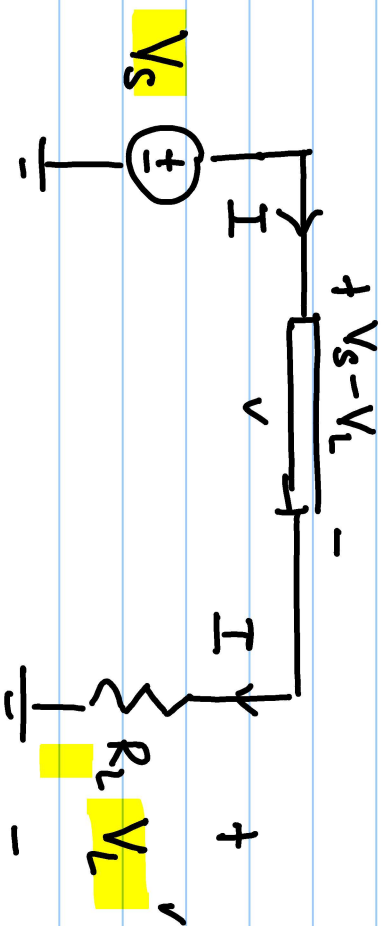


$$I = f(V) = f(V_S - V_L) \quad (1) \quad V$$

$$I = \frac{V_L}{R_L} \quad (2) \quad V$$

Ex:  $f(V) = a_1 V + a_3 V^3 + a_5 V^5 + \dots$
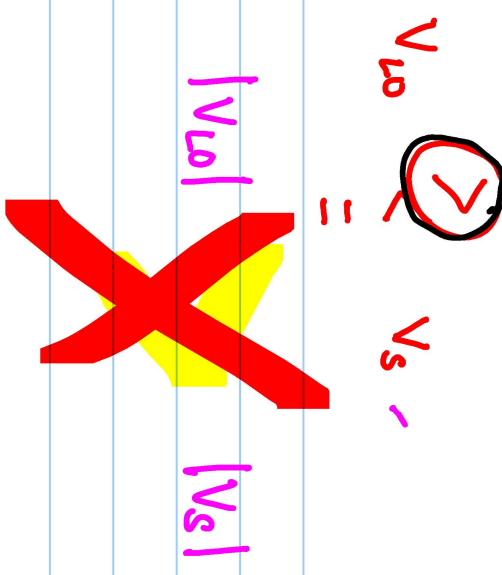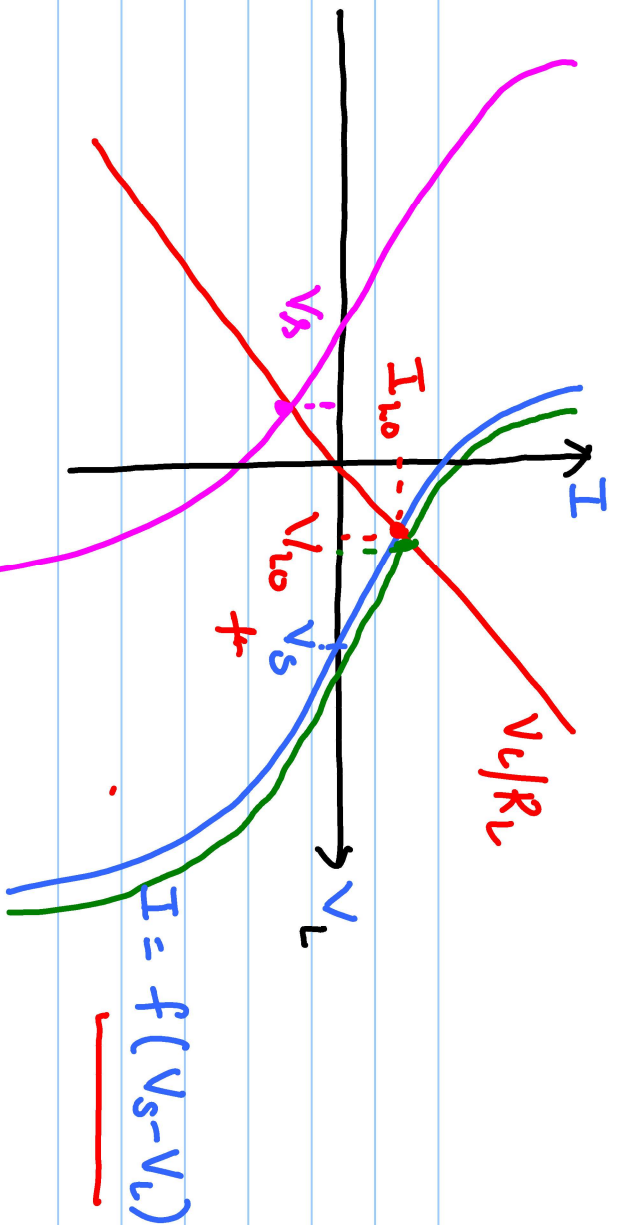
$$I = a_1 (V_S - V_L) + a_3 (V_S - V_L)^3 + \dots = \frac{V_L}{R_L} \quad \checkmark$$



$$f(V) \rightarrow f(V_S - V_L)$$

$$f(V) \rightarrow f(-V) \rightarrow f(-(V_L - V_S)) = f(V_S - V_L)$$

$$V_S = V_{S0} \rightarrow V_{S0} + V_S \checkmark$$

What happens to  $V_L$ .