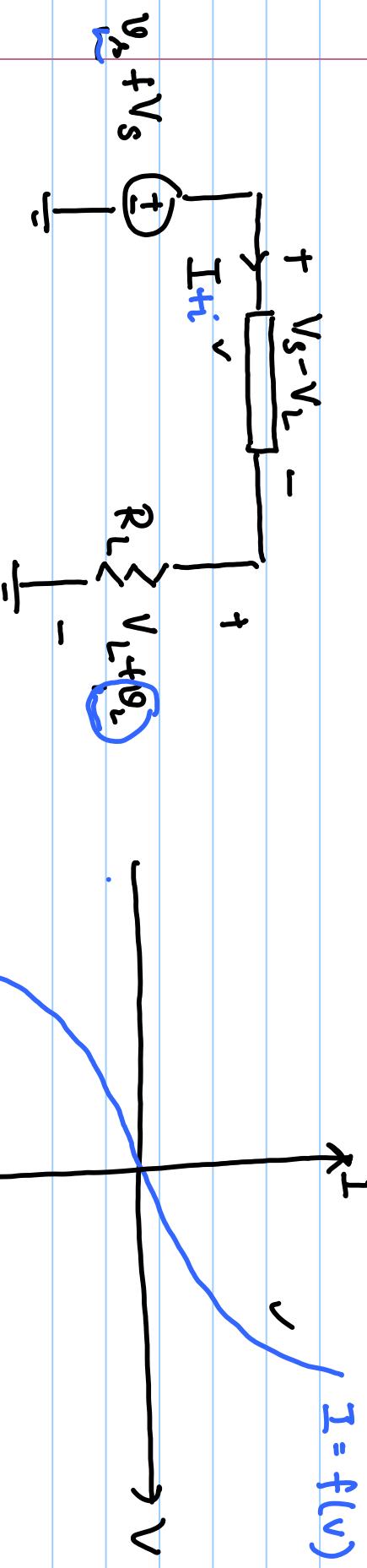



# Lecture # 02

Note Title

05-08-2021




$$I = f(V_s - V_L) = \frac{V_L}{R_L}$$

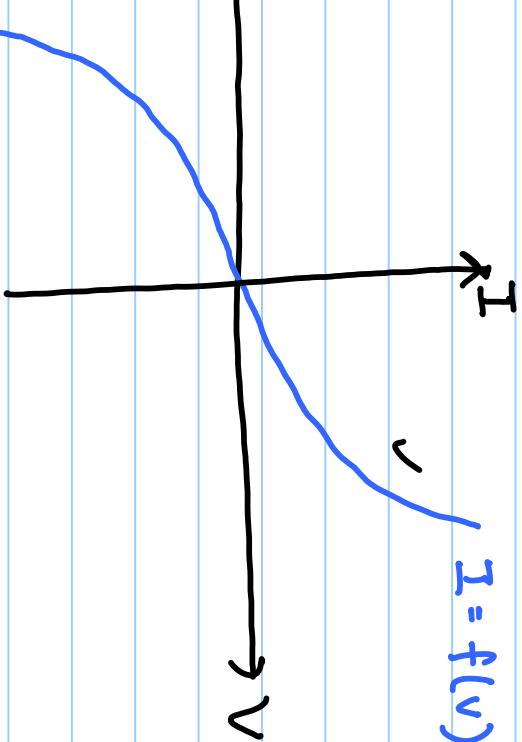

$$I_o = f(V_{s0} - V_{L0}) = f(V_{s0} - V_{L0}) = \frac{V_{L0}}{R_L}$$
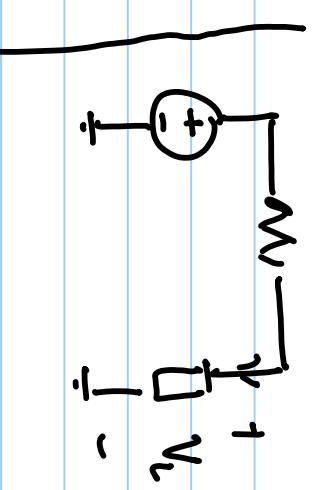
$$V_s: V_{s0} \rightarrow V_{s0} + \vartheta_s \quad \rightarrow \quad V_L: V_{L0} \rightarrow V_{L0} + \vartheta_L$$



$$I = f(V_{S0} + V_s - V_{L0} - V_L) = f(\underbrace{V_{S0} - V_{L0}}_R + \underbrace{V_s - V_L}_r) \cdot$$

$$I_0 + i = f(V_{S0} - V_{L0}) + f'(V_{S0} - V_{L0}) \cdot \frac{(V_s - V_L)^2}{2!} + \dots$$


$$\frac{V_L}{R} = i = f'(V_{S0} - V_{L0}) (V_s - V_L) + f''(V_{S0} - V_{L0}) \frac{(V_s - V_L)^2}{2!}.$$

If:  $\sum_{k \geq 2} f^k(V_{S0} - V_{L0}) \frac{(V_s - V_L)^k}{k!} \ll f'(V_{S0} - V_{L0}) (V_s - V_L)^2 + f'''(V_{S0} - V_{L0}) \frac{(V_s - V_L)^3}{3!} + \dots$


$$i = \frac{V_L}{R_L} \approx f'(V_{S0} - V_{L0}) (V_s - V_L)$$

$$\frac{V_L}{R_L} = \frac{V_s - V_L}{\underbrace{f'(V_{S0} - V_{L0})}_{R_n}} = \frac{V_s - V_L}{R_n}$$

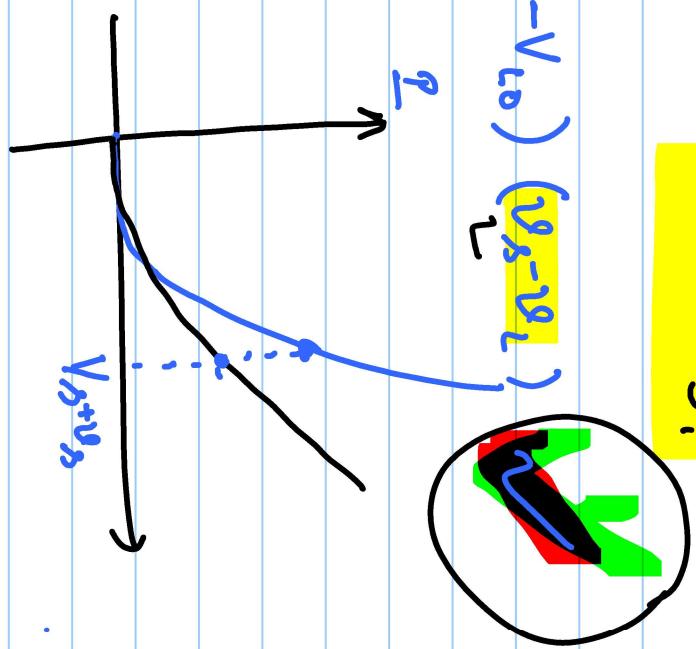
$$\Rightarrow \boxed{V_L = \frac{R_n}{R_L + R_n} V_s} \text{ for } V_s = V_{S0}, V_L = V_{L0}$$




$$(V_{SO} - V_{LO} + V_{BE} \cdot v_L)$$

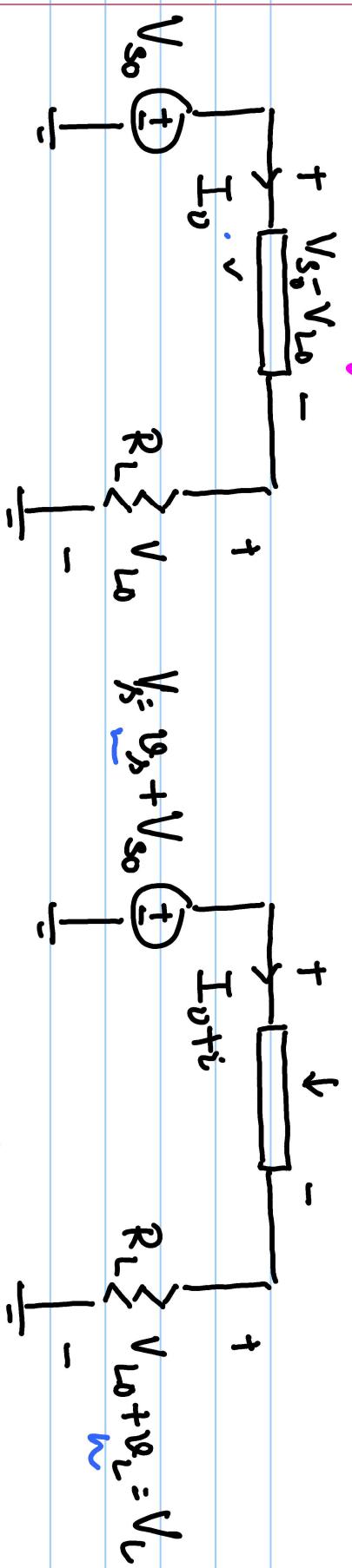

#1

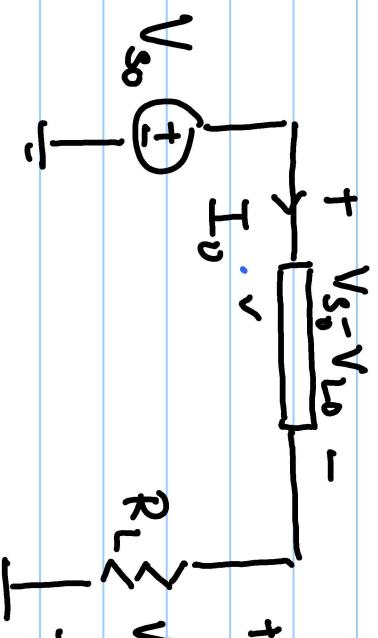

Non-linear Analysis /

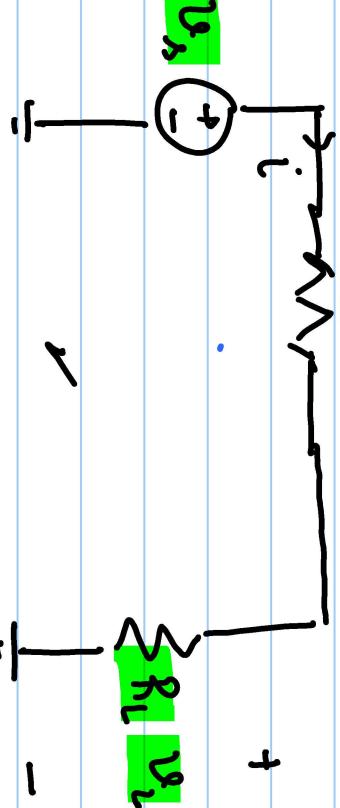

~~$v_{r=0}$~~


$$R_n = \frac{1}{f'(V_{SO} - V_{LO})}$$

Linear Ckt. Analysis ✓

$R_n$



Volume

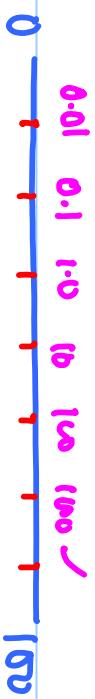

db 5 10 15 20

Brightness

- Small changes in i<sub>fp</sub> at given operating condition.

-  $V_{g0}$ ,  $V_{l0}$  : operating points  
bias condition.

-  $v_s$ ,  $v_l$ ,  $i$  are small signals

Given a non-linear element

- Non-linear analysis to get operating points ( $V, I$ )


- linearise non-linear elements using first derivative for I-V relation

$$\text{Non-lin. Eq: } I = f(V) = a_1 V + a_2 V^2 + \dots$$

- Replace non-linear element with their linear counterpart.

- Analyze new ckt. for small changes in the i<sub>fp</sub>.

"Diode"

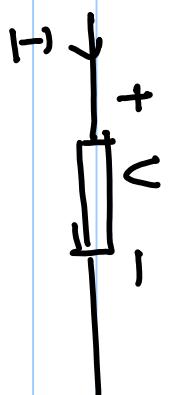

$$I = f(V)$$

$$I = I_s \left[ \exp\left(\frac{V}{V_T}\right) - 1 \right]$$

