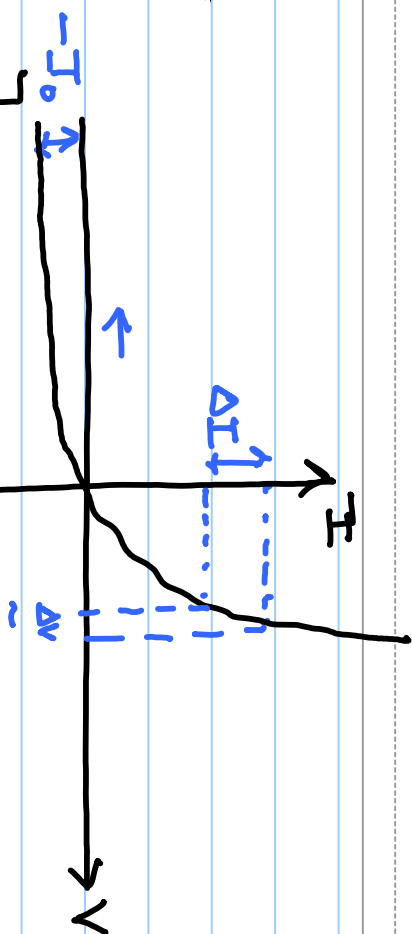


$$I = I_0 \left[\exp\left(\frac{V}{V_T}\right) - 1 \right]$$

I_0 : Reverse saturation current.



V : Potential difference across diode.

V_T : Thermal voltage

$$V_T = \frac{kT}{q} = \underline{25.9 \text{ mV}} @ 300 \text{ K}$$

k : Boltzmann's constant

T : Temperature in Kelvin

q :

$V < 0$: Diode is reverse biased



$V > 0$: Diode is forward biased.

$$I \approx I_0 \exp\left(\frac{V}{V_T}\right)$$

$$V = V_T \ln\left(\frac{I}{I_0}\right)$$

When I changes by $10\times$
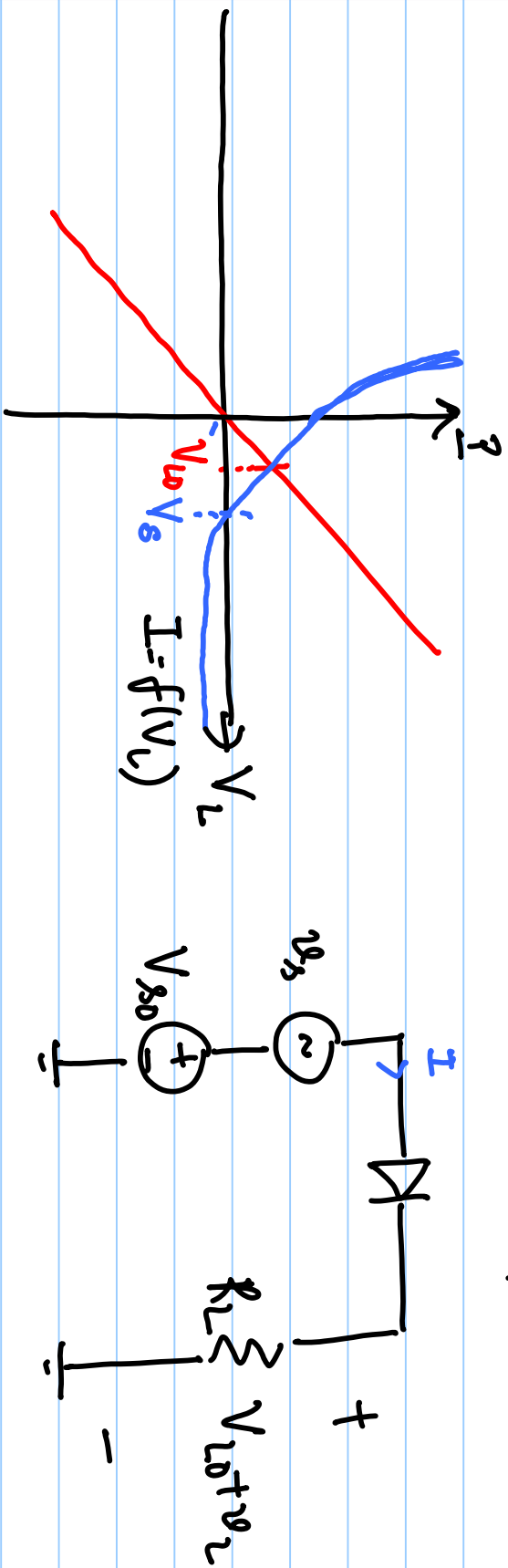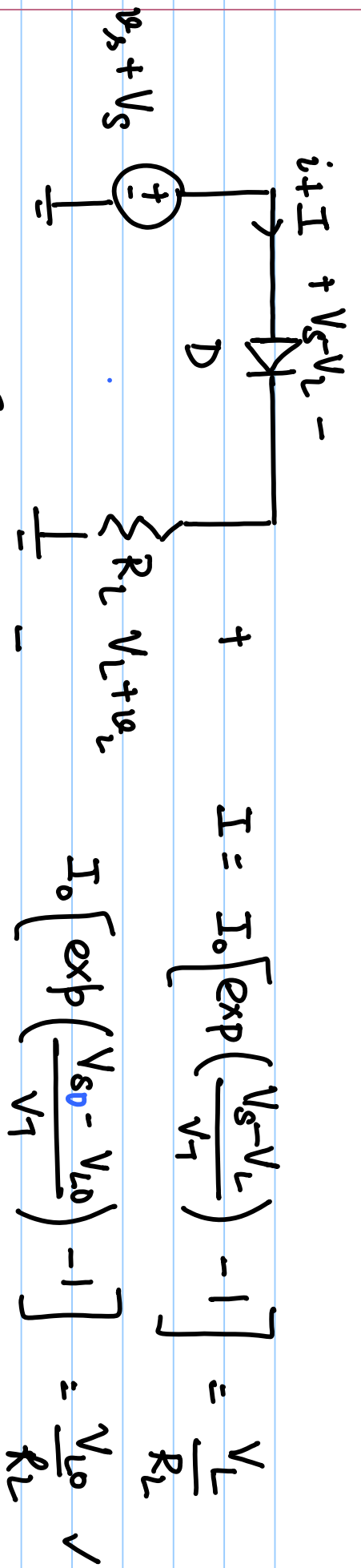
$$\Delta V = V_T \ln(10) = 60 \text{ mV}$$



$$I + i = I_0 \left[\exp\left(\frac{V_{s0} + v_s - V_{L0} - v_L}{V_T}\right) - 1 \right] = \frac{V_{L0} + v_L}{R_L}$$

#1. Operating point of non-linear system. $V_{s0}, V_{L0} \checkmark$

#2.

$$I = \underbrace{I_0 \left[\exp \left(\frac{V_b - V_L}{V_T} \right) - 1 \right]}_{f(x)}$$

$$I_b = I_0 \left[\exp \left(\frac{V_{s0} - V_{L0}}{V_T} \right) - 1 \right]$$

$$I_0 = 10^{-14} \text{ A}$$

$$= I_0 \left[\exp \left(\frac{V_{s0} - V_{L0}}{V_T} \right) - 1 \right] + \frac{I_0}{V_T} \exp \left(\frac{V_{s0} - V_{L0}}{V_T} \right) \times \frac{v_s - v_L}{1!}$$

$$+ \frac{I_0}{V_T^2} \exp \left(\frac{V_{s0} - V_{L0}}{V_T} \right) \times \frac{(v_s - v_L)^2}{2!} + \dots$$

$$= \underbrace{I_b + \frac{I_0 \exp \left(\frac{V_{s0} - V_{L0}}{V_T} \right)}{V_T}}_{(v_s - v_L)} + \dots$$

$$\approx I_b + \frac{I_0}{V_T} (v_s - v_L) + \frac{I_0}{V_T^2} \frac{(v_s - v_L)^2}{2!} + \dots$$

$$I_{b+i} \approx I_b + \frac{I_0}{V_T} (v_s - v_L)$$


$$I_{b+i} = \cancel{I_b} + \frac{I_0}{V_T} (v_s - v_L) = \cancel{I_b} + \frac{v_L}{R_L}$$

$$\frac{V_S - V_L}{R_D} = \frac{V_L}{R_L}$$

$$V_L = \frac{R_L}{R_L + R_D} V_S$$

$$I = f(V)$$

$$R_D = \frac{1}{f'(V)}$$

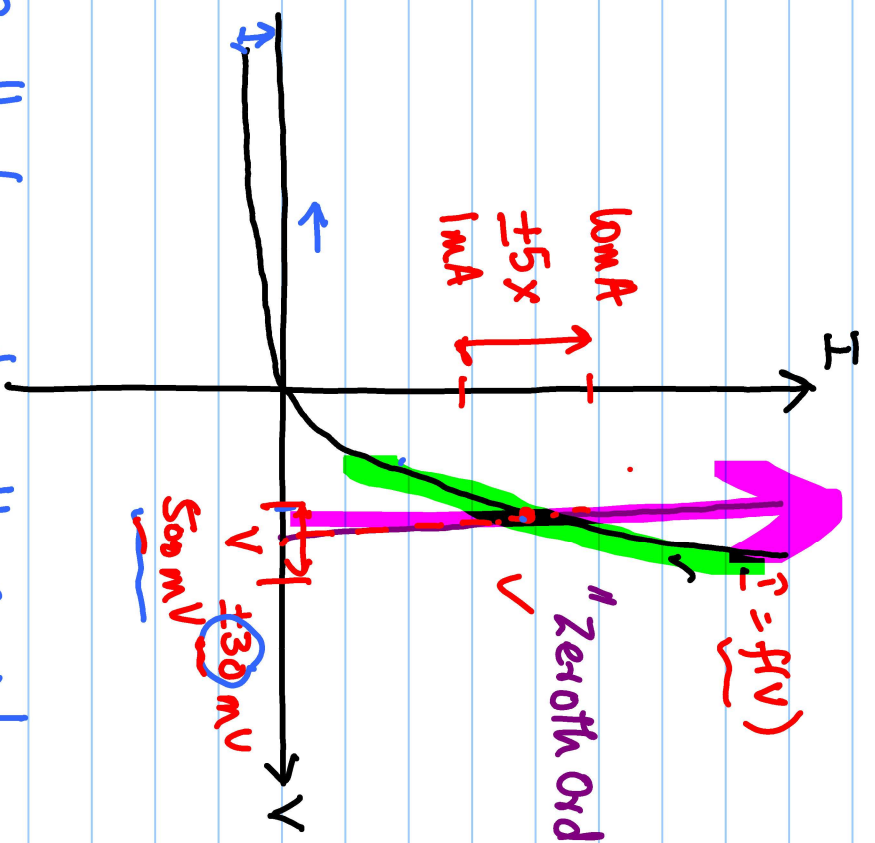

Small change in voltage \Rightarrow large change in current.

Zeroth Order Approx. $I = I_0 \left[\exp\left(\frac{V}{V_T}\right) - 1 \right]$



ex: $V = 500 \text{ mV}$, $I = 1 \text{ mA}$

$$\exp\left(\frac{V}{V_T}\right) = \exp\left(\frac{500}{25}\right)$$

$$= \underline{1.8 \times 10^8}$$

$I: 1 \text{ mA} \rightarrow 10 \text{ mA}$ $V = 60 \text{ mV}$.
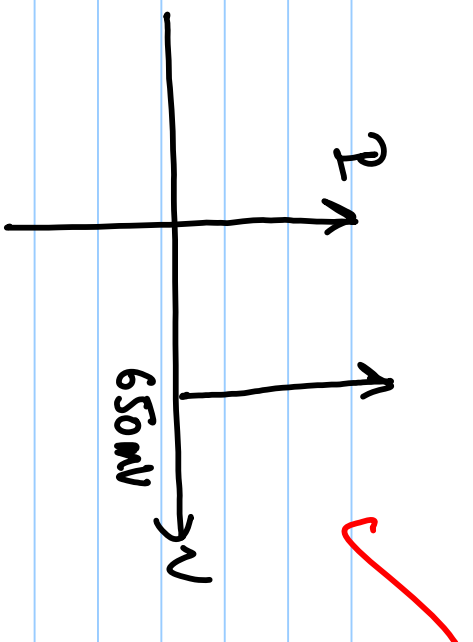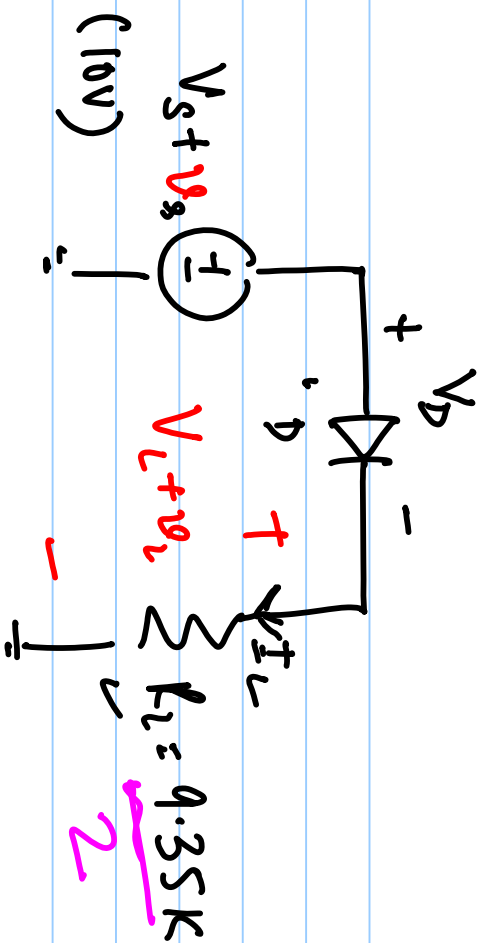
$$\hat{e}^{\left(\frac{550}{25}\right)} = 35 \times 10^8$$



$$I_L = \frac{V_S - V_D}{R_L}$$

$$V_D: 0.65V$$

$$I: V_D = 0.650V$$

$$= \frac{10 - 0.65}{9.35K} = 1mA, \quad V_L = 9.35V$$

$$1mA \quad 0.650V$$

$2mA$

$$I = \frac{10 - 0.65}{9.35/2} = 2mA$$

$$V = V_T \ln\left(\frac{I}{I_0}\right)$$

$$0.650 = 0.025 \ln\left(\frac{I}{I_0}\right) \xrightarrow{I \rightarrow 2I} \Delta V = 0.025 \ln(2) = 17.3mV$$